

Course Details

Course Title: Antennas & Wave Propagation

Module: \_\_\_\_\_

Instructor: \_\_\_\_\_

Total Marks: 30

Student Details

Name: Ibkar Ali

Student ID: 13008


Q1.	(a)	<p>Voltage standing wave pattern in a lossless transmission line with characteristic impedance <math>50 \Omega</math> and resistive load is shown in the figure.</p> <p><b>Qu.</b> The value of the load resistance is</p> <p>(A) <math>50 \Omega</math> (B) <math>200 \Omega</math> (C) <math>12.5 \Omega</math> (D) <math>0</math></p>	Marks 6 CLO 2
	(b)	<p><b>Draw &amp; Explain Equivalent circuit model of a Transmission line</b></p>	Marks 4 CLO 1
Q2.	(a)	<p>A microwave circuit consisting of lossless transmission lines <math>T_1</math> and <math>T_2</math> is shown in the figure. The plot shows the magnitude of the input reflection coefficient <math>\Gamma</math> as a function of frequency <math>f</math>. The phase velocity of the signal in the transmission lines is <math>2 \times 10^8</math> m/s.</p> <p>The length <math>L</math> (in meters) of <math>T_2</math> is _____.</p> <p>[Set - 02]</p>	Marks 6 CLO 2

	(b)	<p><b>Derive transmission line equation and describe what it says</b></p>	Marks 4 CLO 1
Q3.	(a)	<p>Voltage standing wave pattern in a lossless transmission line with characteristic impedance <math>50 \Omega</math> and resistive load is shown in the figure.</p> <p><b>Qu.</b> The reflection coefficient is given by</p> <p>(A) <math>-0.6</math> (B) <math>-1</math> (C) <math>0.6</math> (D) <math>0.2</math></p>	Marks 4 CLO 2
	(b)	<p><b>Explain two Impedance Matching techniques in detail?</b></p>	Marks 6 CLO 2

(1)

Q1)

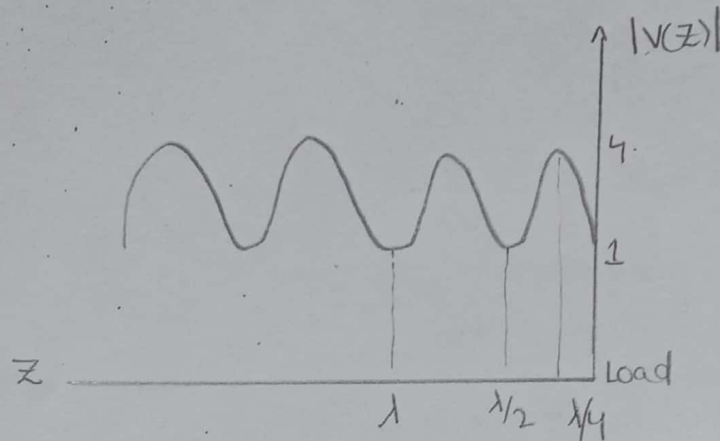(a) Voltage standing wave pattern in a lossless transmission line with characteristics impedance  $50\Omega$  and resistive load as shown in figure.



Solution:

Given Data:

$$Z_0 = 50\Omega$$

$$V_{max} = 4$$

$$V_{min} = 1$$

Required Data:

$$Z_L = ?$$

$$S \cdot \text{wave ratio} = ?$$

As we know that

$$S \cdot \text{wave ratio} = \frac{V_{max}}{V_{min}} \quad \text{--- (1)}$$

Putting values in eq (1)

(2)

$$= \frac{4}{1}$$

S. wave ratio = 4

Now find  $Z_L$

$$\text{s. wave ratio} = \frac{Z_0}{Z_L}$$



$$Z_L = \frac{Z_0}{\text{s. wave ratio}} \quad \text{---(2)}$$

Putting values in eq - (2)

$$Z_L = \frac{50}{4}$$

$Z_L = 12.5 \Omega$  Answer.

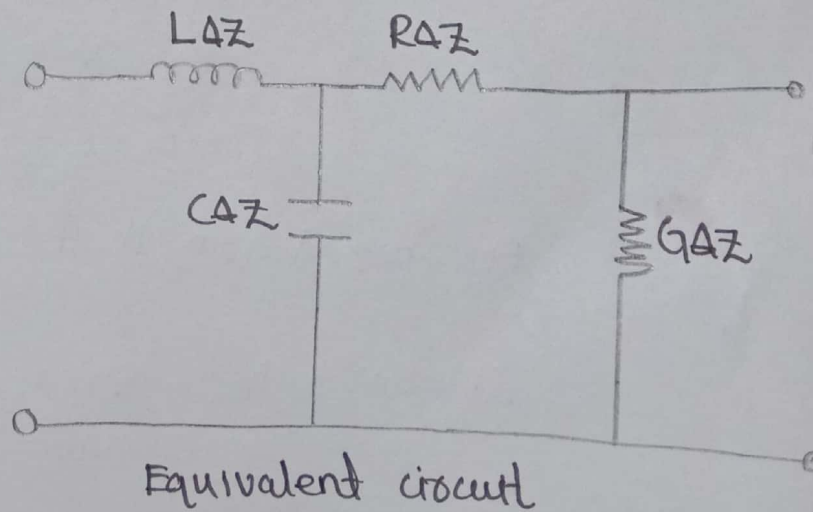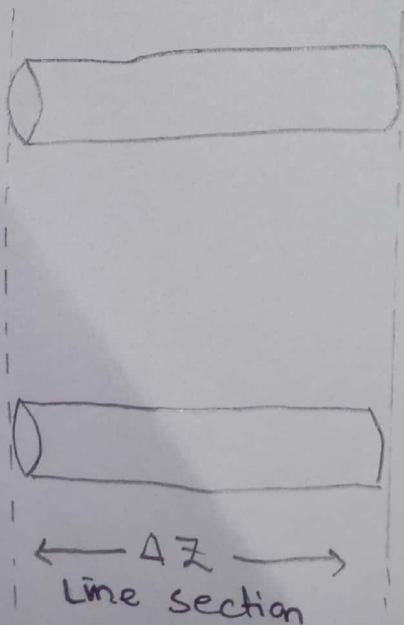
(b) Draw and explain Equivalent circuit model of a transmission line.





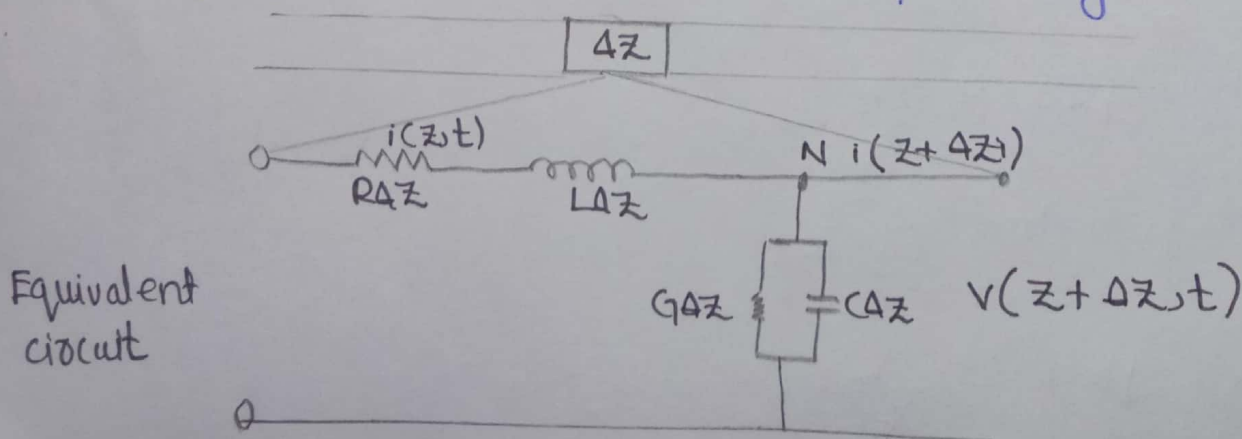
(3)

$R, L, G, C$  are primary line constants.  
Since the voltage and current of a transmission line vary with position  $z$  (and time  $t$ ), we have no characterise it by a "distributed" circuit model.  
Consider an infinitesimal line of length  $\Delta z$ , the current set up magnetic field between the conductors (by Ampere's Law) causing magnetic flux. When current are time-varying, so the magnetic flux and a voltage variation along the conductors electromotive force (emf) is induced in an attempt to drive the current oppositely. This behaviour can be modeled by a series inductor  $[v = L \frac{di}{dt}]$ .  
Meanwhile two separated conductors form a capacitor. Since the upper and lower conductors of adjacent infinitesimal lines are connected respectively, the capacitive behaviour of an infinitesimal lines can be modeled by a shunt capacitor. In the presence of imperfect conducting and imperfect insulating materials, voltage drop along the conducting line and leakage current between them exist, which can be modeled by a series resistor and a shunt conductor respectively.



(4)

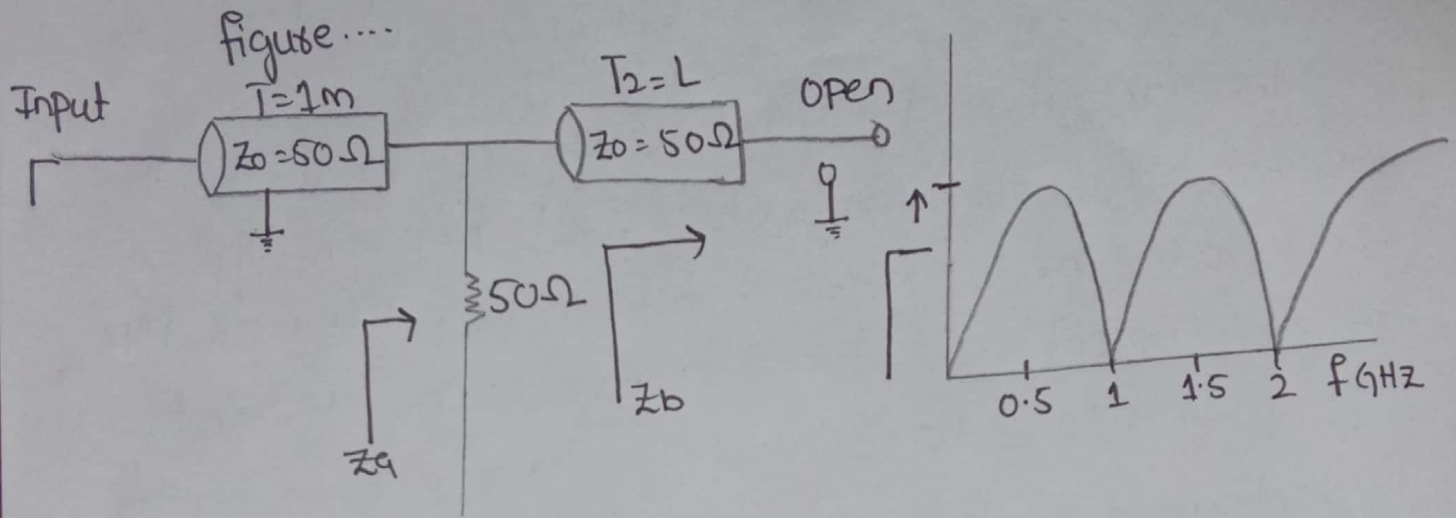Q2) (a) A microwave circuit consisting of lossless transmission lines  $T_1$  and  $T_2$  is shown in



Solution :-

As we know that

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}, f = 1 \text{ GHz}$$

In this case  $\Gamma = 0$

$$Z_a = 50 \Omega$$

$$Z_b = jZ_0 \cot \beta L$$

$$Z_{eq} = Z_a \parallel Z_b = 50 \Omega$$

Here  $Z_b = \alpha$

so

$$Z_b = -jZ_0 \cot \frac{2\pi}{\lambda} \cdot L$$

Putting values of  $Z_0$

$$Z_b = -j50 \cot \frac{2\pi}{\lambda} \cdot L$$

(5)

if 
$$\cot \frac{2\pi}{\lambda} \cdot L = \alpha$$

and if  $L = \lambda/2$

so 
$$\cot \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \alpha$$

Now

$$L = \lambda/2$$

$$v_p = 2 \times 10^8$$

$$v_p = \omega/\beta$$

$$\frac{\omega}{\beta} = 2 \times 10^8$$

$$\omega = \frac{2\pi f}{2\pi} \times \lambda = 2 \times 10^8$$

At  $f = 1 \text{ GHz}$

$$\lambda = \frac{2 \times 10^8}{1 \times 10^9}$$

$$\lambda = 0.2 \text{ m}$$

Now

$$L = \lambda/2$$

$$= 0.2/2$$

$$L = 0.1 \text{ m Ans.}$$



(6)


(b) Derive transmission line equation and describe what it says?

Ans)

Transmission line equation:

A Typical engineering

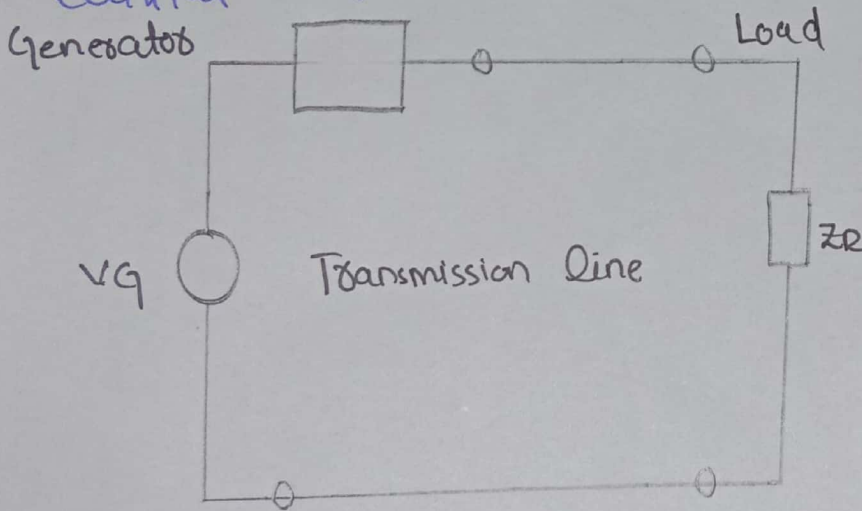Problem involves the transmission of a signal from a generator to a load. A transmission line is the part of the circuit that provides the direct link between generator and load. Transmission line can be realized in a number of ways. Common examples are parallel-wire line and the coaxial cables.



Transit Time effect :

$$T \gg t_0$$

$$T \gg \frac{l}{v}$$

$$\frac{1}{f} \gg \frac{l}{v}$$

$$\frac{v}{f} \gg l$$



$$\lambda \gg l$$

$$t_0 = \frac{l}{v}$$

$l$  = length


$v$  = velocity

$T$  = Time period of signal

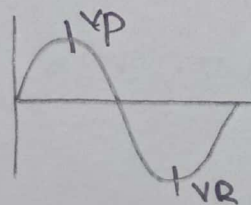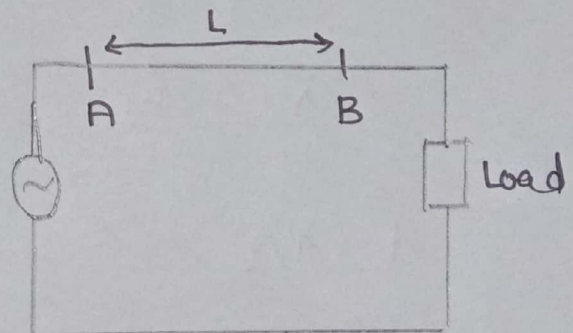

(7)

Primary constant of Transmission line :

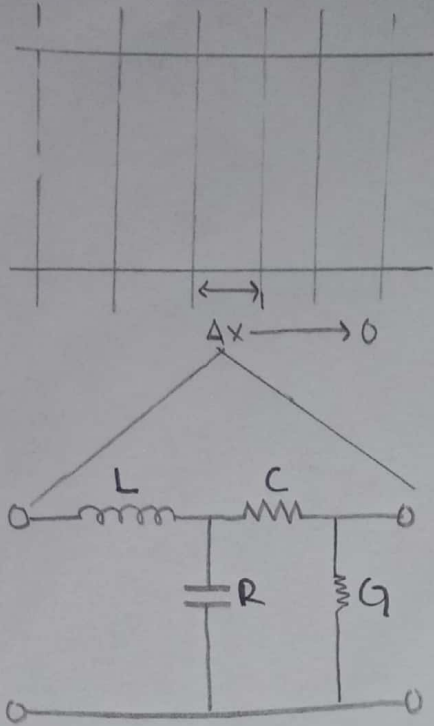


$$L \rightarrow \text{H/m}$$

$$C \rightarrow \text{F/m}$$

$$R \rightarrow \Omega/\text{m}$$

$$G \rightarrow \text{S/m}$$

Transmission line equation :

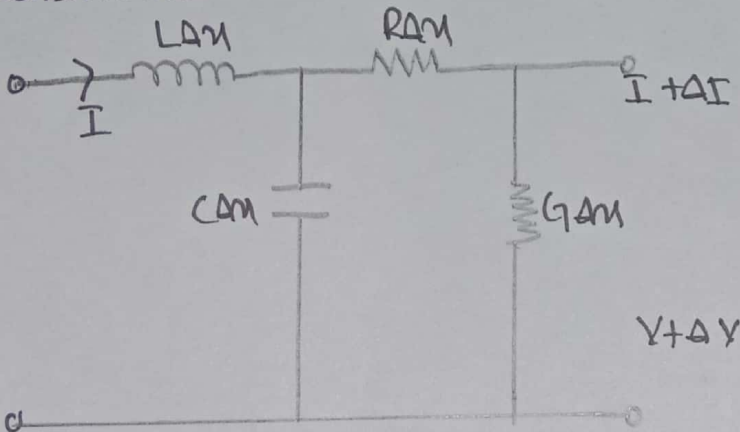

Solution

$$\Delta I = -(G\Delta x + j\omega C\Delta x)V$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C)V$$

$$\frac{dI}{dx} = -(G + j\omega C)V \quad \text{--- (1)}$$

$$\Delta V = -(R\Delta x + j\omega L\Delta x)I$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = -(R + j\omega L)I$$



(8)

$$\frac{dv}{dx} = -(R+j\omega L)I \quad (2)$$

again derivative:

$$\frac{d^2v}{dx^2} = -(R+j\omega L) \frac{dI}{dx}$$

$$\frac{d^2v}{dx^2} = (R+j\omega L)(G+j\omega C)v$$

As we know that

$$(R+j\omega L)(G+j\omega C) = \gamma^2$$

$$\boxed{\frac{d^2v}{dx^2} = \gamma^2 v}$$

Now

$$v(x,t) = (V^+ e^{-\gamma x} + \bar{V} e^{+\gamma x}) e^{j\omega t}$$

$$= V^+ e^{-j\beta x} e^{j\omega t} + \bar{V} e^{j\beta x} e^{j\omega t}$$

$$= V e^{+j(\omega t - \beta x)} + \bar{V} e^{-j(\omega t + \beta x)}$$

Now we know that

$$\vec{E} = E_0 e^{-\alpha z} \cos(\omega t - \beta z) \hat{u}$$

$$\vec{E} = E_0 \cos(\omega t - \beta z) \hat{u} \quad \left\{ \begin{array}{l} \text{Loss less line} \\ \downarrow \\ \text{wave equation} \end{array} \right.$$

$$v(x,t) = V^+ \cos(\omega t - \beta x) + \bar{V} \cos(\omega t + \beta x)$$


↓  
travelling +x  
direction

↓  
travelling -x  
direction

Voltage & current in a transmission line behave like a wave.

(9)

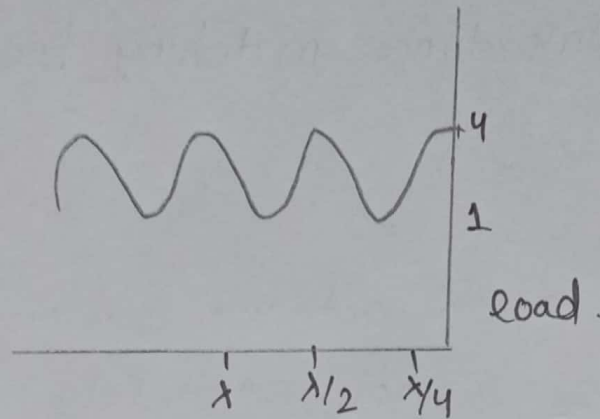Q3) (a) Voltage standing wave pattern in a lossless transmission line with characteristics impedance  $50\Omega$  and resistive load is shown in figure.



Solution:-

Given data:-

$$Z_0 = 50\Omega$$

$$Z_L = 12.5\Omega$$

Required = ?

Reflective co-efficient = ?

So we know that

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{--- (1)}$$

Putting values in eq (1)

$$\Gamma = \frac{12.5 - 50}{12.5 + 50}$$

(10)

$$= \frac{-37.5}{62.5}$$

$$\Gamma = -0.6 \text{ Ans.}$$

(b) Explain two impedance matching techniques in detail=?

Ans)

The operation of an antenna system over a frequency range is not completely dependent upon the frequency response of the antenna element itself but rather on the frequency characteristics of the transmission line-antenna element combination.

↳ In practice, the characteristics impedance of the transmission line is usually real whereas that of the antenna element is complex. Also the variation of each as a function of frequency is not the same.

### TYPES

- 1) Stub Matching
- 2) Quarter-wave length Transformers



## 1) Stub Matching:

Ideal matching at a given frequency can be accomplished by placing a short or open circuited shunt a distance from the transmission line antenna element connection.

↳ Assuming a real characteristics impedance the length is controlled so as to make the real part of the antenna element impedance equal to the characteristics impedance.

↳ A single stub with a variable length cannot always match all antenna (load) impedance. A double stub arrangement positioned a fixed distance from the load with the length of each stub variable and separated by a constant length will match a greater range of antenna impedance.

## 2) Quarter-wave length Transformers:

1) Single section

2) Multiple section


3) Binomial design

## 1) single section:

Another technique that can be used to match the antenna to the transmission line is to use a  $\lambda/4$  transformer. If the impedance of the antenna is real, the transformer is attached directly to the load.


↳ However if the antenna impedance is complex the transformer is placed a distance away from the antenna. The distance is chosen so that input impedance towards the load is real and designated as  $R_{in}$ .

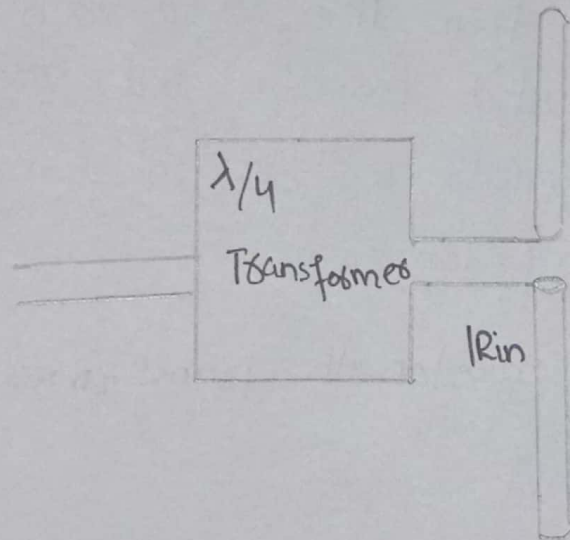↳ The transformer is usually another transmission line with the desired characteristic impedance.



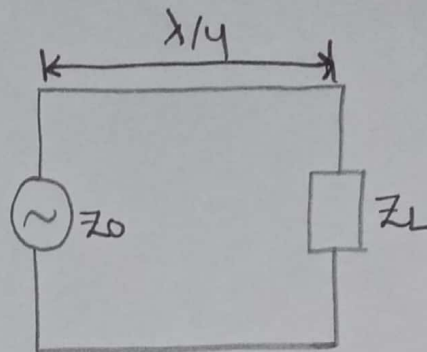(13)

Input Impedance of  $\lambda/4$  length of transmission Line:



$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4}$$

$$= \pi/2$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_{in} = Z_0 \left\{ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right\}$$

$$Z_{in} = Z_0 \tan \beta l \left\{ \frac{Z_L}{\tan \beta l} + jZ_0 \right\}$$

$$\tan \beta l \left\{ \frac{Z_0}{\tan \beta l} + jZ_L \right\}$$

$$Z_{in} = Z_0 \times \frac{jZ_0}{jZ_L} = \frac{Z_0^2}{Z_L}$$