

①

Name :- Aqib Shukairb

ID :- 6978

Subject :- Electronic devices & circuit.

Question 1 :-

The 1N4747 zener diode used in the regulation circuit in fig is 20V

$$V_Z = 20V \quad I_Z = 12.5mA$$
$$I_{ZK} = 0.25mA \quad Z_Z = 22\Omega$$

a) for I_{ZK}

$$V_{out} = V_Z - \Delta I_Z \cdot Z_Z$$
$$= 20V - (I_Z - I_{ZK}) Z_Z$$
$$= 20V - (12.5mA - 0.25mA) 22\Omega$$
$$= 20V - (12.25mA) 22\Omega$$
$$= 20V - 0.267V$$
$$V_{out} = 19.73V$$

For I_{ZM}

$$PD(\text{Max}) / V_Z = I_{ZM} / 20V = 50mA$$


$$V_{out} = V_Z + \Delta I_Z Z_Z$$
$$= 20V + (I_{ZM} - I_Z) Z_Z$$
$$= 20V + (50mA - 12.5mA) 22\Omega$$
$$= 20V + (37.5mA) 22\Omega$$
$$= 20V + 0.825V$$
$$= 20.825V$$

(2)

$$b) R = \frac{V_{in} - V_{out}}{I_{ZM}}$$
$$= \frac{24V - 20.825V}{50mA}$$

$$R = 63.5 \Omega$$

$$R = 70 \Omega$$

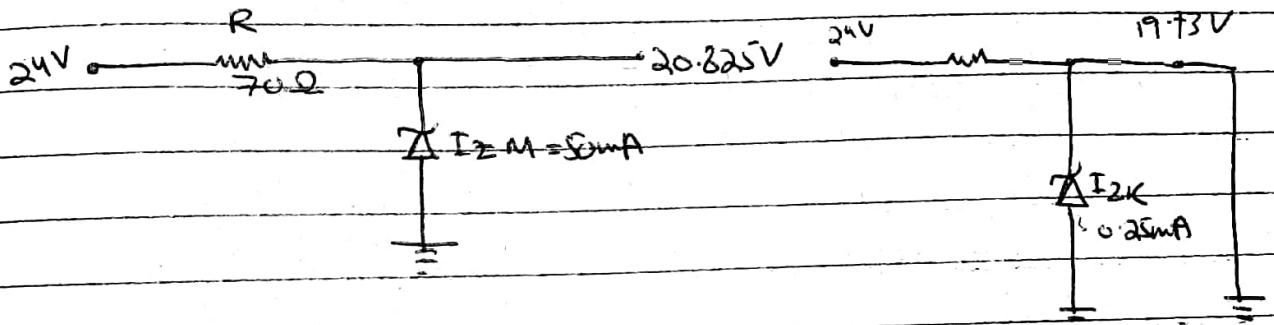

c) for maximum load Resistance (max current)
the Zener diode current minimum ($I_{ZK} = 0.25$)

$$I_i = \frac{V_{IN} - V_{out}}{R}$$
$$= \frac{24V - 19.73V}{70 \Omega}$$
$$= 0.061A$$

3

Question 2:-

$$\text{Sol:- } V_{BE} = 0.7V$$

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{3.9k\Omega} = \boxed{1102\mu A}$$

$$\Rightarrow I_C = \beta_{DC} \cdot I_B \Rightarrow (150)(1102\mu A) = \boxed{165.3mA}$$

$$\Rightarrow I_E = I_C + I_B = 165.3mA + 1102\mu A = \boxed{166.4mA}$$

Solve for V_{CE} & V_{CB}

$$V_{CE} = V_{CC} - I_C R_C = 15V - (165.3mA)(180\Omega) \\ = 15V - 29.7V = \boxed{-14.7V}$$

$$V_{CB} = V_{CE} - V_{BE} \Rightarrow -14.7V - 0.7V \\ = -15.4V$$

Since the collector is at a lower voltage than the base, the collector base junction is forward biased.

Question 3:-


⇒ BJT:-

1) It was invented in Dec 1947 at bell's lab USA.


2) It is a three terminal device and it is used for amplification of weak signals in switching operation.

Structure


NPN

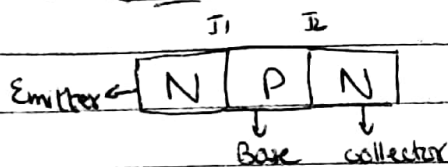

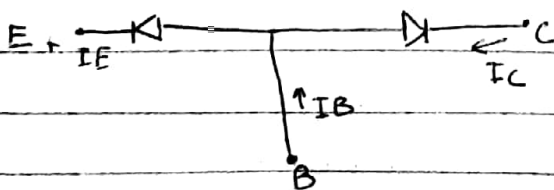-) 2 Junction (N)
-) 1 Junction (P)
-) $J_1 \rightarrow$ emitter - base
-) $J_2 \rightarrow$ collector base
-) There is depletion region at J_1
-) There is depletion region at J_2 .




PNP

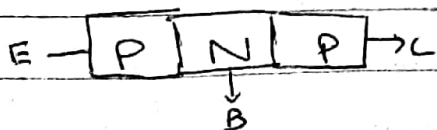

width $C > E > B$
 doping = $E > C > B$



(5)

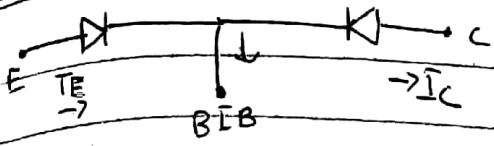


Cross Section View

NPN

PNP

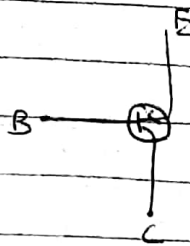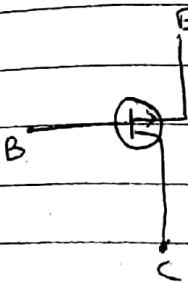


Post and

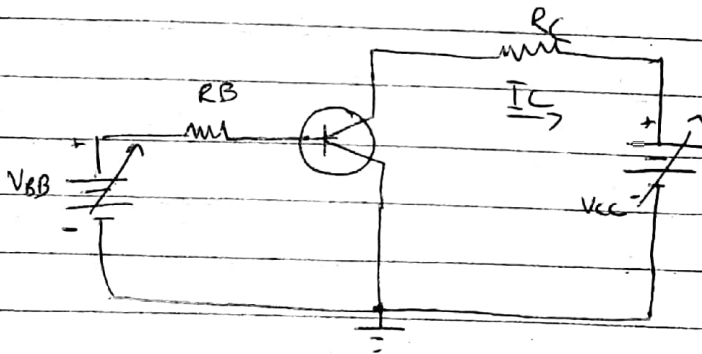

Using the relationship $I_C = \beta_{DC} I_B$ value of I_C are calculated and tabulated in below table. The resulting curves are plotted.

Table

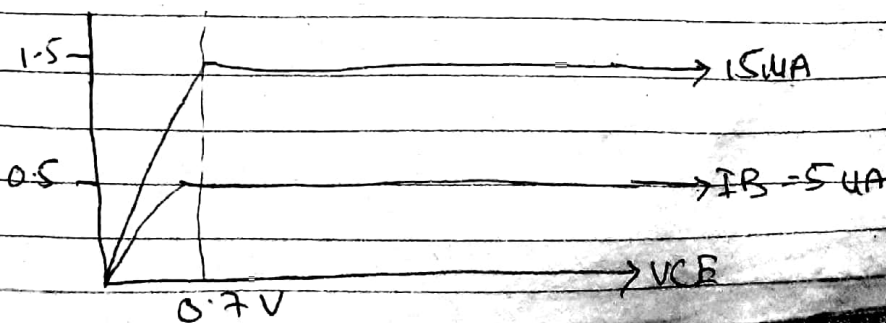I_B
 $5\mu A = 0.5\text{ mA}$
 $15\mu A = 1.5\text{ mA}$



6

Question 4:-

Transistor Fully ON (ON)

Transistor Fully OFF (OFF)

Input and base are at 0V (OFF)

Collector current $I_c = 0$ (OFF)

$V_{CE} = V_{CC}$ (OFF)

BE junction is reverse bias (OFF)

BC junction is forward bias (OFF)

Maximum of saturation current I_c flows (ON)

BE junction is forward bias (ON)

BC junction is forward bias (ON)


$V_{CE} = 0V$ (ON)

BE junction is less than 0.7V (OFF)


—————x

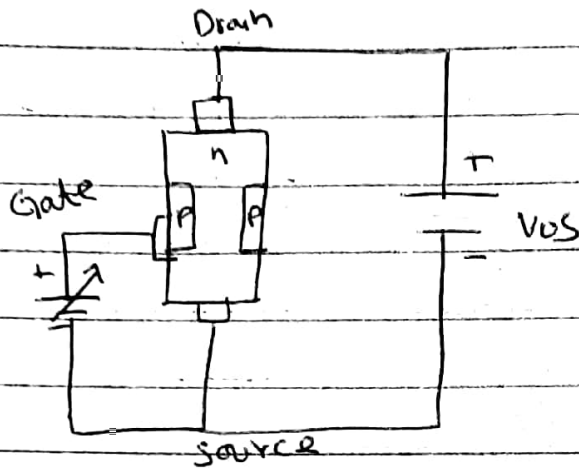Question 5 :-

JFET is a type of junction field effect transistor which is voltage controlled device as differ from BJT which is current controlled




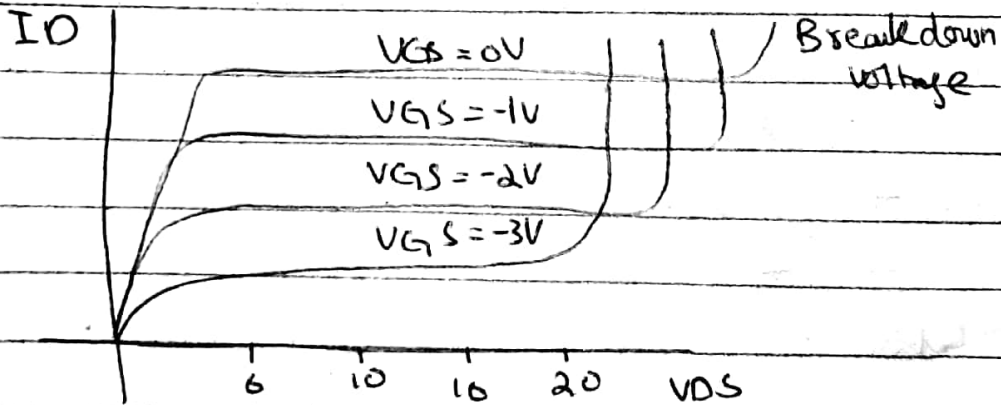In FET the drain to source current is controlled by the width of the channel the electric field is produced by the gate to source voltage.




So if we see to the graph with no voltage applied to the gate then the current flows freely

(8)

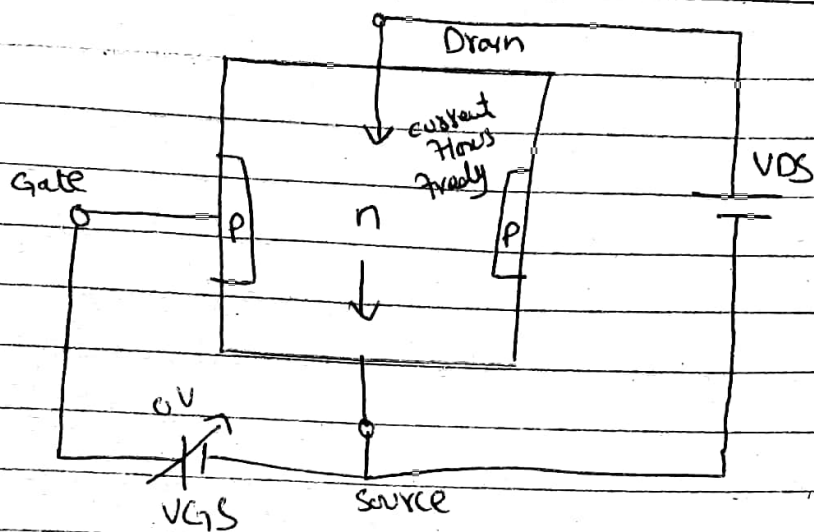

The channels are wider and drain current moves freely.

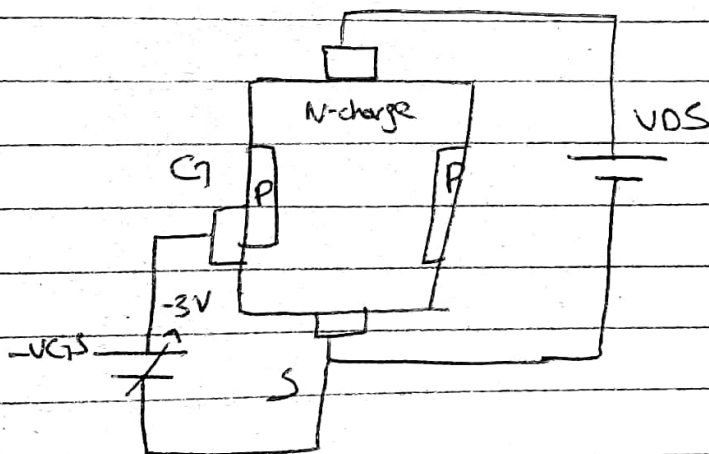If we move ~~the~~ V_{GS} to negative value the channel width starts to decrease and current cannot move.



So V_{GS} is more negative so no current flows & this effect is called Pinch off region no current or less current flows.

9

Question 6:-

a) $V_{CE} = ?$ $V_{in} = 0V$

When $V_{in} = 0V$ then transistor is in cutoff mode.
 $V_{CE} - V_{CC} = 10V$

b) min $I_B = ?$

$\beta_{DC} = 125$

$V_{CE(sat)} = 0.4V$

$$I_C(sat) = \frac{V_{CC}}{R_C} = \frac{10V}{1.0K\Omega}$$
$$= 10mA$$

$$I_B(min) = \frac{I_C(sat)}{\beta_{DC}} = \frac{10mA}{125}$$

$I_B(min) = ~~80\mu A~~ 80\mu A$