

Department of Electrical Engi

Final Assignment

Date 24/06/2020

course Details

Course Title: Linear circuit
Analysis

Module: 2

Instructor: Sohail Imran sir

Student Detail

Name Amjad A1


ID 16012

(1)

Question 1.

Find the value of i_x .
For the circuit using.

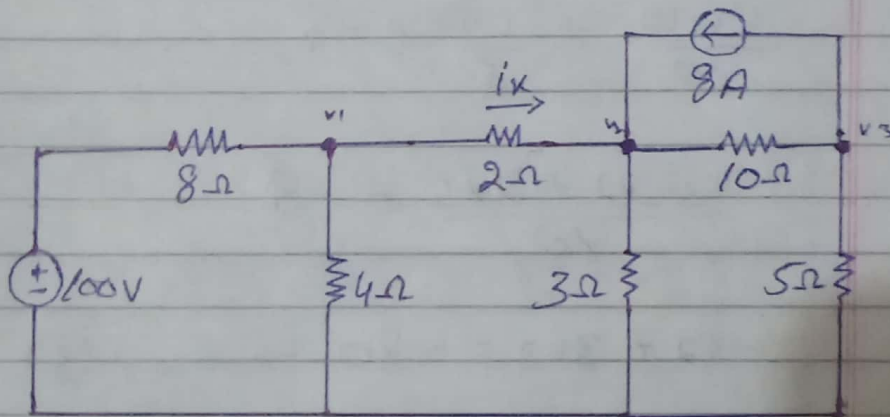- (1) Nodal Analysis
- (2) Mesh Analysis
- (3) Superposition theorem
- (4) Compare the number of steps and degree of difficulty of all the three methods with each other.



Solution: (i) Nodal Analysis

Applying KCL on node 1

$$\frac{v-100}{8} + \frac{v}{4} + \frac{v-v_2}{2} = 0$$

$$\frac{7v-100+2v+4v-4v_2}{8} = 0$$

$$7v - 4v_2 = 100 \quad \text{--- (1)}$$

(2)

Applying KCL on node 2:

$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{10} = 8$$

$$\frac{30v_2 - 30v_1 + 20v_2 + 3v_2 - 3v_3}{60} = 8$$

$$-30v_1 + 53v_2 - 3v_3 = 480 \quad \text{--- (2)}$$

Applying KCL on node 3:

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = -8$$

$$\frac{v_3 - v_2 + 2v_3}{10} = -8$$

$$-v_2 + 3v_3 = -80 \quad \text{--- (3)}$$

Applying KCL on node 1:

Taking eq (1)

$$7v_1 - 4v_2 = 100$$

$$v_1 = \frac{4v_2 + 100}{7} \quad \text{--- (A)}$$

(3)

Taking eq (2)

$$-v_2 + 3v_3 = -80$$

$$v_3 = \frac{v_2 - 80}{3} \quad \text{(B)}$$

Putting eq (a) and (b)

in eq (2)

$$\begin{aligned} -30(0.57v_2 + 14.28) + 53v_2 - 3(0.33v_2 - 26.67) \\ = 480 \end{aligned}$$

$$-17.1v_2 - 428.4 + 53v_2 - 0.99v_2 + 80.01 = 480$$

$$34.91v_2 = 828.39$$

$$v_2 = \frac{828.39}{34.91}$$

$$\boxed{v_2 = 20.31}$$

putting in eq (a)

$$v_2 = \frac{4(20.31) + 100}{7}$$

$$v_1 = 25.89$$

next page


(4)

$$i_x = \frac{v_1 - v_2}{2}$$

$$= \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

(ii) Mesh Analysis

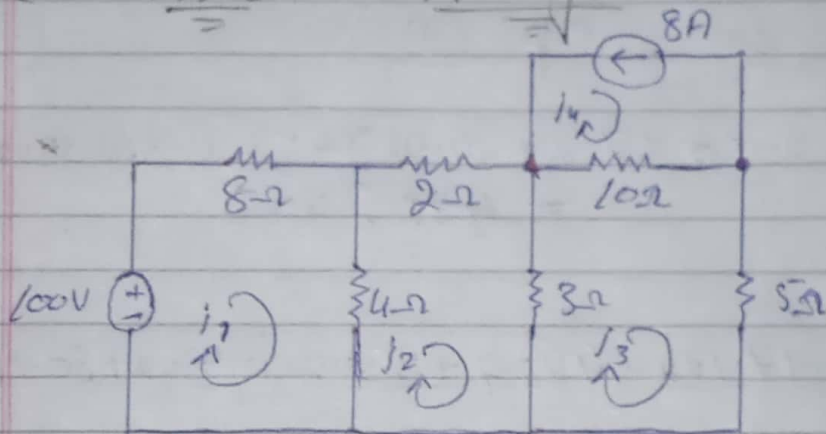

Applying KVL on Loop 1:

$$8i_1 + 4(i_1 - i_2) = 100$$

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Applying KVL on Loop 2:

$$2i_2 + 4(i_2 - i_1) + 3(i_2 - i_3) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_2 - 3i_3 = 0$$

(5)

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3:

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (4)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 + 80}{18} \quad \text{--- (b)}$$

putting eq (a) and (b)
in eq (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

(6)

$$7.2i_2 = +20$$

$$i_2 = 20/7.2$$


$$i_2 = 2.79 \text{ A}$$

$$i_2 = i_x$$

$$\boxed{i_x = 2.79 \text{ A}}$$

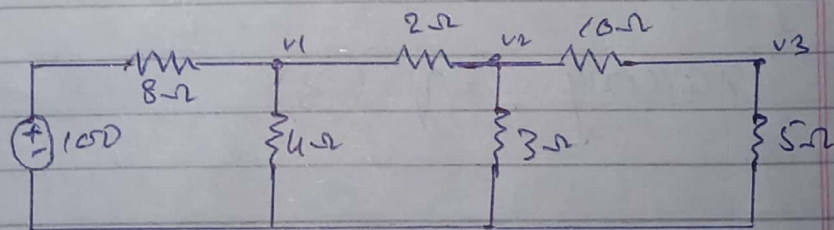(iii) Superposition Theorem

First removing the current source and making it an open circuit. Redrawing the circuit.



Apply KCL on node 1:

$$\frac{-100 + v_1}{8} + \frac{v_1 - v_2}{2} + \frac{v_1}{4} = 0$$

$$\frac{v_1 - 100 + 4v_1 - 4v_2 + 2v_1}{8} = 0$$

$$7v_1 - 4v_2 = 100 \quad \text{--- (1)}$$

(1)

Applying KCL on node 2

$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{10} = 0$$

$$-30v_1 + 53v_2 - 3v_3 = 0$$

Applying KCL on node 3:

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = 0$$

$$\frac{v_3 - v_2 + v_3}{10} = 0$$

$$-v_2 + 2v_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) and (3)

$$7v_1 - 4v_2 = 100$$

$$v_1 = \frac{4v_2 + 100}{7} \quad \text{--- (a)}$$

Now

$$-v_2 + 3v_3 = 0$$

$$v_3 = \frac{v_2}{3} \quad \text{--- (b)}$$

Put eq (a) and (b) in eq (2)

$$-30(0.577v_2 + 14.28) - 4v_2 + 2(0.33v_2) = 0$$

(8)

$$-171v_2 - 428.4 - 4v_2 + 0.66v_2 = 0$$

$$20.44v_2 = 428.4$$

$$v_2 = -20.95$$


putt. in eq (a)

$$v_2 = 2.31$$

$$i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = 11.63$$

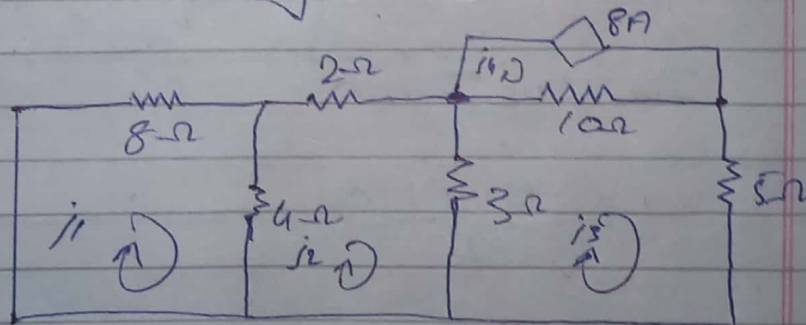Now Removing voltage source
and making it short circuit
Re drawing circuit.



$$j_4 = 8A$$

Apply KVL on loop 1

$$8j_1 + 4(j_1 - j_2) = 0$$

$$8j_1 + 4j_1 - 4j_2 = 0$$

(9)

$$12j_1 - 4j_2 = 0$$

$$3j_1 - j_2 = 0 \quad \text{--- (1)}$$

Applying KVL on loop 2

$$2j_2 + 3(j_2 - j_3) + 4(j_2 - j_1) = 0$$

$$2j_2 + 3j_2 - 3j_3 + 4j_2 - 4j_1 = 0$$

$$-4j_1 + 9j_2 - 3j_3 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3

$$10j_3 + 5j_3 + 3j_3 - 3j_2 + 8(10) = 0$$

$$-3j_2 + 18j_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$3j_1 - j_2 = 0$$

$$j_1 = 0.33j_2 \quad \text{--- (a)}$$

Taking eq (3)

$$-3j_2 + 18j_3 = -80$$

$$j_3 = \frac{3j_2 - 80}{18} \quad \text{--- (b)}$$

(10)

$$-4(0.33i_1) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$$

$$i_2 = 1.354$$

$$\text{Now } i_x = i_1 + i_2$$

$$i_x = 1.44 + 1.35$$

$$i_x = 2.79 \text{ A}$$

(iv) Compare the number of steps and degree of easiness of all the three methods with each other.

Solution

The number of steps in nodal and mesh analysis are almost equal but in superposition the number of steps are almost of mesh and nodal analysis.

Degree of easiness:

According to opinion mesh analysis is easier than nodal analysis and superposition theorem.


(11)

(1)


Question 2:

Consider the $200\ \Omega$'s resistor in Figure as load resistor and develop.

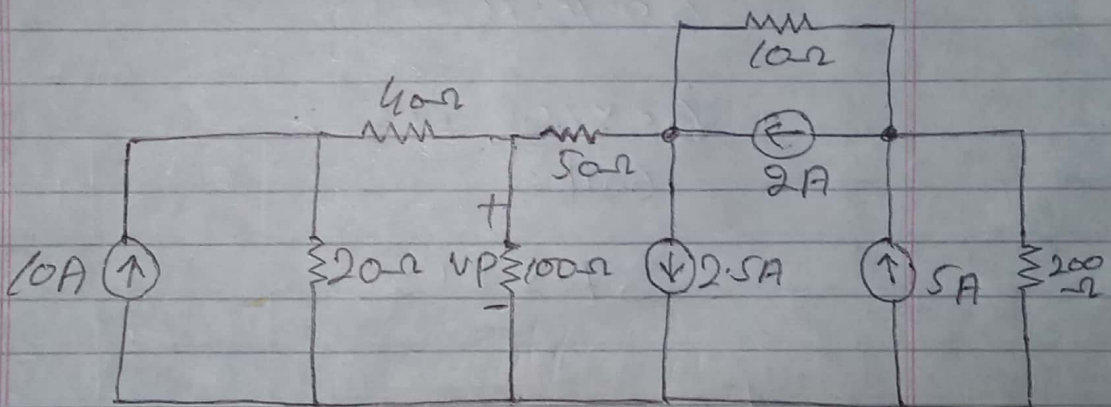- (i) Thevenin equivalent circuit.
- (ii) Norton equivalent circuit.
- (iii) Find out what value of Thevenin resistor should be used to deliver maximum power to the load.




Solutions (i) Solving for Thevenin.

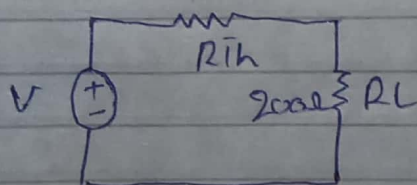

We will find R_{th} for which we will remove all the current source and short circuit the load resistor.

(12)

Redrawing the circuit

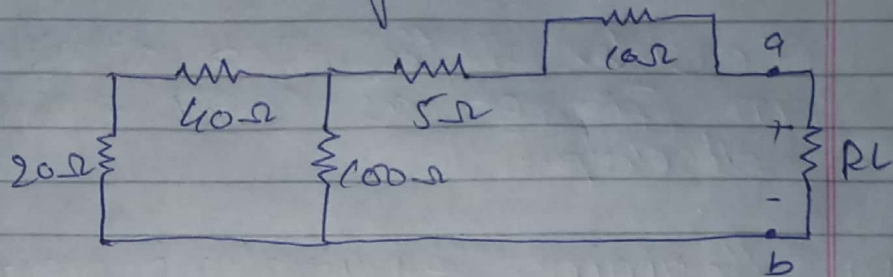

adding all resistor

$$20 + 40 \parallel 100 + 5 + 10$$

$$60 \parallel 100 + 15$$


$$\frac{60 \times 100}{60 + 100} + 15$$

$$37.5 + 15$$

$$R_{Th} = 52.5$$

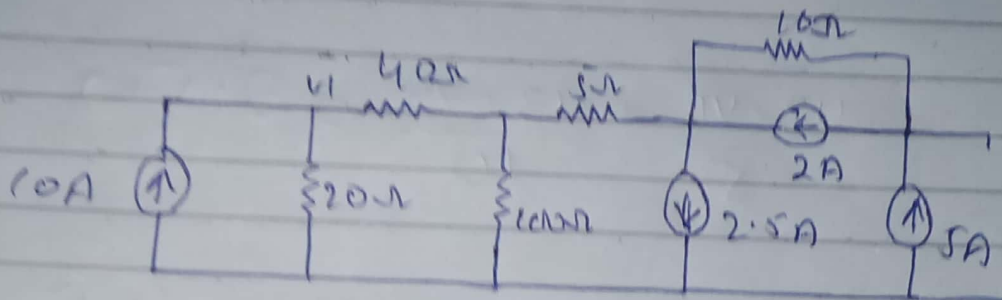(13)

For finding V_{th} applying
nodal analysis.



Apply KCL on V_1

$$\frac{V_1 - V_2}{40} - \frac{V_1}{20} = 10$$

$$\frac{V_1 - V_2 + 2V_2}{40} = 10 \quad \text{--- (1)}$$

Apply KCL on node 2

$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{5}$$

$$\frac{50V_2 - 5V_1 + 20V_2 + 400V_3 - 400V_3}{2000}$$

$$\frac{-50V_1 + 70V_2 - 400V_3}{2000} = 0$$

$$2000$$

(11)

$$-0.05V_1 + 0.035V_2 - 0.2V_3 = 0 \quad \text{--- (2)}$$

Apply KCL on node (3)

$$\frac{V_3 - V_1}{5} + \frac{V_3 - V_4}{10} = 2.5 + 2$$

$$\frac{2V_3 - 2V_2 + V_3 - V_4}{10} = 4.5$$

$$-2V_2 + 3V_3 - V_4 = 45 \quad \text{--- (3)}$$

Apply KCL on node (4)

$$\frac{V_4 - V_3}{10} = 5 - 2$$

$$V_4 - V_3 = 30 \quad \text{--- (4)}$$

Solving by using calculator

$$V_1 = 275$$

$$V_2 = -124.9$$

$$V_3 = -87.5$$


$$V_4 = -57.5$$

(15)

$$I_{Th} = \frac{5-1}{52.5+200}$$

$$I_{Th} = 0.02$$

(ii) For Norton theorem

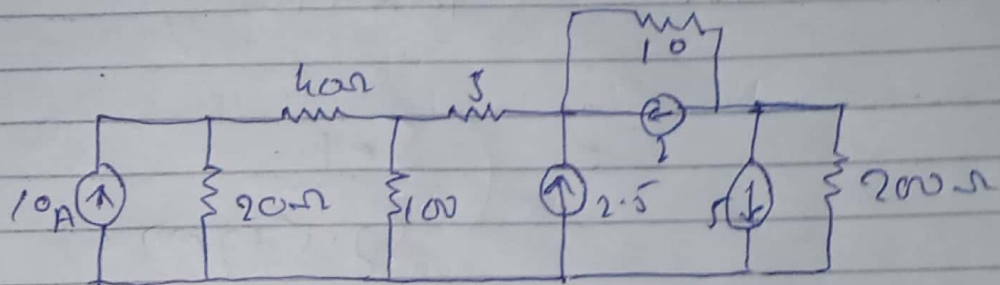

For R_N will be the same

$$R_N = R_{Th}$$

$$R_N = 52.5$$

$$\text{Find } I_n = \frac{V_{Th}}{R_N}$$

$$I_n = 0.02$$

As the circuit are same
So we find it directly

(18)

Using Thevenin for
Finding power.

We know that


$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

$$= \left(\frac{5 \cdot 1}{52 \cdot 5 + 200} \right)^2 \cdot 200$$

$$P = 0.08 \text{ W}$$

(17)

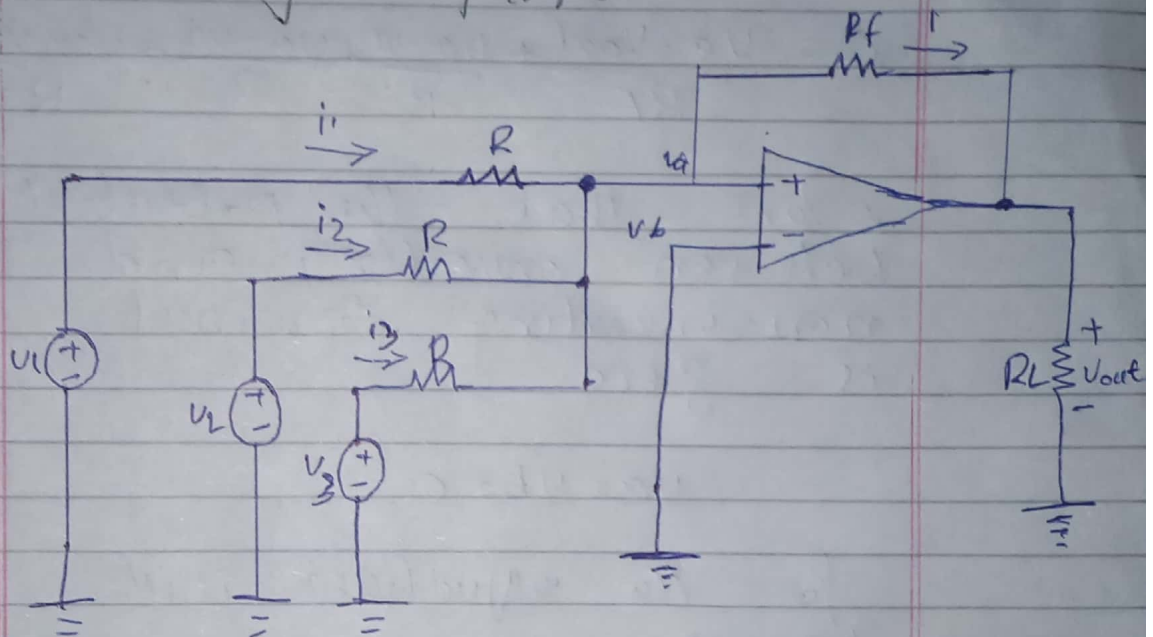Q3: obtain an expression for V_{out} in terms of v_1, v_2 and v_3 for the op amp circuit in figure, also known as a summing amplifier.



Solution:

We know that all the current is entering to the inverting terminal or we know that the current entering to inverting or non-inverting are virtually zero.

$$\text{Now } i = i_1 + i_2 + i_3$$

Therefore we are taking node v_a as maintain on the circuit above

(18)

As current I is flowing from v_a to v_{out} as v_a will be at high potential writing equation.

$$0 = \frac{v_a - v_{out}}{R_f} + \frac{v_a - v_1}{R} + \frac{v_a - v_2}{R} + \frac{v_a - v_3}{R}$$

Now that the potential between inverting and non-inverting terminal is zero.

$$v_a = v_b = 0$$

So the equation will become:

$$0 = \frac{v_{out}}{R_f} + \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R}$$

$$-\frac{v_{out}}{R_f} = \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R}$$

$$-v_{out} = R_f \left(\frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R} \right)$$

$$v_{out} = -\frac{R_f}{R} (v_1 + v_2 + v_3)$$

(19')

In this case where

$$v_2 = v_3 = 0$$

We see that our rules
Agrees.
