

# IQRA NATIONAL UNIVERSITY PESHAWAR

Name :- Mohammed Iqbal Khan

ID :- 161134

Semester :- 2nd

Subject :- LCA (Linear Circuit Analysis)

Teacher :- Dr. Sahid Imran

Date :- 24-06-2020

①


07077

Date / /

### Question Number 1

Find the value of  $i_x$  for the circuit using

(i) - Node Node Analysis :-

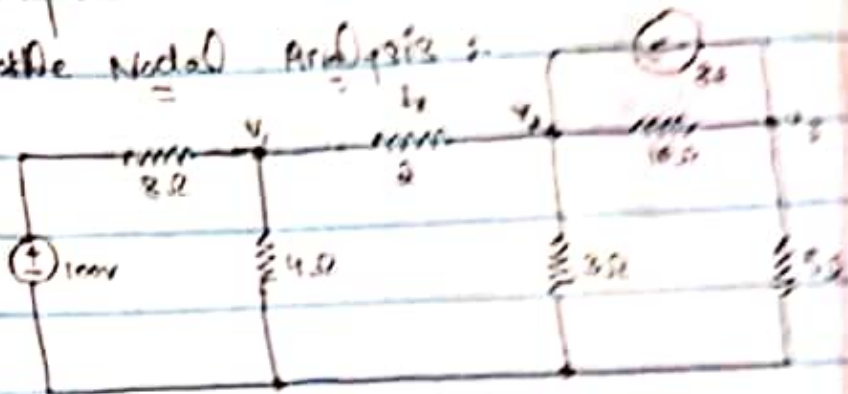

Solution :-

Applying KCL on node 1 :-

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 - 100 = 0$$

Multiplying '8' on both sides.

$$8 \times \frac{7V_1 - 4V_2 - 100}{8} = 8 \times 0$$

$$7V_1 - 4V_2 - 100 = 0$$

$$7V_1 - 4V_2 - 100 = 0 \quad \text{①}$$

Now taking equation (1)

we get.

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Now taking equation (2)

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting eq (a) and (b) in eq (3)

$$-30(0.57V_2 + 14.28) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.1V_2 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

Putting "V<sub>2</sub>" in eq (a)

$$V_1 = \frac{4(20.31) + 100}{7}$$

$$V_1 = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

Now :-

Applying KCL on node 2n :-

$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{18} = 8$$

$$\frac{30v_2 - 30v_1 + 20v_2 + 3v_2 - 3v_3}{60} = 8$$

$$\frac{-30v_1 + 53v_2 - 3v_3}{60} = 8$$

Multiplying "60" o.B.S.

$$60 \times \frac{-30v_1 + 53v_2 - 3v_3}{60} = 8 \times 60$$

$$-30v_1 + 53v_2 - 3v_3 = 480 \quad \text{--- (2)}$$

Now :-

Applying KCL on node 3n :-

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = -8$$

$$\frac{v_3 - v_2 + 2v_3}{10} = -8$$


$$-v_2 + 3v_3 = -8$$

Multiplying "10" on both sides.

$$10 \times \frac{-v_2 + 3v_3}{10} = -8 \times 10$$

$$-v_2 + 3v_3 = -80 \quad \text{--- (3)}$$

(ii) - Mesh analysis :-

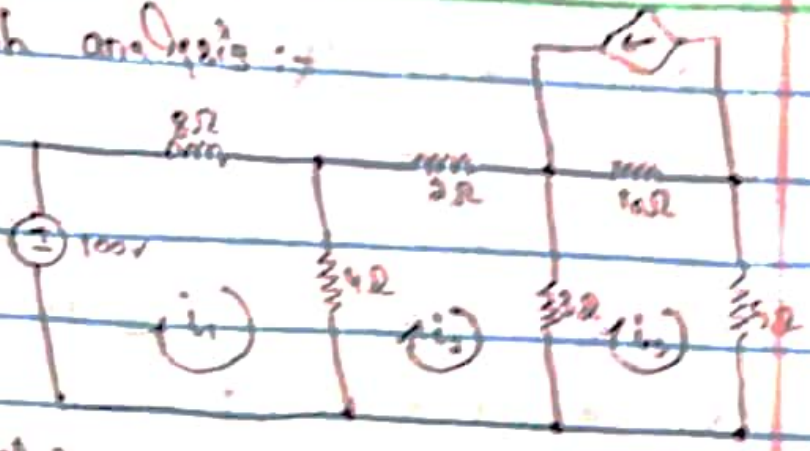

Applying KVL on Loop 1

$$8i_1 + 4(i_1 - i_2) = 100$$

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Now:-

Applying KVL on Loop 2

$$2i_2 + 4(i_2 - i_1) + 3(i_2 - i_3) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_2 - 3i_3 = 0$$

$$-4i_1 + 9i_2 - 3i_3 = 0$$

Again

Applying KVL on Loop 3

$$3(i_3 - i_2) - 10(i_3 - i_1) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_1 + 5i_3 = 0$$

$$3i_3 - 3i_2 + 15i_3 = 10i_1$$

$$-3i_2 + 18i_3 = 10i_1 \quad \text{--- (2)}$$

Taking eq. (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (3)}$$

(5)

Q.17.

Date: / /

Taking equation (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (b)}$$

Putting equation (a) and (b) in equation

(2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

$$7.2i_2 = 20$$

$$i_2 = \frac{20}{7.2}$$

$$i_2 = 2.79 \text{ A}$$

$$i_2 = I_x$$


So,

$$I_x = 2.79 \text{ A}$$

(iii) - Superposition Theorem:-

First removing the current source if making it an open circuit.

Re-drawing the circuit

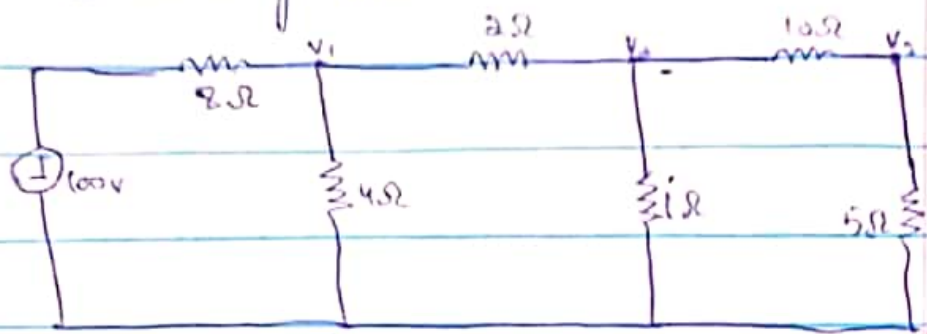

Applying KCL on node 1n:

$$-\frac{100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 4V_1 - 4V_2 + 2V_1}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Now:-

Applying KCL on node 2n:-

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

So,

$$-30V_1 + 53V_2 - 3V_3 = 0 \quad \text{--- (2)}$$

Again

Applying KCL on node 3

$$\frac{v_3 - v_1}{10} + \frac{v_3}{1} = 0$$

$$\frac{v_3 - v_2 + v_3}{10} = 0$$

$$= v_2 + 2v_3 = 0 \quad \text{--- (1)}$$

Now taking eq (1)

$$7v_1 - 4v_2 = 100$$

$$7v_1 = 100 + 4v_2$$

or

$$7v_1 = 4v_2 + 100$$

$$v_1 = \frac{4v_2 + 100}{7} \quad \text{--- (2)}$$

8

$$-v_2 + 3v_3 = 0$$

$$v_3 = \frac{1}{3}v_2 \quad \text{--- (3)}$$

By putting in eq (2)

$$-30(0.57v_2 + 14.28) - 4v_2 + 2(0.33v_2) = 0$$

$$-17.1v_2 - 428.4 - 4v_2 + 0.66v_2 = 0$$

$$20.44v_2 = 428.4$$

or

$$v_2 = \frac{428.4}{20.44}$$

$v_2 = 20.95$



Put  $v_a$  in eq (2)


$$v_1 = 2.31$$

$$\text{or } i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = \frac{23.26}{2}$$

$$i_1 = 11.63 \text{ A}$$

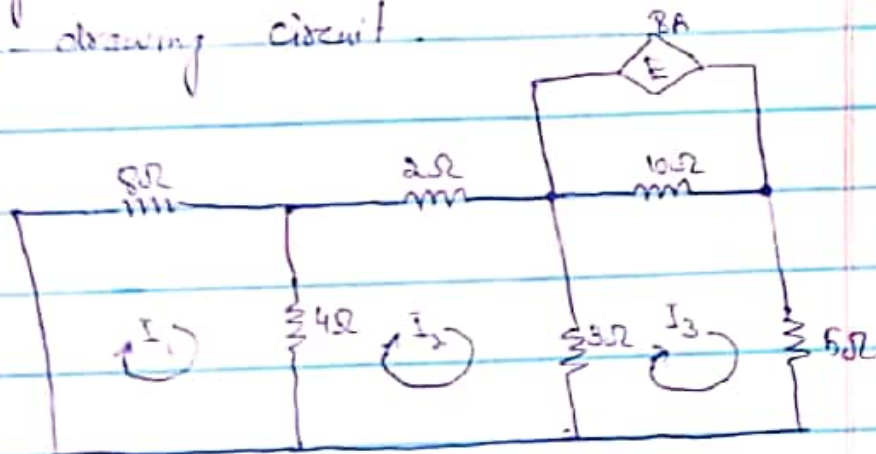Now recovering voltage source  $\rightarrow$   
making it short circuit.  
Re-drawing circuit.



$$i_4 = 8 \text{ A}$$

Apply KVL on loop 1

$$5i_1 + 4(i_1 - i_2) = 0$$

$$5i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Apply KVL on loop 2

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_3 = 0$$

$$-4i_1 + 4i_2 - 3i_3 = 0$$

$$-4i_1 + 4i_2 - 3i_3 = 0 \quad \text{--- (3)}$$

Now:

Applying KVL on Loop 3.

$$10i_2 + 5i_2 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking equation (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \quad \text{--- (a)}$$

Taking equation (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (b)}$$

$$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 12.33 = 0$$

$$i_2 = 1.354$$


Now:

$$i_x = i_1 + i_2$$

$$i_x = 1.44 + 1.35$$

$$i_x = 2.79 \text{ A}$$

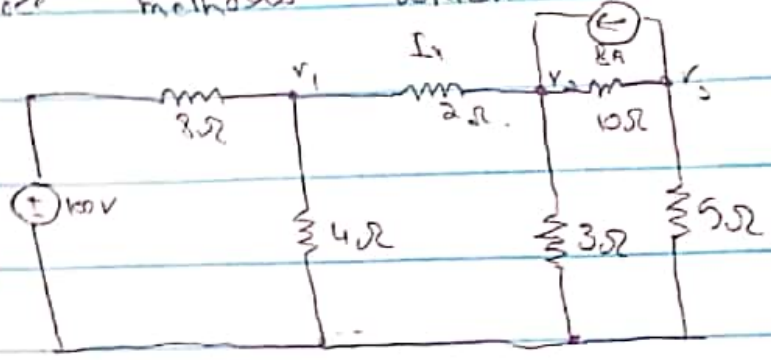(iv) - Compare the number of steps & degree of cosines of all the these methods which each other.



Applying KCL on node 1.

$$\frac{V_1 - 100}{3} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 - 100 + 2V_1 + 4V_1 - 4V_2 = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

now

Applying KCL on node 2.

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_2 - V_3}{18} = 0$$

$$30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3 = 0$$

Multiplying "60" o.p.s

$$-30V_1 + 53V_2 - 3V_3 = 0 \quad \text{--- (2)}$$

Now:

Applying KCL on node 3.

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$V_3 - V_2 + 2V_3 = -8$$

" Multiplying "10" o.B.s

$$10 \times \frac{V_3 - V_2 + 2V_3}{10} = -8 \times 10$$

$$-V_2 + 3V_3 = -80$$

Taking eq (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad (a)$$

Taking eq (2)

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad (b)$$

Putting (a) and (b) in eq (2)

$$-30(0.57V_2 + 14.29) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.2V_2 - 428.4 + 53V_2 - 0.99V_2 - 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

Putting in eq (5)

$$V_2 = \frac{4(20.31) + 100}{1}$$

$$V_2 = 25.84$$

or

$$i_x = \frac{V_1 - V_2}{2}$$

$$i_x = \frac{25.84 - 20.31}{2}$$


$$i_x = \frac{5.53}{2}$$

$$i_x = 2.79 \text{ Ams}$$




Question Number 2

Ans: - Figure:

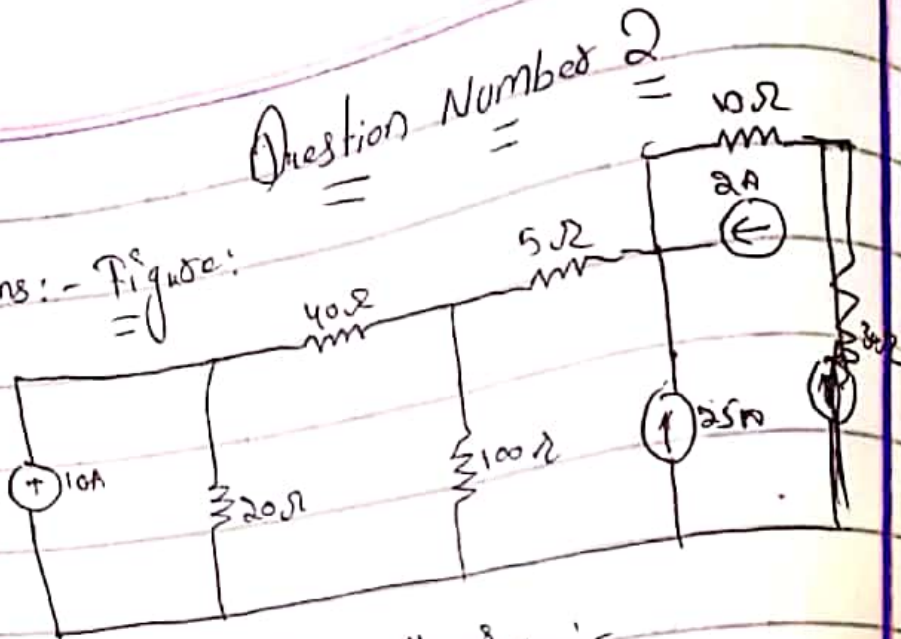


① Solving for the given :-

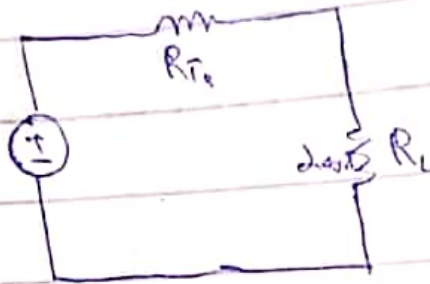

we will find  $R_{th}$  for which we will remove all the current source by short circuit the load resistor.

Redrawing the circuit

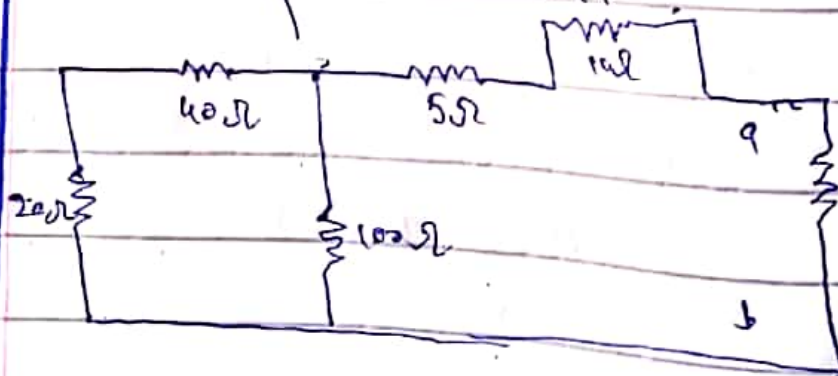

adding all resistor  
 $20 + 40 \parallel 100 \times 5 + 10$


$$60 \parallel 100 + 15$$

$$\frac{60 \times 100}{60 + 100} + 15$$

$$37.5 + 15$$

$$R_{TH} = 52.5$$

for finding  $I_{TH}$  apply  $10V$

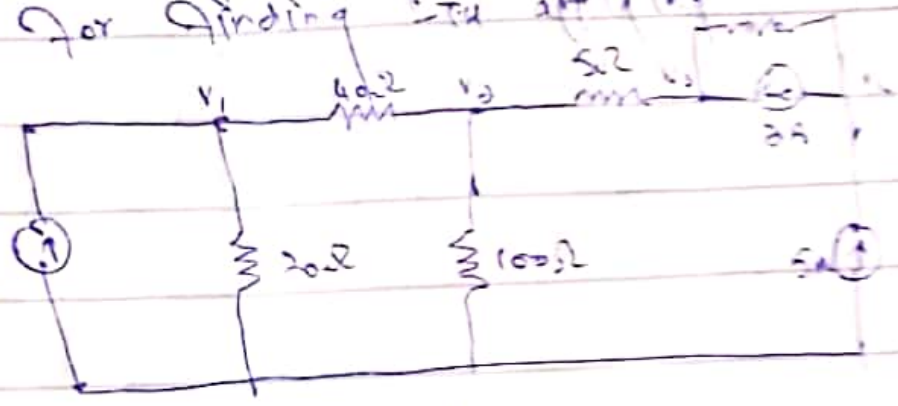

applying KCL on  $v_1$

$$\frac{v_1 - v_2}{40} + \frac{v_1}{20} = 10$$

$$\frac{v_1 - v_2 + 2v_1}{40} = 10$$

$$\frac{3v_1 - v_2}{40} = 10$$

$$3v_1 - v_2 = 400 \quad \text{--- (1)}$$

applying KCL on node 2.

$$\frac{v_2 - v_1}{40} + \frac{v_2}{100} + \frac{v_2 - v_3}{5}$$

$$\frac{50v_2 - 50v_1 + 20v_2 + 400v_2 - 400v_3}{2000}$$

$$-0.05v_1 + 0.035v_2 - 0.2v_3 = 0$$

$$-0.05v_1 + 0.035v_2 - 0.2v_3 = 0$$

applying KCL on node 3

$$\frac{v_3 - v_2}{5} + \frac{v_3 - v_4}{10} = 2.572$$

$$\frac{2v_3 - 2v_2 + v_3 - v_4}{10} = 4.5$$

$$-2v_2 + 3v_3 - v_4 = 45 \quad (3)$$

Applying KCL on node 4

$$\frac{v_4 - v_3}{100} = 5 - 2$$

$$v_4 - v_3 = 30 \quad (4)$$

Solving them.

$$v_1 = 27.5$$

$$v_2 = 124.9$$

$$v_3 = -87.5$$


$$v_4 = -57.5$$



$$I_{rx} = \frac{5.1}{152.5 + 200}$$

$$I_{rx} = 0.02$$

(ii) For Norton Theorem :-

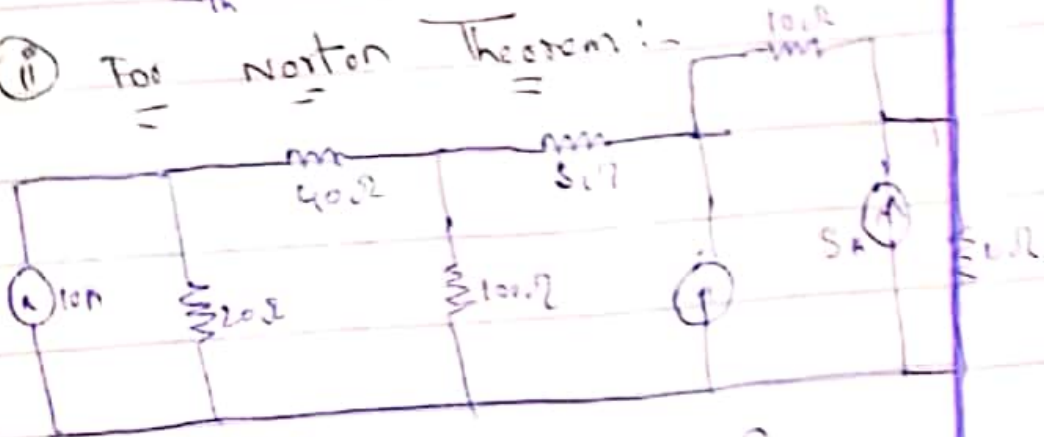

For  $R_N$  will be the same

$$R_N = R_{Th}$$

$$R_N = 52.5$$

$$\text{Find } I_n = \frac{V_{Th}}{R_N}$$

$$I_n = 0.09$$

As the circuit are same

So, we find it directly.

(iii) Using Thevenin for finding Power.

We know that

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$= \left( \frac{5.1}{52.5 + 200} \right)^2 \cdot 200$$


$$P = 0.0844$$

(17)

Date: / /
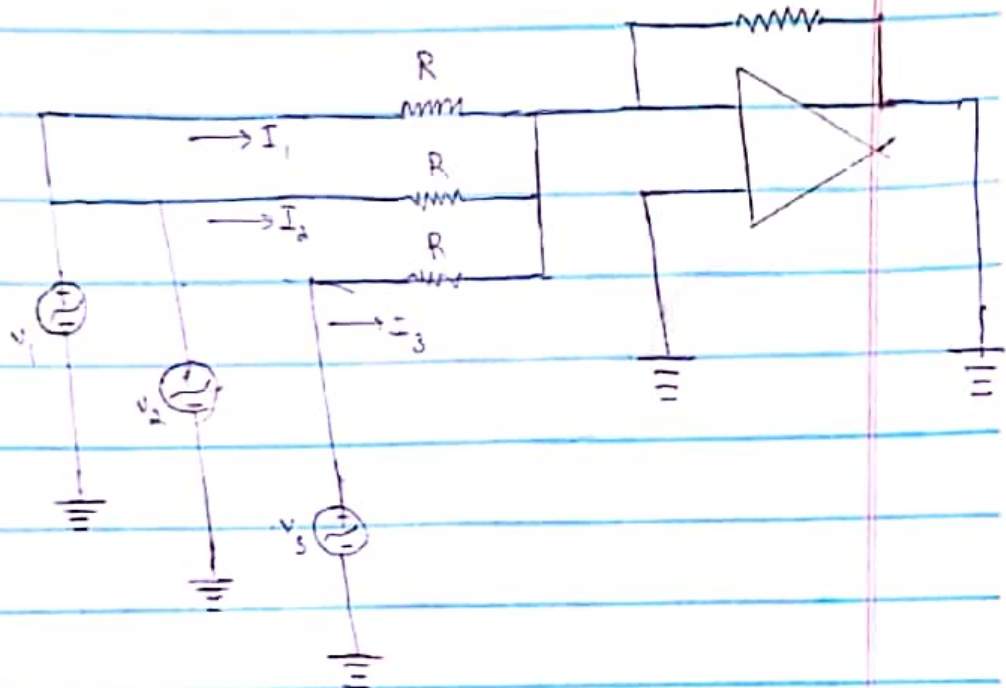
### Question Number 3

Obtain an expression for  $V_{out}$  in terms of  $V_1$ ,  $V_2$  and  $V_3$  for amp circuit also known as a summing amplifier.



Solution :-

The goal is to obtain an expression for  $V_{out}$  in terms of the inputs ( $V_1$ ,  $V_2$  and  $V_3$ )

Since :-

No, current can flow into the inverting input terminal.

we can write

$$i = i_1 + i_2 + i_3$$

Therefore, we can write this following equation at the node labeled  $V_a$

$$0 = \frac{V_a - V_{out}}{R_f} + \frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - V_3}{R}$$

As this equation contains both  $V_{out}$  and the input voltages but unfortunately it also contains the nodal voltage  $V_a$

Now:

we need to write an additional equation that related  $V_a$  to  $V_{out}$ , the input voltages,  $R_f$  and  $R$ .

At this point we have not yet used ideal amp rule 2 and that we will almost certainly require the use of both rules when analyzing an op-amp circuit.

Thus,

$$\text{Since } V_a = V_b = 0$$

we can write following.

(9)

Principles of Electronics

Unit 1

$$0 = \frac{V_{out}}{R_2} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

by Re-arranging  
we obtain the following  
expression for  $V_{out}$

$$V_{out} = -\frac{R_2}{R} (V_1 + V_2 + V_3)$$

In this case, where  $V_2 = V_3 = 0$   
we see that our result agrees,  
which was derived for essentially  
the same circuit.

