



Name: Naveed Ali


ID No. 16753

Subject: Electronic Circuit Design.


Darlington connection for multistage amplifier's.

A very popular connection of two bipolar Junction transistors for operation as one "Superbeta" transistor is Darlington connection. The main feature of darlington connection is that the composite transistor acts as a signal single unit with a current gain that is the product of current gain of the individual transistor. if the connection is made using two separate transistor having current gain of  $\beta_1$  and  $\beta_2$  the Darlington connection provides a current gain of  $\beta_0 \equiv \beta_1 \beta_2$ .



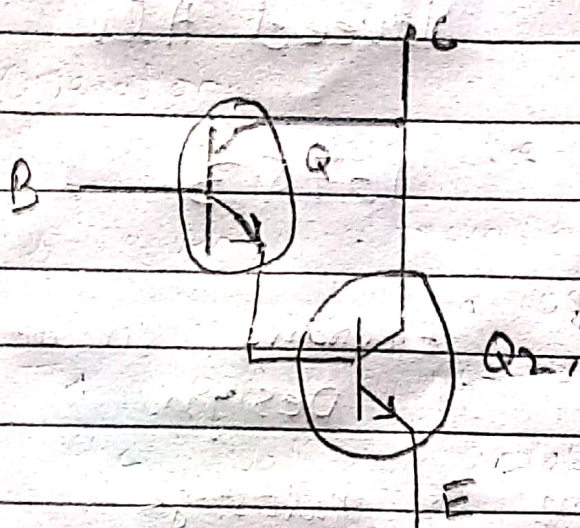

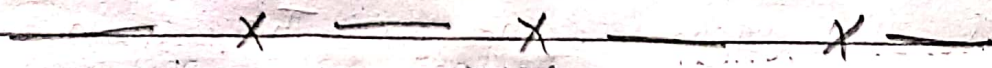Circuit diagram of darlington connection of multistage Amplifier's.



Q2:


Colpitts Oscillator:

A colpitts oscillators look like the Hartley oscillator but the inductors and capacitors are replaced with each other.

Construction.

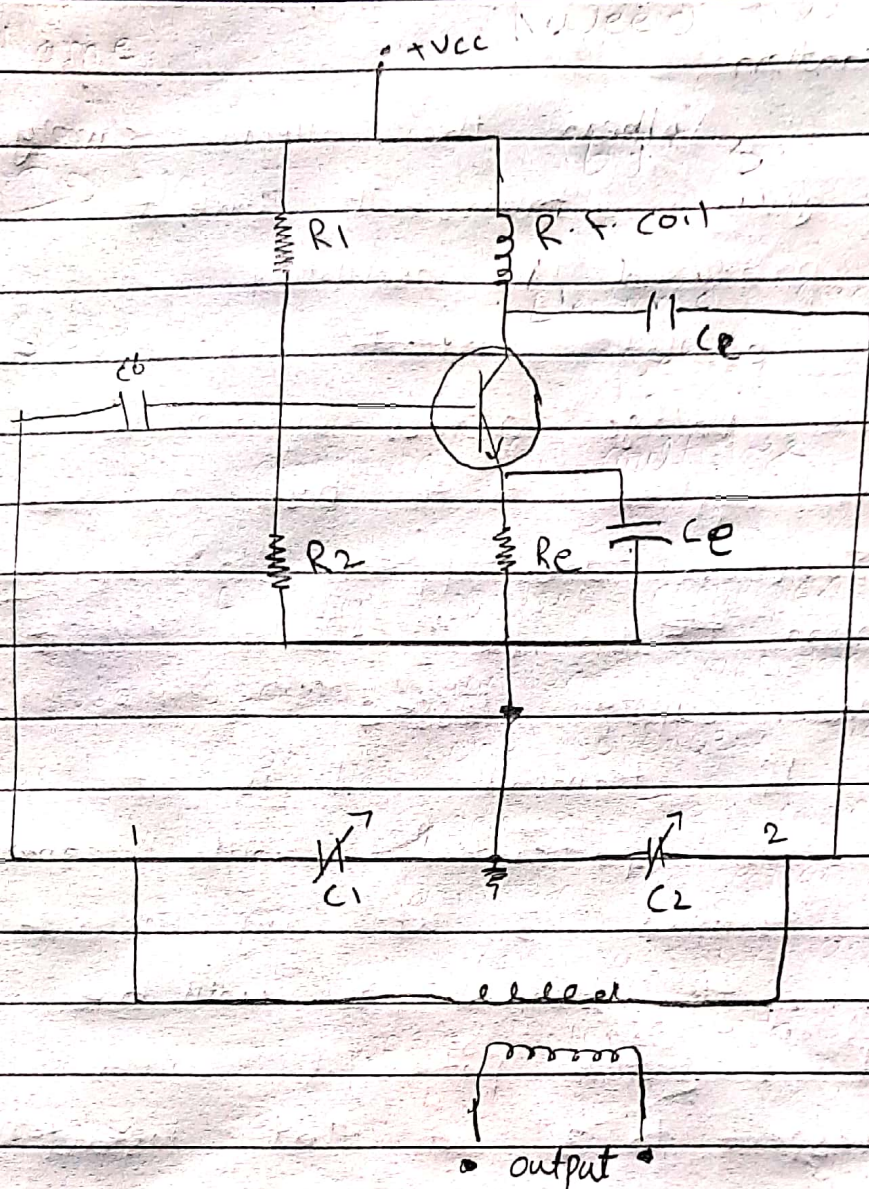Let us first take a look of circuit diagram of colpitts oscillator.





The resistor  $R_1$ ,  $R_2$  &  $R_e$  provide necessary bias condition for the circuit. The capacitor  $C_e$  provides a.c ground thereby providing an signal degeneration.

The capacitor  $C_e$  and  $C_b$  are employed to block d.c. and provide an ac path.



Operation.

When the collector supply is given, a transient current is produced in oscillator.

The oscillator current produce A.C voltage across  $C_1$ , which are applied to the base emitter Junction and appear in amplified form ~~the~~ in the collector circuit and supply losses.

If terminal 1 is at positive potential with respect to terminal 3 at any instant then the terminal 2 will be at negative potential with respect to 3 at that instant because terminal 3 is ground.

Therefore, points 1 and 2 are out of phase by  $180^\circ$ .

Frequency.

The equation for frequency of colpitts oscillator is given as.



$$f = \frac{1}{2\pi \sqrt{LC_T}}$$

$$f = \frac{1}{2\pi \sqrt{LC_T}}$$

$C_T$  is the total capacitance of  $C_1$  and  $C_2$  connected in series.

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

~~$$LC_T = LC_1 + LC_2$$~~


Hartley oscillators.

A very popular local oscillator circuit that is mostly used in Radio receivers in the Hartley oscillator's.

The construction & operation of Hartley oscillators are given below.



## Construction

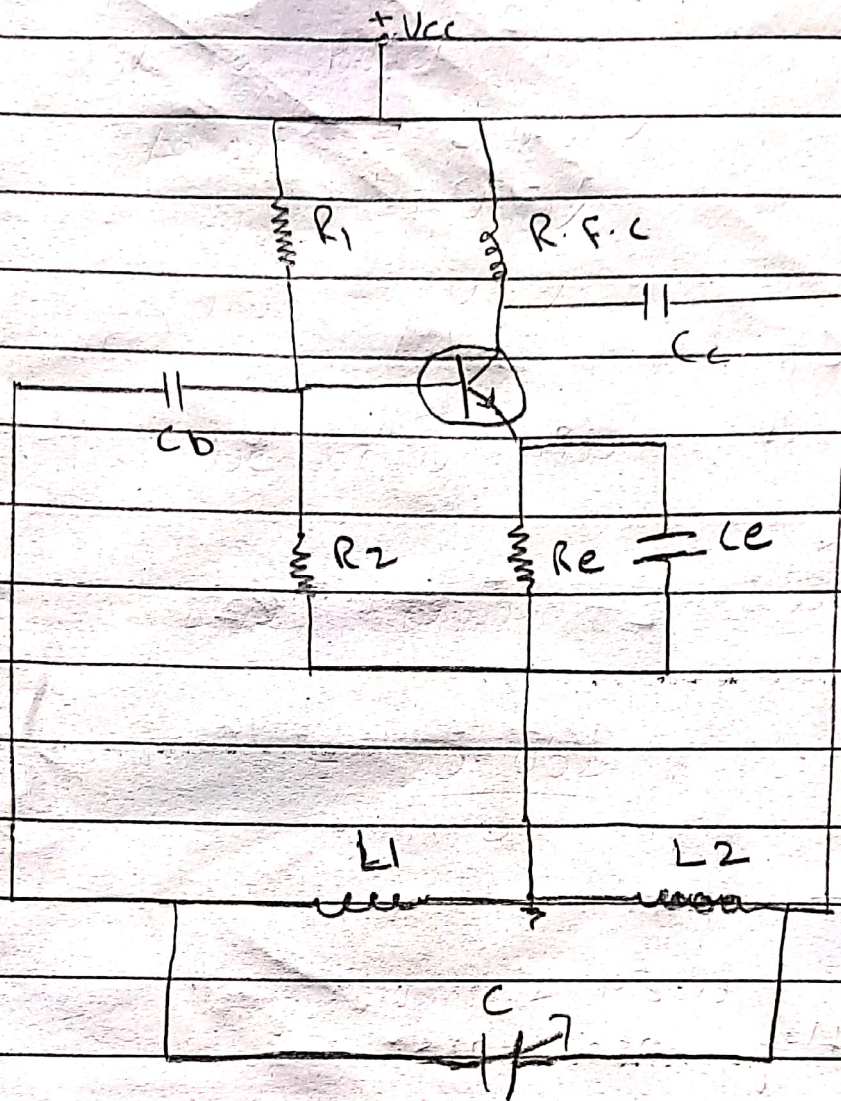

In this circuit diagram of a Hartley oscillator, the resistors  $R_1$ ,  $R_2$  and  $R_e$  provide necessary bias condition for the circuit.

The capacitor  $C_e$  provides ac ground thereby providing any signal deformation.

The capacitor  $C_c$  and  $C_b$  are employed to block dc and



provide an ac path.

Operation.

When the collector supply is given a transient current produced in oscillator. The oscillator's ~~current~~ circuit produces an ac voltage across  $L_T$ . The auto-transformer made by the inductive coupling  $L_1$  and  $L_2$  help in determining the frequency.

Frequency.

The equation of frequency of Hartley oscillator is given.

$$f = \frac{1}{2\pi\sqrt{L_T C}}$$

$$f = \frac{1}{2\pi\sqrt{L_T C}}$$

$$L_T = L_1 + L_2 + 2M$$

$$L_T = -L_1 + L_2 + 2M.$$

— x — x — x — x



Q1(b)

Sol<sup>n</sup> Given data.

$$\Delta V_{out} = 0.062V$$

$$\Delta V_{in} = 4.5V$$

$$V_{out} = 40V$$

As we know that

$$\text{Line Regulation} = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100$$

$$= \frac{0.062}{4.5} \times 100$$

$$\text{Line Regulation} = 1.3\%$$


Now

$$\text{line Regulation} = \left( \frac{\Delta V_{out}/V_{out}}{\Delta V_{in}} \right) \times 100\%$$

$$= \left( \frac{0.062}{40/4.5} \right) \times 100$$

$$\text{Line Regulation} = 0.0344\%$$

$$= \boxed{0.0344\% / V}$$

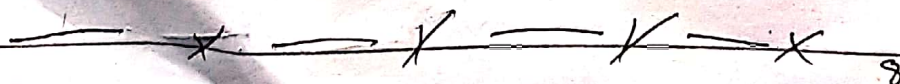



Q3. (A) ...


## Class B Amplifiers.

Class B Amplifier were invented as a solution to the efficiency and heating problems associated with previous Class A Amplifier. The basic class B amplifier uses two complimentary transistor, either bipolar or FET for each half of the waveform with its output stage configured in a "push-pull" type arrangement. So, that each transistor device amplifies only half of the output waveform.


In the class B amplifier, there is no DC bias current as its quiescent current is zero. So that DC power is small & therefore its efficiency is much higher than that of the class A amplifier. However the price paid for the improvement in the efficiency is the linearity of the switching device.



# Circuit Diagram

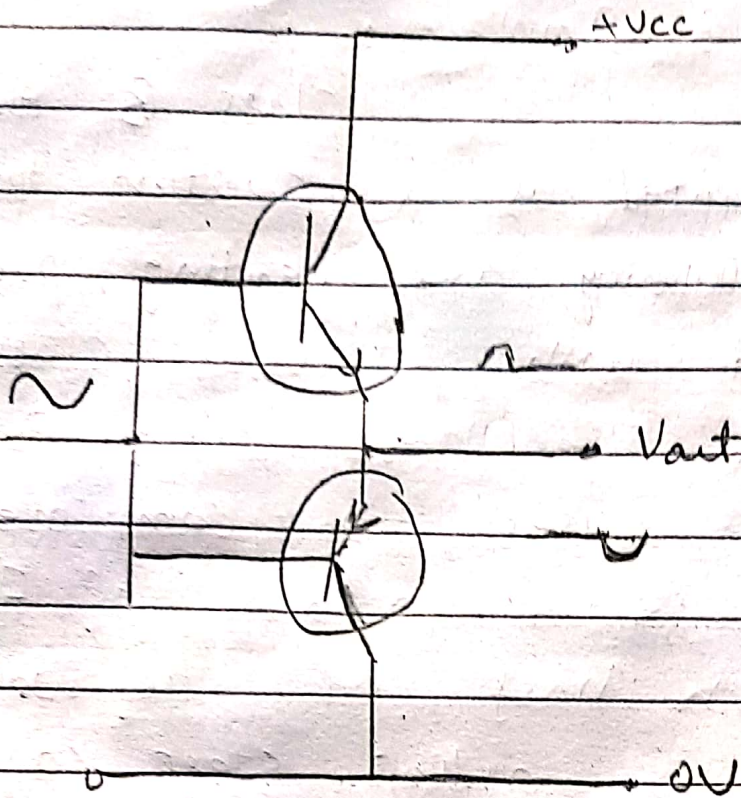

## Operating Curve.

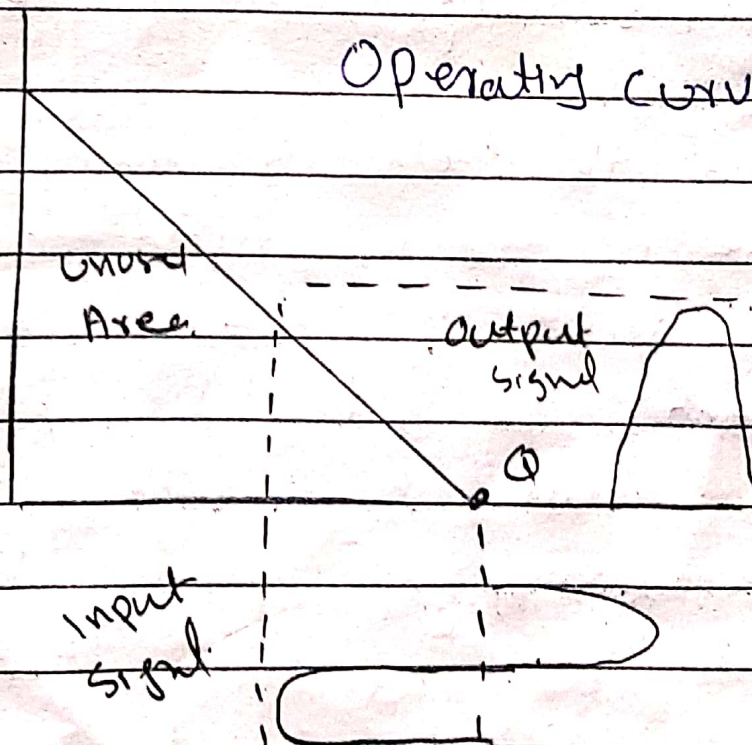



When the input signal goes positive. The positive biased transistor conducts while the negative transistor is switched off.

When the input signal goes negative. The positive transistor switches 'off' while negative biased transistor turns 'ON' and conducts the negative portion of the signal.

Thus the transistor conducts only half of the time.

either positive or negative half cycle of the input signal.

Q3

(b)

Different types of voltage regulator.

Voltage regulators are integrated circuits designed to regulate the voltage at their input to constant, fixed voltage at their output, ~~in~~ irrespective of changes



in load current or input voltage.

Types of Regulator:

There are two types of voltage regulators

1. Linear Voltage Regulators
2. Switching Voltage Regulators

1. Linear <sup>Voltage</sup> Voltage Regulator.

Linear voltage regulator use the principles of voltage divider to transform the voltage at their input to the desired voltage at their output.

Typical implementation of Linear voltage regulator involve the use of FET as on side of voltage divider with feedback loop connected to the gate transistor.



choosing it as required to ensure consistency in the output voltage.

While this use of transistor as resistors help simplify the design & implementation of linear regulators, its contribution largely to the inefficiency associated with the regulator's.

## 2. Switching Voltage regulator's.

Although they feature a more complex design & require more companion components to function, switching voltage regulator are super-efficient regulators used in scenarios where power loss, as in the linear regulators, cannot be condoned.

The voltage regulation mechanism in ~~switch~~ switching voltage regulator, involves rapidly switching an element connected in series with an



energy storage component (Capacitor or Inductor) to periodically intercept the flow of transform the voltage from one value to other.

Unlike in linear voltage regulator, the switching element is either in a fully conducting or switched-off state. It dissipates no power and allows the regulator to attain high level of efficiency beyond that of the linear regulator's.

— x — x — x —

Q5. Difference between Low pass & high pass filter.

(a)

Low pass filter's.


①

LPF circuit

allows the frequency underneath cut off frequency for flowing through it.



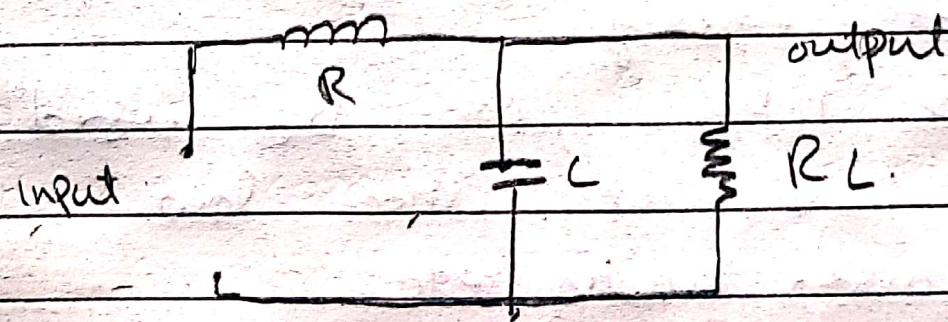- \* It can be built with a resistor which is followed by a capacitor.
- \* It is important in eliminating the aliasing effect.
- \*  $f_c$  is lesser than the cut-off frequency.
- \* The LPF can be used as anti-aliasing filter in communication circuits.




Circuit diagram of Low Pass Filter.


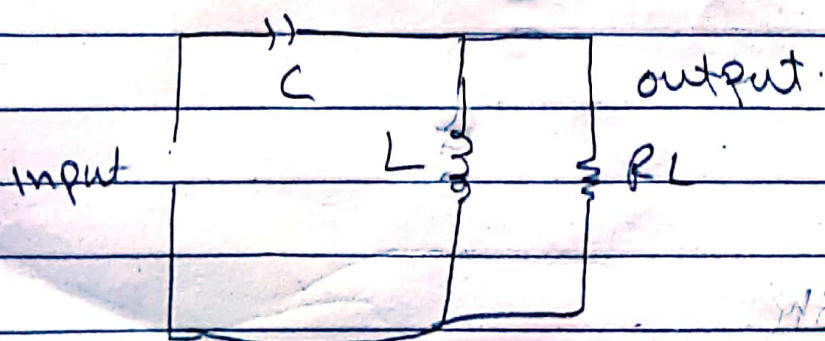
## High Pass Filter.

- \* HPF circuit allows the frequencies over cut-off frequency for flowing through it.
- \* It can be built with a capacitor which is followed by a resistor.
- \* It is important whenever the distortion occurs because of low frequency signal like noise is ~~not~~ to be detected.
- \* It is high than cut off frequency.
- \* The HPF can be used in amplifier like low noise, audio, etc.



Circuit diagram of high pass filter.



Q5  
(b)

Active filter's.

- \* Active filters need outside source for their operation.
- \* Active filters have capability of amplifying filter output.
- \* Active filters are costlier than passive filter due to extra added active element & external power required to operate an active element.
- \* Active filter have bandwidth limitation due to involvement of active element, which operate properly in only specific frequency ranges.

Passive filter's

- \* Passive filter's do not need any outside source for their operation.
- \* Passive filters consume the power of input signal & cannot amplify the output signal.
- \* Passive filter are designed using capacitor's resistor, & inductors.



Due to the involvement of fewer elements passive filter are less complex & easy to design as compared to equivalent active filters.

— X — X — X — X

Q4. Working of Flash ADC.

The flash ADC also called parallel ADC, is very easy to understand. Its work by comparing the input voltage.

i.e. the analog signal - to a reference voltage, which would be the maximum value achieved by the analog signal. for example.

if the reference voltage is of 5 volts this means means that the peak of analog signal would be 5 volts.

on an 8-bit ADC when the input signal reached 5 volts we would find



a 255 (11111111) value on the ADC output. i.e. the maximum value possible.

Then the voltage reference is lowered through a resistor network and other components added. So the input voltage (analog signal) can be compared to other values.

19.

