

Date \_\_\_\_\_

Name ≠ Asad Shoab Khalid.

ID ≠ 13095

Assignment ≠ 1

Subject ≠ Electronic Circuit Device.

Teacher ≠ Engr. Mujtaba Ihsan.

SMH<sub>Notes</sub>




## Question # 1

Answer :-
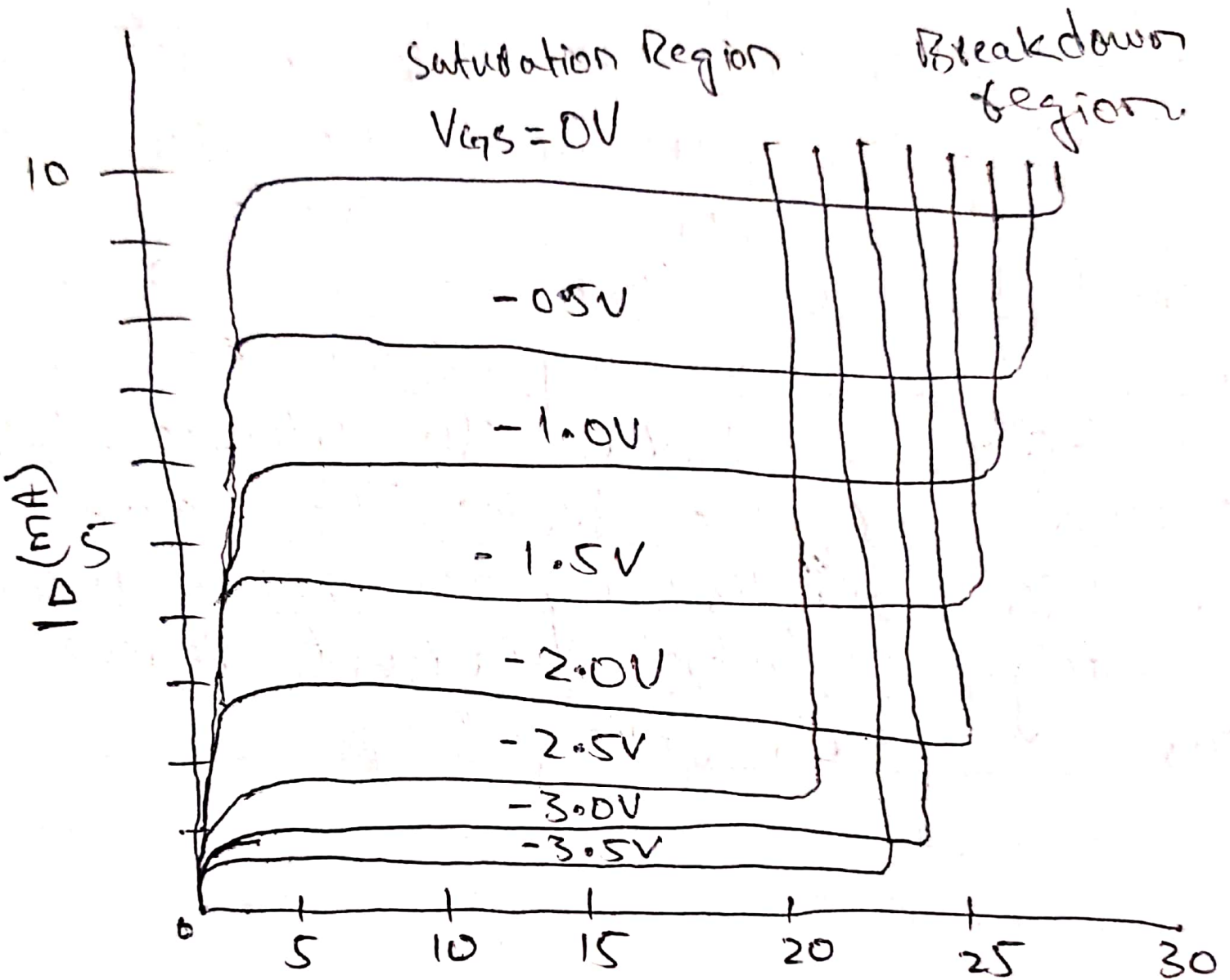
## \* JFET characteristic Curve :-

You can see that for a given value of Gate voltage, the current is very nearly constant over a wide range of source-to-drain voltages. The control element for the JFET comes from depletion of charge carriers from the  $n$ -channel. When the gate is made more negative, it depletes the majority carriers from a larger depletion zone around the gate. This reduces the current flow for a given value of source-to-drain voltage modulates the current flow through the device.

The transfer characteristic for the JFET is used for visualizing the gain from the device & identifying the region of linearity. The gain is proportional to the slope of transfer curve. The current value  $I_{DSS}$  represents the value of when the Gate is shorted to ground, the maximum current for the device. The value will be part of data supplied by the manufacturer. The Gate voltage at which current reaches zero is called the "pinch voltage"  $V_p$ .





## Question # 2.

Answer:-

\* Practical OP Amp characteristics:-

The Practical OP Amp characteristics can be approximated closely enough, for many practical op-amp. But basically the OP Amp characteristics are little bit different than the ideal op-amp characteristics.

The various characteristics of Practical OP-Amp are below.

(i). Open loop gain:- It is the voltage gain of the op-amp when no feedback is practically it is several thousands.

(ii). Input Impedance:- It is finite & typically greater than  $1\text{ M}\Omega$ . But using FETs for the input stage it can be increased upto several hundred M.

(iii) Output Impedance:- It is typically few hundred ohms. with the help. of negative feedback, it can be reduced to a very small value like 1 or 2 ohms.

(iv) Bandwidth:- The bandwidth of Practical op-amp in open loop configuration is very small. By application of negative feedback, it can be increased to a desired value.

(v) Input offset voltage:- When ever both the IP terminals of the op-amp are grounded, ideally the output voltage should be zero. However, in this condition the practical op-amp shows a small non zero input output voltage. To make this output voltage zero, a small voltage in millivolts

SMK1205



is required to be applied to one of the input such as voltage make the output exactly zero. The d.c voltage, which make the output voltage zero. When the other terminal is grounded is called input offset voltage. denoted as  $V_{ios}$ .

(vi) Input current bias:- For ideal op-amp, no current flows into the input the practical op-amps have some input currents current are very small of the order of  $10^{-6}A$  to  $10^{-16}A$ .  
Mathematically it is expressed as,

$$I_b = \frac{|I_{b1}| + |I_{b2}|}{2}$$

(g) Input offset current:- The difference in magnitudes of  $I_{b1}$  &  $I_{b2}$  is called I/P offset current and is denoted as  $I_Q$  Thus,

$$I_{ios} = |I_{b1} - I_{b2}|$$

The magnitude of this current is very small. of the order of 20 to 60 nA. It is measured under the condition of that input voltage to op-amp is zero.



## Question #3.

Answer:-

~~Answer:-~~

\* To find:

output voltage for summing amplifier.

\* Solution:-

According to Ohm's law.  $V = IR$ 

$$V_1 = IR_1$$

Therefore

$$I_1 = V_1 / R_1$$

$$I_2 = V_2 / R_2$$

$$I_3 = V_3 / R_3$$

Put these values in eq. 3.

$$V_{out} = - \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] R_F \rightarrow \text{eq. (4)}$$

$$V_{out} = - \left[ \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R} \right] R$$

$$V_{out} = - [V_1 + V_2 + V_3] \rightarrow \text{eq. (5)}$$

$$V_{out} = - [V_1 + V_2 + V_3 + \dots + V_n]$$

So putting the value in eq.

$$V_{out} = - [V_1/R + V_2/R + V_3/R] R$$

$$V_{out} = [0.2/6 + 0.5/6 + 2/6] 6$$

$$V_{out} = 2.116$$



Question # 4.

Part (a).

Answers:-

- (i) Class C amplifiers are never used for audio circuits
- (ii) They are commonly used in RF circuit.
- (iii) class C amplifier operate the O/P transistors in a state that results in tremendous distortion
- (iv) However the RF circuit where class C amplifier are used employ filtering so that the final signal is completely acceptable
- (v) Class C amplifiers are quite efficient.

Reasons:- class-C.

output devices conduct for less than 180 degrees (180 to 150 degree)- Radio frequencies only - cannot be used for audio. This is the sound heard when one of the output devices goes open circuit in an audio amp!



## Question # 4.

Part (b).

Answers-

(i) Amplifiers:- It is an electronic device that increases or boosts voltage, current or power of a signal.

Applications of Amplifiers:- hearing aids, music system, Audio Amplifier, operational Amplifier.

(ii) Rectifiers:- The purpose of the rectifier section is to convert the incoming AC signal from a transformer or other AC power source to some form of pulsating DC.

Applications of Rectifiers:- The primary application of rectifier is to derive DC power from an AC supply. Rectifiers are used inside the power supplies of virtually all electronic equipment. AC/DC power supplies may be broadly divided into linear power supplies & switched-mode power supplies.