

Khalid Khan


(1)

13880

Q(1)

Part(A)

solution

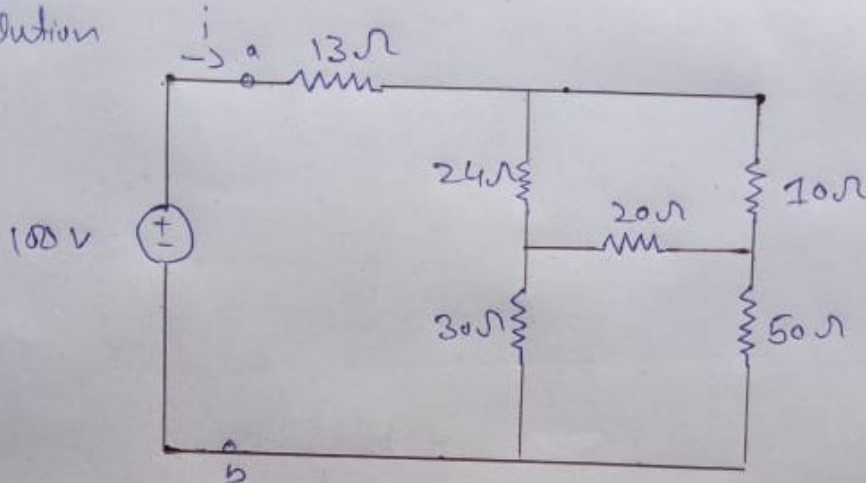


we first find the equivalent

resistance, R . we convert the delta

sub-network to a wye connected

form

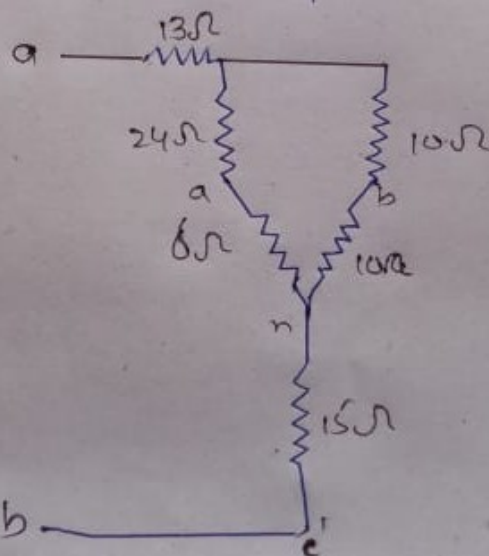

Khalid Khan

(2)

13880

$$R_{a'n} = 20 \times 30 / [20 + 30 + 50] = 6 \text{ ohms}$$

$$R_{b'n} = 20 \times 50 / 100 = 10 \text{ ohms}$$


$$R_{c'n} = 30 \times 50 / 100 = 15 \text{ ohms}$$

$$\begin{aligned} \text{Thus, } R_{ab} &= 13 + (24 + 6) \parallel (10 + 10) + 5 = 28 \\ &+ 30 \times 20 / (30 + 20) = 40 \text{ (ohms)} \end{aligned}$$

$$I_0 = 100 / R_{ab} = 100 / 40 = 2.5 \text{ amps}$$

Q(1)

Part (B)

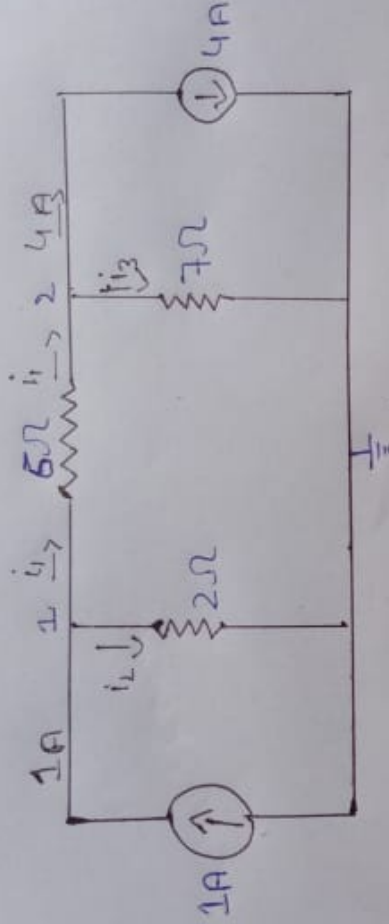

solution:- Now I finding the node voltages in the circuit

So At Node 1,

$$1 = i_1 + i_2 \longrightarrow 1 = \frac{V_1 - V_2}{6} + \frac{V_1 - 0}{2}$$

$$6 = 4V_1 - V_2 \quad (1)$$

At node 2,

$$i_1 = 4 + i_3 \longrightarrow \frac{V_1 - V_2}{6} = 4 + \frac{V_2 - 0}{7}$$

$$168 = 7V_1 - 13V_2 \quad (2)$$

solving (1) & (2) gives $V_1 = -2V$, $V_2 = -14V$

Khalid Khan (4)

13880

Q2)

(9)

Ans: Supernode is a supernode is a

--- Theoretical construct

That can be used to solve a ckt.

This is done by viewing a voltage

source on a wire as a point

source voltage in relation to

other point voltage located at

various nodes in the ckt. relative

to ground node assigned a zero

or negative charge.

P.T.O

Khalid Khan (S)

13880

Properties of Supernode

=> Always The difference b/w the voltage of two non reference

nodes is known at supernode

A supernode requires application

of both KCL & KVL to solve

it. Any element can be

connected in parallel with the

voltage source forming the

Supernode.


Khalid Khan (6)

13880

Q22)

(B)

Solution

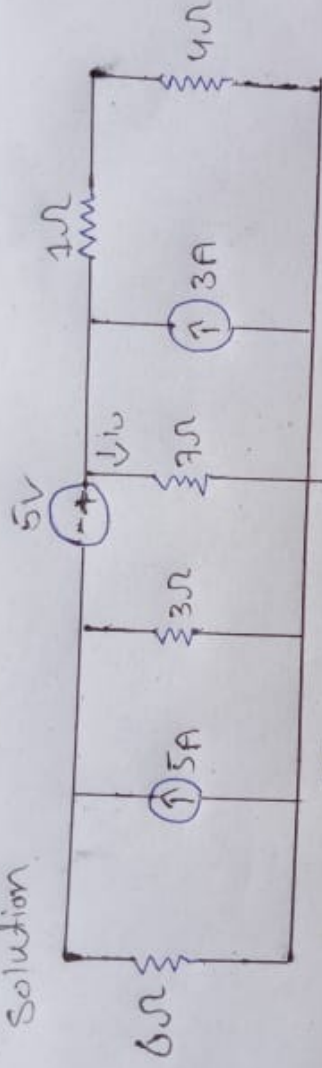

Combining the $6\text{-}\Omega$ & $3\text{-}\Omega$ resistors in

Parallel gives $(6 \times 3) / (6 + 3) = 2\text{ }\Omega$

Adding the $1\text{-}\Omega$ and $4\text{-}\Omega$ resistor

in series gives $1 + 4 = 5\text{ }\Omega$

Transforming the left current source

in parallel with $2\text{-}\Omega$ resistor gives


the equivalent circuit

P.T.O.

Khatid


(7)

13880

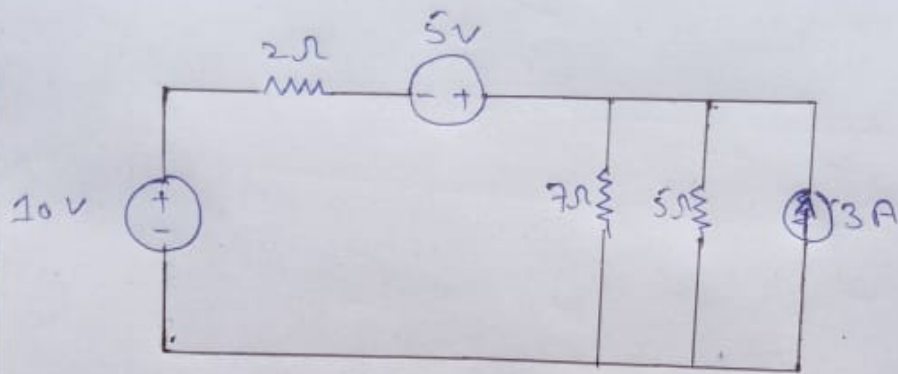

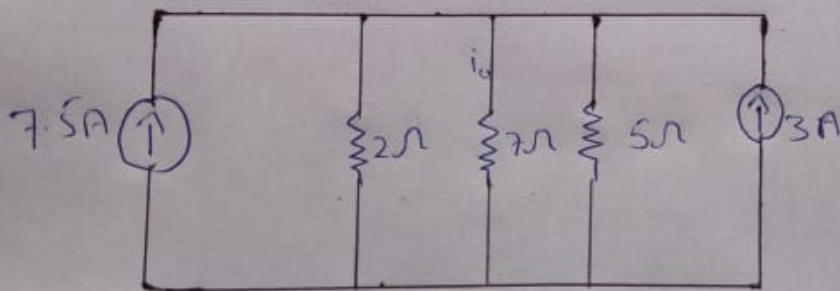(a)
Adding the 10-v and 5-v voltage sources give a 15-v voltage source


Transforming the 15-v voltage source in series with the 2-Ω resistor gives the equivalent circuit.



(b)
Combining the two current sources and the 2-Ω and 5-Ω resistors leads to the circuit (P.T.O.)

Khalid Khan (8)

13880

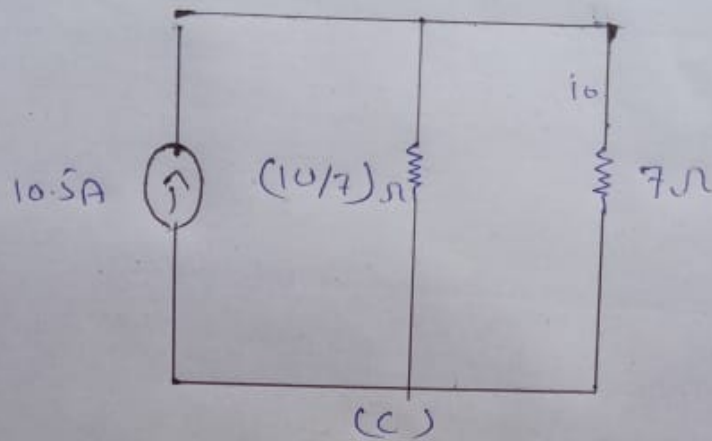

using current division

$$i_o = \frac{\frac{10}{7}}{\frac{10}{7} + 7} (10.5) = 1.78A$$

Khalid Khan


(Q1)

13880


Q(3)

(A)

Solution

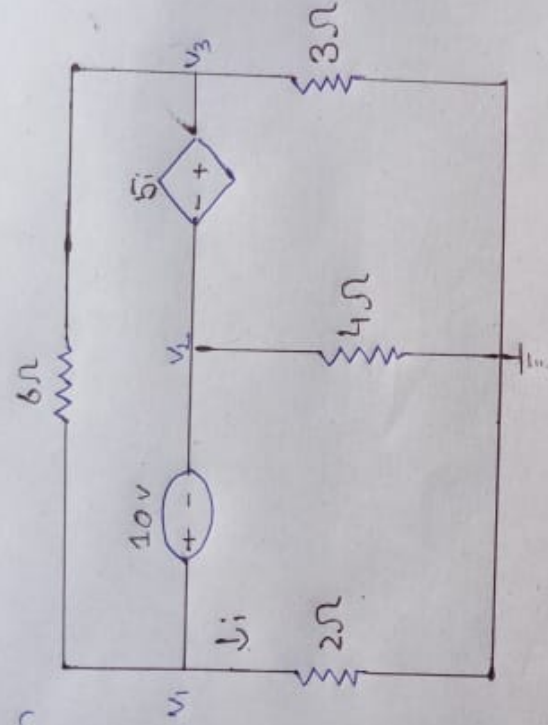

Now we apply KCL

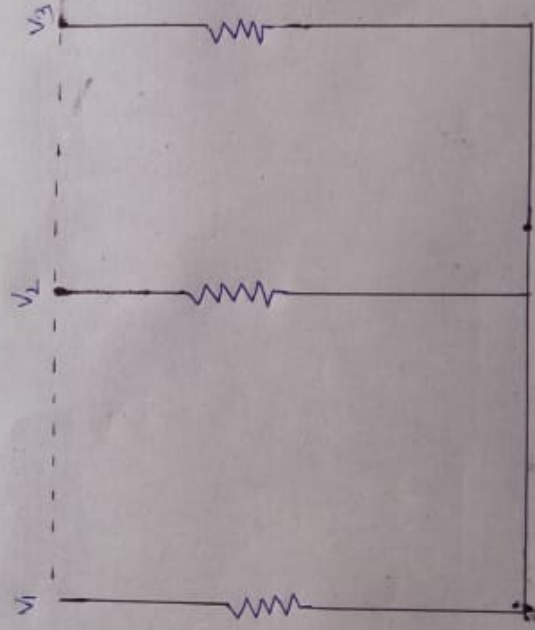

$$\frac{v_1}{2} + \frac{v_2}{4} + \frac{v_3}{3} = 0 \rightarrow 6v_1 + 3v_2 + 4v_3 = 0$$


P.T.O

Khalid Khan

(10)

13880

Now we apply KVL

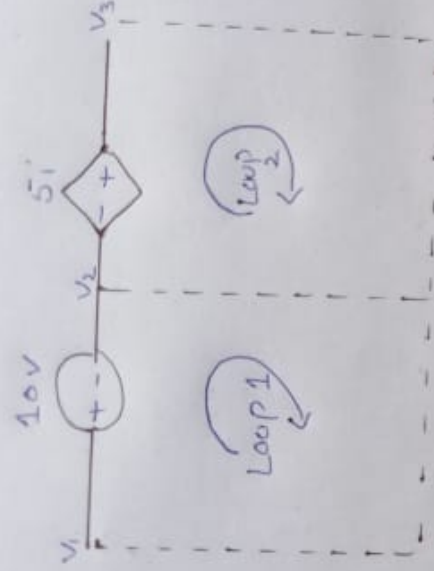

Loop 1

$$-V_1 + 10 + V_2 = 0$$

$$\rightarrow V_1 = V_2 + 10 \quad (2)$$

Loop 2

$$-V_2 - 5i + V_3 = 0$$

$$\rightarrow V_3 = V_2 + 5i \quad (3)$$

Solving (1) to (3) we obtain

$$V_1 = 3.043V, \quad V_2 = -6.956V$$


$$V_3 = 652.2mV$$

Khalid Khan (11)

13880

(B)

Solution

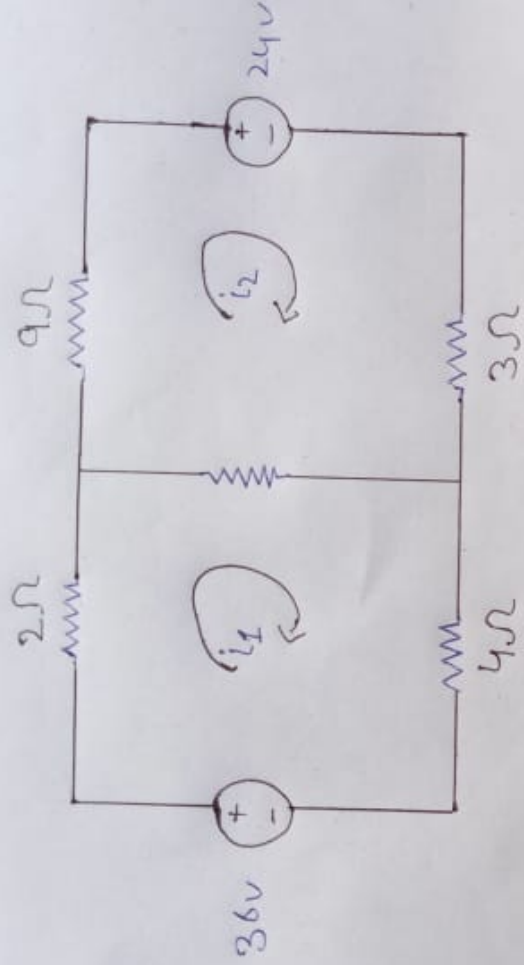

Now we apply KVL

$$-36 + 18i_1 - 12i_2 = 0$$

$$\text{Mesh 1} \quad 3i_1 - 2i_2 = 6 \quad (1)$$

$$24 + 24i_2 - 12i_1 = 0$$

$$\text{Mesh 2} \quad -3i_1 + 6i_2 = -6 \quad (2)$$

From (1) and (2) we get

$$i_1 = 2 \text{ A} \quad i_2 = 0 \text{ A}$$


Khalid Khan

(12)

13880

Q(4)


(A)

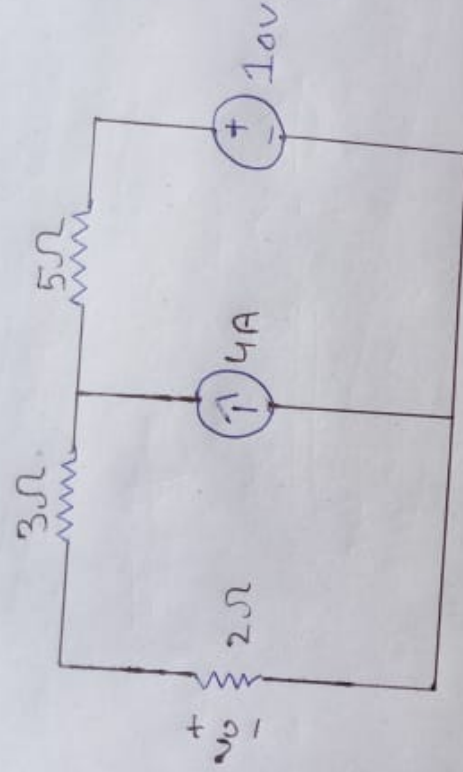

Solution \Rightarrow

$$\text{Let } v_0 = v_1 + v_2$$

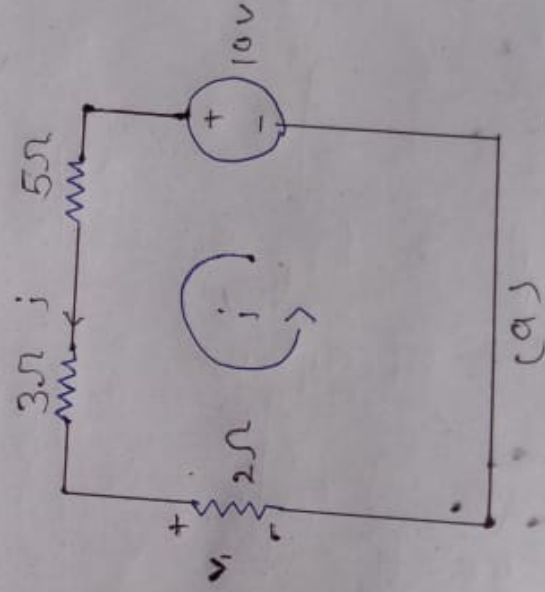where v_1 and v_2 are contribution to the 10V and 4A sources respectively



P.T.O

Khalid Khan

(13)

13880


Apply Ohm's Law

To get V_1 consider the circuit

$$(2 + 3 + 5)i = 10$$

$$i = 10 / (10) = 1A$$

$$V_1 = 2i = 2V$$

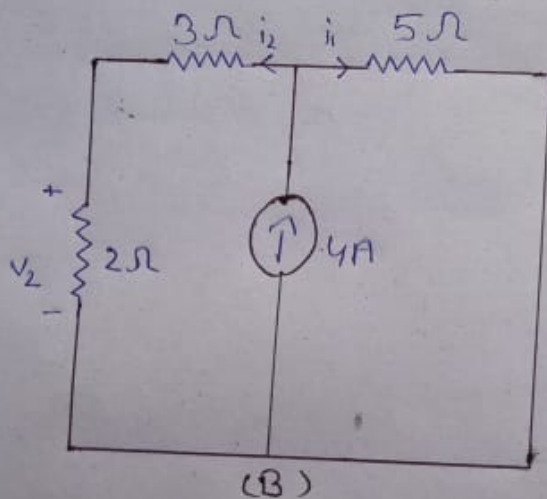

To get V_2 consider the circuit

$$i_1 = i_2 = 2A, \quad V_2 = 2i_2 = 4V$$

Thus

$$V = V_1 + V_2 = 2 + 4 = 6V$$

Khanid Khan

(14)

13880

(B3)

Thevenin's Theorem \Rightarrow

// // //

\Rightarrow Any linear circuit containing several voltages and resistance can be replaced by just one single

voltage in series with a single resistance connected across the load. in other words

it is possible to simplify any electrical circuit. no matter how complex, to an equivalent

Two Terminal circuit with just a single constant voltage source in series with a resistance or impedance.

Knaid Khan

(15)

13880

Thevenin's theorem is especially useful in the circuit analysis of power or battery systems Σ other inter connected resistive circuit where it will have an effect on the adjoining part of the circuit.


Khalid Khan

(16)

13880

Q5)

(A)

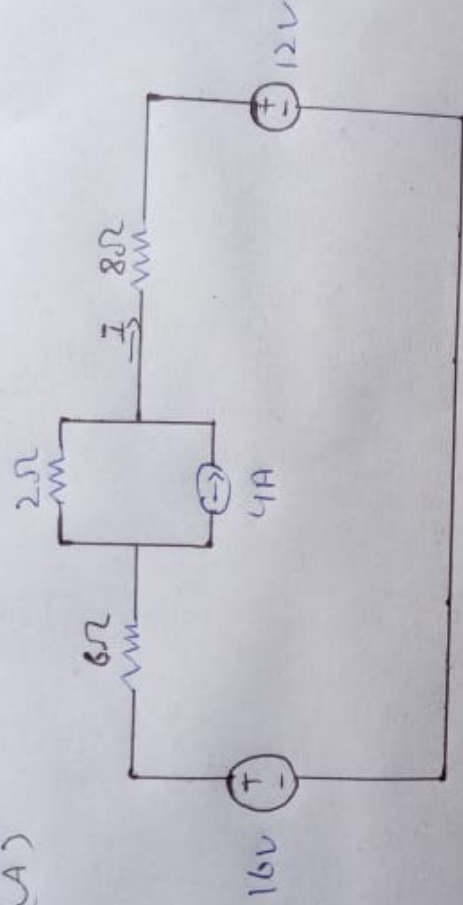


Solution

$$\text{Let } i = i_1 + i_2 + i_3$$

where i_1 , i_2 and i_3 are contribution

due to 16V, 4A, 12V source

respectively

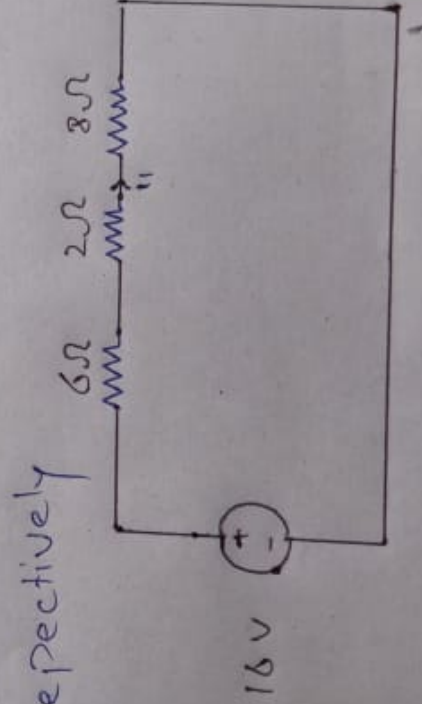

Apply Ohm's Law

For i_2


$$i_2 = \frac{16}{6+2+8} = 1A$$

P.T.O

Khalid Khan

(17)

13880

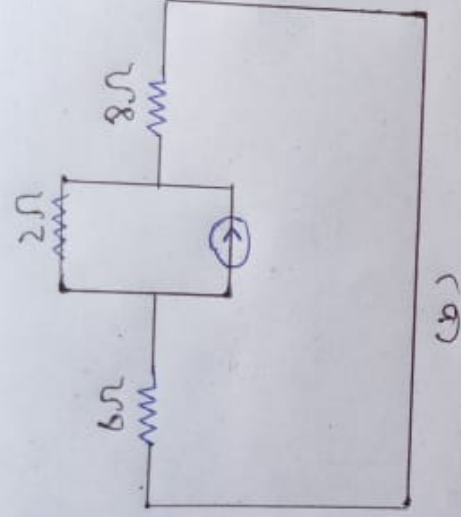

Apply Current Division

For i_2

By current division




$$i_2 = \frac{2}{2+14} (4) = 0.5$$

P.T.O

Khalid Khan

(18)

13880

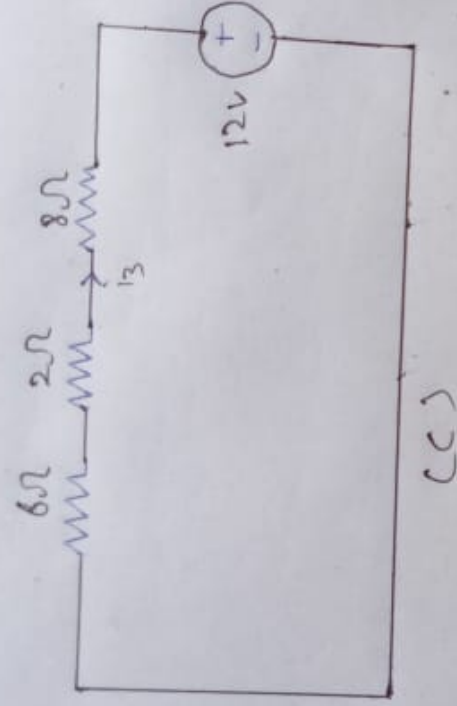

Apply Ohm's Law

For i_3

$$i_3 = \frac{-12}{16} = -0.75A$$

Thus $i = i_1 + i_2 + i_3$

$$= 1 + 0.5 - 0.75$$

$$= 750mA$$