

# Department of Electrical Engineering

## Assignment

Date: 14/04/2020

### Course Details

Course Title: Electronic Circuit Design  
 Instructor: \_\_\_\_\_

Module: 04  
 Total Marks: 30

### Student Details


Name: Mansoor khan Jadoon

Student ID: 16637

Q1.	(a)	<p><b>Explain</b> the drain characteristic curve of D-MOSFET given below.</p> <div style="text-align: center;"> </div>	Marks 07
			CLO 1
	(b)	<p><b>Sketch</b> the hybrid model and write equations for the transistor in common emitter configuration.</p>	Marks 06
			CLO 1
Q2.		<p>A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. <b>Evaluate</b> the CMRR &amp; express it in decibels.</p>	Marks 05
			CLO 2
Q3.	(a)	<p><b>Explain</b> the concept behind negative feedback in operational amplifiers.</p>	Marks 06
			CLO 2
	(b)	<p><b>State</b> the following statement as <b>True</b> or <b>False</b> and also give the reason for your answer:                      "The output of a summing amplifier is positive"</p>	Marks 06
			CLO 2

①

Q1 (a)

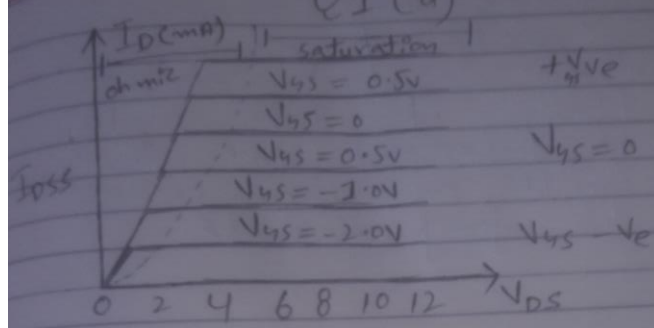

The give  $V-I$  - characteristic give the information about the voltage and current. The voltage that is  $V_{DS}$  and the current that is  $I_D$ . Actually  $V_{DS}$  is voltage of Drain to source and  $I_D$  is current of drain. And this curve actually gives the relation between  $V_{DS}$  and  $I_D$ . Drain and source have a channel between it. This channel act as a good conductor. This channel width and drain current depends on gate voltage. If gate voltage is

(2)



negative the decrease in width of channel and drain's current occur while if gate voltage is (increase) time then width and drain current is going increase.

3

Q1 (b)

Ans:

Common emitter hybrid Model:

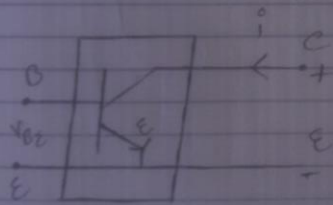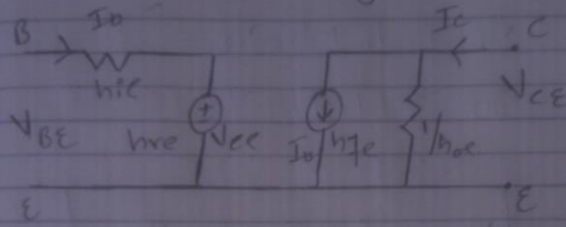

$$h_{ie} = \left. \frac{V_{be}}{I_b} \right|_{V_{ce}=0} = \left. \frac{\partial V_{be}}{\partial I_b} \right|_{V_{ce}}$$

$$h_{re} = \left. \frac{V_{be}}{V_{ce}} \right|_{I_b=0} = \left. \frac{\partial V_{be}}{\partial V_{ce}} \right|_{I_b=0}$$

$$h_{fe} = \left. \frac{I_c}{I_b} \right|_{V_{ce}=0} = \left. \frac{\partial I_c}{\partial I_b} \right|_{V_{ce}}$$

(4)

$$h_{oe} = \frac{I_c}{V_{ce}} \Big|_{I_b=0} = \frac{\partial i_c}{\partial v_{ce}} \Big|_{i_b=0}$$

$$V_1 = h_{ie} I_1 + h_{re} V_2$$

$$I_2 = h_{fe} I_1 + h_{oe} V_2$$

So:

$$V_{be} = h_{ie} I_b + h_{re} V_{ce}$$

$$I_c = h_{fe} I_b + h_{oe} V_{ce}$$

(5)

Q2 Ans:

Given:

Common mode gain

$$A_{cm} = 0.6$$

Open loop differential

$$\text{voltage gain} = A_{od} = 400,000$$

Find:

$$CMRR = ?$$

Solution:

As we know:

$$CMRR = \frac{A_{od}}{A_{cm}}$$

putting values:

$$= \frac{400,000}{0.6}$$

$$\boxed{CMRR = 666,666.6}$$

(6)

Now:

CRRM in decibels:

$$CRRM = 20 \log(A_d/A_{CM}) \rightarrow (i)$$

$$\text{As } (A_d/A_{CM}) = 666,666.6$$

putting in (i).

$$CRRM = 20 \log(666,666.6)$$

$$CRRM = 115.47 \text{ dB}$$

(7)

Q3 (a) Ans:

Negative Feedback

Operational Amplifier:

If we connect the output of an op-amp to its inverting input and apply a voltage signal to non-inverting of op-amp closely follows that input voltage. I've neglected to draw in the power supply  $+V/-V$  wires and ground symbol for simplicity.


As  $V_{in}$  increase,  $V_{out}$  will increase in accordance with the differential gain. However as  $V_{out}$  increase that output voltage is feed back to the inverting input, thereby acting to decrease the voltage differential between input.



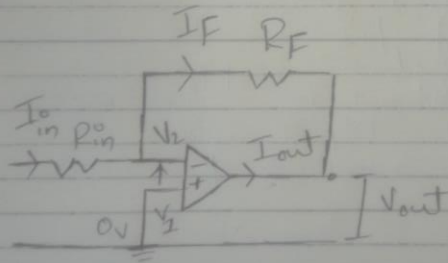(8)

which act to bring the output down.

“Taking the op-amp's output voltage and coupling it to the inverting input is negative feedback”



(9)

Q 3 (b)

"The output of summing amplifier is positive"

This statement is true.

In non-inverting summing amplifier the output is positive.

Using the non-inverting amplifier input voltage are applied this input voltage are applied to the non-inverting input terminal and a part of the output is feedback to the inverting input terminal through bias feedback. And when the summing point of summing amplifier is connected with non-inverting input then it will give sum of the input voltage. Also the input resistor are selected as

(10)

large as possible. if  
more input resistor  
are connected this allow  
the output voltage calculate  
easily. And these resistors  
are connected to the  
amplifier inverting input  
terminal.