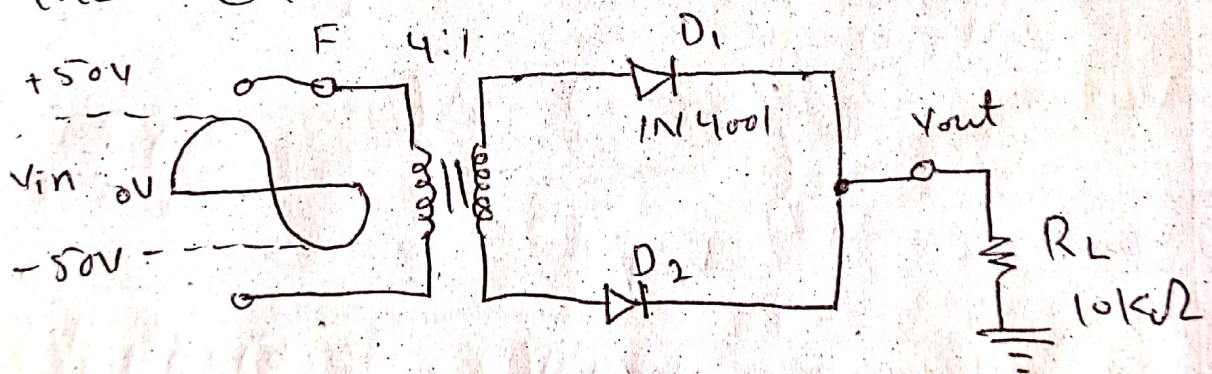





Name	Fawad Niaz
ID#	14568
Module	Summer
Subject	Electronic Devices and Circuits
Instructor	Dr.Engr.Shahryar Shafique Qureshi

Q no 1 :- For the circuit give in figure 1, answer and ----

- what type of circuit this?
- what is the total peak secondary voltage?
- Find the peak voltage across half of the secondary.
- what is the peak current through each diode?
- what minimum PIV rating must the diodes have?




Ans :-

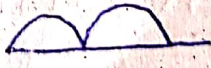(a) This is a center-tapped Full-wave Rectifier circuit.  → wave form.

(b) The transformer turns ratio $n = 0.25$
 so the total peak secondary voltage is
 $V_p(sec) = n V_p(Prim) = 0.25 (50V)$
 $V_p(sec) = 12.5$

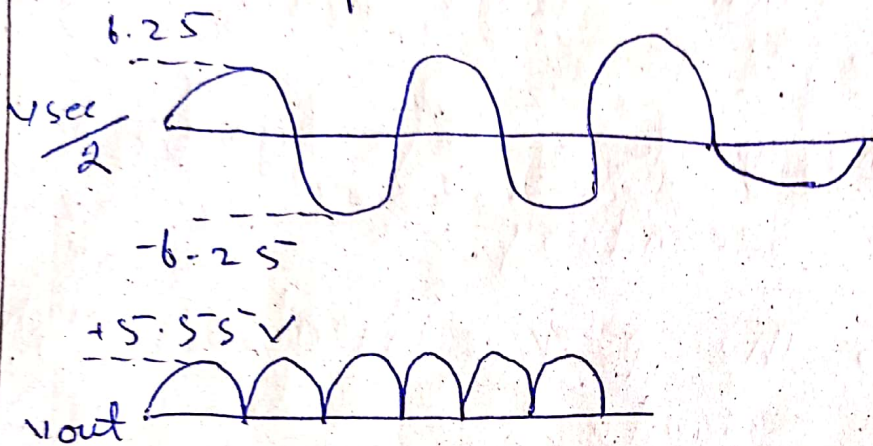(c) so There is 6.25V peak across each half of The secondary with respect to ground. The output load voltage has a peak value of 12.5V, less the 0.7 drop across the diode.



(d) Peak current through each diode

$$I_F = \frac{V_p(\text{sec}) - 0.7}{2} \cdot \frac{1}{R_L} = \frac{5.55V}{10k\Omega}$$


$$I_F = 0.00055 \text{ A} = \boxed{0.555 \text{ mA}}$$

(e) Each diode must have a minimum PIV rating of

$$PIV = 2V_p(\text{out}) + 0.7 = 2(5.55) + 0.7$$

$$\boxed{PIV = 11.8V} \rightarrow \text{Ans.}$$

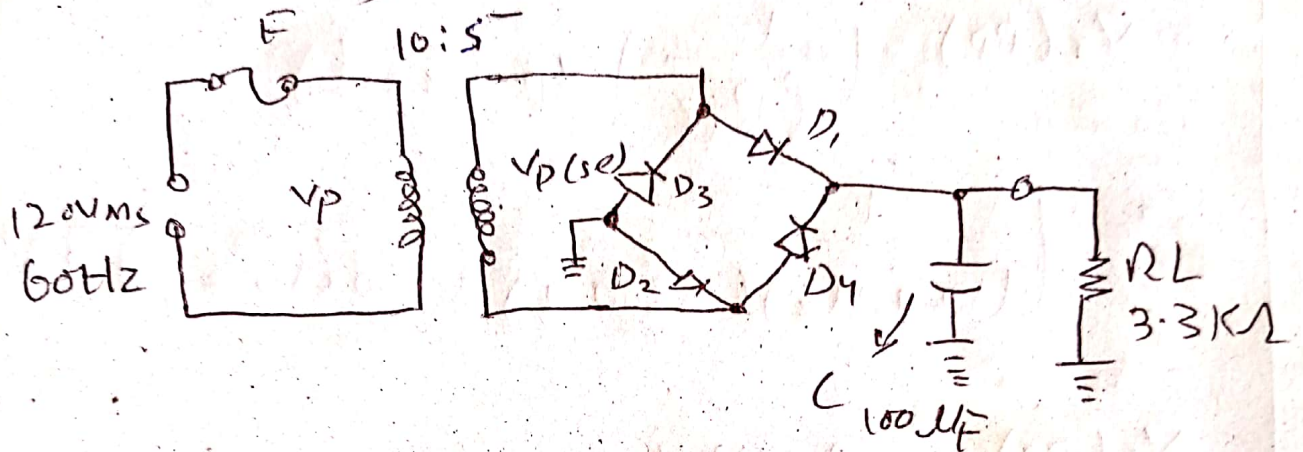Q. no 2 :- Determine The ripple factor for The filtered bridge rectifier with a load as indicated in Figure 2



Ans :-

The transformer turns ratio is

$$n = 0.5$$

so The Peak Primary voltage is

$$V_p(\text{Pri}) = 1.414 V_{\text{rms}} = 1.414 (120) = 170\text{V}$$

The Peak secondary voltage is

$$V_p(\text{Sec}) = n V_p(\text{Pri}) = 0.5 (170\text{V}) = 85\text{V}$$

The unfiltered Peak full-wave rectified voltage is

$$V_p(\text{rect}) = V_p(\text{sec}) - 1.4\text{V}$$

$$\text{//} = 85 - 1.4\text{V}$$

$$V_p(\text{rect}) = 83.6\text{V}$$

Frequency of a full-wave rectified voltage is 120 Hz. The approximate peak ripple voltage at the output

$$V_r(PP) = \left(\frac{1}{fR_L C} \right) V_p(\text{rect})$$

$$= \left(\frac{1}{(120 \text{ Hz})(3300 \Omega)(100 \times 10^{-6} \text{ F})} \right) 83.6 \text{ V}$$

$$V_r(PP) = 2.11 \text{ V}$$

Approximate dc value of the output voltage is determined as follows.

$$V_{DC} = \left(1 - \frac{1}{2fR_L C} \right) V_p(\text{rect})$$

$$V_{DC} = \left(1 - \frac{1}{(240)(3300)(100 \times 10^{-6})} \right) (83.6)$$

$$V_{DC} = \left(1 - \frac{1}{79.2} \right) 83.6$$

$$V_{DC} = (1 - 0.0126) 83.6$$

$$= (0.9874) 83.6$$

$$V_{DC} = 82.5$$



Resulting ripple factor is

$$V_r(PP) = \frac{2.11}{82.5}$$



$$= 0.025$$

Ans


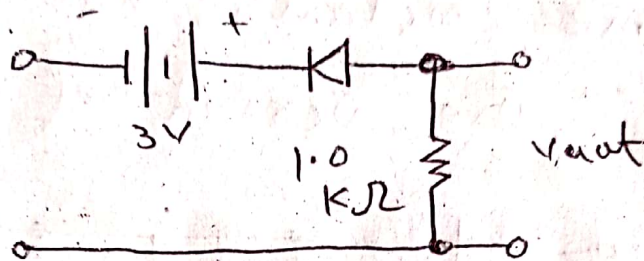
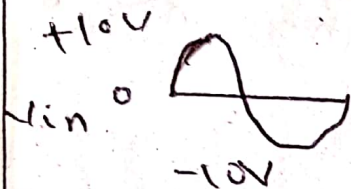
Q No 3:- Determine the output voltage waveform for the circuit given in Figure 3




Ans:-

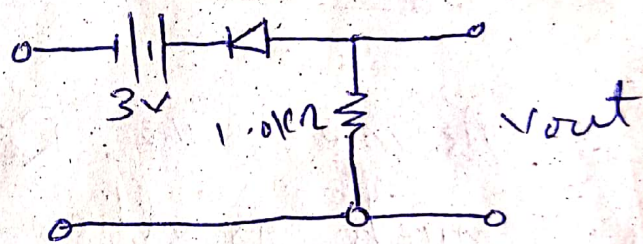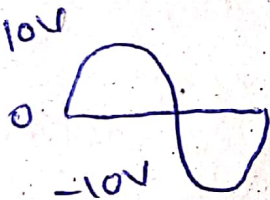

output waveform of clipper circuit

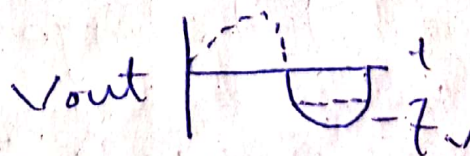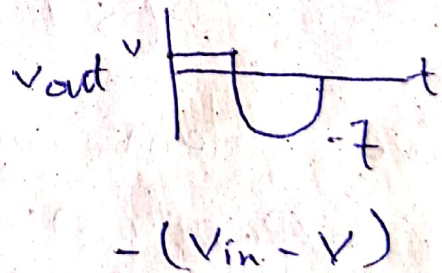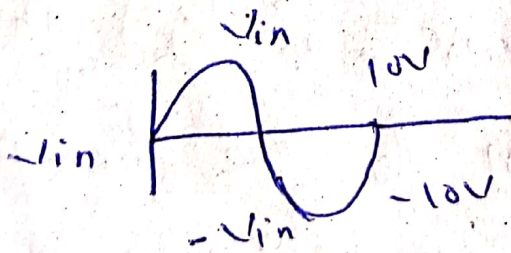

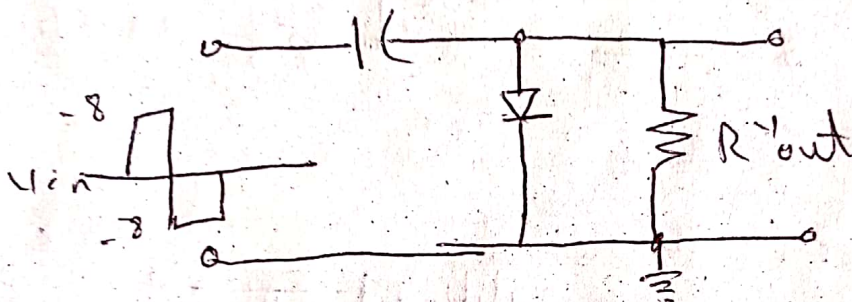Q No 4 Determine The output voltage waveform for the circuit given in Figure 4. Assume the RC time constant is much greater than the period of the input.



Ans.

Assume the RC time constant is much greater than period of input.

So if we take

$$(5T \text{ discharge} \geq 0.8 T/2) \text{ Thus}$$


we obtain condition for the clamping operation

$$T \text{ discharge} \geq 5T$$

so

$$V_o = V_i - V + V_D (0V)$$

T is the period of input signal.

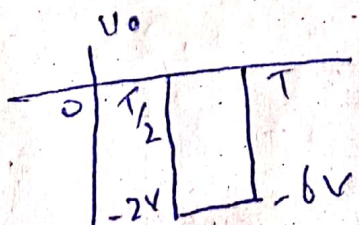


Q no 5 :: Answers The following question

(a) what is power supply filter? and diagram.


A power supply filter ideally eliminates the fluctuations in the output voltage of a half wave or full-wave rectifier and produces a constant level of voltage.

Diagram.

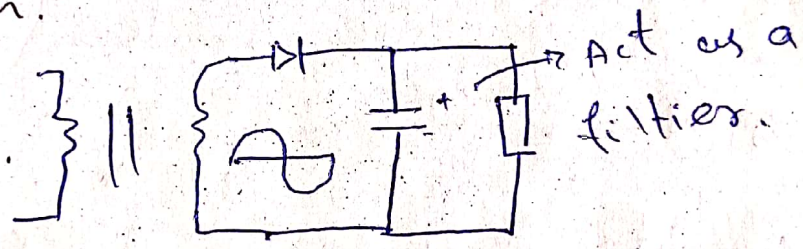

~~~~~ → Reducing Ripples  
As capacitor charging and discharging.

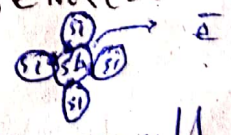(b) n-type and p-type semiconductors  
n-type semiconductors :-




amount of pentavalent impurity added to a pure silicon-crystal. It forms n-type semiconductor.  
The addition of pentavalent impurity produces a large no of free electron in host crystal.


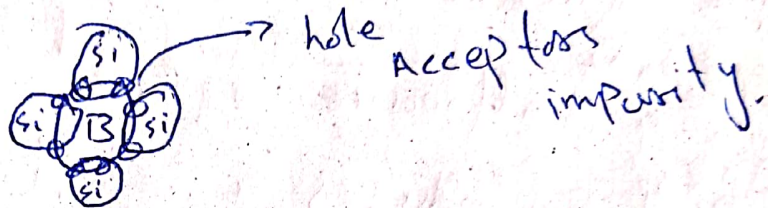
## P-type semiconductor:-

is formed when a trivalent impurity is added to a pure semiconductor in a small amount and as a result a large number of holes are created.




(c) Diode Limiters and positive and negative limiters.

Diode Limiter:- It is a type of circuit which is designed to clip a part of signal or AC signal to desired waveform.



Positive Diode Limiter:-

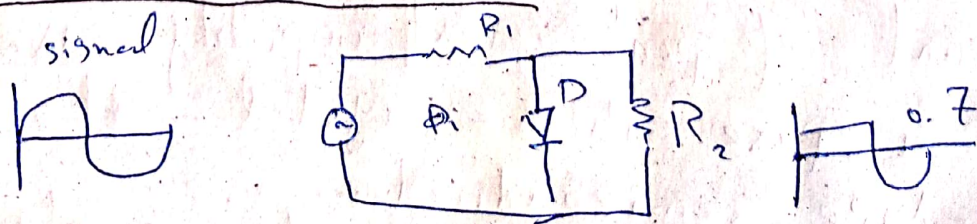


It is used to clip +ve half



(8)  
cycle of sinusoidal wave.

-ive Diode Limiter

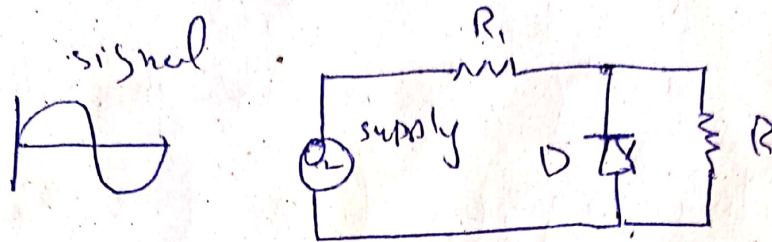


It is used to clip -ive half of cycle to a desired level.

(d) what component in a clamping circuit -----

capacitor effectively act as a battery in a clamping circuit.

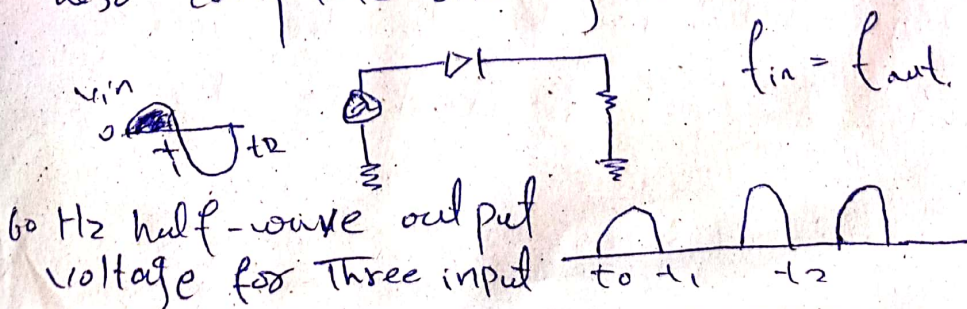(e) when 60 Hz sinusoidal voltage -----

The output frequency of half wave rectifier is equal as input. This means as input complete one cycle at output also complete one cycle.





(f) If load resistor connected ---


If the load resistor to filtered power supply decreases. The charging and discharging time of capacitor also discharging so take longer time to charge and discharge.

time decreased time

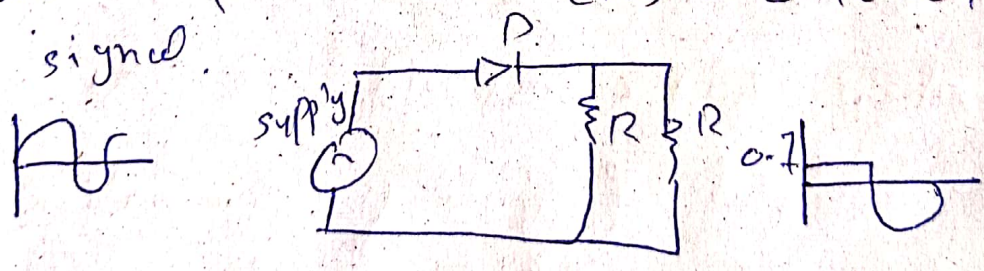(g) Diode limiter and clippers ---

Diode Limiter :-

It is a circuit which is used to clip a sinusoidal wave form at a desired level. signal.





It is used as a voltage regulator to keep the voltage at a desired level.


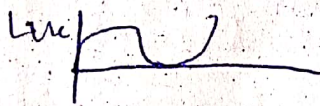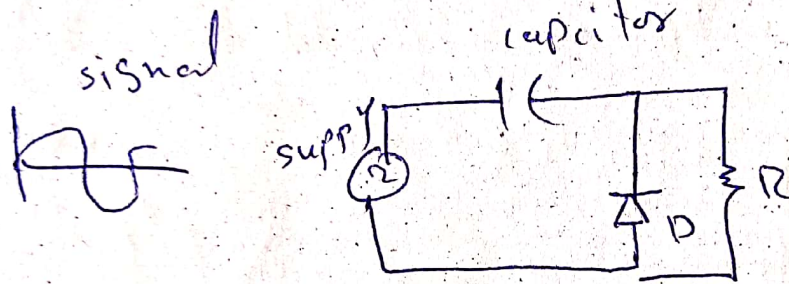
# Diode Clamper:-

Diode clamper is used to add a DC offset of a ~~sinusoidal~~ +ve and -ve half cycle of a sinusoidal waveform.

It clamps the whole signal at a desired level.



It is used as a voltage doubler.

