

Digital Logic Design


Assignment 2
Sir. Muhammad Amin




HASSAN MEHDI

15453
Csc-201

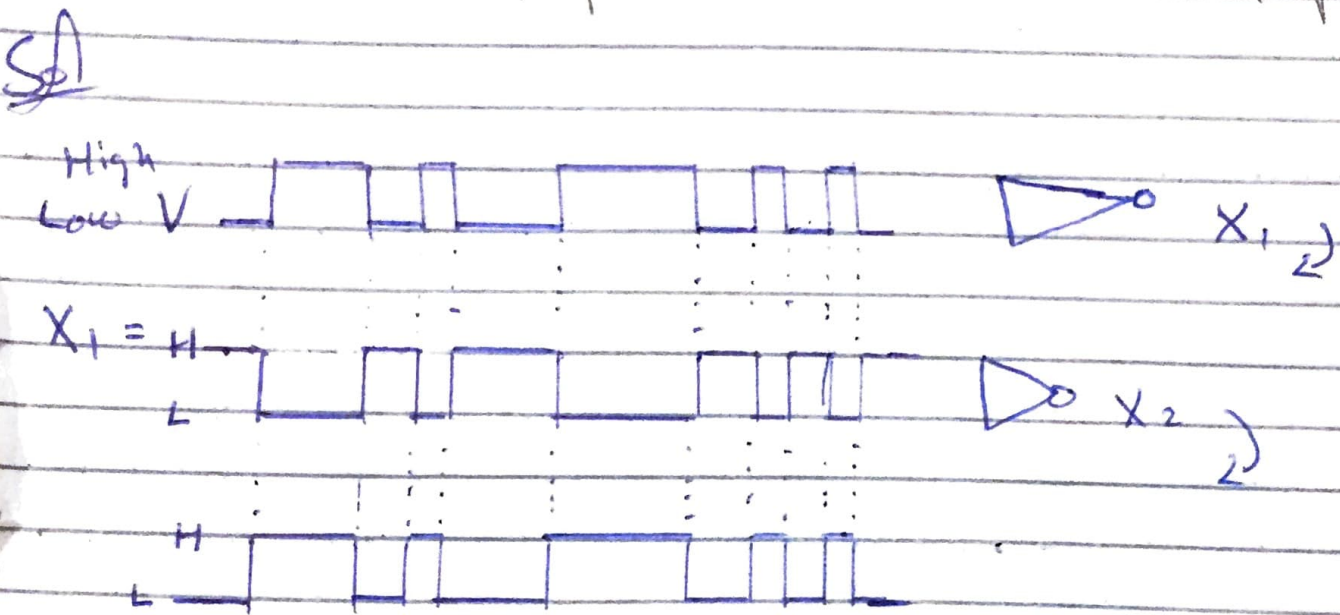Q1: The input waveform in figure is applied to a system of two inverters connected in series. Draw the output waveform across each inverter in proper relation to the input.



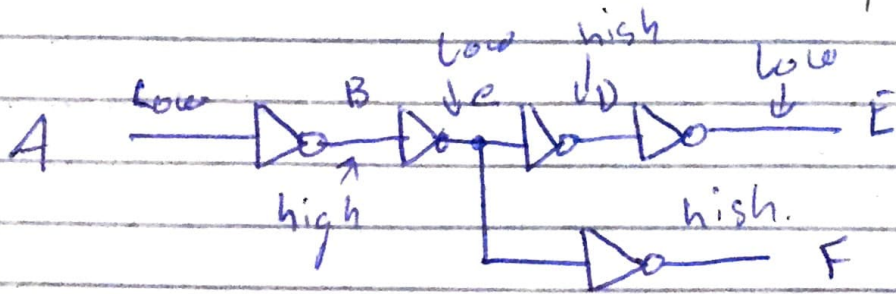Q2: A combination of inverters is shown in figure. If a low is applied to the point A, determine the waveform output at point E and F.








E = low

F = High


Q3: if waveform in Q1 is applied to figure in Q2 at point A. Determine the waveform from point B to F.

Sol

     



Q4: Determine the output, X for a 2 input AND gate with the input waveforms in figure.

As

 


Ans

 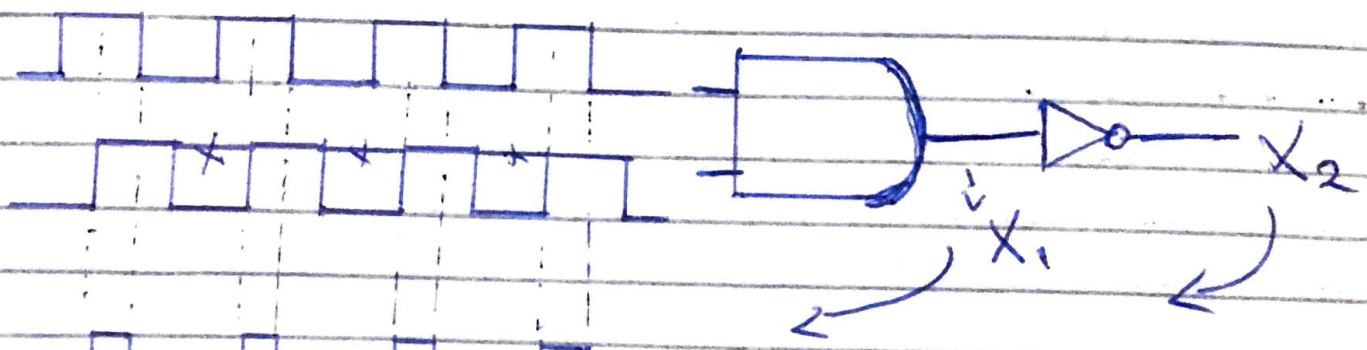Q5: The waveform in figure are applied to point A and B of a 2 input AND gate followed by an inverter. Draw the output waveform.




Ans

 
(6) The input waveform applied to 3-input AND gate are as indicated in figure. show the output waveform in proper relation to the inputs with the time diagram.



 
(7) The input waveform applied to a 4 input AND gate is as indicated in figure, the output is fed to an inverter. Draw the net output.



 
Q8: Determine the output for a two input OR gate when input waveforms are as in figure Q5 and draw a time diagram.



Q9: Repeat Q.6 for 3 input OR gate

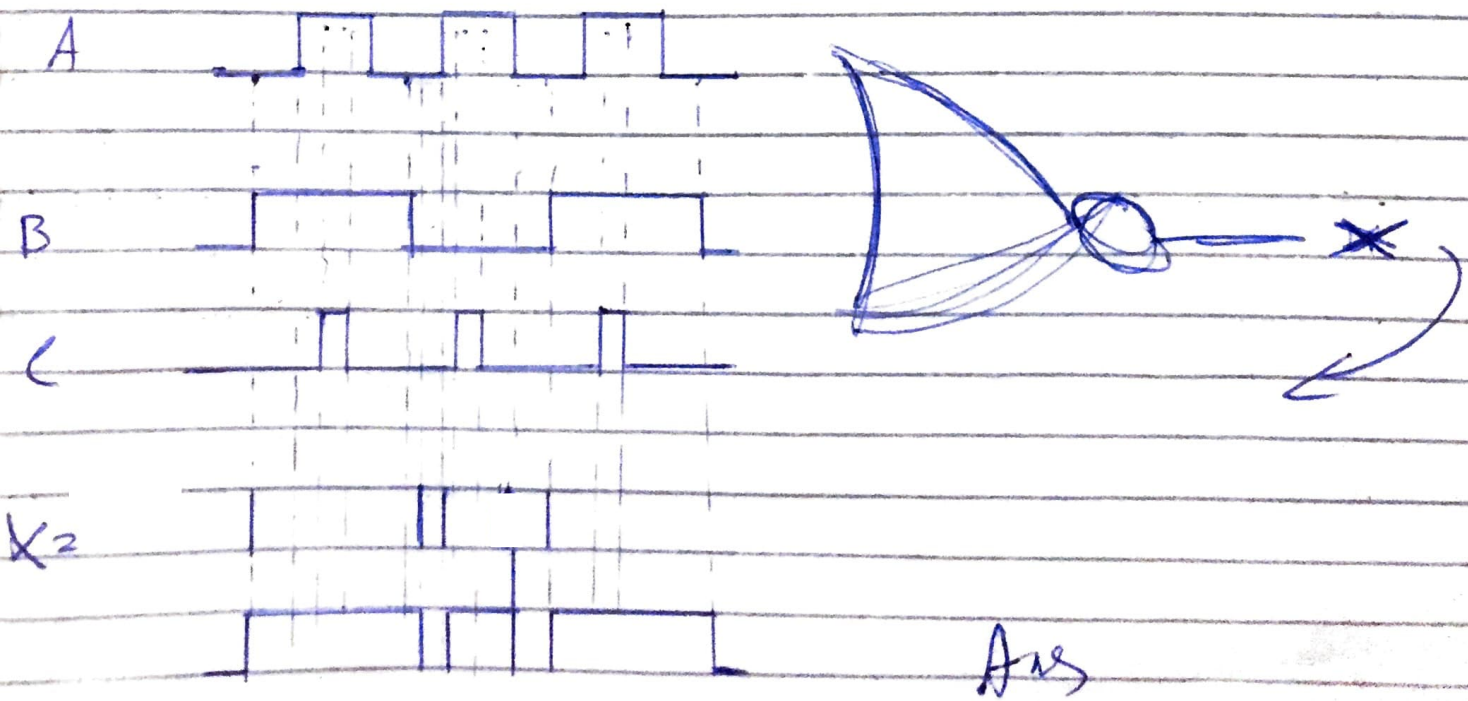

Q10: Repeat Q7 for 4 input OR gate.

 


Q11: For the waveforms given in figure, A and B are ANDed with output F, D and E are ANDed with output G, C, F, and G are ORed, Draw the net output waveform.

Sol

$$(AB) = F$$


$$(DE) = G$$

$$(C + F + G) = X,$$

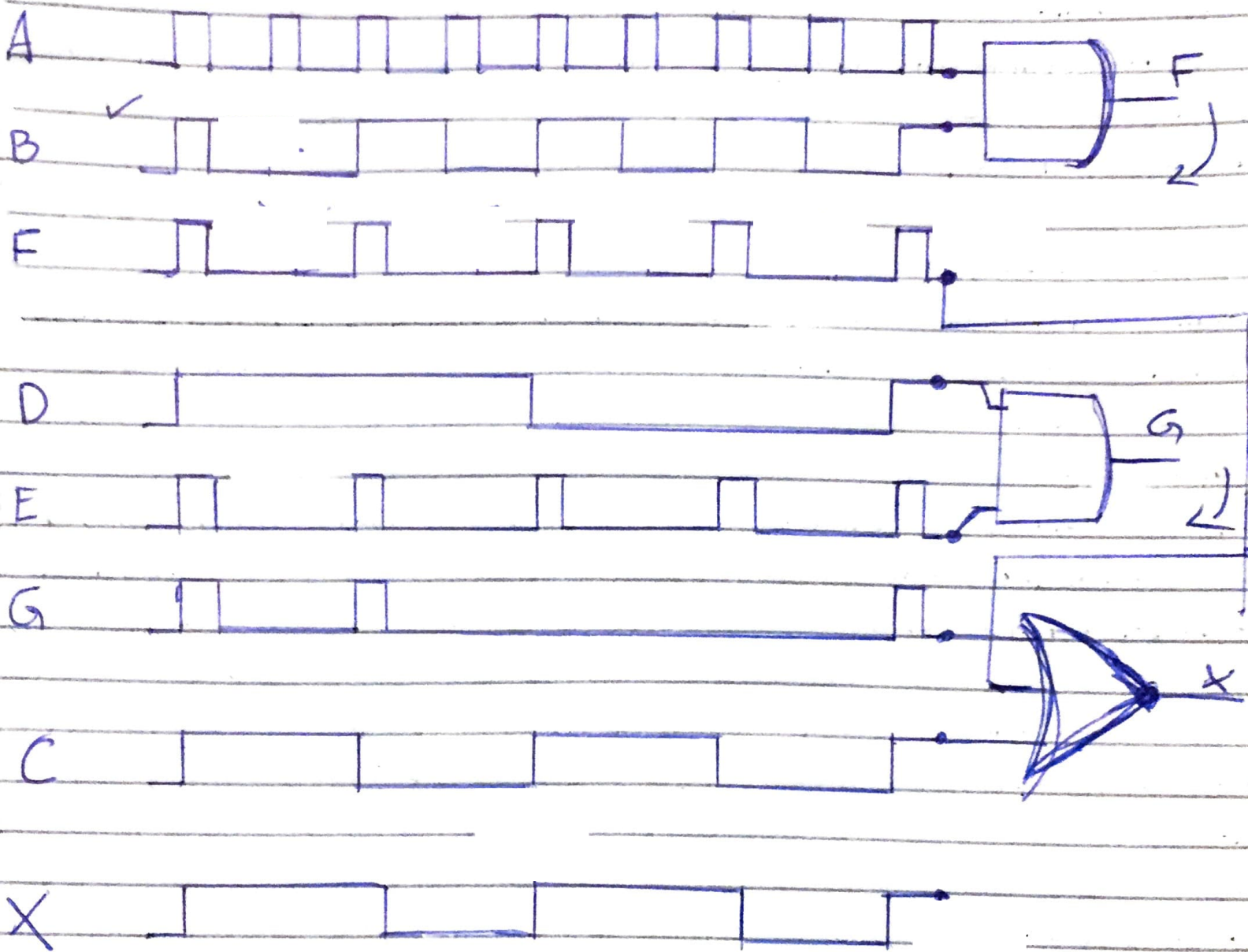


Q12: Show the truth table for a system of a 3 input or gate followed by an inverter.


A	B	C	$(A+B+C)$	$\neg(A+B+C)$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

 

 
Q13: For the set of input waveforms, determine the output for the gate shown in the timing diagram.



 
Q14: Determine the gate output for the input waveforms in figure and draw the timing diagram.



 
Q15: Determine the output waveform in figure.



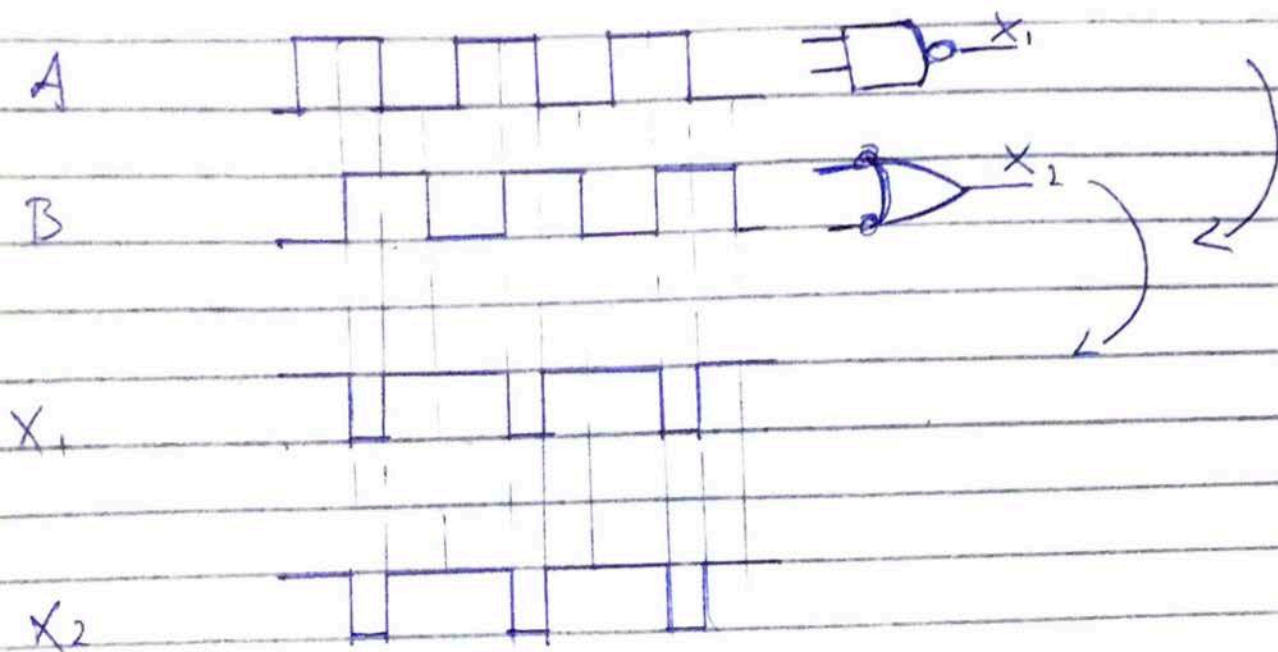
Q16: The two logic symbols shown in Figure 11 represent equivalent operations. The difference between the two is strictly from a functional viewpoint. For the NAND symbol, look for two HIGHS on the inputs to give a LOW output. For the negative-OR, look for at least one LOW on the inputs to give a HIGH on the output. Using these two functional viewpoints, show that each gate will produce the same output for the given inputs.




Q17: Repeat Q13 for 2 input Nor gate.

 

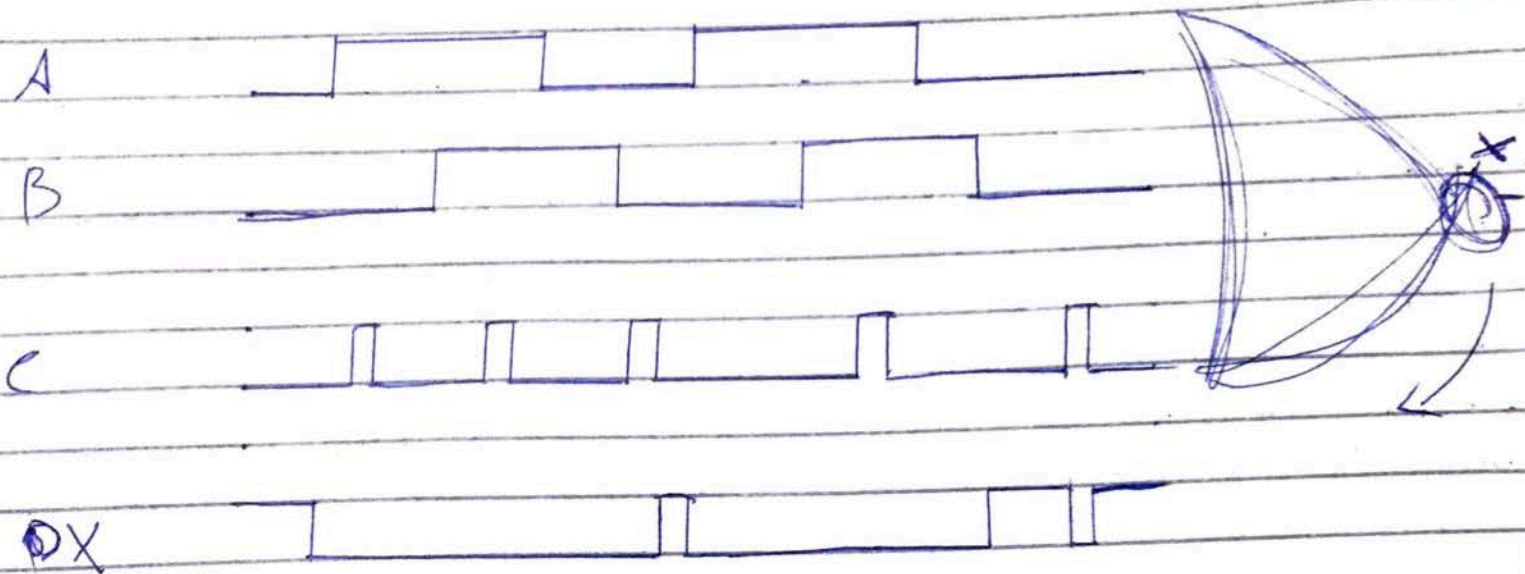Q18: Determine the output waveform in Figure, and draw the timing diagram.




 (P1) Repeat Q 15 for four input NOR gate.




 Q20:

The NOR and the negative-AND symbols represent equivalent operations, but they are functionally different. For the NOR symbol, look for at least one HIGH on the inputs to give a LOW on the output. For the negative-AND, look for two LOWs on the inputs to give a HIGH output. Using these two functional points of view, show that both gates in Figure 12 will produce the same output for the given inputs.



Q21: Repeat Q.5 for Exclusive-OR gate

 

Q22: Repeat Q5 for \oplus exclusive NOR gate

