

NAME # KIRAMATULLAH

ID NO # 13290

SUBJECT # POWER ELECTRONICS

DEPARTMENT # BEE

SEMESTER # 8<sup>th</sup>

TEACHER ↘

ENGR. SIR SHAYAN

TARIQ JAN

## QUESTION # 01


### Rectifier:

It is the electronic device which is used to convert AC into DC is called Rectifier.

#### 1) 1- $\phi$ uncontrolled Half-wave Rectifier:

A rectifier is a circuit that convert an AC signal in to unidirectional signal. Diodes are used commonly in rectifiers. A single phase half wave rectifier is the simplest type is not normally used in industrial applications. However it is useful in understanding the principle of rectifier operation.


#### Circuit diagram:

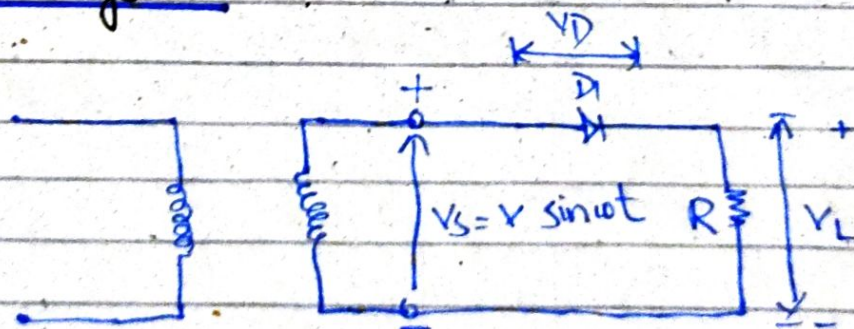

During positive half cycle, the input voltage diode  $D_1$  is forward biased and conduct and input voltage appears

across the load. During the negative half cycle of the input voltage the diode is blocking conductor and output voltage is zero.


waveform :-

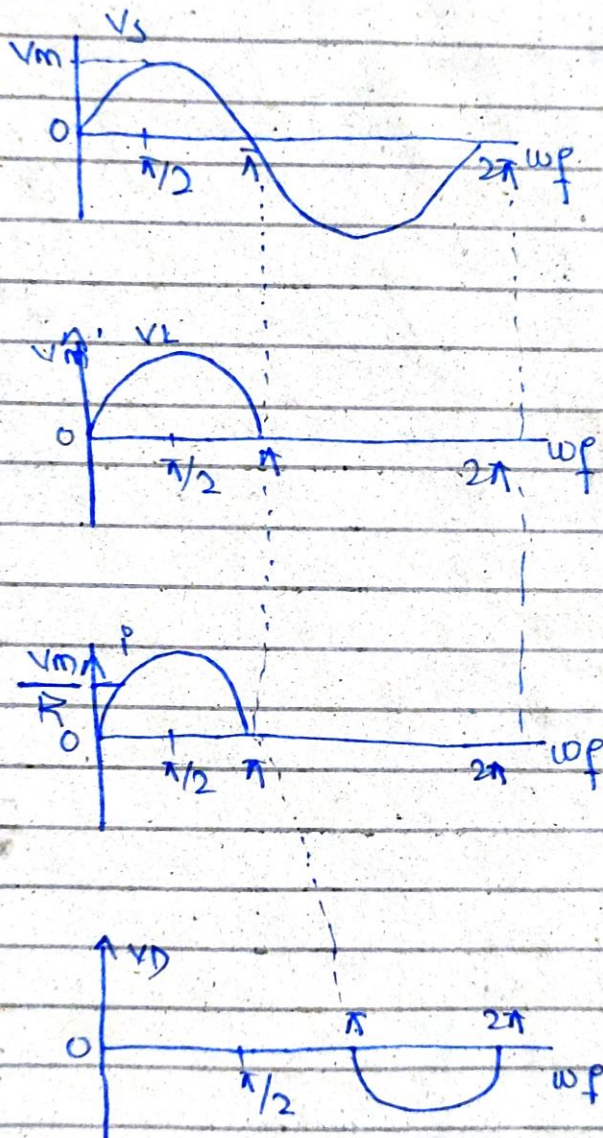




2) 1- $\phi$  uncontrolled Full wave bridge Rectifiers :

In use four diodes in bridge Rectifier circuit

Circuit Diagram:

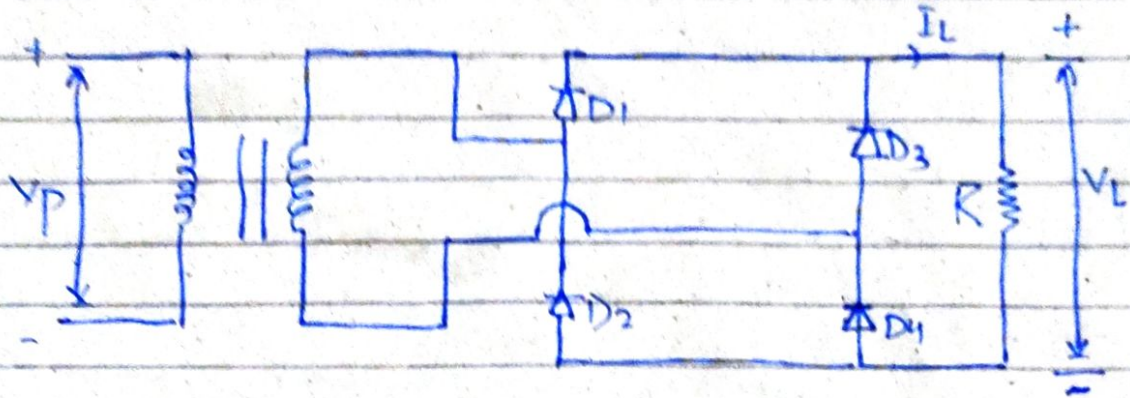


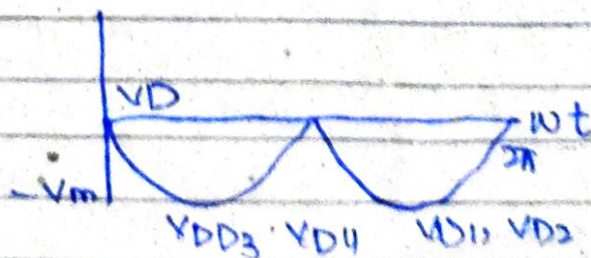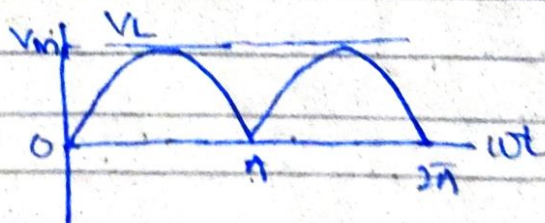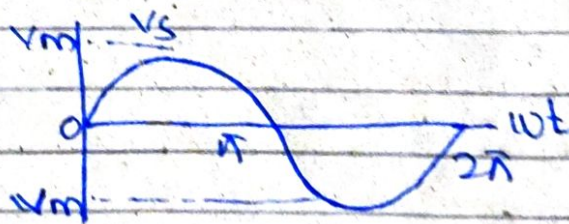During positive half cycle of the input voltage the current flows through the load through diodes  $D_1$  and  $D_2$ . During negative cycle diodes  $D_3$  and  $D_4$  conducts. The peak inverse voltage of a diode is  $V_{in}$ .



Similarities / Differences:


- ↳ Both uses diode
- ↳ During positive half cycle both conduct
- ↳ During negative half cycle bridge Rectifier conduct but not conduct the half wave Rectifier.

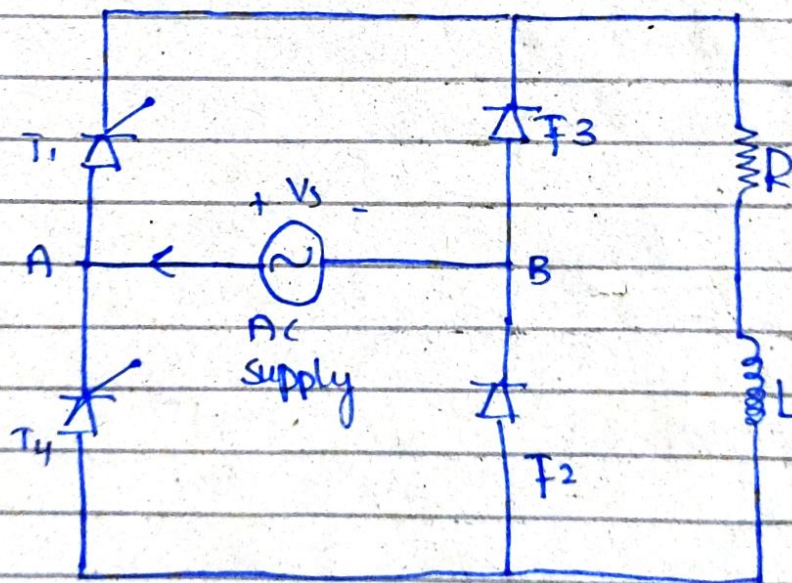2-  $\phi$  controlled bridge rectifier:circuit diagram:

Its function is basically subdivided into two parts positive half and negative half cycle.  $T_1$  and  $T_2$  will become forward bias. If we give gate pulse the  $T_1$  and  $T_2$  current will flow in the loop. During

negative half cycle terminals A is negative with respect to terminal B,  $T_3$  and  $T_4$  will be in forward bias. If we give gate pulse to  $T_3$  and  $T_4$  current will flow in another loop.

Graph:

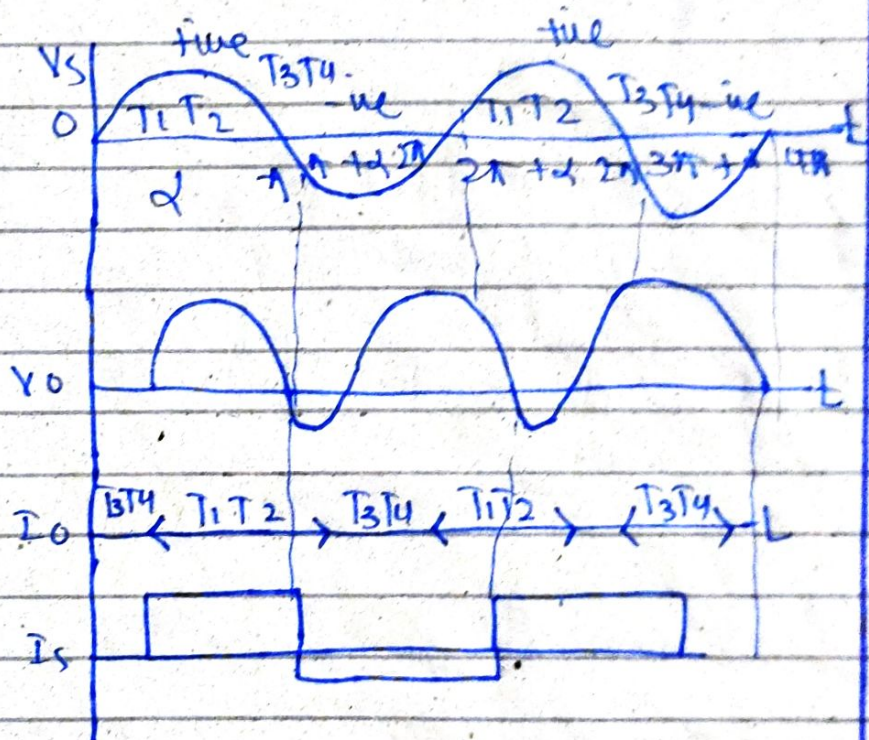

Similarities and difference:


- ↳ uncontrolled rectifiers uses diodes.
- ↳ controlled rectifiers uses SCR
- ↳ In controlled Rectifier we control the output by using the gate pulse. when we give gate pulse than it triggers otherwise not.

QUESTIONNO2Given :-

$$V_m = 90V$$

$$R = 13\Omega$$

$$I_m = \frac{V_m}{R_L} = \frac{90}{13} = 6.29A$$

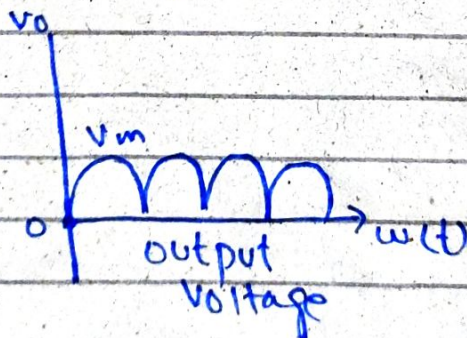i) $I_{dc} = ?$ First we will find  $I_{dc}$  in full wave rectifier

$$I_{dc} = \frac{V_m}{\pi R} = \frac{90}{3.14 \times 13} = \frac{90}{40.82}$$

$$= 2.204A$$

$$V_{DC} = \frac{V}{\pi} = 28.66$$

$$V_{rms} = \frac{V_m}{2} = \frac{90}{2} = 45V$$

$$I_{rms} = \frac{90}{2R}$$

$$= \frac{90}{2(13)} = \frac{90}{26}$$

$$I_{rms} = \boxed{3.46 A}$$

1- $\phi$  Full wave rectifier can controlled

$$V_s = V_{dc} = \frac{2V_m}{\pi} = \frac{2(90)}{3.14}$$

$$= \frac{180}{3.14} = 57.32$$

$$I_{dc} = \frac{V_m}{R} = \frac{90}{13} = 6.92 A$$

$$V_{rms} = \frac{1}{\sqrt{2}} V_s$$

$$= \frac{1}{\sqrt{2}} (57.32)$$

$$= 1.41 (57.32)$$

$$= 81.06$$

$$I_{Rms} = I_m / 2$$



Kiramatuallah


Fig (8)

ID#13290

$$= \frac{6.29}{2}$$

$$I_{RMS} = \boxed{3.145A}$$

Ans///

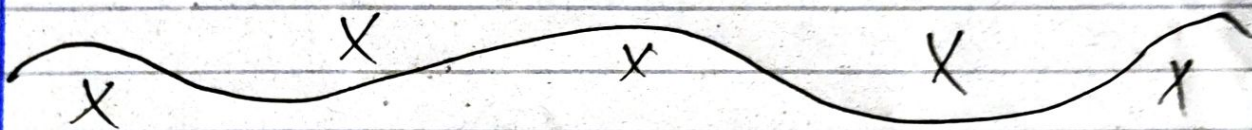

Question NO:- 3 Part (A)Principal of Buck Converter:-

→ The main working principle of buck converter is that the inductor in the input circuit resists sudden variation in input current. When switch is ON the inductor stores energy from the input in the form of magnetic energy & discharge it when switch is closed. The capacitor in the output is assumed large enough that the time constant of RC circuit, in the output stage is high. The large time compared to switching period ensures that in the steady state a constant output voltage  $V_o(t) = V_o(\text{constant})$  exists across load terminal.


Working of Buck Converter:-

The working of a buck converter into a few

Steps.

Step 1:-

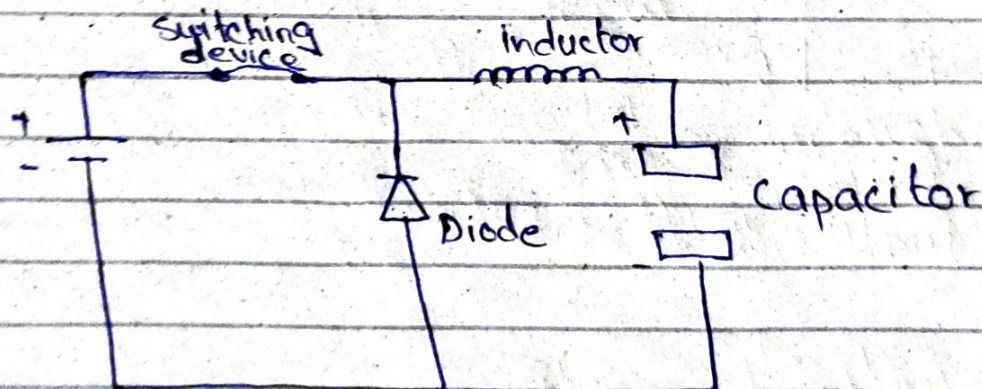
The switch ON  $\epsilon_p$  let current flow to the output capacitor, charging it up. Since the voltage across the capacitor cannot rise instantly  $\epsilon_p$  since the inductor limits the charging current the voltage across the cap during the switching cycle is not the full voltage of the power source.



Step 2:-

The switch turns OFF. Since the current in an inductor cannot change only suddenly, then the inductor creates a voltage across it.

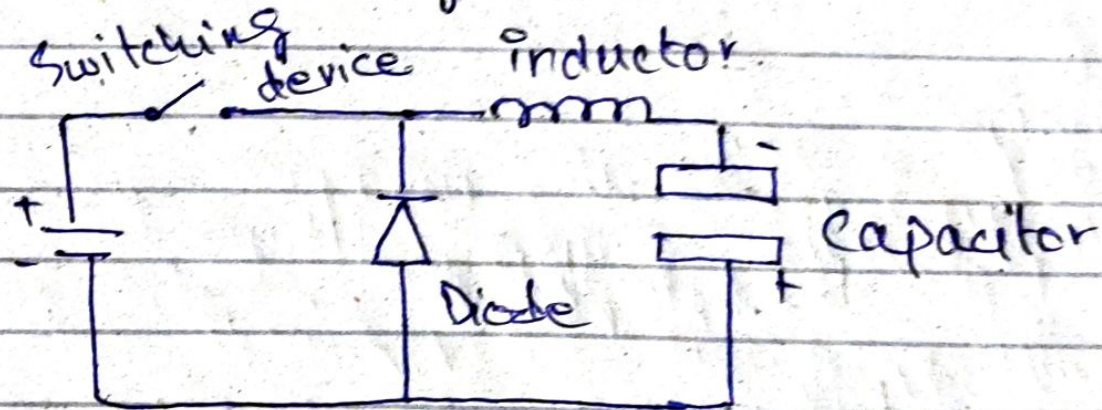This voltage is allowed to charge the capacitor & power the load through the diode when the switch is turned off maintaining current output throughout the switching.



Question:- 3(B) Part (B)

Given:-

$$V_{in} = 50V$$

$$\text{duty cycle} = 90\% = 0.90$$

$$R = 13\Omega$$

$$f = 20\text{kHz} = 20000\text{Hz}$$

i)

$$V_{out} = ?$$

$$V_o = d (V_i)$$

$$= 0.90(50)$$

$$V_o = 45V$$

(ii)  $I_{out} = ?$

$$I_{out} = \frac{V_o}{R}$$

$$= \frac{45}{13}$$

$$= 3.46A$$

(iii)  $I_{in} = ?$

$$I_{in} = \frac{V_{in}}{R}$$

$$I_{in} = \frac{50}{13}$$

$$I_{in} = 3.84 \text{ A}$$

(iv) Inductor(?) = ?

$$L = \frac{I_{OFF} LR}{2}$$

As we know that

$$v_o = d v_i$$

$$d = \frac{v_o}{v_i} = \frac{45}{50}$$

$$d = 0.9$$

$$\frac{I_{ON}}{T} = 0.9$$

$$T_{ON} = 0.9 * T$$

$$T = \frac{1}{f}$$

$$T_{ON} = \frac{0.9}{f}$$

$$T_{ON} = \frac{0.9}{20(10^3) \text{ Hz}} = 4.5 \text{ } \mu\text{B}$$

Also from eq we have

$$\frac{I_{ON}}{I} = 0.9$$

$$\frac{I_{ON}}{0.71} = I \Rightarrow \frac{1.6065}{0.9} = 1.78$$

now

$$I = I_{ON} + I_{OFF}$$

$$I_{OFF} = I - I_{ON}$$

$$= 1.78 - 4.5$$


$$= -2.72$$

Question no 4:- Part (A)

Ans:-

Boost chopper:-


A boost converter is one of the simplest type of switch mode converter. It takes an input voltage & boost it. All consist of is an inductor, a semi conductor switch, a diode & a capacitor. It is also called as step-up converter.

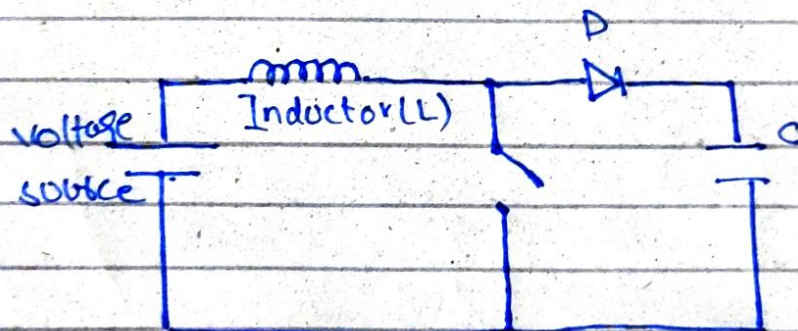Working Principle


The main working principle of boost converter is that the inductor in the input circuit resists sudden variation in input current. When switch is OFF, the



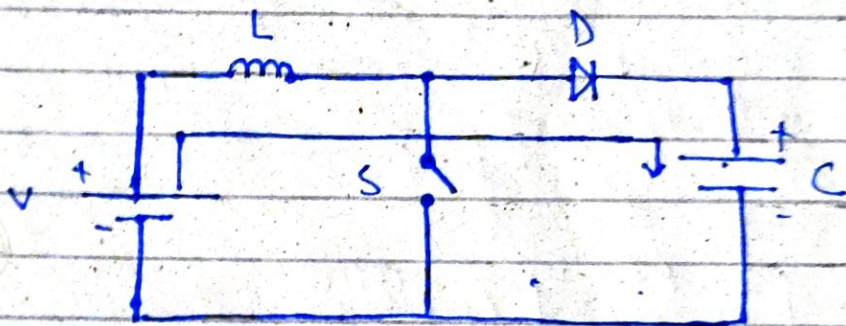Inductor ~~source~~ stores energy in the form of magnetic energy & discharges it when switch is closed. The capacitor in the output circuit is assumed large enough that the time constant of RC circuit in the output stage is high.



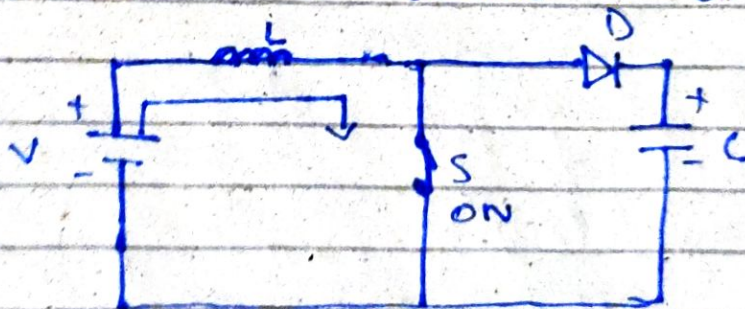The output capacitor is charged to the input voltage minus one diode drop.



When the switch is on, our signal source goes high turning on the MOSFET. All the current is diverted through to the MOSFET.

through the inductor. The output capacitor stays charge since it can't discharge through the now back-biased diode. It is ON for a time  $t_{ON}$  & is OFF for a time  $t_{OFF}$ . We defined the time period,  $T$ , as  $T = t_{ON} + t_{OFF}$  & the switching frequency

$$f_{switch} = \frac{1}{T}$$

Now define another term duty cycle.

$$D = \frac{t_{ON}}{T}$$


Boost converter in steady state operation for this mode using KVL.

$$V_{in} = V_L$$

$$V_L = L \frac{di_L}{dt} = V_{in}$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_{in}}{L}$$

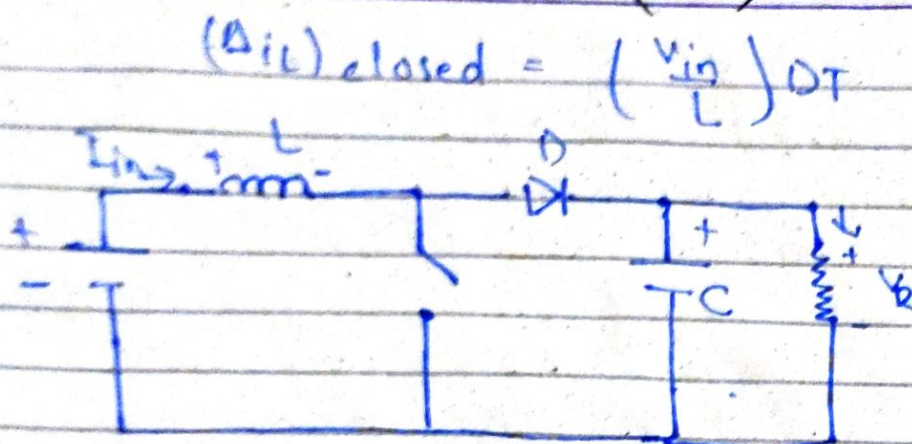Since the switch is closed for a time  $t_{ON} = DT$  we can say that  $\Delta t = Dt$



In this mode the polarity of the inductor is reversed. The energy stored in the inductor is released & is ultimately dissipated in the load resistance & this help to maintain the flow of current in the same direction through the load & also step up the voltage as the inductor is now also acting as a source in conjunction with the input source.

Analyze the circuit using KVL  
Boost converter in steady state operation for mode


$$V_{in} = V_L + V_o$$

$$V_L = L \frac{di_L}{dt} = V_{in} - V_o$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-d)T} = \frac{V_{in} - V_o}{L}$$

Since the switch is open  
for a time  $T_{OFF} = T - T_{ON} =$   
 $T - DT = (1-D)T$  we can say  
that

$$\Delta t = (1-D)T$$

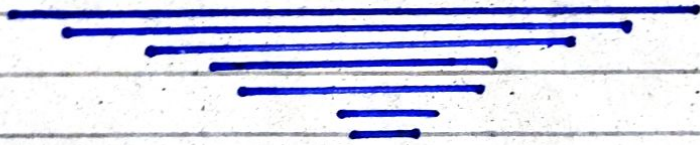

Question No 1,Part (B)

Given:-

$$V_{in} = 50V$$

$$D = 90 = 0.90$$

$$R = 13 \Omega$$

$$f = 20Hz$$

Find:-

- i)  $V_{out}$
- ii)  $I_{out}$
- iii)  $I_{in}$
- iv) Inductance ( $L$ )

we know that

$$\Rightarrow i) V_{out} = \frac{V_s}{1-D} = \frac{50}{1-0.90} = \frac{50}{0.1}$$

$$V_{out} = \boxed{500 V}$$

$$\Rightarrow ii) I_{out} = \frac{500}{13} = \frac{V_{out}}{R}$$

$$I_{out} = \boxed{38.46 A}$$

/// Ans ///

$$L = \frac{I_{out}}{I-D}$$

$$= \frac{38.46}{1-0.90} = \frac{38.46}{0.1}$$

$$\text{Inductor} = \boxed{384.6 \text{ L}}$$

Inductor

~~$$= \frac{I_{out}}{I-D}$$~~

Ans

~~$$= \frac{384.6}{1-0.90} = \frac{384.6}{0.1}$$~~

~~$$= \boxed{3846}$$~~

Ans


Question NO 5: Part (A)Buck Boost converter

The buck boost converter is a large of DC-DC that has output voltage magnitude that is either greater than its then the input voltage magnitude. It is equalized to a flyback converter using a single inductor instead of a transformer.

Principle of working of buck converter,

The main working principle of buck converter is that the inductor in the input circuit result sudden variations in input current. When switch is on the inductor store energy & discharge it when switch is closed the capacitor in the output circuit is assumed large enough that the time constant of RC circuit

in the output stage is high  
the large time constant  
compare to switching period  
ensure a constant output  
voltage

$$V_o(t) = V_o (\text{constant})$$




Question :- 5 (B)PART BGiven:-

$$V_{in} = 50$$

$$V_{out} = 90\% = 0.90$$

$$R = 13\Omega$$

$$f = 20\text{kHz}$$

$$1-D = \frac{-V_{in}}{V_o - V_{in}}$$

$$-D = \frac{-V_{in} - 1}{V_o - V_{in}}$$

$$+D = \frac{V_{in} + 1}{V_o + V_{in}}$$

$$= \frac{50 + 1}{0.90 + 50} = \frac{5}{50.90} \approx 0.098$$

$$= 1.00$$

(2)

$$I_{out} = \frac{V_o}{R} = \frac{0.90}{13}$$

$$= 0.069$$

(3)

$$I_{in} = \frac{I_0 D}{1-D} = \frac{0.069(1.00)}{1-1.00}$$

$$= \frac{0.069}{0}$$

$$= 0$$

(4)

$$I = \frac{V_{in} \times D}{f \times \Delta I}$$

$$= \frac{50 \times 1.00}{20,000(I_{out} - I_{in})}$$

$$= \frac{50}{20,000(0.069 - 0)}$$

$$= \frac{50}{1380} = 0.036$$



\* THE END \*