

**Department of Electrical Engineering**  
**Assignment**

**Date: 13/04/2020**

**Course Details**

**Course Title:** Electrical Network Analysis  
**Instructor:** \_\_\_\_\_



**Module:** 4th  
**Total Marks:** 30


**Student Details**

**Name:** \_\_\_\_\_

**Student ID:** \_\_\_\_\_

**Student Signature:** \_\_\_\_\_

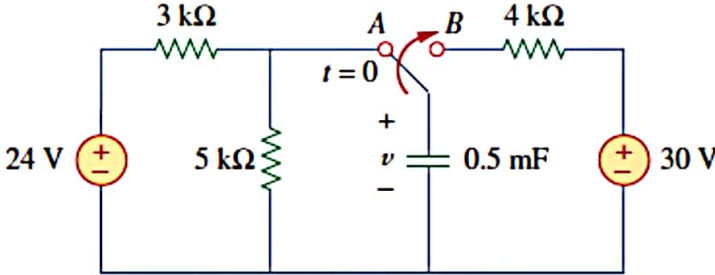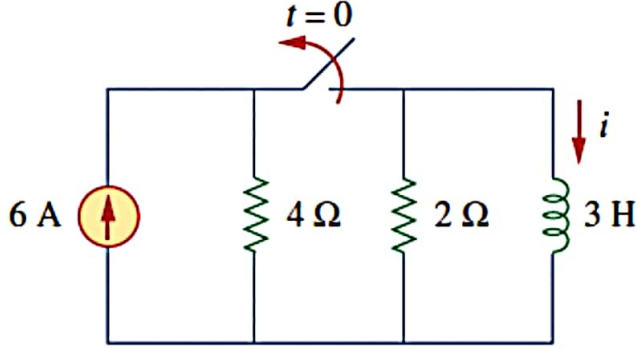
Q1.	<p>The switch in Fig. 1 has been in position A for a long time. At <math>t = 0</math> the switch moves to B. Determine <math>v(t)</math> for <math>t &gt; 0</math> and calculate its value at <math>t = 2\text{s}</math> and <math>8\text{s}</math>.</p>  <p style="text-align: center;"><b>Figure 1</b></p>	<p>Marks 06 CLO 01</p>
Q2.	<p>Determine the inductor current for both <math>t &gt; 0</math> and <math>t &lt; 0</math> for the circuit in Fig. 2.</p>  <p style="text-align: center;"><b>Figure 2</b></p>	<p>Marks 06 CLO 01</p>
Q3.	<p>A series RLC circuit is described by</p> $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$ <p>Find the response when <math>L = 0.5\text{ H}</math>, <math>R = 4\ \Omega</math> and <math>C = 0.2\text{ F}</math>. Let <math>i(0) = 1</math>, <math>di(0)/dt = 0</math></p>	<p>Marks 06 CLO 01</p>

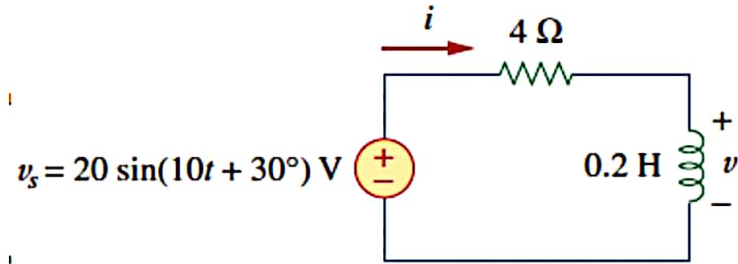Q4.	A series RLC circuit has $R = 100\Omega$ , $L = 240\text{ H}$ and $C = 10\text{mF}$ . If the input voltage is $v(t) = 10\cos 2t$ , find the current flowing through the circuit.	Marks 06 CLO 03
Q5.	<p>Find <math>v(t)</math> and <math>i(t)</math> in the circuit shown in figure 3.</p>  <p style="text-align: center;"><b>Figure 3</b></p>	Marks 06 CLO 03

①

Name : Naveed Ali  
ID : 16753

Q NO 1 :-

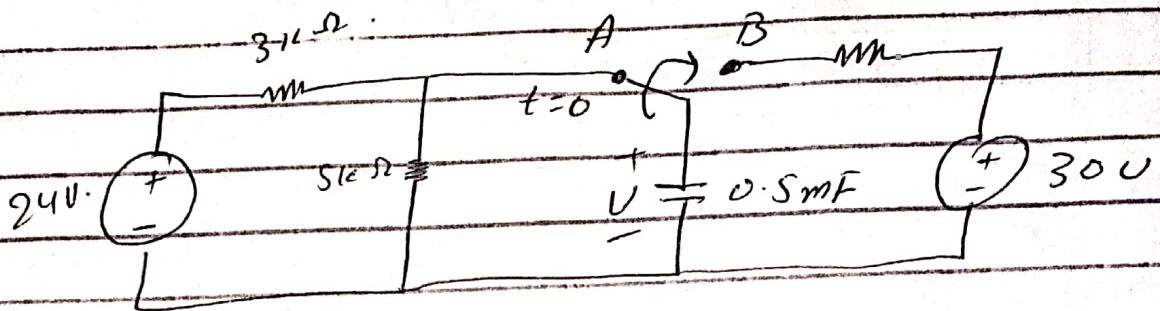

Solution :- for t < 0

$$V(0^-) = \frac{5}{5+3} (24) = 15V$$

As it is DC so

$$V(0) = V(0^-) = V(0^+) = 15V$$

for t > 0,

$$R_{TH} = 4k\Omega$$

so

$$\tau = R_{TH} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ sec} \dots$$

As capacitor acts like open ckt so

$$V(\infty) = 30V$$

so

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$V(t) = 30 - 15 e^{-0.5t}$$

P.T.O

(2)

for  $t = 2 \text{ sec}$ .

$$V(t) = 30 - 15e^{-0.5(t)}$$

$$V(2) = 30 - 15e^{-1}$$

$$V(2) = 30 - 5.517$$

$$\boxed{V(2) = 24.48 \text{ V}}$$

for  $t = 8 \text{ sec}$ .

$$V(8) = 30 - 15e^{-0.5(8)}$$


$$V(8) = 30 - 15e^{-4}$$

$$V(8) = 30 - 15(0.018)$$

$$\boxed{V(8) = 29.73 \text{ V}}$$

③

Q NO 2 :->

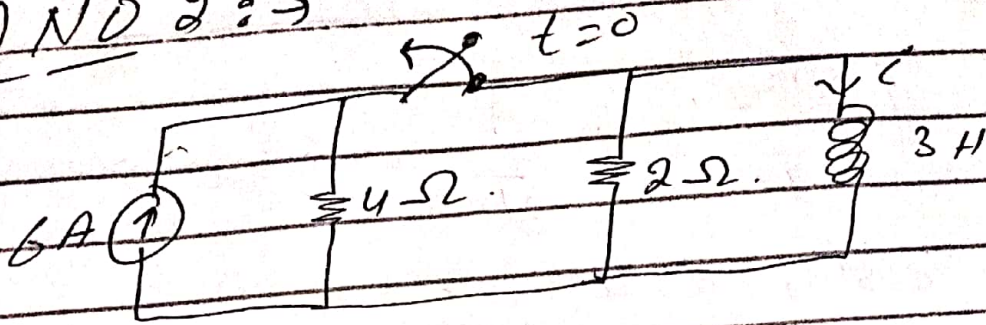

Solution:-

for  $t < 0$ .  
Switch is closed & inductor acts  
like short circuit so

$$i = 6A$$

for  $t > 0$ .

Switch is open and

$$\tau = \frac{L}{R}$$

$$\tau = \frac{3}{2}$$

So

$$i(t) = 6e^{-\frac{t}{\tau}}$$

(4)

Q NO 3 :->

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

$$L = 0.5H, R = 4\Omega, C = 0.2F$$

Solution :->

=> ~~Q~~

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{10}{L}$$

$$\text{Let } C = 0.2F$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{2}{LC}$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \quad \text{--- (1)}$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC} \quad \text{--- (2)}$$

Now

$$\alpha = \frac{R}{2L} = \frac{8}{1} = 4 \text{ rad/sec}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\omega_0 = \sqrt{10} \text{ rad/sec}$$

(5)

$$\alpha > \omega_0$$

So

$$s_0 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_0 = -4 \pm \sqrt{4^2 - (10)^2}$$

$$s = -4 \pm j6 \text{ rad/sec}$$

So

$$I_s = 20 \times LC \Rightarrow L_s = 20 \times 0.2 = 9A.$$

Now

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{--- (3)}$$

$t=0$

$$i(0) = I_s + A_1 + A_2$$

$$\Rightarrow A_1 + A_2 = -1 \quad \because \text{As } I_s = 1A.$$

Now

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}.$$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2.$$

$$\Rightarrow (-4 + j6) A_1 + (-4 - j6) A_2 = 0.$$

$$\Rightarrow A_1 = -1.316$$


$$A_2 = 0.316.$$

$$\text{(3)} \Rightarrow i(t) = 9 - 1.316 e^{(-4+j6)t} + 0.316 e^{(-4-j6)t}$$

Ans

⑥

Q No 4 :->

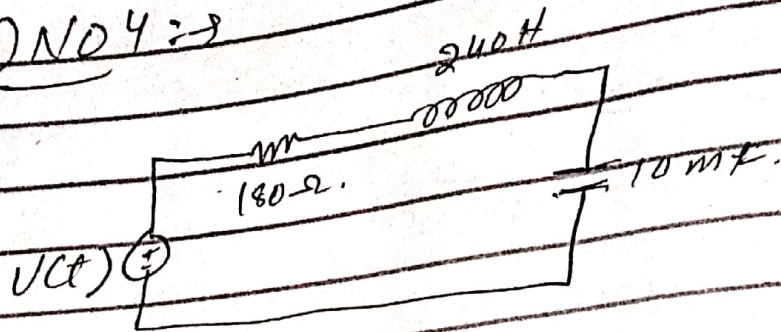

Sol :->

$$\Rightarrow V(t) = 10\angle 0^\circ \text{ V}$$

Now.

$$X_L = \omega L$$

$$X_L = 2 \times 240 \Rightarrow X_L = 480 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2 \times 10}$$

~~$$X_C = 10 \mu\text{F}$$~~

$$X_C = 50 \Omega$$

Now

$$Z = R + jX_L + jX_C$$

$$Z = 180 + j480 + j50$$

$$Z = (180 + j430) \Omega$$

$$Z = 441.97 \angle 79.90^\circ \Omega$$

P.T.O



(7)

Now

$$I = \frac{V(L)}{Z}$$

$$I = \frac{10 \angle 0}{441.47 \angle 76.9}$$

$$I = \frac{10}{441.47} \angle -76.9$$


$$I = 22.6 \times 10^{-3} \angle -76.9$$

$$I = 22.6 \angle -76.9 \text{ mA}$$

P.T.O

(8)

Q NO 53P

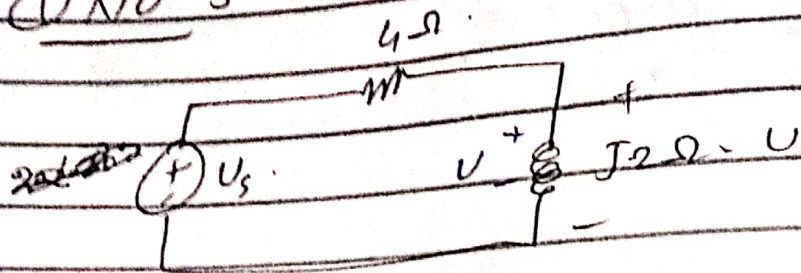

Sol:

$$U_s = 20 \sin(10t + 30^\circ) \text{ V}$$

$$\Rightarrow U_s = 20 \cos(10t + 30 - 90)$$

$$U_s = 20 \cos(10t - 60)$$

$$U_s = 20 \angle -60^\circ \text{ V}$$

$$\omega = 10 \text{ Rad/sec}$$

$$X_L = j\omega L$$

$$X_L = j \times 10 \times 0.2$$

$$X_L = j2 \Omega$$

$$Z = (4 + j2) \Omega$$

$$Z = 2\sqrt{5} \angle 26.6^\circ$$

$$I = \frac{U}{Z}$$

$$I = \frac{20 \angle -60^\circ}{2\sqrt{5} \angle 26.6^\circ}$$

$$I = \frac{20}{2\sqrt{5}} \angle -86.6^\circ$$

$$I = \sqrt{2} \angle -86.6^\circ \text{ A}$$

(9)

$$V = I X_L$$

$$V = (2\sqrt{5} \angle -86.6) (2 \angle 90^\circ)$$

$$V = 4\sqrt{5} \angle 3.4^\circ \text{ V}$$

Ans