

Department of Electrical Engineering

Assignment

Date: 13/04/2020


Course Details



Course Title:	<u>Electrical Network Analysis</u>	Module:	<u>4th</u>
Instructor:	<u>Dr shehryar Shafique qureshi</u>	Total	<u>30</u>
		Marks:	

Student Details

Name: M.Salman shahid **Student ID:** 15006

Student Signature: _____

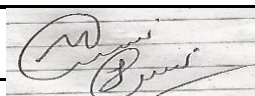

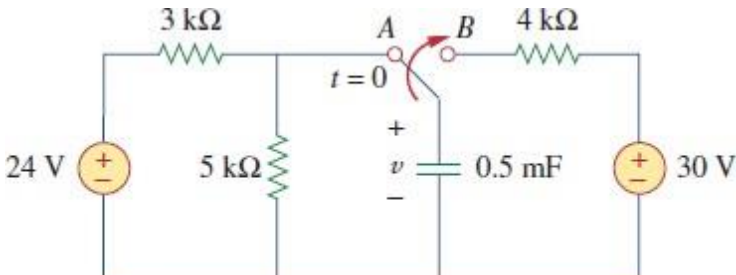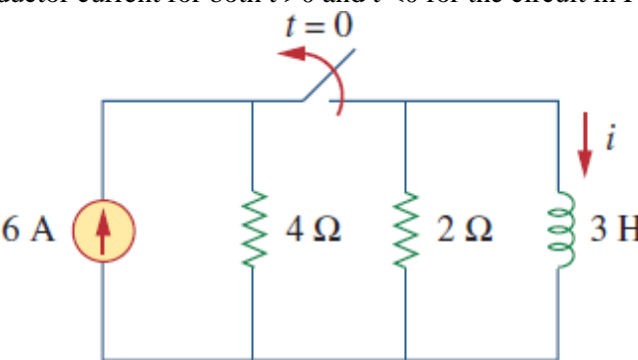Q1.	<p>The switch in Fig. 1 has been in position A for a long time. At $t = 0$ the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 2\text{s}$ and 8s.</p> <div style="text-align: center;">  <p>Figure 1</p> </div>	Marks 06 CLO 01
Q2.	<p>Determine the inductor current for both $t > 0$ and $t < 0$ for the circuit in Fig. 2.</p> <div style="text-align: center;">  <p>Figure 2</p> </div>	Marks 06 CLO 01
Q3.	<p>A series RLC circuit is described by</p> $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$ <p>Find the response when $L = 0.5\text{ H}$, $R = 4\ \Omega$ and $C = 0.2\text{ F}$. Let $i(0) = 1$, $di(0)/dt = 0$</p>	Marks 06 CLO 01

Q4.	A series RLC circuit has $R = 100\Omega$, $L = 240\text{ H}$ and $C = 10\text{mF}$. If the input voltage is $v(t) = 10\cos 2t$, find the current flowing through the circuit.	Marks 06 CLO 03
Q5.	<p data-bbox="324 189 893 231">Find $v(t)$ and $i(t)$ in the circuit shown in figure 3.</p> <div data-bbox="470 252 1218 525" style="text-align: center;"> <p>The diagram shows a series circuit. On the left is a voltage source $v_s = 20 \sin(10t + 30^\circ) \text{ V}$ with the positive terminal at the top. To its right is a resistor labeled 4Ω. A red arrow labeled i points to the right through the resistor. On the far right is an inductor labeled 0.2 H. The voltage across the inductor is labeled v, with the positive terminal at the top and the negative terminal at the bottom.</p> </div> <p data-bbox="795 546 909 588">Figure 3</p>	Marks 06 CLO 03

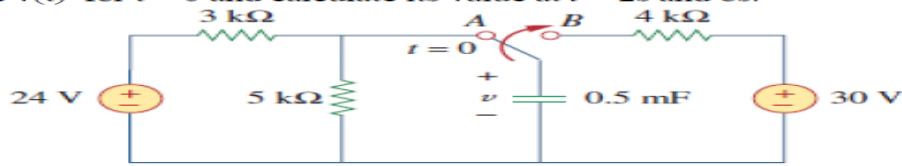


Figure 1

Solution:- for $t < 0$ the switch is open at position A. The capacitor acts like an open switch to DC but v is the same as the voltage across the $5k\Omega$ resistor. Hence the voltage across the capacitor just before $t = 0$ is obtained by voltage division

In series the voltage is divide across resistor's

So to determine voltage at $5k\Omega$ resistor

$$V(0^-) = \frac{R_2}{R_1 + R_2} V_1 = \frac{5}{5+3} (24) = 15V$$

Using the fact that capacitor voltage cannot change simultaneously.

$$V(0) = V(0^-) = V(0^+) = 15V$$

for $t > 0$, the switch is at position B. The Thevenin resistance connected to the capacitor is $R_{th} = 4 \text{ k}\Omega$. & the time constant is

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

Since the capacitor acts like an open circuit to D-C at steady state $v(\infty) = 30 \text{ V}$

Thus

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$= 30 + (15 - 30) e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V}$$

So now at $t = 2$

$$v(2) = 30 - 15e^{-1} = 24.48 \text{ V}$$

at $t = 8$

$$v(8) = 30 - 15e^{-4} = 29.72 \text{ V}$$


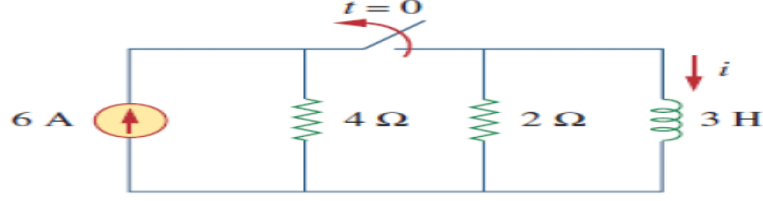


Figure 2

Sol:-
For $t > 0$ the switch is open.

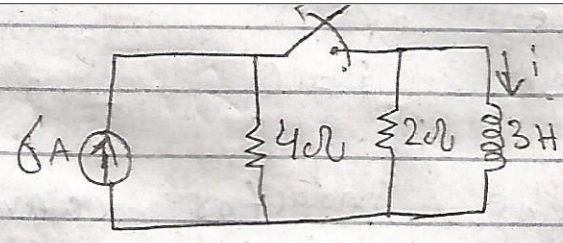

and the current flows toward resistor only
first we find voltage

$$V = iR$$

$$= (6A)(4)$$

$$= 24$$

The switch is opened so the inductor current cannot change instant

$$i(0^-) = \frac{24}{4} = 6A$$

$$i(0) = i(0^-) = i(0^+) = 6A$$

So the inductor current at opened switch $t > 0$ is


$$i(0) = 6A$$

Now for $t < 0$ and the switch is closed

When $t < 0$ the switch is closed

$$i(\infty) = \frac{24}{1.33} = 18.004$$

$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

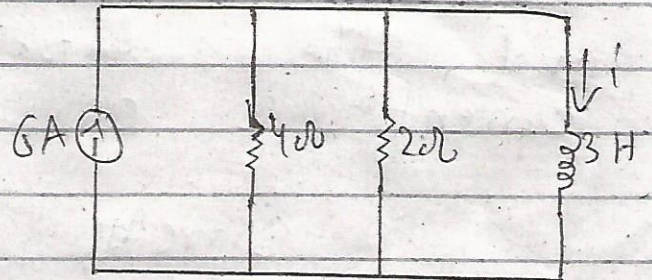

$$R_{th} = \frac{4 \times 2}{4 + 2} = 1.33 \Omega$$

Now to find time Const τ

$$\tau = \frac{L}{R_{th}} = \frac{3H}{1.33\Omega} = 2.250$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 18.004 + [6 - 18.004] e^{-t/2.250}$$

$$= 18.004 + (-12A) e^{-t/2.250}$$

$$i(t) = 6.004 e^{-2t}$$

So for $t > 0$


$$i(t) = 6A$$

$t < 0$ $i(t)$ is equal to

$$i(t) = 6.004 e^{-2t}$$

Solution:

$$v(t) = 10\cos 2t$$

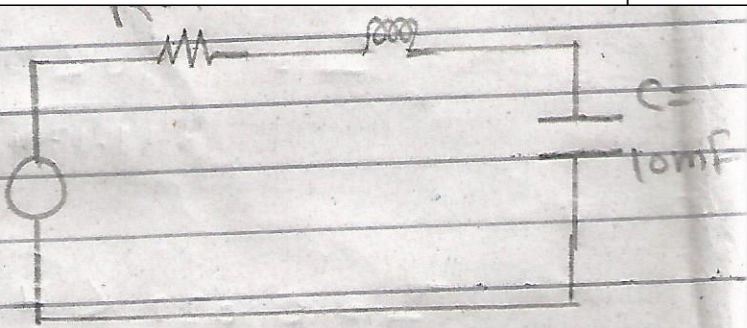

Conversion of time domain to Phasor

$$\omega = 2$$

$$v(t) = 10\cos(2t)$$

$$V = 10\angle 0^\circ$$

$$Z_L = j\omega L = j \times 2 \times 240\text{ H}$$

$$Z_L = j480$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 0.01} = -j50$$

Total impedance Z equal

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= 100 + j480 - j50$$

$$Z = 100 + j430$$

conversion to Phasor

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1}\left(\frac{430}{100}\right)$$

$$Z = 441.474 \angle 76.908$$

$$\bar{I} = \frac{V_s}{Z}$$

$$\bar{I} = \frac{10 \angle 0^\circ}{447.474 \angle 76.908}$$

$$I = 0.022 \angle -76.9$$

$$I_t = 0.022 \cos(2t - 76.908)$$


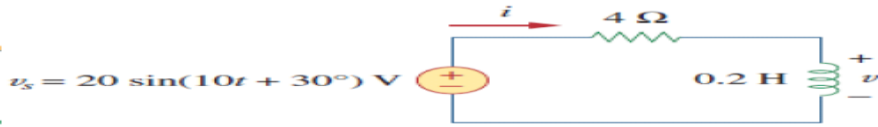


Figure 3

Solution:-

$$V_s = 20 \sin(10t + 30^\circ)$$

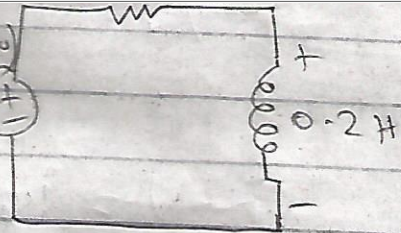

from voltage source
 $20 \sin(10t + 30^\circ)$

$$\omega = 10$$

$$V_s = 20 \angle 30^\circ \text{ V}$$

inductive impedance equal to

$$Z_L = j\omega L$$

from circuit figure

$$= j10 \times 0.2$$

$$= j2 \Omega$$

Now impedance Z

$$Z = R + j\omega L$$

$$= 4 + j2$$

Conversion to sinusoidal

$$\sqrt{(2)^2 + (4)^2} \angle \tan^{-1}\left(\frac{2}{4}\right)$$

$$Z = 4.47 \angle 26^\circ$$

Now

$$\bar{I} = \frac{V_s}{Z} = \frac{20 \angle 30^\circ}{4.47 \angle 26^\circ} = 4.472 \angle 4^\circ$$

$$i(t) = 4.472 \sin(10t + 4^\circ)$$

Now to find $v(t)$
from eq

$$V = j\omega LI$$

$$V = j10 \times 0.2 \times 4.472 \angle 4^\circ$$

Now Conversion to sinusoidal
 $j10 \times 0.2$

$$\tan^{-1}\left(\frac{10}{0.2}\right) \leq 90^\circ$$


$$V = 0.2 \angle 90^\circ \times 4.472 \angle 4^\circ$$

$$V = 0.894 \angle 94^\circ$$

$$V = 8.94 \sin(10t + 94^\circ)$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

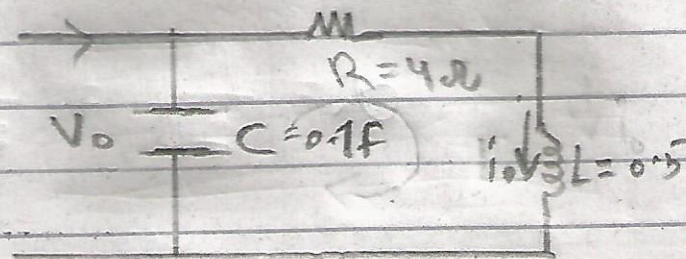Find the response when $L = 0.5 \text{ H}$, $R = 4 \Omega$ and $C = 0.2 \text{ F}$. Let $i(0) = 1$, $di(0)/dt = 0$



Applying KVL

$$iR + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt + V_0 = 0$$

initial voltage in the capacitor
= V_0

Second order

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$Ri(0) + L \frac{di(0)}{dt} + V_0 = 0$$

initial value of derivative

$$\frac{di(0)}{dt} = -\frac{1}{L} (Ri(0) + V_0)$$

$$\frac{di(0)}{dt} = -\frac{1}{0.5} (R(1) + 10)$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

So ~~know~~

$$\alpha = \frac{R}{2L} = \frac{4}{2(0.5)} = 4$$

$$\omega_0 = \frac{1}{\sqrt{(0.5)(0.2)}} = 3.162$$

$$\alpha > \omega_0$$

response So

overdamped