

NAME = HASNAT KHAN

ID = 16631

SEMESTER = 2<sup>ND</sup>


Dept : = ELECTRICAL ENG.

SUBJECT = Linear Circuit  
Analysis

TEACHER = Sir SOHAIL IMRAN

Date = 24 Jun, 2020

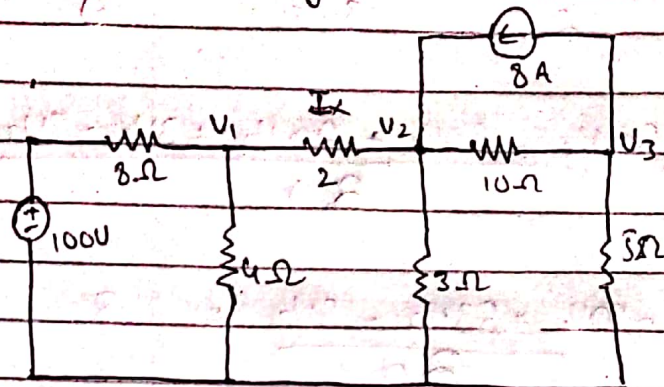(V1) Find the value of  $i_x$   
 i) Nodal Analysis:



Solution:

Applying KCL on node 1:

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 - 100 + 2V_1 + 4V_1 - 4V_2 = 0$$

$$\frac{7V_1 - 4V_2 - 100}{8} = 0$$

multiply 8 on both

$$8 \times \frac{7V_1 - 4V_2 - 100}{8} = 0 \times 8$$

$$7V_1 - 4V_2 - 100 = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Now

Applying KCL on node 2n:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 8$$

$$\frac{30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3}{30} = 8$$

$$\frac{-30V_1 + 53V_2 - 3V_3}{30} = 8$$

Multiply 30 on b.s

$$30 \times \frac{-30V_1 + 53V_2 - 3V_3}{30} = 8 \times 30$$

$$-30V_1 + 53V_2 - 3V_3 = 240 \quad \text{--- (2)}$$

Now

Applying KCL on node 3n:-

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$\frac{-V_2 + 3V_3}{10} = -8$$

Multiply 10 on b.s

$$10 \times \frac{-V_2 + 3V_3}{10} = -8 \times 10$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (3)}$$

3

Now taking eq ①

We get

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Now taking eq ②

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting eq (a) & (b) in eq ②  
we get

$$-30(0.57V_2 + 14.28) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.1V_2 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

Putting  $V_2$  in eq (a)


$$V_1 = \frac{4(20.31) + 100}{7}$$

$$V_1 = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

ii.) Mesh analysis:-

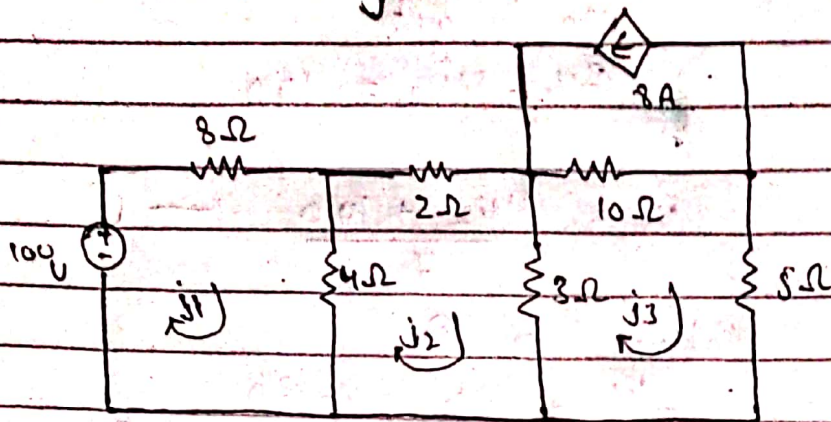

Applying KVL on loop 1.

$$8i_1 + 4(j_1 - j_2) = 100$$

$$8i_1 + 4j_1 - 4j_2 = 100$$

$$12i_1 - 4j_2 = 100 \quad \text{--- (1)}$$

Now

Applying KVL on loop 2:

$$2i_2 + 4(j_2 - j_1) + 3(j_3 - j_2) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_3 - 3i_1 = 0 \quad \text{--- (2)}$$

Again

Applying KVL on loop 3:

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

5

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (a)}$$

taking eq (2) (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (b)}$$

Putting eq (a) & (b) in eq (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$


$$7.2i_2 = 20$$

$$i_2 = \frac{20}{7.2}$$

$$i_2 = 2.79 \text{ A} \Rightarrow \boxed{i_x = 2.79 \text{ A}}$$
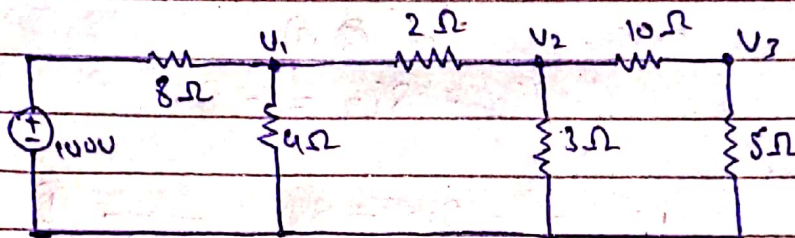
## iii.) Superposition Theorem:-

First removing the current source if making it an open circuit.  
Re-drawing the circuit.



Applying KCL on node 1n:

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$\frac{V_1 - 100 + 4V_1 - 4V_2 + 2V_1}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Now

Applying KCL on node 2n:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

So,

$$-30V_1 + 53V_2 - 3V_3 = 0 \quad \text{--- (2)}$$

7

Again

Applying KCL on node 3n.

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + V_3}{10} = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq ① & eq ②

$$7V_1 - 4V_2 = 100$$

$$7V_1 = 100 + 4V_2$$

or

$$7V_1 = 4V_2 + 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (4)}$$

$$\text{Eq. } -V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3} V_2 \quad \text{--- (5)}$$

Putting in eq ②

$$-30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 428.4 - 4V_2 + 0.60V_2 = 0$$

$$20.44V_2 = 428.4$$

or

$$V_2 = \frac{428.4}{20.44}$$

$$\boxed{V_2 = 20.95}$$



Put  $v_2$  in eq (a)


$$v_1 = 2.31$$

$$\text{or } i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = \frac{23.26}{2}$$

$$\boxed{i_1 = 11.63 \text{ A}}$$

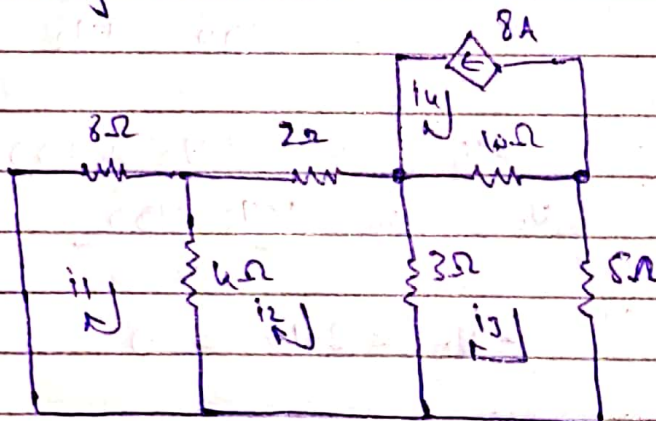Now removing voltage source &  
making it short circuit.  
Re-drawing circuit.



$$i_4 = 8 \text{ A}$$

Apply KVL on Loop 1

$$8i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Applying KVL on Loop 2

$$2i_2 + 3(i_2 - i_3) + 4(i_3 - i_1) = 0$$

9

$$2i_2 + 3i_2 - 3i_2 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + 4i_2 - 3i_2 = 0$$

$$-4i_1 + 4i_2 - 3i_2 = 0 \quad \text{--- (3)}$$

Now

Applying KVL on loop 3

$$10i_3 + 5i_3 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \quad \text{--- (4)}$$

taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (5)}$$

$$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$$

$$i_2 = 1.354$$

Now

$$i_x = i_1 + i_2$$

$$i_x = 1.44 + 1.35$$

$$\boxed{i_x = 2.79 A}$$

iv.) Compare the no of ~~step~~ step & degree of easiness of all the three method with each other.


Sol.

The no of steps in nodal & mesh analysis are almost equal but in superposition the no of steps are almost of mesh & nodal analysis.


Degree of easiness:-

According to opinion mesh analysis is easier than nodal analysis & superposition theorem.

(V2)

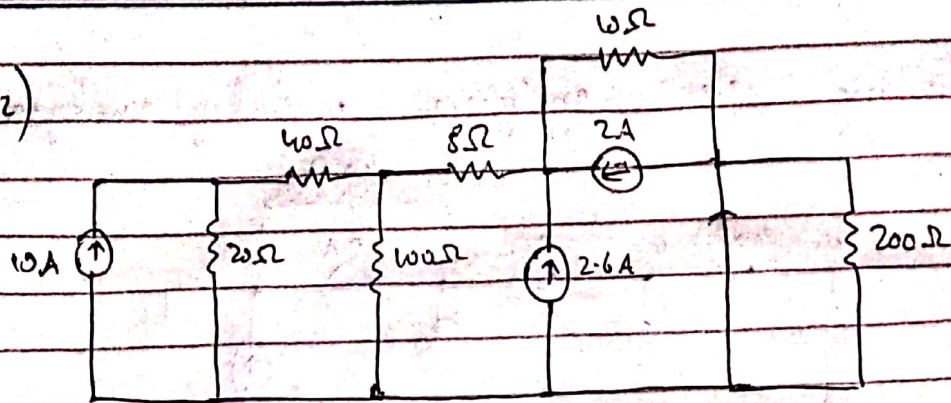


i) Solving for thevenin -

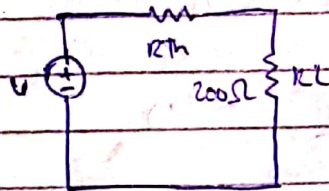

We will find  $R_{th}$  for which we will remove all the current source by short circuit the load resistor.

Re-drawing

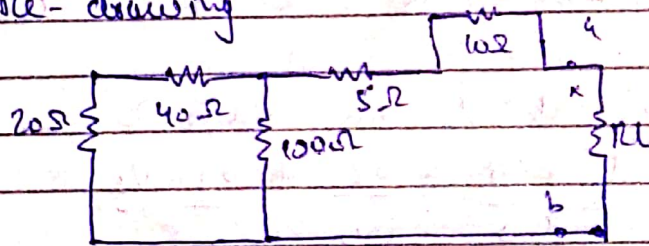

adding all the resistor

$$20 + 40 \parallel 100 + 8 + 10$$

$$60 \parallel 100 + 18$$


$$\frac{60 \times 100}{60 + 100} + 18$$

$$37.5 + 18$$

$$R_{th} = 55.5$$

$$R_{th} = 55.5$$

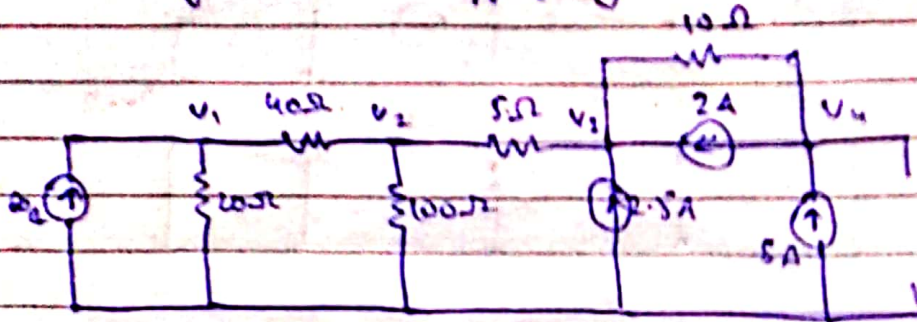Finding  $V_{th}$  applying nodal analysis



applying KCL on  $V_1$

$$\frac{V_1 - V_2}{40} + \frac{V_1}{20} = 10$$

$$\frac{V_1 - V_2 + 2V_2}{40} = 10$$

$$V_1 - V_2 + 2V_2 = 40 \quad \text{--- (1)}$$

applying KCL on node 2

$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{5}$$

$$\frac{80V_2 - 50V_1 + 20V_2 + 400V_2 - 400V_3}{2000}$$

$$-80V_1 + 70V_2 - 400V_3 = 0$$

$$-0.05V_1 + 0.03V_2 - 0.2V_3 = 0 \quad \text{--- (2)}$$

Applying KCL on node 3

$$\frac{V_3 - V_2}{5} + \frac{V_3 - V_4}{10} = 2.5 + 2$$

$$2V_3 - 2V_2 + V_3 - V_4 = 4.5 \times 10$$

$$-2V_2 + 3V_3 - V_4 = 45 \quad \text{--- (3)}$$

Applying KCL on node 4

$$\frac{V_4 - V_3}{10} = 8 - 2$$

$$V_4 - V_3 = 30 \quad \text{--- (4)}$$

Solving


$$V_1 = 27.5$$

$$V_2 = -124.9$$

$$V_3 = -87.5$$

$$V_4 = -57.5$$

ii) For Norton Theorem

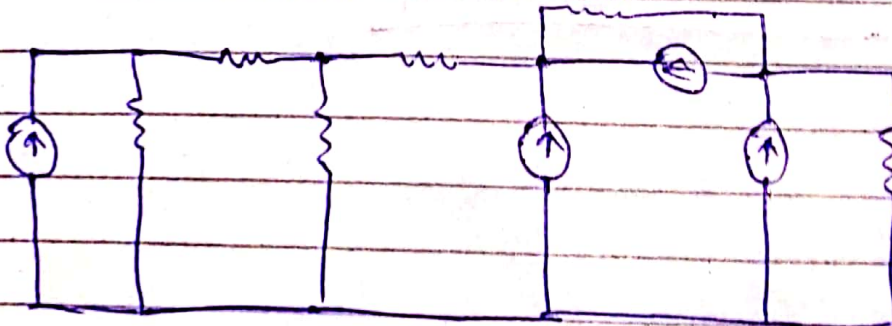

For  $R_N$  will be the same

$$R_N = R_{Th}$$

$$R_N = 52.5$$

And

$$I_N = \frac{V_{Th}}{R_N}$$

$$I_N = 0.09$$

if the circuit are same  
So then find it directly

ii) Using thevenin for finding  
we know that

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$= \left( \frac{5.1}{52.5 + 200} \right)^2 \cdot 200$$

$$P = 0.88 \text{ W}$$

### iii.) To find Thevenin's Equivalent Circuit

If the circuit contains resistor & independent source

you should do

- 1) Connect open circuit b/w a & b.
- 2) Find the voltage across the open circuit which is  $V_{oc}$ .  $V_{oc} = V_{th}$ .
- 3) Deactivate the independent sources. Voltage source  $\rightarrow$  open circuit. Current source  $\rightarrow$  short.
- 4) Find  $R_{th}$  by circuit resistance reduction.

Resistor & dependent sources or independent sources

o) If these are both dependent & independent sources so, then,


- 1) Connect a short circuit b/w a & b.
- 2) Determine the current b/w a & b.
- 3)  $R_{th} = V_{oc} / I_{ab}$

If these are only dependent sources.

- 4) Connect 1 ampere current source flowing from terminal b to a.  $I_t = 1 [A]$
- 5) Then  $R_{th} = V_{oc} / I_t = V_{oc} / 1$



(V3)

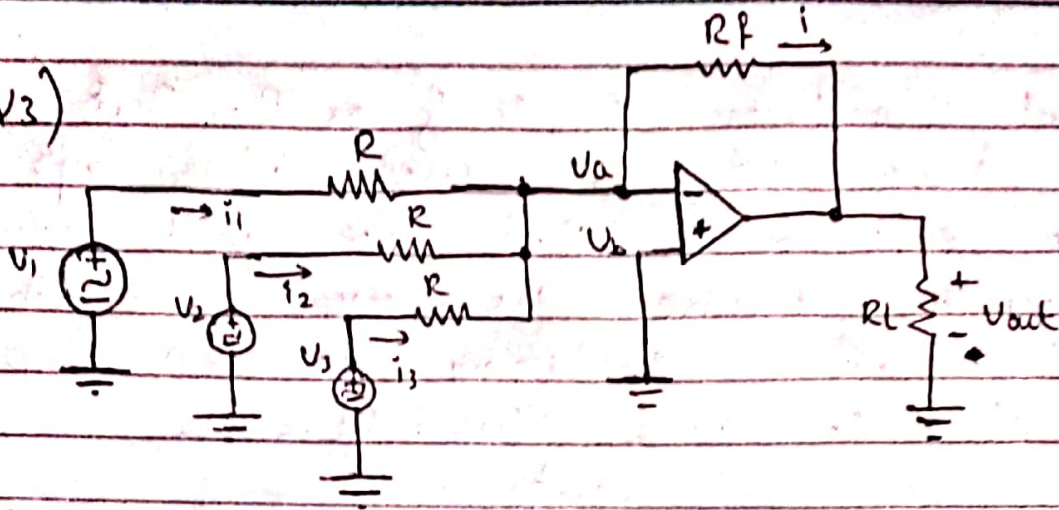

Soln-

Again the goal is to obtain an expression from  $V_{out}$  (which in this case appears across a load resistor  $R_L$ ) in terms of the input ( $V_1$ ,  $V_2$  &  $V_3$ ).

Since no current can flow into the inverting input terminal, So,

$$i = i_1 + i_2 + i_3$$

Therefore we can write the following equation at the node as  $V_a$ .

$$0 = \frac{V_a - V_{out}}{R_f} + \frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - V_3}{R}$$

This equation contains both  $V_{out}$  & the input voltages but it also contains the ~~voltage~~ nodal voltage  $V_a$ .

To remove this unknown quantity from our expression, we need to write an additional equation that relates  $V_a$  to  $V_{out}$  the

input voltages  $V_1$ ,  $V_2$  or  $R$ . That we have not yet used ideal op amp rule 2  $V_a = V_b$  that we will almost certainly require the use of both rule when analyzing an op amp circuit  $V_a = V_b = 0$ . So we can write

$$0 = \frac{V_{out}}{R_f} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

Rearranging the following expression as:

$$V_{out} = \frac{R_f}{R} (V_1 + V_2 + V_3)$$

In this equation where  $V_2 = V_3 = 0$ . We see that this equation derived for essentially the same circuit.

finish

x-----x-----x-----x