

Name: Miandad Khan

ID: 14130

Programs: BC (CS)

Subject: Digital Logic Design


Major Assignment Final-Term Course

Summer Semester 2020

Q10 (a)

A circuit for adding or Subtracting two 4-bit

No. 2

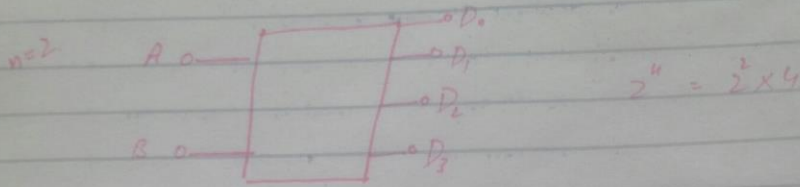

$$2^n = 2^2 \times 4$$

A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$0 = \bar{A} \cdot \bar{B}$$

$$1 = A \cdot B$$


SOP

$$D_0 = \bar{A} \cdot \bar{B}$$

$$D_1 = \bar{A} \cdot B$$

$$D_2 = A \cdot \bar{B}$$

$$D_3 = A \cdot B$$

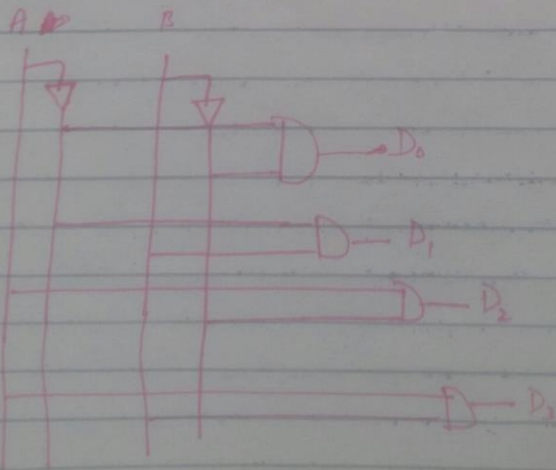

Q1 = (C) Decimal to BCD encoder
 $(345)_{10} = (?)_{BCD}$

$\frac{3}{0011} \quad \frac{4}{0100} \quad \frac{5}{0101}$


$(0011 \ 0100 \ 0101)$

$(345)_{10} = (0011 \ 0100 \ 0101)_{BCD}$ Ans

Q2: For the 4 input multiplexer, data inputs are given as: $D_0=0, D_1=1, D_2=0, D_3=1$



Find the output Y if the selected input are given as:

Sol: a) $S_0=1$ ~~(Ans)~~ $S_1=0$

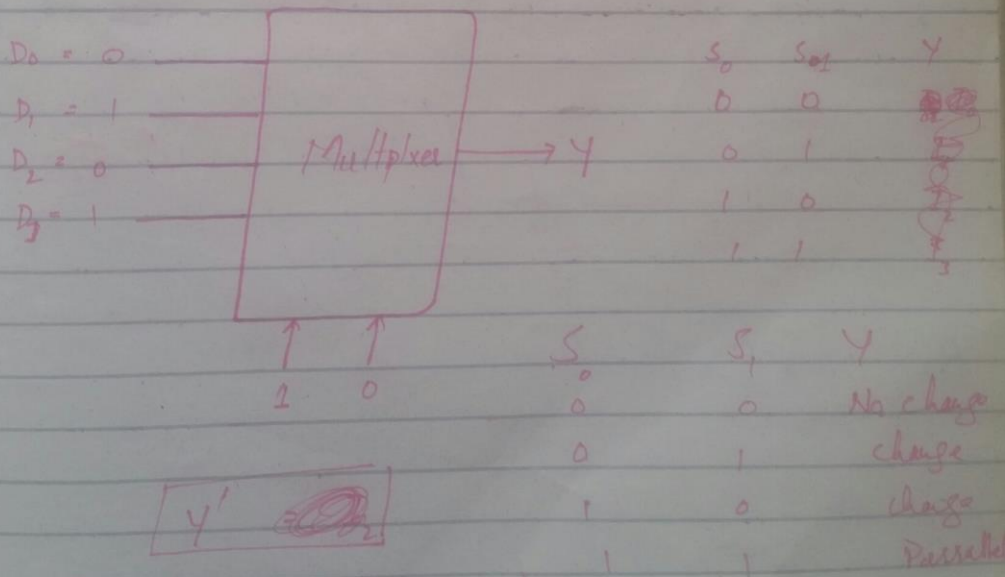

$Y = Y, Y', Y', Y'$ Ans
 $\frac{5}{5}$

Q5

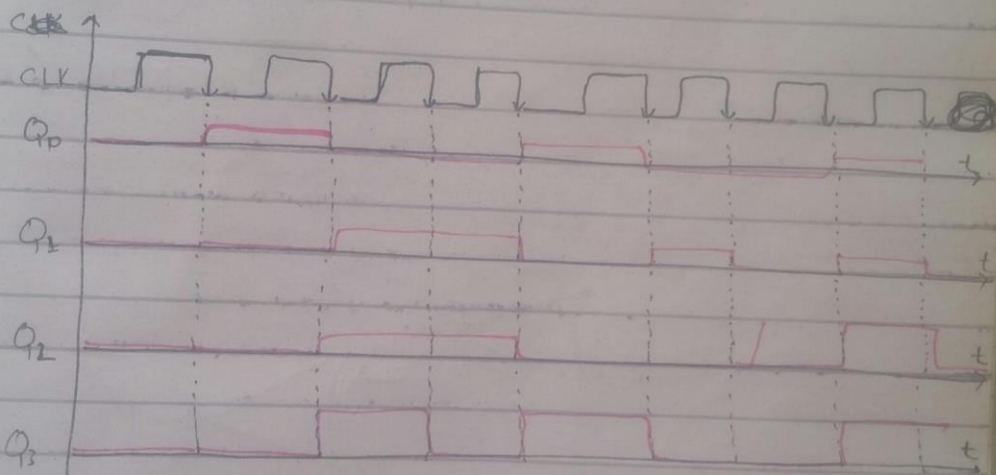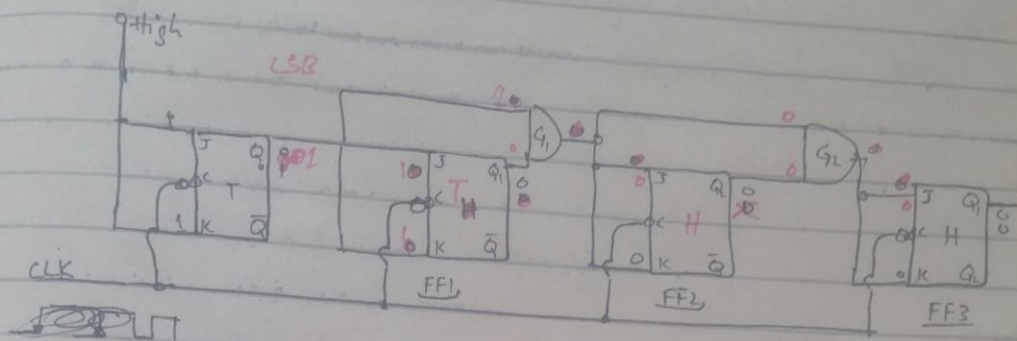

J	K	Q
0	0	NC Hold
0	1	Reset ($Q=0$)
1	0	set ($Q=1$)
1	1	Toggle

Q3:- Timing diagram in Fig 01 show inputs to a 9 bit parity checker- Draw the Σ Even and Σ odd output for the even parity checking.


Sol: Even Parity

B_2	B_1	B_0	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$P = B_2 \oplus B_1 \oplus B_0$

0


(Full adder Sum)

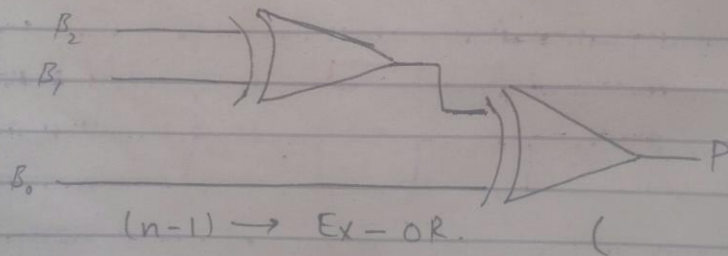

Parity Circuit checker For Even

Odd Parity:

B_2	B_1	B_0	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

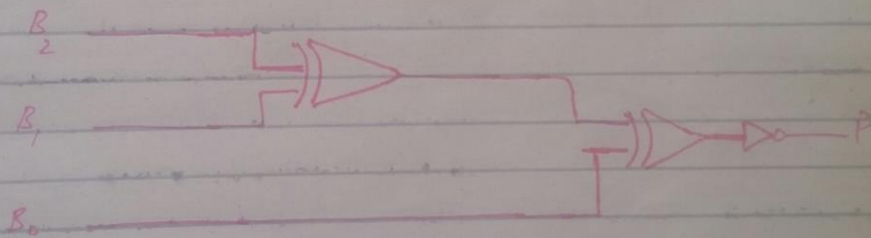

odd parity checker Circuit.

The $1J$, $1K$, $1CLK$, $1\overline{PRE}$, and $1\overline{CLR}$ waveforms in Figure 7–30(a) are applied to one of the negative edge-triggered flip-flops in a 74HC112 package. Determine the $1Q$ output waveform.

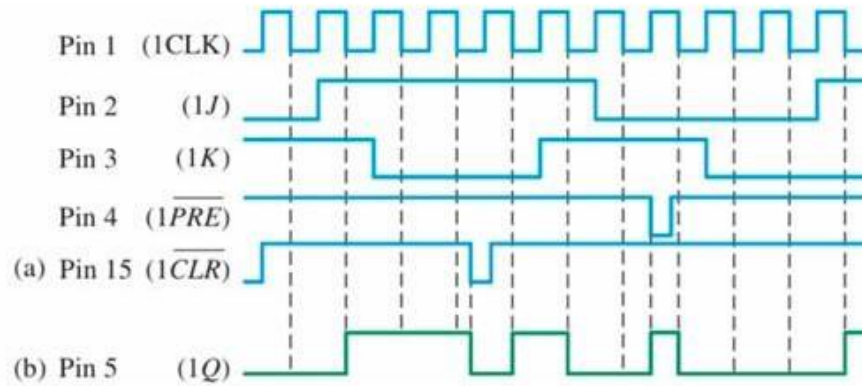


FIGURE 7–30

Solution

The resulting $1Q$ waveform is shown in Figure 7–30(b). Notice that each time a LOW is applied to the $1\overline{PRE}$ or $1\overline{CLR}$, the flip-flop is set or reset regardless of the states of the other inputs.

Related Problem

Determine the $1Q$ output waveform if the waveforms for $1\overline{PRE}$ and $1\overline{CLR}$ are interchanged.

Q4: Ans