

①

Name :- Muhammad Saad

I d # 16097

Subject :- Basic Electro-Mechanical

Teacher :- Sir Ashraf Ali

Q1 (a) There are two well-known formula for calculating the total resistance ----- Write these two formula?

Ans

For two resistance

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

For more than two resistance.

②

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

---

Q

1(b) A quantity often useful in electric circuit analysis is conductance -----  $G = 1/R$

In a series ----- parallel resistor.

Ans In a parallel circuit resistance decrease and conductance increase with the addition of more resistors. because

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\text{So } G_{T1} = \frac{1}{R_1}, \quad G_{T2} = \frac{1}{R_2}$$

$$G_T = G_{T1} + G_{T2}$$

---

3

Q2 In the given circuit, three resistors receive the same amount of voltage (24 Volts) from single source. Calculate the amount of voltage across each resistor.

Ans Given:-

$$R_1 = 1 \Omega$$

$$R_2 = 2 \Omega$$


$$R_3 = 3 \Omega$$

$$\text{Volts} = 24 \text{ V}$$

\* Required

$$I_1, I_2, I_3 = ?$$

$$P_1, P_2, P_3 = ?$$

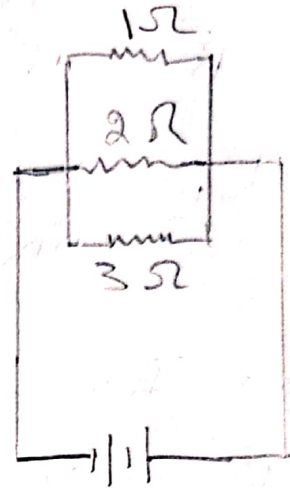

Solution:-

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}$$

$$\frac{1}{R_{eq}} = \frac{6 + 3 + 2}{6}$$

$$= \frac{11}{6}$$

$$R_{eq} = \frac{6}{11} = 0.54 \Omega$$

(4)

⇒ for  $I_1$

$$V = I_1 R$$

$$\frac{V}{R} = \frac{I_1 R}{R}$$

$$I_1 = \frac{V}{R_1} = \frac{24}{1} = 24 \text{ A}$$

⇒ for  $I_2$

$$I_2 = \frac{V}{R_2} = \frac{24}{2} = 12 \text{ A}$$

⇒ for  $I_3$

$$I_3 = \frac{V}{R_3} = \frac{24}{3} = 8 \text{ A}$$

\* Power

for  $P_1$ ,  $I_1 = 24 \text{ A}$ ,  $V = 24 \text{ V}$

$$\begin{aligned} P_1 &= I_1 \times V \\ &= 24 \times 24 \\ &= 576 \text{ watts} \end{aligned}$$

for  $P_2$ :  $I_2 = 12 \text{ A}$ ,  $V = 24 \text{ V}$

$$P_2 = I_2 V$$

(5)

$$P_2 = 12 \times 24$$

$$P_2 = 288 \text{ watts}$$

For  $P_3$ ,  $I_3 = 8 \text{ A}$ ,  $V = 24 \text{ Volts}$

$$P_3 = I_3 V$$

$$= 8 \times 24$$

$$P_3 = 192 \text{ watts}$$

Resistor	Voltage	Current	Power
1 $\Omega$	24 V	24 Amp	576 watts
2	24 V	12 Amp	288 watts
3	24 V	8 Amp	192 watts

Q3 Differentiate b/w the Following

(a) Current and Voltage :-

### Current

\* Def:- Current is the rate at which electric charge flows past a point in a circuit.

\* Symbol :-  $I$

\* Unit :- Ampere (A)

\* SI Unit :-

$1 \text{ amp} = 1 \text{ coulomb/second}$

\* Field created :-

A magnetic field

\* In series connection :-

current is the same through all components connected in series

\* In parallel :-

gets distributed over components connect in parallel

### Voltage

voltage is the P.D in charge b/w two points in an electrical field.

$V$

volts (V)

$1 \text{ volt} = 1 \text{ J/coulomb (V=WC)}$

An electrostatic field.

voltage get distributed over component connect in series.

It is the same across all component connect in parallel

⑥

⑦

(b) Resistance &amp; conductance :-

Resistance

Conductance

\* It is a property of a conductor which tells us how much the resistor resist or opposes the current to pass through it.

It is a property of a conductor which tells us how much the resistor allows the current to pass through it.

\* Unit :- Ohm ( $\Omega$ )

unit :- Siemens (S)

\* Depend on resistivity of material

Depends on conductivity property of material.

(c) Power &amp; Energy :-

Power

Energy

\* It is the rate at which work is done, or energy is transmitted.

It is the capacitor to do work. ~~Energy~~ Energy is power integrated over time.

\* Unit :- Joules = watt  $\times$  second

watt = joules / second

\* Symbol :- W

P

\* Energy can be transformed from one form to another

Power is the rate at which energy is transferred.



### (d) Inductance

- \* The effect of an inductor in a circuit is measured as inductance.
- \* It is a property of a current carrying conductor which generates a M.F around conductor
- \* Unit:- Henry (H)

### (e) Capacitance:-

- Each capacitor is built to have a specific amount of capacitance.
- It is a property of a device to hold & store electric charges.
- Farad

### (e) Synchronous

- \* machine whose rotor speed & the speed of the stator M.F is equal.  $N = N_s = \frac{120f}{P}$
- \* Does not have slip. The value of slip is zero
- \* Efficiency is greater than Asynchronous motor.
- \* It is costly as compared to Asynchronous motor.

### Asynchronous motor.

- machine whose rotor rotates at the speed less than synchronous speed  $N < N_s$ .
- Have slip, values of slip is not equal to zero.
- Less efficient
- Less costly