

Name Nehad
Muhammad

Course Electric
power
distribution
utilization

I-D 14912

department B-tech (E)

instructor Engr. M. Saleed
Jan

date 26-6-2020

Question 3

Given data

Resistance of load across the positive outer, $= 7\Omega$

Resistance of load across the negative outer is, $= 9\Omega$


Resistance of each conductor is $= 0.2\Omega$

voltage between any outer and neutral is, $v = 260V$

Required data

feeding end voltage = ?

Solution

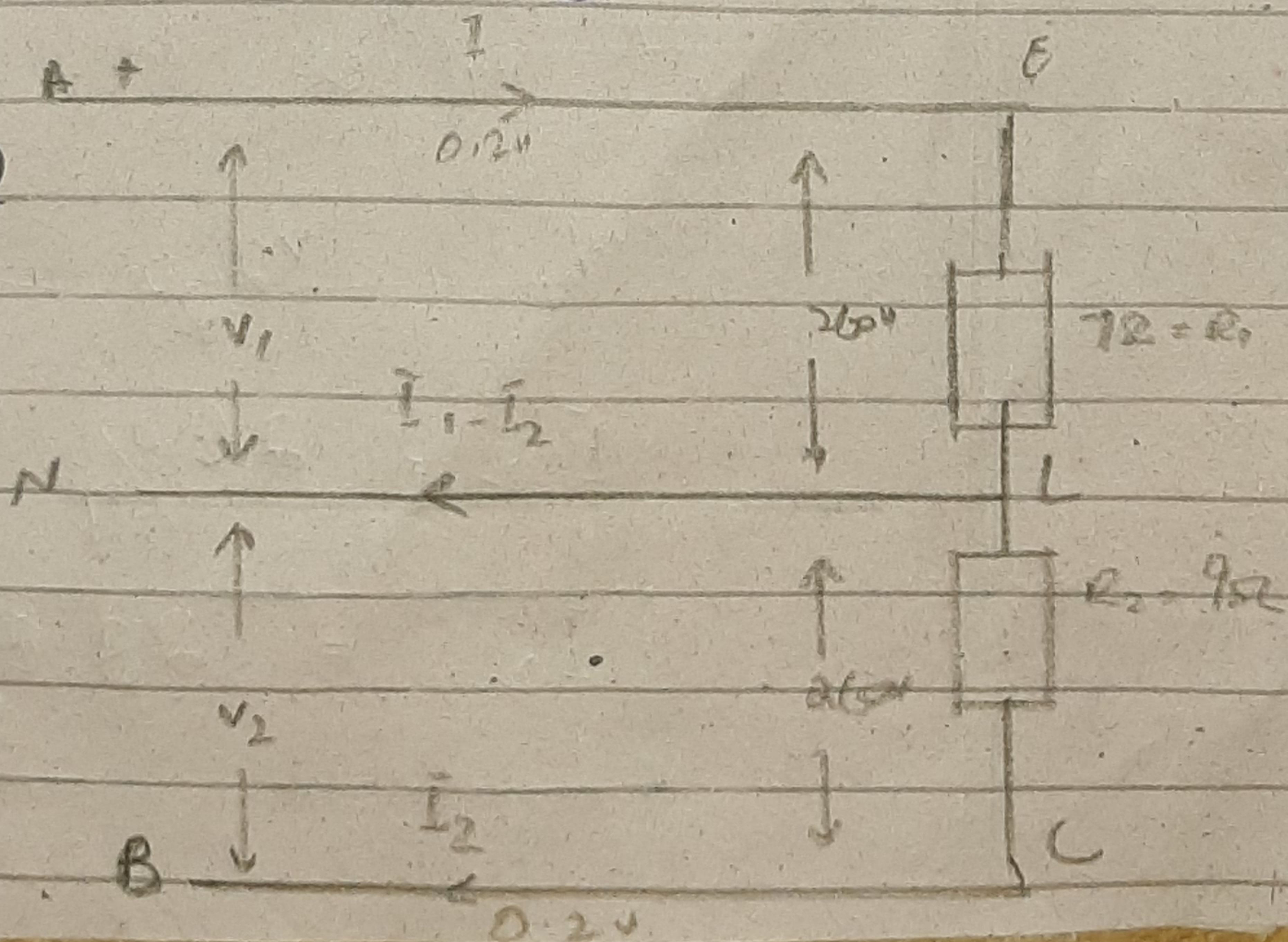

first we find

* Current I_1 on the +ve output
so we know that from
Ohm law.

$$I_1 = \frac{V_1}{R_1} \rightarrow (1)$$

put value in equation 1

$$I_1 = 260/7$$

$$I_1 = 37.14 \text{ A}$$

* Current on -ve output $I_2 = ?$

So we know that

$$I_2 = \frac{V_2}{R_2} \rightarrow (2)$$

put value in (2)

$$I_2 = \frac{260}{9} \rightarrow (2)$$

$$I_2 = 28.88 \text{ A}$$

$$I_2 = 28.88 \text{ A}$$

Current in neutral is $I_1 - I_2 \rightarrow$

put value in equation 3)

$$= 37.14 - 28.88$$

$$I_1 - I_2 = 8.26 \text{ A}$$

Now

voltage between +ve outer and neutral at feeding end is

$$V_1 = V_{EL} + I_1 R_{AE} + (I_1 - I_2) R_{NL} \rightarrow (4)$$

put value in equation (4)

$$V_1 = 260 + 37.14 \times 0.2 + (8.26) \times 0.2$$

$$V_1 = 260 + 7.428 + 1.652$$

$$V_1 = 269.08 \text{ V}$$

Now voltage b/w -ve outer and neutral is

$$V_2 = V_{EL} - (I_1 - I_2) R_{NL} + I_2 R_{SC} \rightarrow (5)$$

put value in equation 5)

$$V_2 = 260 - (8.26)(0.2) + 28.88 \times 0.2$$

$$V_2 = 260 - 1.652 + 5.776$$

$$V_2 = 265.776 - 1.652$$

$$V_2 = 264.124 \text{ V}$$

Question 2

Given data

Supply load is

150 A, 200 A, 250 A, 100 A

distances of 500 m, 1300 m,
2300, 3000 m.


the resistance of each
conductor is $R = 0.02$ per 1000 m

potential difference at point
A = 400 V

Required data

potential difference
at each load = ?

Solution

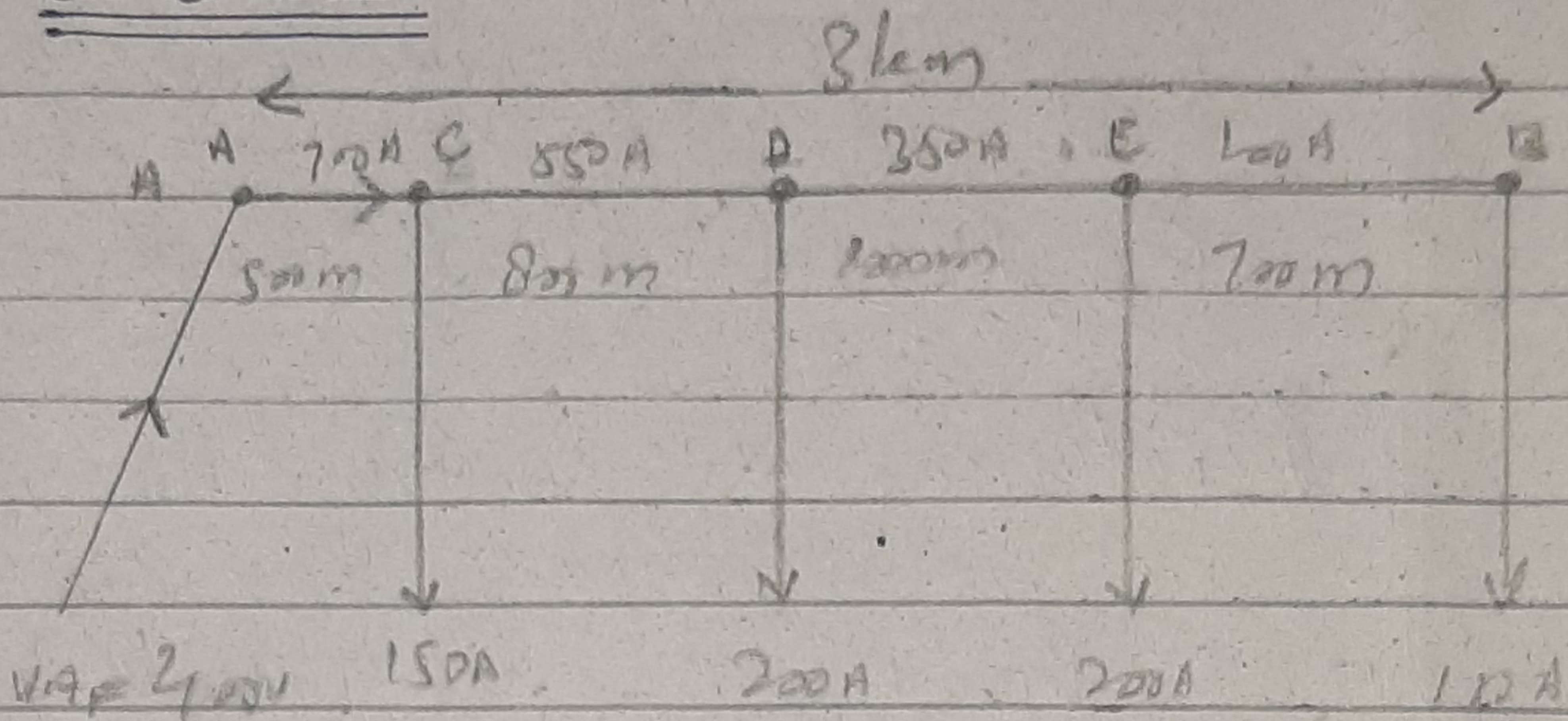

The single line diagram of the distributor with its tapped current.

$$\text{Resistance per } 1000\text{m distributor} \\ \text{is} = 2 \times 0.02 = 0.04 \Omega$$

Resistance of section AC, R_{AC}

$$R_{AC} = 0.04 \times \frac{500}{1000} \\ = 0.04 \times 0.5$$

$$R_{AC} = 0.02 \Omega$$

Resistance of section CD, R_{CD}

$$\cancel{AC}, R_{AC} \quad CD, R_{CD} = \frac{0.04 \times 800}{1000}$$

$$= 0.04 \times 0.8$$

$$CD, R_{CD} = 0.032 \Omega$$

Resistance of section DE, R_{DE}

$$DE, R_{DE} = \frac{0.04 \times 1000}{1000}$$

$$= 0.04 \times 1$$

$$DE, R_{DE} = 0.04 \Omega$$

Resistance of section

$$EB, R_{EB} = \frac{0.04 \times 700}{1000}$$

$$= 0.04 \times 0.7$$

$$EB, R_{EB} = 0.028 \Omega$$

The current in the various sections of distributor are

$$I_{EB} = 100 \text{ A} \quad , \quad I_{DE} = 100 + 250$$

$$= 350 \text{ A}$$

$$I_{CD} = 350 + 200 = 550 \text{ A}$$

$$I_{AC} = 550 + 150 = 700 \text{ A}$$

potential difference at point C = ?

V_C = voltage at A - voltage drop in A.C

$$= V_A - I_{AC} \cdot R_{AC}$$

$$= 400 - 700 \times 0.02$$

$$= 400 - 14$$

$$V_C = 386 \text{ V}$$

potential difference at point D = ?

$$V_D = V_C - I_{CD} \cdot R_{CD}$$

$$= 386 - 550 \times 0.032$$

$$= 386 - 17.6$$

$$= 368.4 \text{ V}$$

$$V_D = 368.4 \text{ V}$$

potential difference at point E = ?

$$\begin{aligned}V_E &= V_D - I_{DE} \cdot R_{DE} \\&= 368.4 - 350 \times 0.04 \\&= 368.4 - 14 \\&= 354.4\text{V}\end{aligned}$$

$$V_E = 354.4\text{V}$$

potential difference at load
point B

$$\begin{aligned}V_B &= V_E - I_{EB} \cdot R_{EB} \\&= 354.4 - 100 \times 0.028 \\&= 354.4 - 2.8\end{aligned}$$

$$V_B = 351.6\text{V}$$

Question 1

Given data

D.C distributor 2-wired
Total length of Dis
= 500m

voltage load, 10A, 40A, 30A, 40A

distance at various load is
from end (X) 100m, 250m, 350m
and 450m.


Cross-sectional area of
conductor = 2cm^2

Resistivity = $1.5 \times 10^{-5} \Omega\text{cm}$

Required data

minimum consumer
voltage = ?

Solution

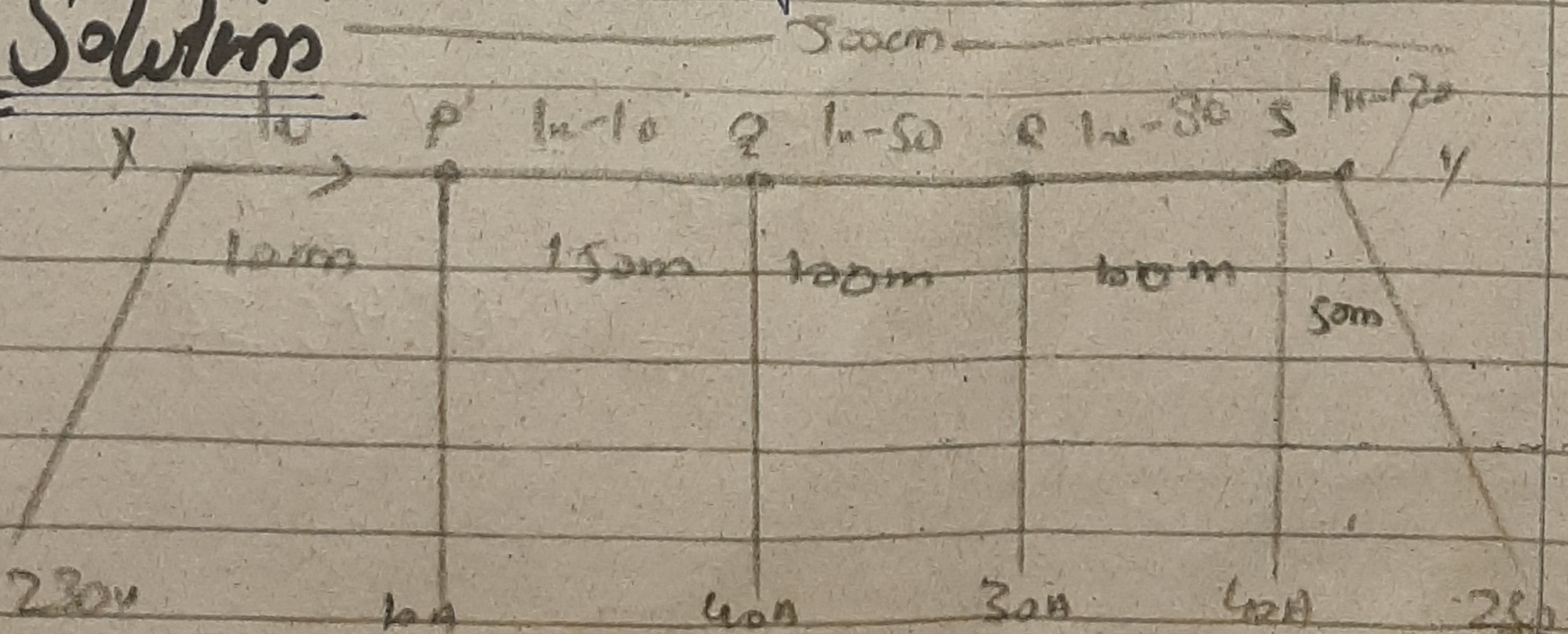

Let I_x amperes be the current supplied from the feeding end (A).
When current in the various sections of the distributor are shown in fig

Resistance of 1m length of distributor = $\frac{2 \times 1.5 \times 10^{-5} \times 100}{1}$

$$= 2 \times 1.5 \times 10^{-3} \Omega$$

$$\text{or} \\ = 3 \times 10^{-3} \Omega$$

Resistance of section XP, R_{XP}

$$R_{XP} = (3 \times 10^{-3}) \times 100$$

$$R_{XP} = 0.3 \Omega$$

Resistance of section PQ, R_{PQ}

$$R_{PQ} = (3 \times 10^{-3}) \times 150$$

$$= 0.45 \Omega$$

Resistance of section R_R, R_{RR}

$$= (3 \times 10^{-3}) \times 100$$
$$= 0.3 \Omega$$

Resistance of section R_S, R_{RS}

$$= (3 \times 10^{-3}) \times 100$$
$$= 0.3 \Omega$$

Resistance of section S_y, R_{Sy}

$$= (3 \times 10^{-3}) \times 50$$
$$= 0.15 \Omega$$

Now

voltage at y = voltage at x - Drop over length $x-y$

$$V_y = V_x - (I_x R_{Rp} + (I_x - 10) R_{RQ} + (I_x - 50) R_{RR} + (I_x - 80) R_{RS} + (I_x - 120) R_{Sy}) \rightarrow$$

$$V_y = 230 - (0.3 I_x + 0.45(I_x - 10) + 0.3(I_x - 50) + 0.3(I_x - 80) + 0.15(I_x - 120))$$

$$V_y = 230 - (0.3 I_x + 0.45 I_x - 4.5 + 0.3 I_x - 15 + 0.3 I_x - 24 + 0.15 I_x - 18)$$

$$230 = 230 - (1.65 I_x - 61.5)$$

$$230 = 230 - 1.65 I_n + 61.5$$

$$1.65 I_n = 61.5$$

$$I_n = \underline{61.5}$$

$$1.65$$

$$I_n = 37.27 \text{ A}$$

Knowing the value of I_n , current is any section can be determined thus current in Section PQ

$$I_{PQ} = I_n - 10 \Rightarrow 37.27 - 10$$

$$I_{PQ} = 27.27 \text{ A}$$

Section QR

$$\text{from Q to R} = -12.73$$

$$\text{R to Q} = 12.73$$

$$I_{QR} = I_n - 50$$
$$= 37.27 - 50$$

$$I_{QR} = -12.73 \text{ A}$$

Section $I_{RS} = ?$

$$I_{RS} = I_n - 80$$

$$= 37.27 - 80$$

$$\left[\begin{array}{l} \text{from } R_{tos} = -42.73 \\ \text{from } S_{tor} = 42.73 \end{array} \right]$$

$$\boxed{I_{Rs} = -42.73A}$$

Section $I_{Sy} = ?$

$$\text{from } S_{toy} = -82.73$$


$$I_{Sy} = I_x - 120$$

$$\text{from } Y_{tos} = 82.73$$

$$= 37.27 - 120$$

$$\boxed{I_{Sy} = -82.73A}$$

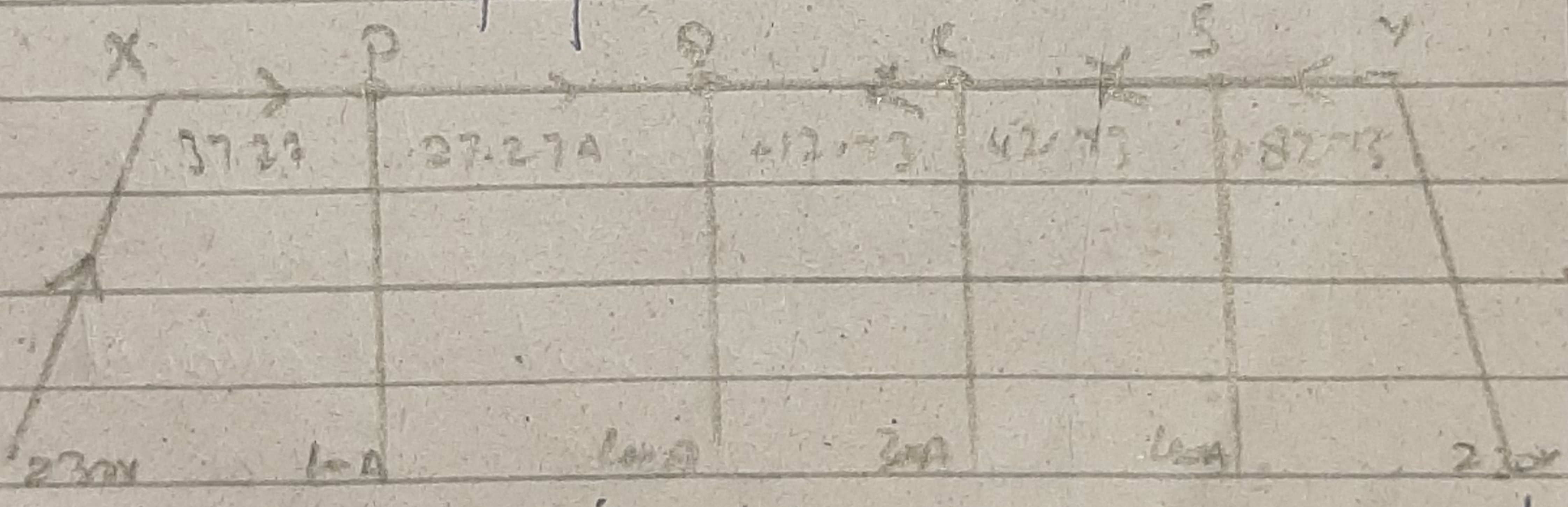The actual distribution current of various section is show in fig



From the figure it's clear that current are coming to load point Q from both end. Hence Q is the point of maximum potential difference

$$\begin{aligned} V_Q &= V_x - (I_x \cdot R_{xp} + I_{PQ} \cdot R_{PQ}) \rightarrow D \\ &= 230 - (37.27 \times 0.3 + 27.27 \times 0.45) \\ &= 230 (11.181 + 12.2715) \\ &= 230 - 23.4525 \end{aligned}$$

$$\boxed{V_Q = 206.54V \text{ rms}}$$

Question 4 (a)

Answer

When the insulating material used for underground cable is hygroscopic. So it must be enclosed in a water proof covering like a lead sheath.

To protect cable from moisture and the breakdown of cable.

While when it has low electric strength so it cannot avoid the breakdown of the cable.

Q4 (B)

Ans

Rubber cannot be used as an insulating

material for underground

cable. Because

* Rubber may be obtained from
Silky Sap of tropical trees.

* It has relative permittivity
varying between 2 and 3
dielectric strength.

* Although pure rubber has
reasonably high insulating
properties. It suffers from
some major drawbacks.

Q5 (A)

ANSWER

↳ A trench of about 105 meters deep and 45 cm wide is dug.

↳ The cable is laid over the sand bed. The sand bed protects the cable from the moisture from the ground.

↳ When multiple cables are to be laid in the same trench, a horizontal or vertical spacing of about 30 cm is provided to reduce the effect of mutual heating.

↳ This method is the most popular as it is simple and cheap.

The cables to be laid using this method must have the covering of bituminised paper and

hesion tape so as to provide protection against corrosion and electrolysis.

Q.5 B

Answer

The solid system of cable laying is mainly performed where the cable is laid in the wood, cast iron or another non soil surface. Normally cable is laid in the manner which provide good mechanical strength of cable.

* Solid system is expensive compare to the direct laid system and heat dissipation capacity is not much good compare

with other system. But

for toughing material woods

are much cheap so it

is widely used by

Considering the economical
impacts.
