

①

Abdul Aziz ID# 13741 BEE

Q1

Ans

Given data:

Two voltmeters range = 0-300V

$$R_1 = 25 \text{ k}\Omega$$

$$R_2 = 15 \text{ k}\Omega$$


Total voltage $V_I = 500 \text{ V}$

Required

Voltage reading in 1st voltmeter = ?

" " " 2nd voltmeter = $V_2 = ?$

Diagram :-

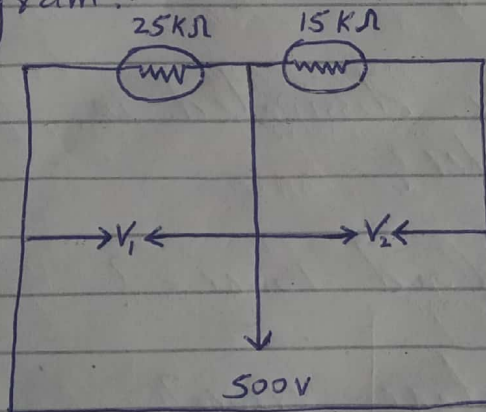

Solution:

Here we use voltage divider rule the reading of the voltmeter are.

$$V_1 = \frac{25 \text{ k}\Omega}{25 \text{ k}\Omega + 15 \text{ k}\Omega} \times 500 \text{ V}$$

$$V_1 = 312.5 \text{ V}$$

(2)

$$V_2 = \frac{15K\Omega}{15K\Omega + 25K\Omega} \times 500$$

$$V_2 = 187.5V$$

Q=2

Ans



Given data:-

$$R_1 = 0.5\Omega$$


$$R_2 = 0.5\Omega$$

$$\text{Power} = P = 200W$$

$$I = 4A$$

Required:

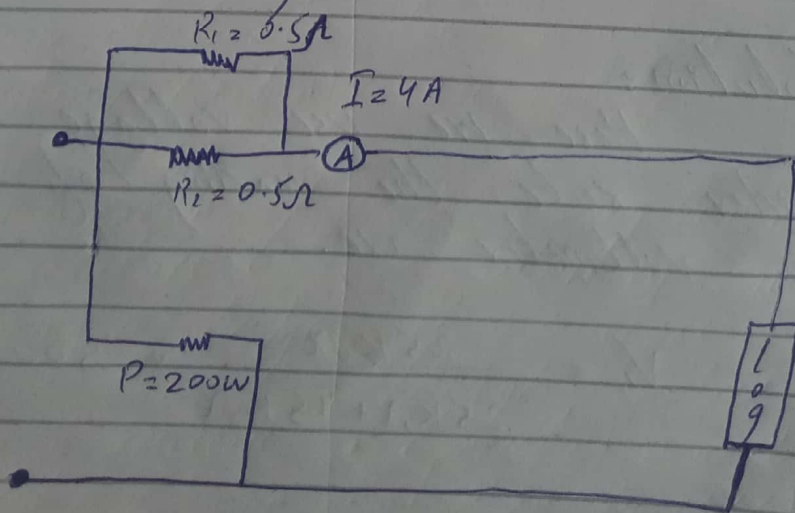- (a) Power dissipated in the voltmeter?
- (b) True Load Power = ?
- (c) Percentage error?



(3)

Solution:

Resistance of current coils

$$R_c = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_c = \frac{0.5 \times 0.5}{0.5 + 0.5}$$

$$R_c = \frac{0.25}{1} = 0.25 \Omega$$

$$\begin{aligned} \text{(a)} \quad I^2 R_c &= (14)^2 \times 0.25 \\ &= 16 \times 0.25 \end{aligned}$$

$$I^2 R_c = 4 \text{ W}$$

$$\begin{aligned} \text{(b)} \quad \text{True load power} &= 200 - 4 \\ &= 196 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad \% \text{ error} &= \frac{P - \text{True load}}{\text{True load power}} \times 100 \\ &= \frac{200 - 196}{196} \times 100 \end{aligned}$$

% error = 2.0408.

Question No # 3 (a)

⇒ Wheatstone Bridge:

The wheatstone bridge was invented by Samuel Christie in 1833 and improved by Sir Charles Wheatstone in 1843.

⇒ Kelvin's Bridge:

Also known as double bridge and in some countries a Thomson bridge, is a measuring instrument used to measure unknown electrical resistance.

Wheatstone Bridge

Kelvin Bridge

- Used to measure unknown electrical resistance. (medium)

Used to measure low resistance very accurately.

- Combination of 4 resistors forming a bridge

When implementing in laboratory, connect all resistors through wires

- Unknown resistors connected to 2 known resistors and Galvanometer

Connecting wire b/w Point m & n having (x). Galvanometer connect to Point m & n.

(5)

Question # 3 (b)

In the bridge configuration, we can apply the KVL in two loops - the upper ($R_1 - R_2$ null indicator) and lower ($R_3 - R_4$ null indicator).

It is more convenient to apply KVL in upper loop (left R - Right R_3 - op-amp input).

Reasoning as follows.

For example. If an input is connected at the inverting input. It sinks current from op-amp output through the right resistor (R). and a voltage drop

$$V_R = I * R$$

Appears across this resistor. The op-amp seeks to this intervention by passing the same current through left resistor R and external load.


Thus producing the same voltage drop

$$V_R = I * R$$

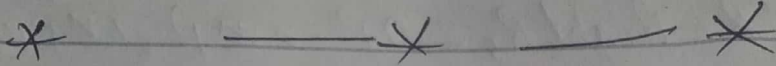(6)

As a result. The
difference b/w two voltage
drops, applied to op-amp
differential input is almost
zero.

So we consider only the
upper loop without minding
what is in lower loop.



Q No # 4 (a)


⇒ Energy Meter:-

It is an instrument which measures the electrical energy.

Since the electrical energy consumed by a load adds up as the time goes on. It is evident that watt hour meter is an integrity type instrument.

It should be noted that the energy meter designed for DC circuits can be used on AC circuits but the reverse is not true.

Induction Principle

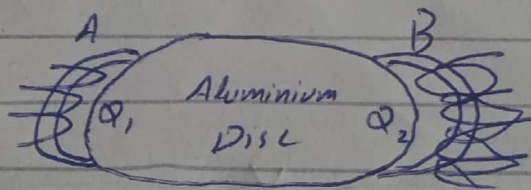

Above figure shows the working principle of induction type energy meters.

(8)


Part (b)

\Rightarrow When $\alpha = 0^\circ$ (i.e. the two fluxes are in phase) then deflecting torque is zero.

\Rightarrow The deflecting torque will be maximum when $\alpha = 90^\circ$ i.e. the flux has a phase difference of 90° .

\Rightarrow The deflecting torque is same of every instant since α_m , ϕ & α , $m \leq 0$ are fixed for a given condition.

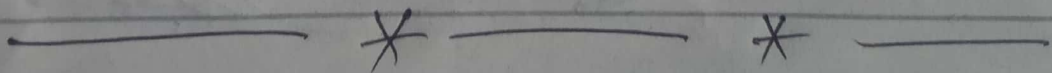\Rightarrow The direction of deflecting torque depends upon which flux is leading the other.



(9)

Q No (5) (a)

Ans The series magnetic is wound with a wire of few axis connected in series with load so that it carries the load current. The coil of this magnetic is highly non-inductive.

(b)

Ans

Meter Constant:

$$N \propto \text{energy}$$
$$N = K \times \text{energy}$$

Where K is constant called meter constant.

$$\therefore \text{Meter constant} = K = \frac{N}{\text{energy}}$$

$$= \frac{\text{No. of revolution}}{\text{Kwh}}$$

Hence the no. of revolutions made by the disc for 1 Kwh of energy consumption is called meter constant.

For example:

if meter constant
of energy meter is 1500 rev/kwh.
it means that for
consumption of 1 kWh the
disc will make 1500
revolution.

* — * — * — * — * — *