


Course Title : Electrical Network
Analysis

Module : 4th

Instructor: Dr Shahryar Shafique


Name : Abdul Basit Khan

Student ID: 14564

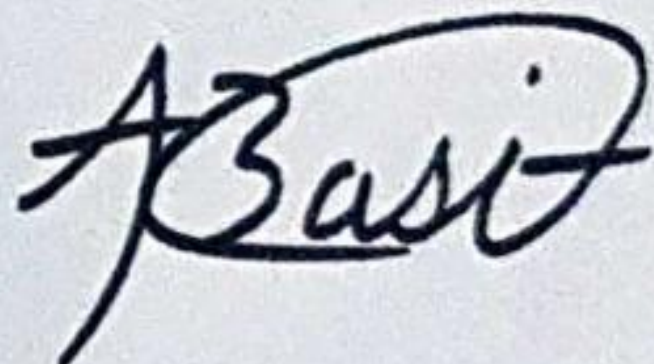Student Signature: 

Date : 14th April, 2020

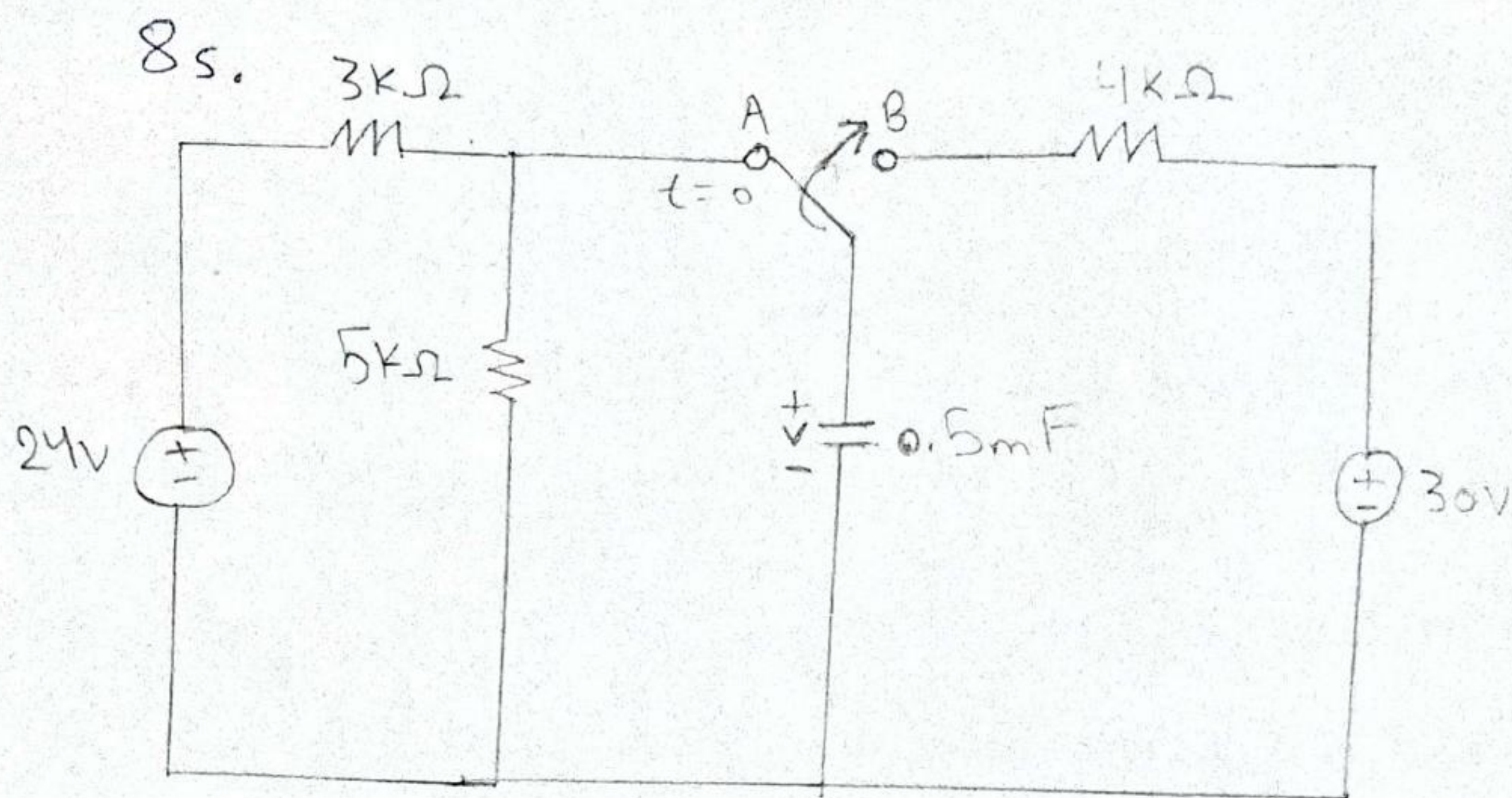Q1 The switch in Fig. 1 has been in Position A for a long time. At $t=0$ the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t=2s$ and $8s$.



Sol:

For $t < 0$, the switch is at Position A. The capacitor acts like an open circuit to dc, but v is same as the voltage across the $5k\Omega$ resistor. Hence the voltage across the capacitor just before $t=0$ is obtained by voltage division as

$$v(0^-) = \frac{5}{5+3} (24) = 15V$$

Using the fact that the capacitor voltage

can not change instantaneously

$$v(0) = v(0^-) = v(0^+) = 15V$$

~~Three switch in position~~

For $t > 0$, the switch is in position B. The Thevenin resistance connected to the capacitor is $R_{Th} = 4k\Omega$, and the time constant is

$$\tau = R_{Th} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2s$$

Since the capacitor acts like an open circuit to DC at steady state,

$V(\infty) = 30V$. Thus,

$$\begin{aligned} V(t) &= V(\infty) + [V(0) - V(\infty)] e^{-t/\tau} \\ &= 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t})V \end{aligned}$$

At $t = 2s$

$$V(2) = (30 - 15e^{-0.5(2)})V$$

$$V(2) = (30 - 15e^{-1})V$$

$$V(2) = (30 - 5.517)V$$

$$V(2) = 24.483V$$

$$V(2) = 24.48V$$

At $t = 8s$

$$V(8) = (30 - 15e^{-0.5(8)})V$$

$$V(8) = (30 - 15e^{-4})V$$

$$V(8) = 30 - 15(0.0183)$$

$$V(8) = 30 - 0.2745$$

$$V(8) = 29.7255$$

$$V(8) = 29.72V$$

Q2

Determine the inductor current for both $t > 0$ and $t < 0$ for the circuit in Fig 2

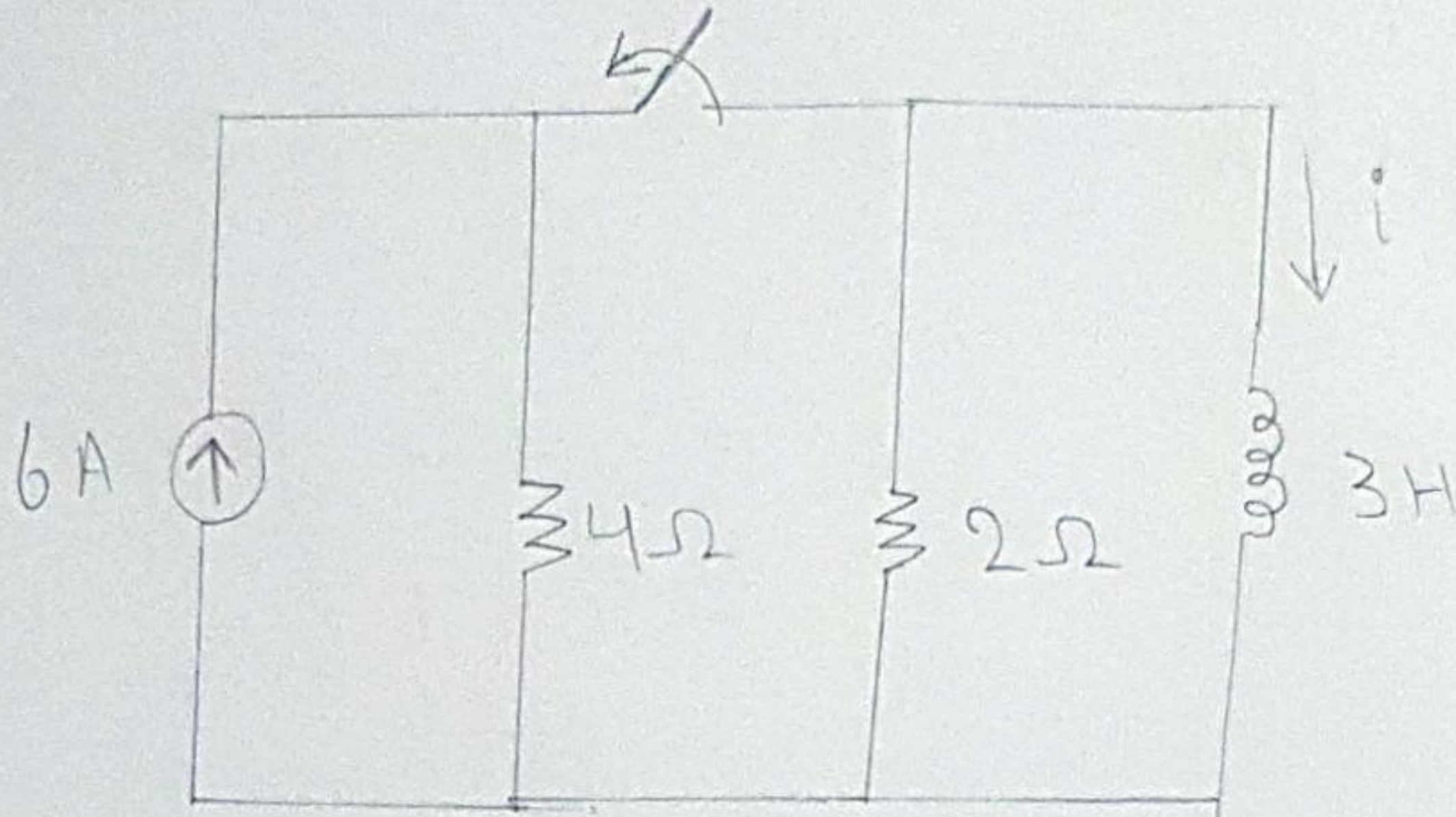


Fig 2

Sol:

For $t < 0$

The switch is closed and inductor acts as short circuit therefore inductor current is

$$i = 6A$$

For $t > 0$

The switch is opened and time constant

$$\tau = L/R$$

$$\tau = \frac{3}{2}$$

Now the inductor current

$$i(t) = 6e^{-t/4}$$

$$i(t) = 6e^{-t/3/2}$$

$$i(t) = 6e^{-\frac{2t}{3}} \text{ (A)}$$

Q3 A Series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Find the response when $L = 0.5 \text{ H}$, $R = 4 \Omega$
and $C = 0.2 \text{ F}$. Let $i(0) = 1$, $di(0)/dt = 0$

Sol

Given $L = 0.5 \text{ H}$

$$R = 4 \Omega$$

$$C = 0.2 \text{ F}$$

$$i(0) = 1 \text{ A}$$

$$\frac{di(0)}{dt} = 0$$

The step response of the branch voltage
of the given RLC circuit is described
by:

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by L ,

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10}{L}$$

For right hand side of the equation
Multiply by $\frac{C}{C}$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{I_0}{LC}$$

And $C = 0.2F$, thus

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{2}{LC}$$

Substitute,

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \dots (1)$$

The general equation for a source free Series RLC circuit is given by:

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC} \dots (2)$$

Compare both the equations 1 & 2

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \dots (4)$$

$$\frac{I_s}{LC} = 20 \dots (5)$$

From (3), α is given by

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/s} \quad \dots (6)$$

The natural frequency ω_0 is given by

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

From (4)

$$\omega_0 = \sqrt{10} \text{ rad/s}$$

From (6) and (7)

From ω_0 and α

$$\therefore \alpha > \omega_0$$

\therefore The circuit is over damped

The roots of the characteristic equation is given by,

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 + \sqrt{4^2 - \sqrt{10}^2}$$

$$= -4 + \sqrt{6} \text{ rad/s}$$

And

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 - \sqrt{4^2 - \sqrt{10}^2}$$

$$= -4 - \sqrt{6} \text{ rad/s}$$

From $\frac{I_s}{LC} = 20$ The steady state current is given by

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2 = 2A \rightarrow (8)$$

The current for the over damped case is given by:

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

Substitute $t = 0$

$$i(0) = I_s + A_1 + A_2$$

Substitute, $1 = 2 + A_1 + A_2$

Thus, $A_1 + A_2 = -1 \rightarrow (10)$

From (9) $i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$ find

$$\frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute $t = 0$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute the values,

$$(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0 \quad \text{--- (11)}$$

Solve for $A_1 + A_2 = -1$ and $(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0$
means solving (10) & (11)

$$A_1 = -1.316$$

$$A_2 = 0.316$$

Substitute $i(t)$ (9)

$$i(t) = 2 - 1.316e^{(-4 + \sqrt{6})t} + 0.316e^{(-4 - \sqrt{6})t} \quad A$$

From (9) damped current $i(t)$ find $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute $t = 0$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute the values,

$$(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0$$

Solve $(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0$ and
 $(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0$

$$A_1 = -1.316$$

$$A_2 = 0.316$$

Substitute in $i(t)$

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t} \quad A$$

Q4: A Series RLC circuit has $R = 100\Omega$
 $L = 240\text{H}$ and $C = 10\text{mF}$. if the
input voltage is $v(t) = 10\cos 2t$,
Find the current flowing through
the circuit.

Sol: Input voltage is $v(t) = 10\cos 2t\text{V}$

Hence

$$\text{Amplitude} = V_m = 10\text{V}$$

$$\text{Angular frequency } \omega = 2\text{ rad/s}$$

$$\text{Phase angle, } \phi = 0^\circ$$

So Phasor for the voltage $v(t)$

$$V(t) = 10\angle 0^\circ\text{V}$$

Now for Inductive reactance

$$X_L = \omega L$$

$$\text{So } \omega = 2\text{ rad/s}, L = 240\text{H}$$

$$X_L = (2)(240)$$

$$X_L = 480\Omega$$

Now For capacitive reactance

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2\text{ rad/s}, C = 10\text{mF}$$

$$= \frac{1}{2(10 \times 10^{-3})}$$

$$= \frac{1}{2 \times 10^2}$$

$$= \frac{1 \times 10^2}{2}$$

$$= \frac{100}{2}$$

$$X_c = 50 \Omega$$

Now for Impedence

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, X_L = 480 \Omega, X_C = 50 \Omega$$

Putting in equation

$$Z = (100 + 480j - 50j) \Omega$$

Represent "Z" in Phasor form

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left(\frac{430}{100} \right)$$

$$Z = \sqrt{10000 + 184900} \angle \tan^{-1} (4.3)$$

$$Z = \sqrt{194900} \angle \tan^{-1} (4.3)$$

$$Z = 441.47 \angle 76.90^\circ \Omega$$

Now for current flowing in the circuit ;

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ, Z = 441.47 \angle 76.90^\circ \Omega$$

Putting in equation

$$i = \frac{10 \angle 0^\circ}{441.47 \angle 76.90^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.90^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.90^\circ \text{ A}$$

$$= 22.6 \angle -76.90^\circ \text{ mA}$$


So,

The general expression for 'i'

$$i = 22.6 \cos(2t - 76.90^\circ) \text{ mA}$$

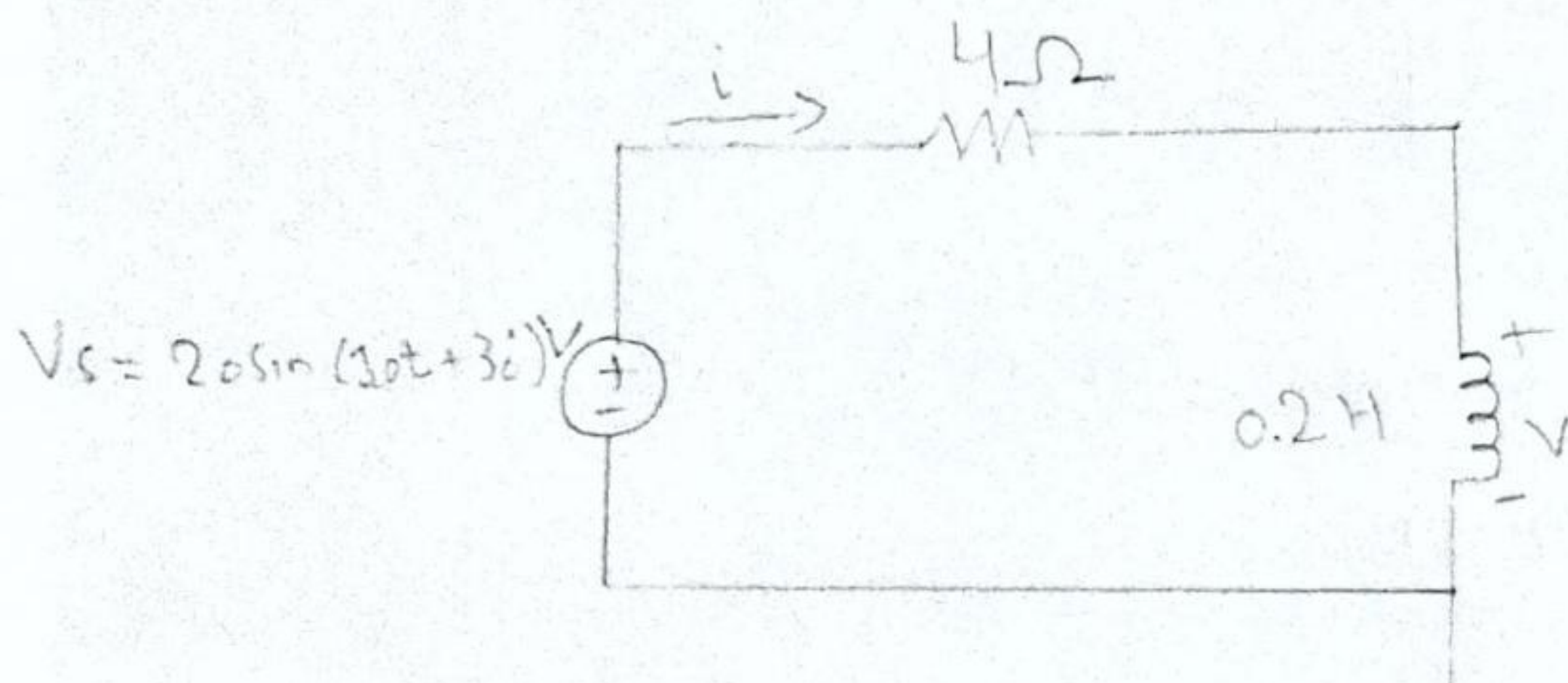Question 5

Find $v(t)$ & $i(t)$ in the circuit in the figure



Sol

For $i(t)$

From the voltage source

$$V_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V}$$

$$V_s = 20 \cos(10t - 60^\circ) \text{ V}$$

$$V_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 10 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 10 \times 0.2$$

$$0.2 \text{ H} = j2 \Omega$$

Given circuit can be represented As ;

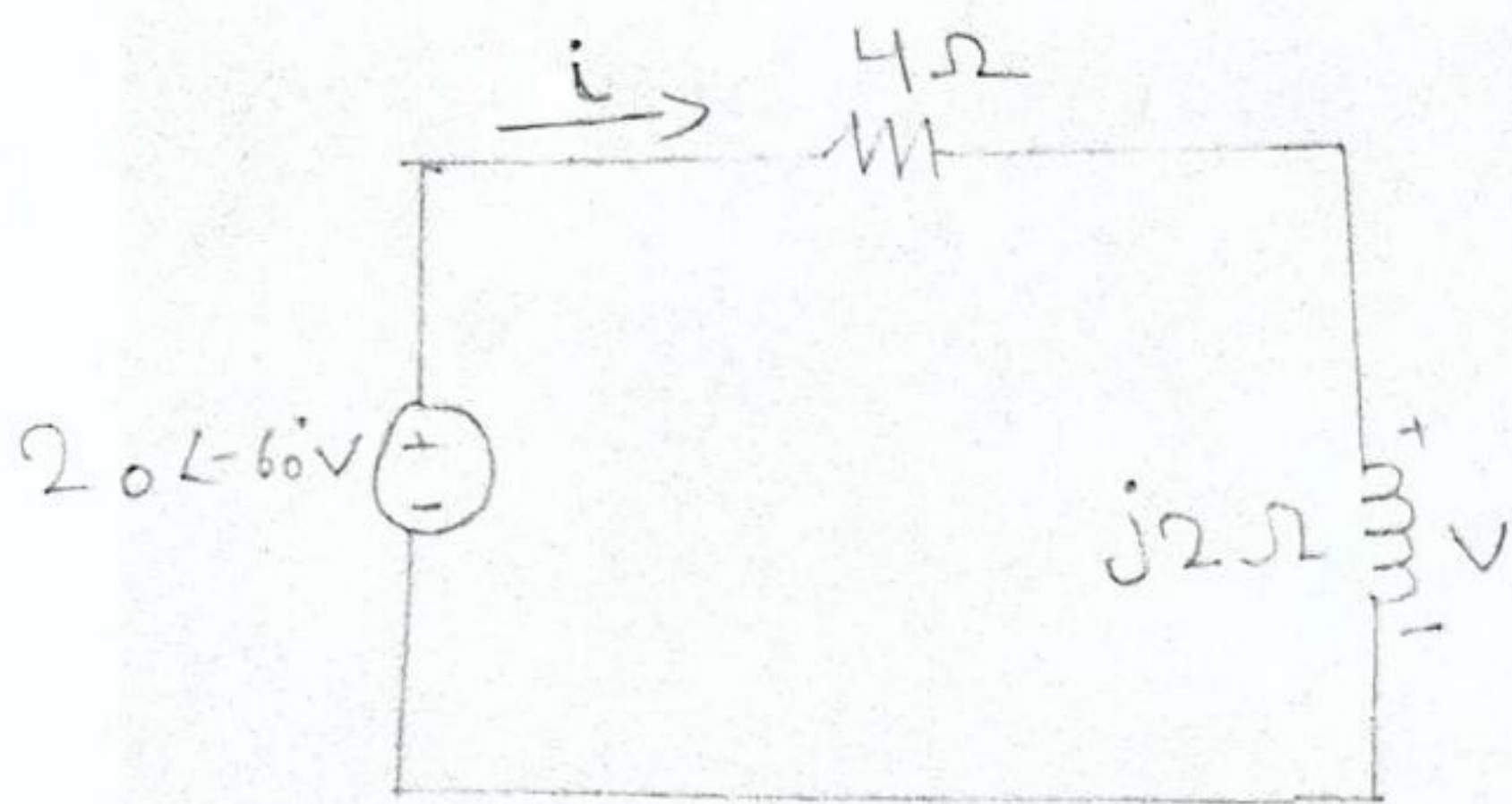

From the above circuit

$$Z = 4 + j2\Omega$$

Hence the above circuit

$$Z = 4 + j2\Omega$$

Hence the current is

$$i = \frac{20\angle-60^\circ}{4 + j2}$$

$$i = \frac{20\angle-60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$

$$i = \frac{20\angle-60^\circ}{4.472 \angle 26.57^\circ}$$

$$i = 4.472 \angle -86.57^\circ$$

Converting this into time domain

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

For $v(t)$:

From the circuit voltage across the inductor ~~is~~.

$$V = j2 \times i$$

$$V = j2 \times (4.472 \angle 86.57^\circ)$$

Converting Polar form to rectangular form we get ;

$$V = j2 \times (0.26756 - j4.464)$$

$$V = 8.928 + j0.53512$$

Converting rectangular form to Polar form

~~is~~

$$V = \sqrt{(8.926)^2 + (0.53512)^2} \angle \tan^{-1} \left(\frac{0.5312}{8.928} \right)$$

$$V = 8.944 \angle 3.44^\circ$$

Converting this into the time domain

$$V(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$V(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$V(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$