

NAME: FAWAD REHMAN

ID: 5053

PAPER: E.M

INST: ENGR. SANABULLAH AHMED

DATE: 25/09/2020

Question No 1.

A.

Answer:

### Speed Control Methods:

- Speed control is intentional change in speed of motor.
- It is different from concept of speed regulation where there is natural change in speed due to loading and unloading of shaft.
- Speed change is done manually or by automatically control devices.


#### 1. Speed Control of DC Series Motor:

##### a). Field Diverter Method:

This method uses a diverter. Here the field flux can be reduced by shunting a portion of motor current around the series field. Lesser the diverter resistance less is the field current, less flux therefore more speed.




\* Diagram:

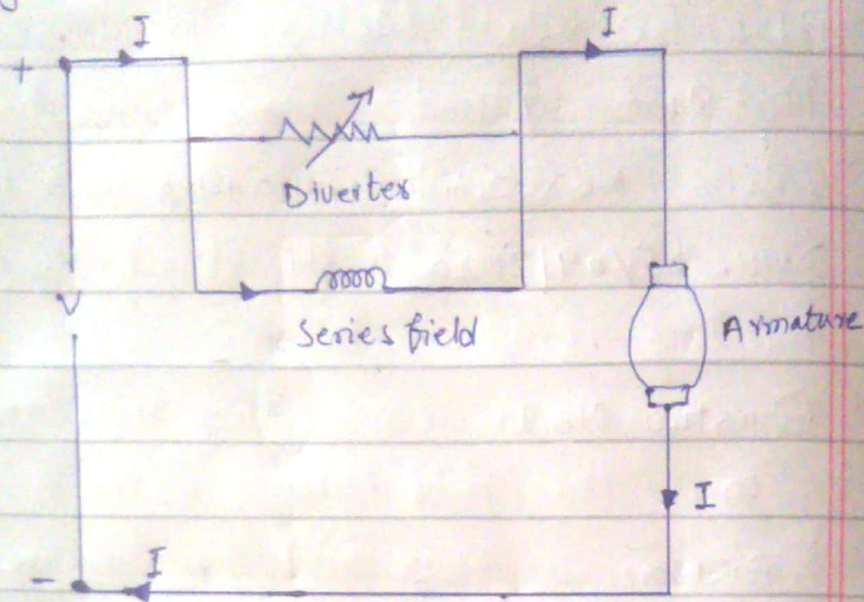

b). Tapped Field Control:

This is another method of increasing the speed by reducing the flux and it is done by lowering number of turns of field winding through which current flows.

\* Diagram:

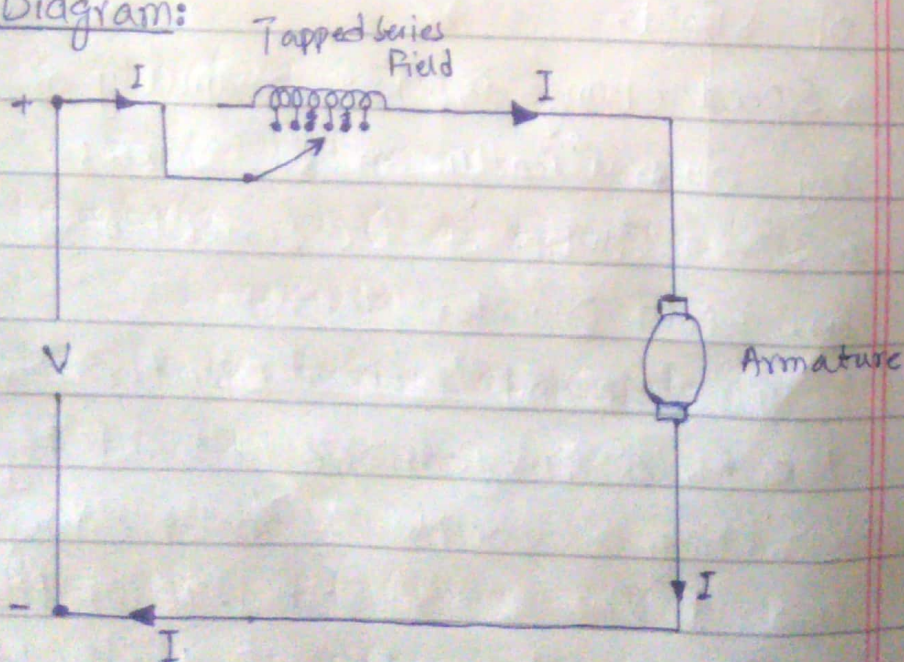




## 2. Speed Control method of DC Shunt M:

### a). Flux control Method:

In this method, a variable resistance (known as shunt field rheostat) is placed in series with shunt field winding as shown below.

An increase in controlling resistance reduces the field current with a reduction in flux and an increase in speed.

### \* Diagram:

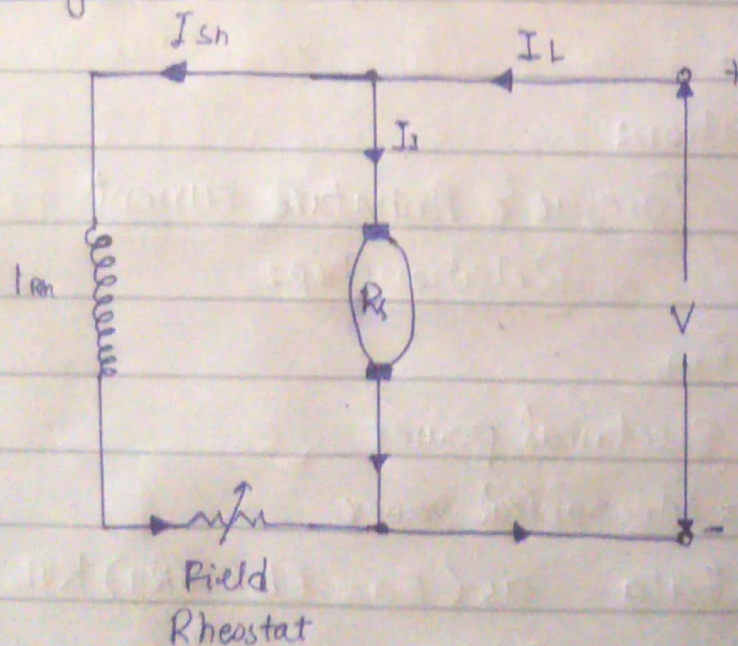


### b). Armature control method:

This is done by inserting a variable resistance  $R_c$  (known as controller resistance) in series with the armature. The flux remains constant while armature current is changed produces



change in speed.

+ Diagram:

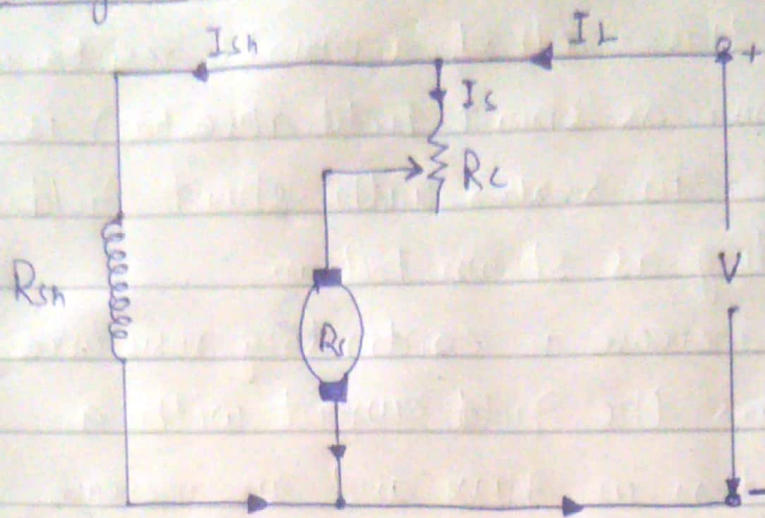

Question No 2.

A).

Solution:

Torque & Armature current  
Relationship:

$$P_e = P_m$$

$P_e$  = Electrical power

$P_m$  = Mechanical power

$$P_e = E_a I_a \quad \text{as } (E_a = E_b + I_a R_a) \text{ KVL}$$

$$P_e = (E_b + I_a R_a) I_a$$

$$P_e = E_b I_a + I_a^2 R_a \quad (\text{as dissipate in form of heat})$$

$$P_e = E_b I_a$$

Now

$$P_m = T \omega \quad \because T (\text{torque in N}\cdot\text{M}) \text{ and } \omega (\text{angular speed in rad/sec})$$

$$1 \text{ radian} = 1/2\pi \quad \because 90 \text{ RPM} = N * 2\pi/60 = \text{rad/sec}$$



$$P_m = T_g N \frac{2\pi}{60}$$

$$P_m = P_e$$

$$T_g N \frac{2\pi}{60} = E_b I_a$$

$$\therefore E_b = \frac{P \cdot \Phi \cdot Z \cdot N}{60 \cdot A}$$

$$T = \frac{P \cdot Z \cdot \Phi \cdot I_a}{2 \cdot \pi \cdot A}$$

Hence  $T_g$  is directly proportional to  $I_a$

Question No 2.

(b).

Answer:

\* Differentiate b/w Lap & Wave winding:

1). Lap winding:

- The coil is lap back to the succeeding coil.
- The end of the armature coil is connected to an adjacent segment on the commutator.
- The numbers of parallel path are equal to the total of number poles.
- Other names parallel or Multiple winding.
- It have less EMF.



- Number of brushes are equal to the number of parallel paths.
- Having types; simplex and Duplex lap winding
- It have less efficiency.
- Having additional coil; equalizer Ring.
- Having high winding cost because more conductor is required.
- It is used in low voltage and high current machine.

## 2. Wave Winding:

- The coil of the winding form the wave shape.
- The end of the armature coil is connected to commutator segments some distance apart.
- The number of parallel paths is equal to two.
- Other names; two circuit or series winding.
- It have more EMF.
- Number of brushes equal to two.
- Having types; Progressive and Retrogressive wave winding.



- It have high efficiency.
- It have additional coil; Dummy coil.
- It has low winding cost.
- It is used in high voltage and low current machine.

### Question No 1.

b).

Solution:

Given Data:

$$\text{no of poles} = 8$$

$$Z = 480$$

$$\text{EMF per 10 conductor} = 2.2 \text{ V}$$

$$\text{current per conductor} = 100 \text{ A}$$

Required Data:

$$\text{Terminal voltage } E = ?$$

$$\text{output current } I = ?$$

power generated for both lap

$$\& \text{ wave winding} = ?$$

Sol:

$$\text{No of conductor per Path}$$

$$= 480/8$$

$$= 60$$

$$\text{e.m.f per conductor} = 0.22 \text{ V}$$

$$P-T-O$$



\* Terminal Voltage:

$$= \text{emf per conductor} \times \text{no of conductor}$$

$$= 0.22 \times 60$$

$$= 13.2 \text{ V}$$

\* Output current:

$$= \text{current per conductor} \times \text{no of parallel path}$$

$$= 100 \times 8 = 800 \text{ A}$$

\* Power generated for lap winding:

$$= \text{output current} \times \text{generated emf}$$

$$= 800 \times 13.2$$

$$= 10,560 \text{ W}$$

\* Power generated for wave winding:

$$\text{no of parallel paths} = 2$$

$$\text{no of conductor per path}$$

$$\text{So } 480/2 = 240$$

terminal voltage

$$= 0.22 \times 240$$

$$= 52.8 \text{ V}$$

output current

$$100 \times 2 = 200 \text{ A}$$

So

$$200 \times 52.8$$

$$= 10,560 \text{ W}$$

" The END "