

Name : Daniyal Alam

ID : 15385


Subject : DLD

Degree : BS. SE

Assignment # 2


Q: 1 \rightarrow

Solution

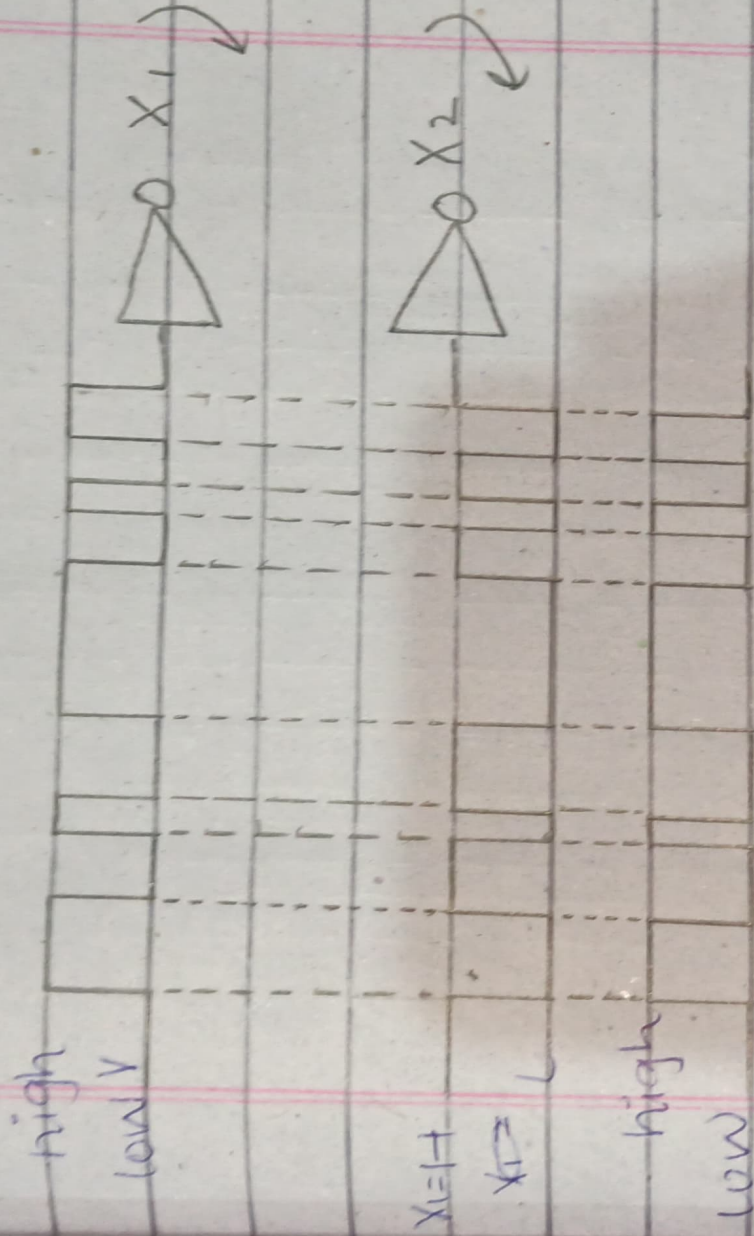

Q: 2

Answer

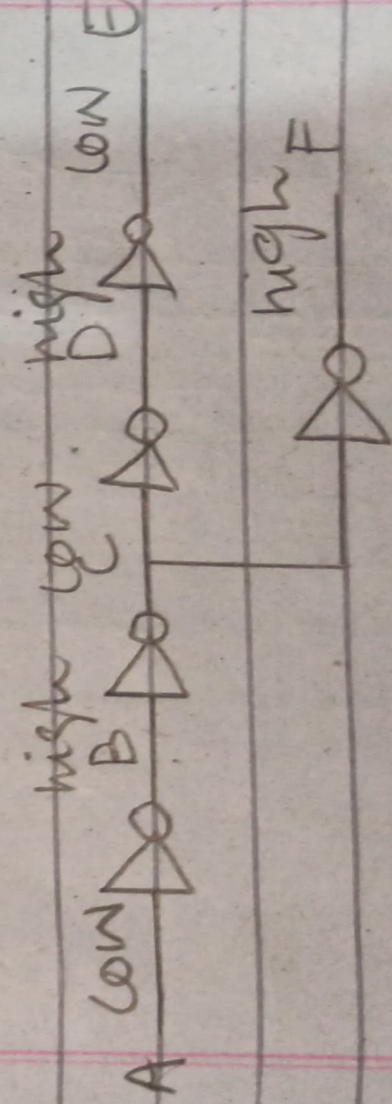


E = low

F = high

Q = 4

Answer.


As

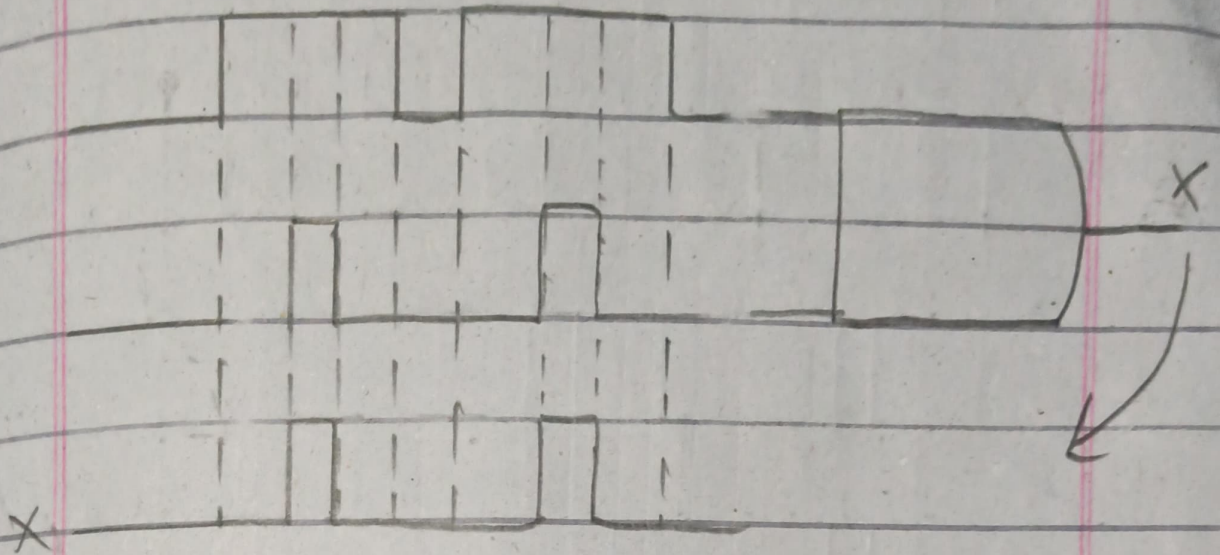

Ans


Q = 5

Answer

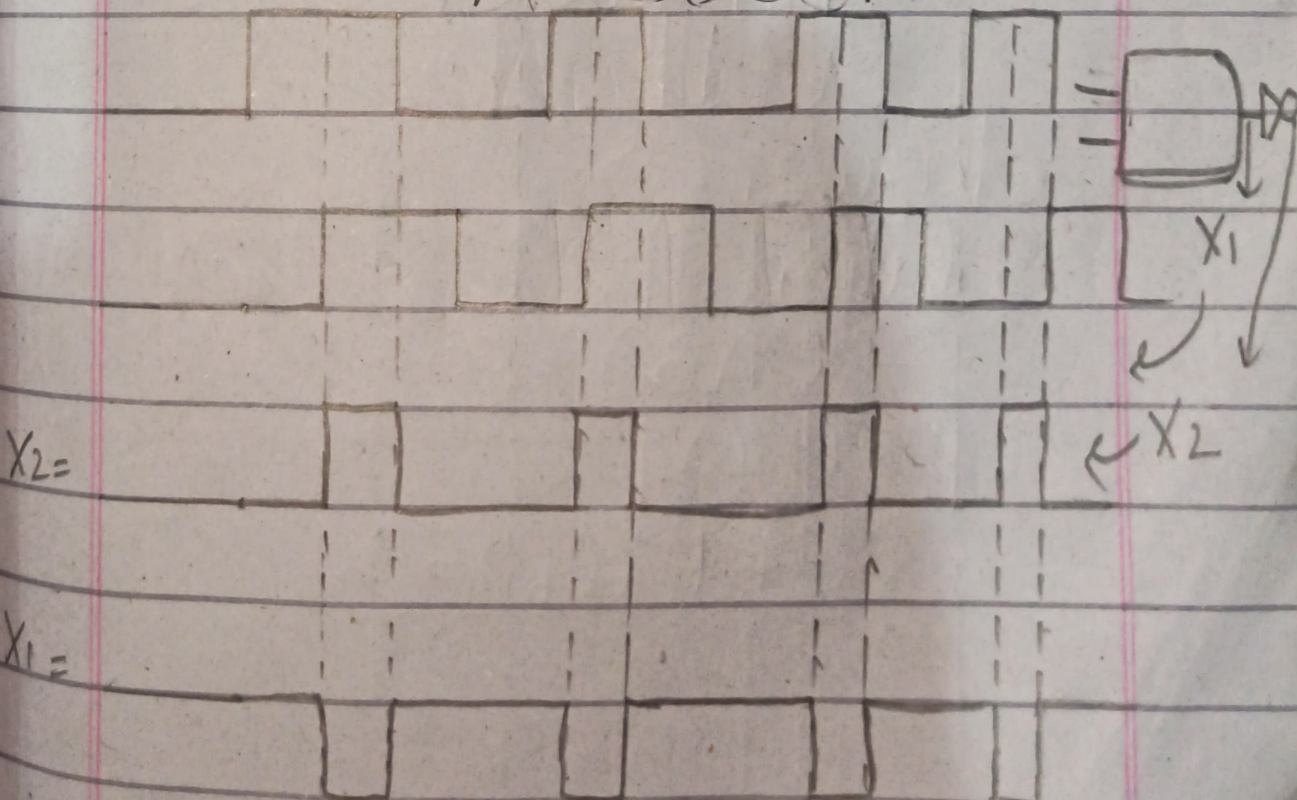


Q : 6

Answer .

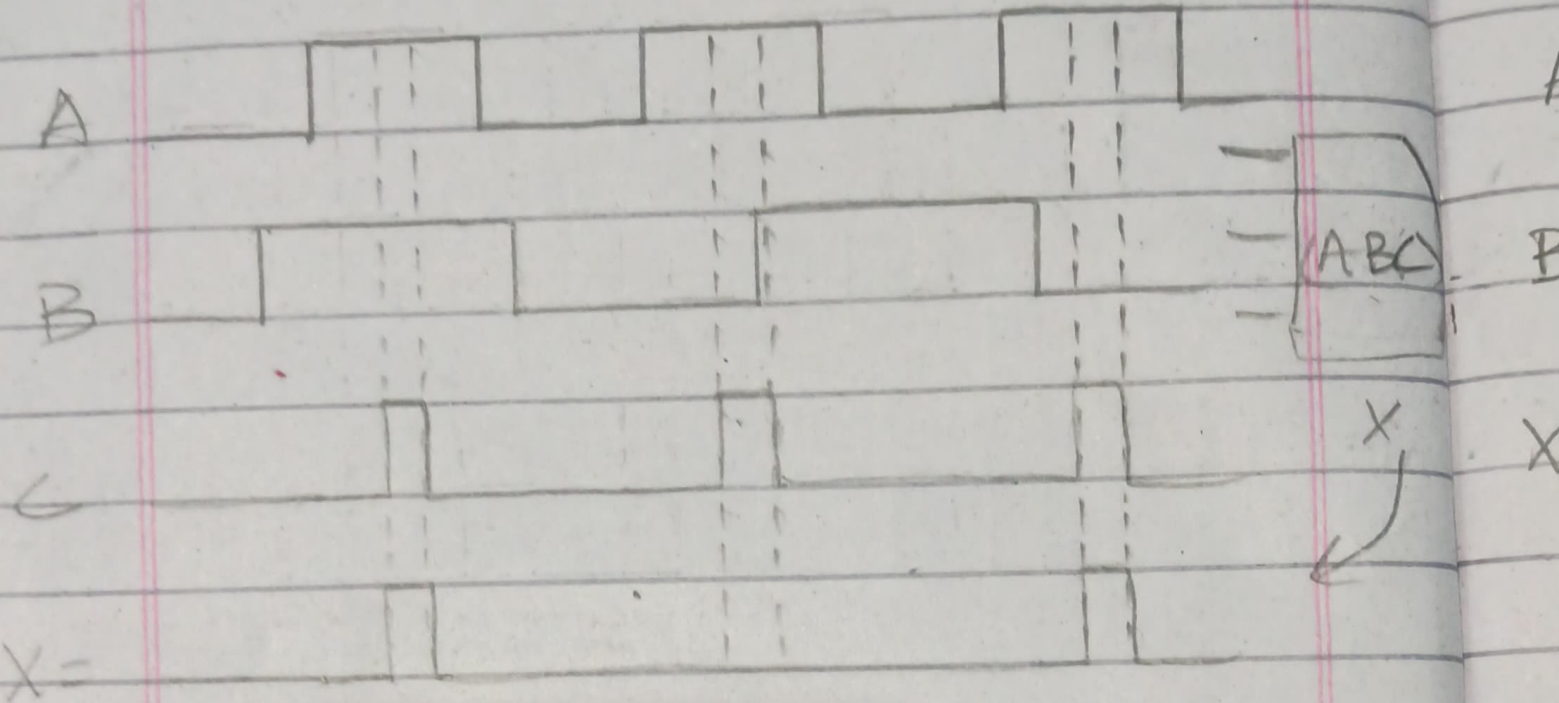


Q : 7

Answer

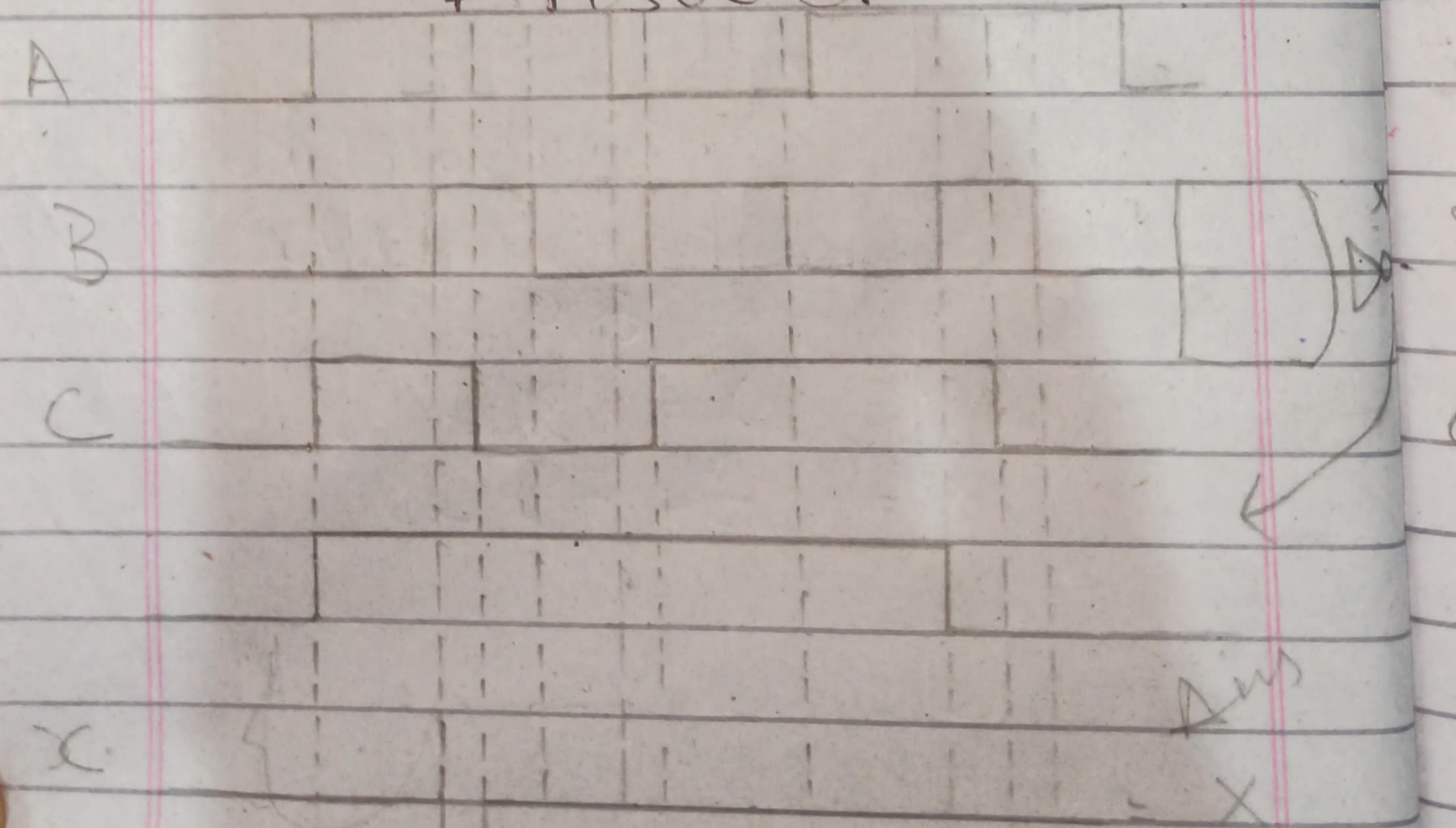

Q: 8


ANSWER: →

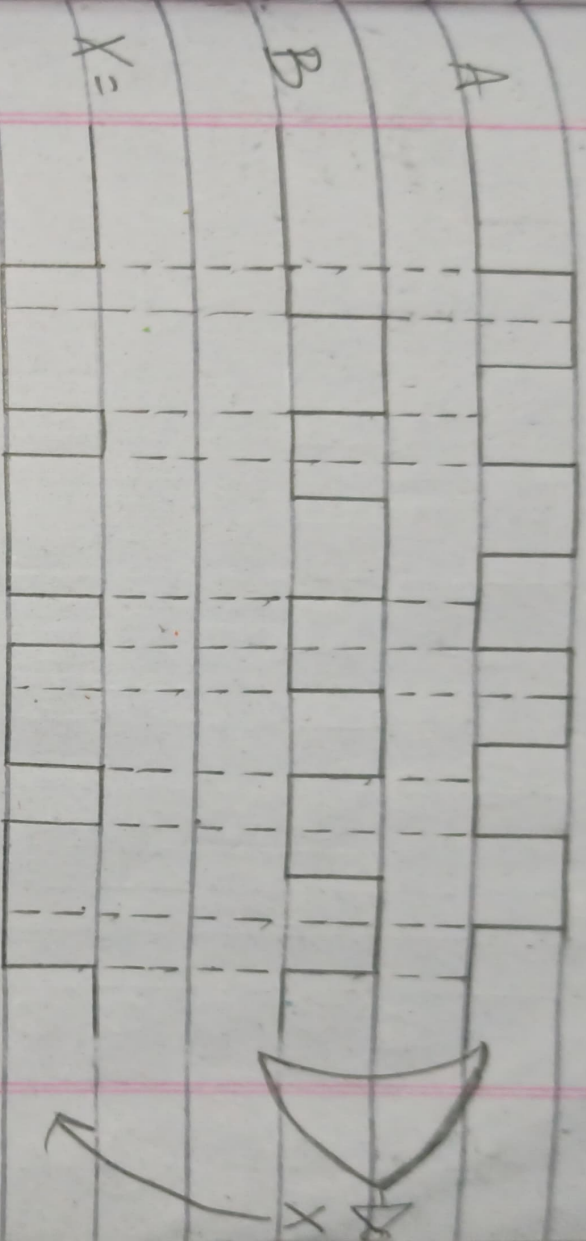

Ans


Q: 9

ANSWER: →

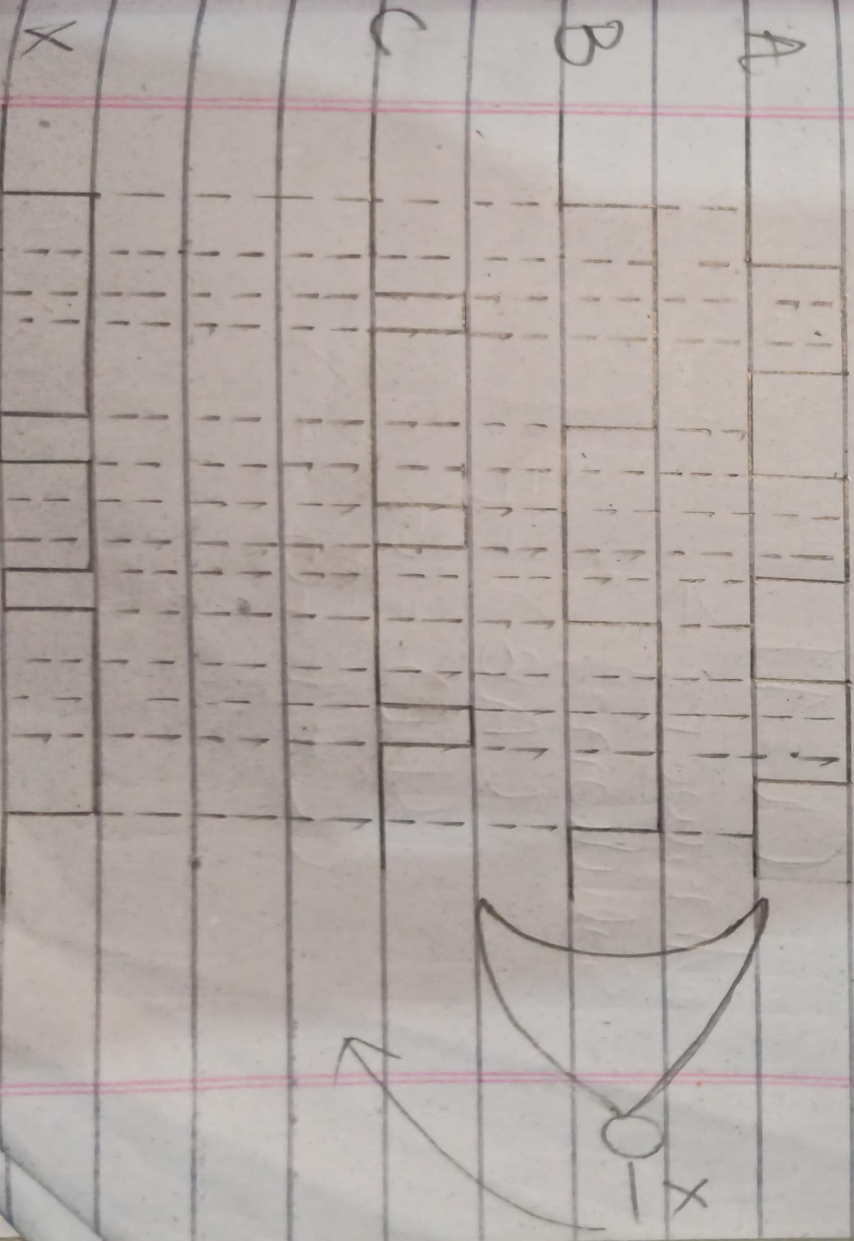


ANSWER


A

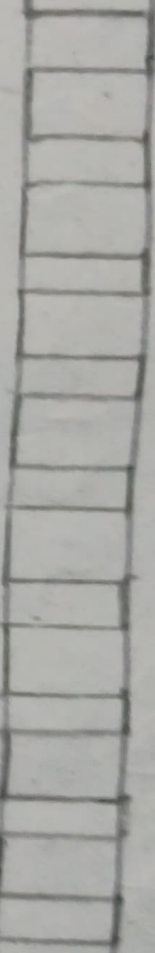


B

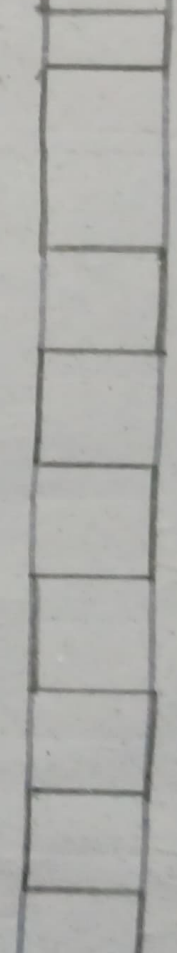


F

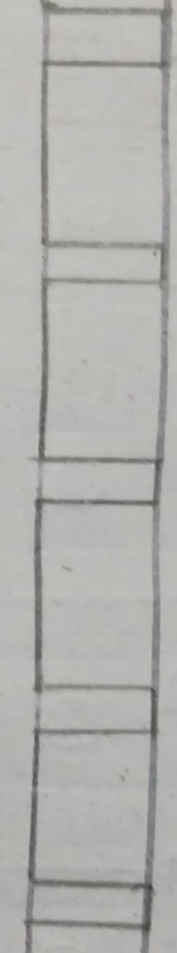


D

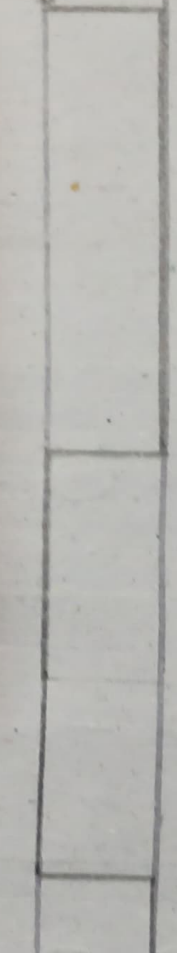


E

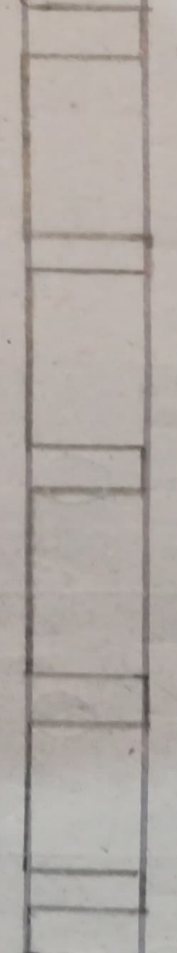





G

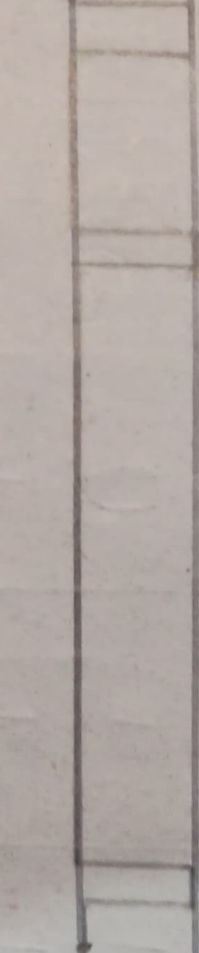

C

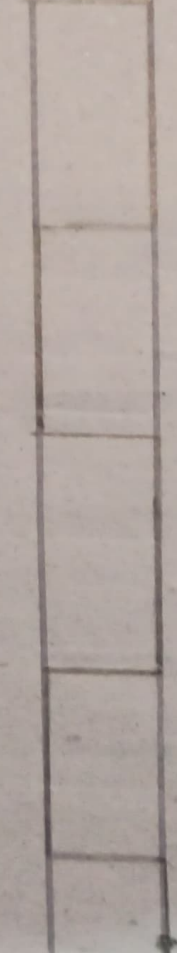


X

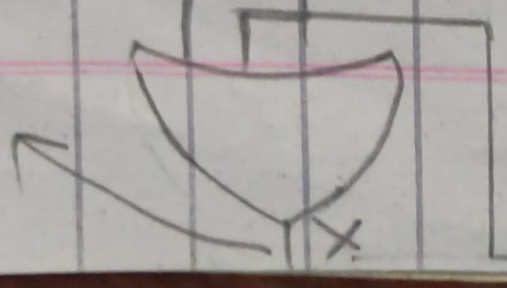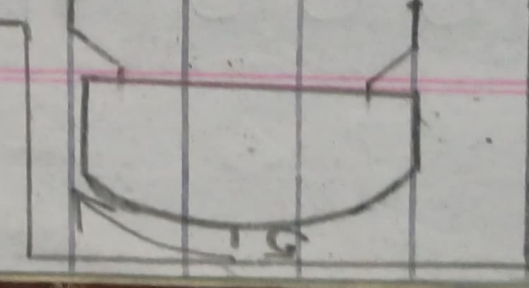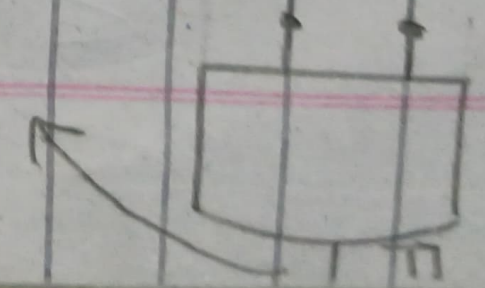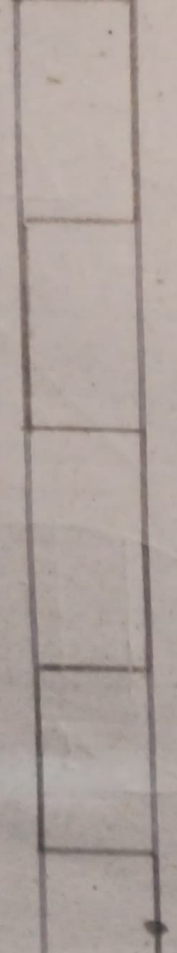

Q:12


Answer: \rightarrow

A	B	C	(A+B+C)	(A+B+C)
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

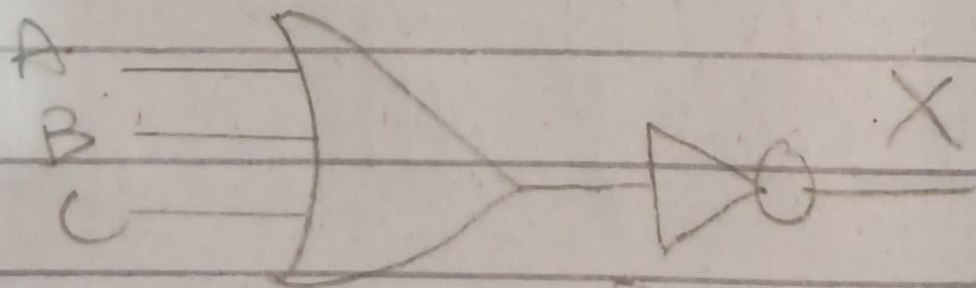


Q: 13

Answer: \rightarrow

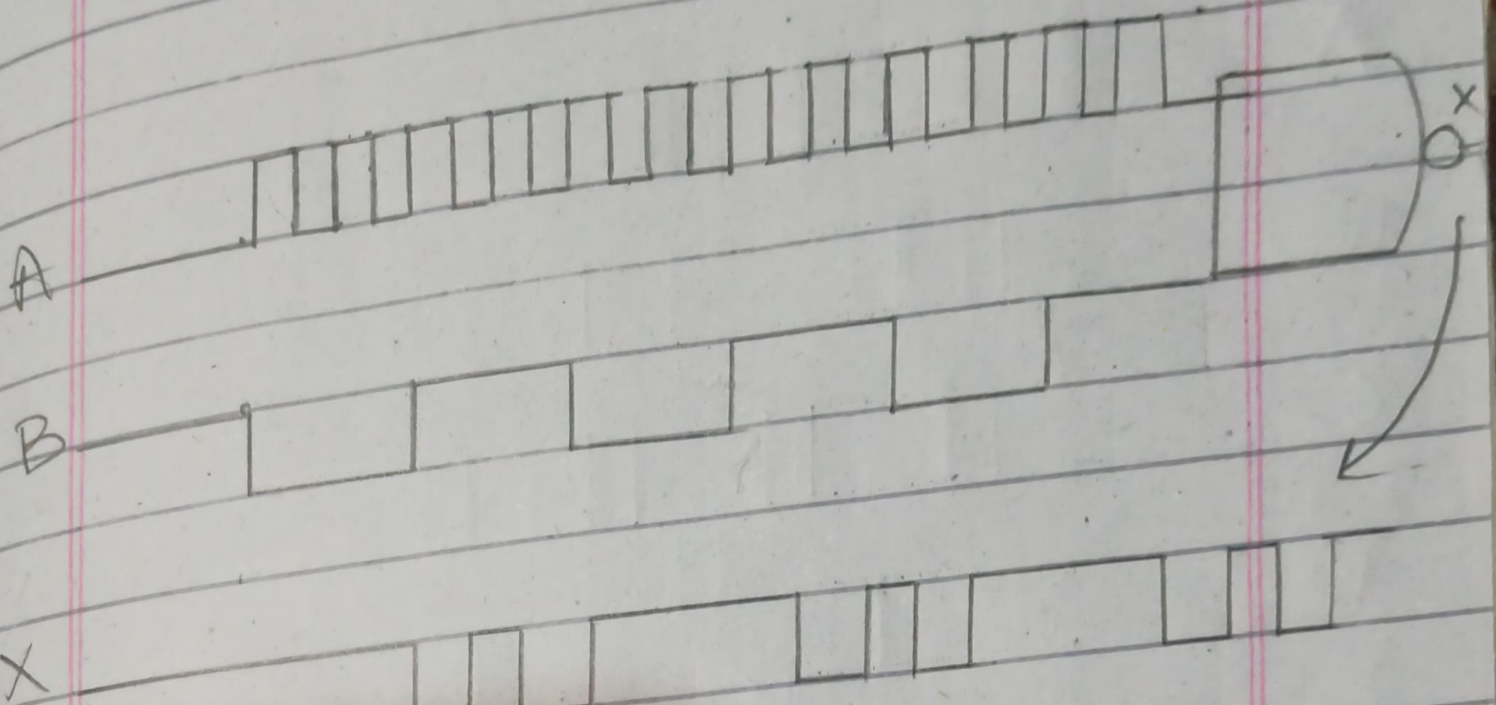

Q: ~~13~~ 14


Answer: \rightarrow

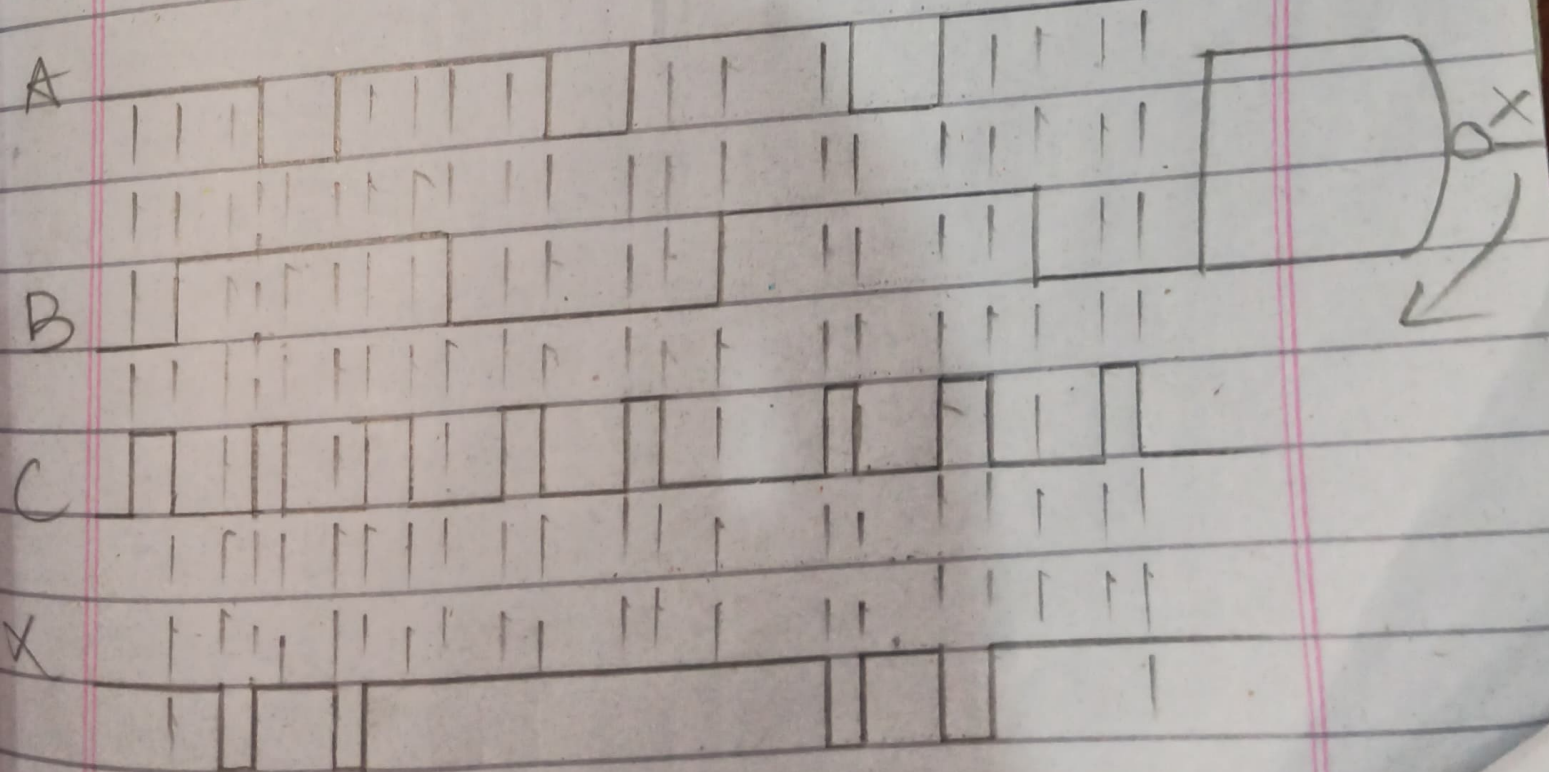


Q: 15

Answer: \rightarrow


A

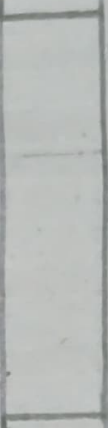


B

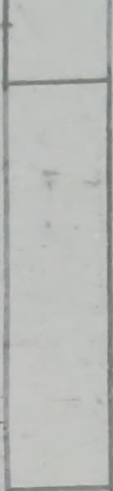


C

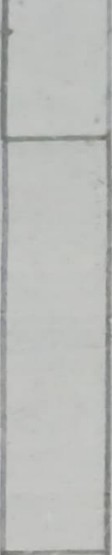

D


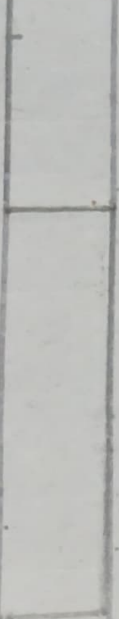


X

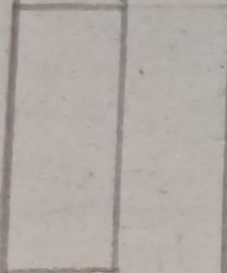


Q:16

Answer: \rightarrow

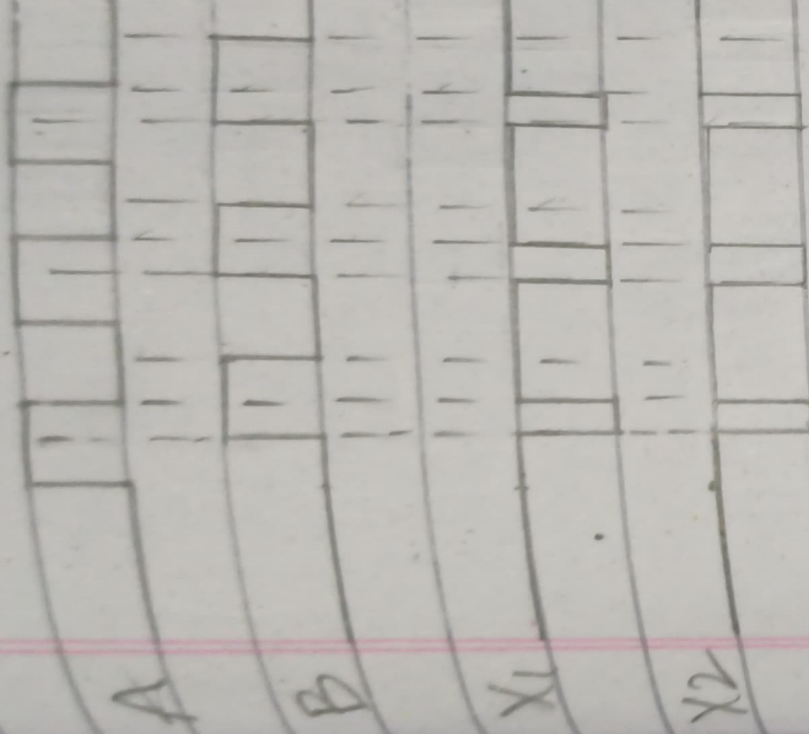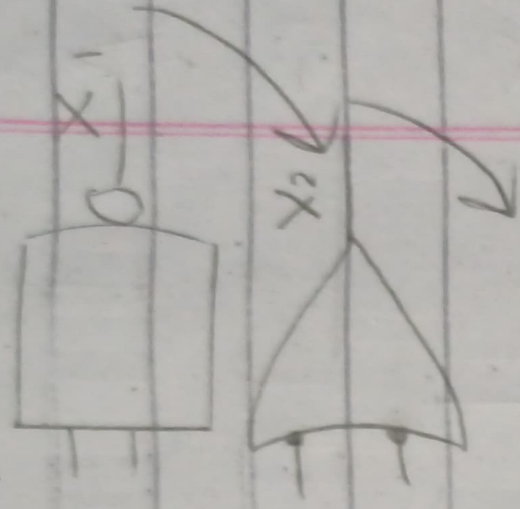

Q:17

Answer: \rightarrow

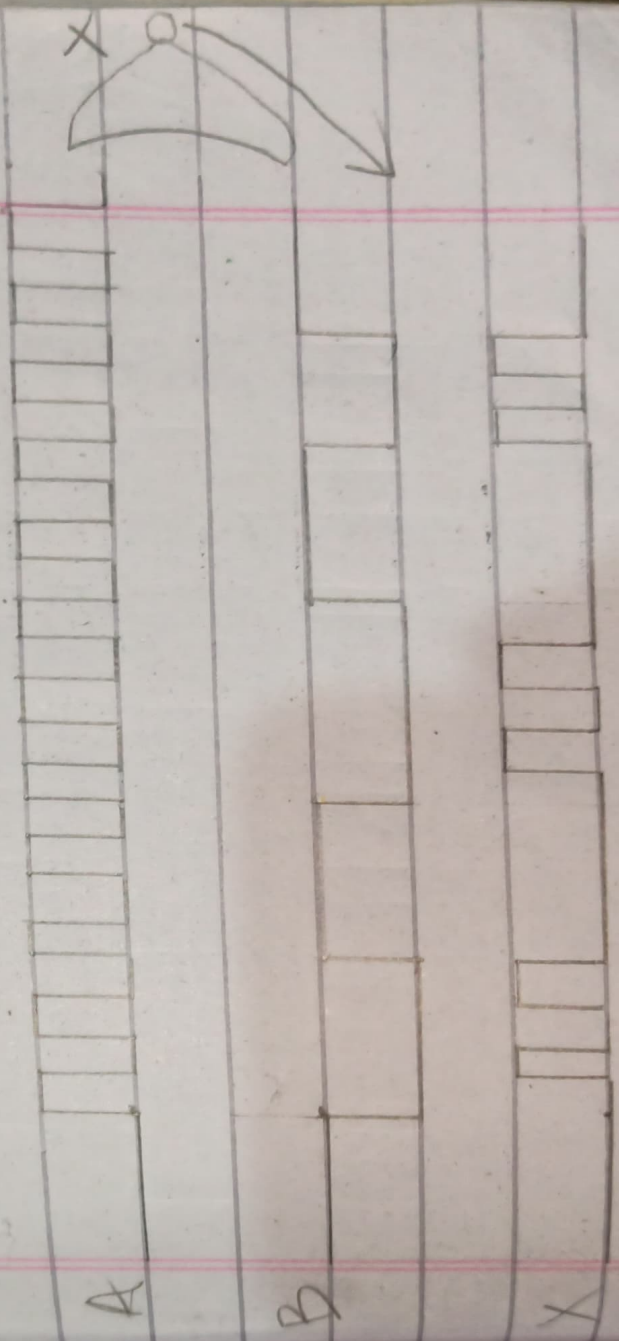

Q: 18


Answer: →

A

B

C

X

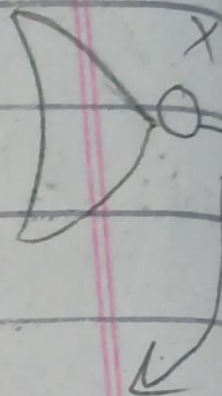

Q : 19

Answer.


A

B

C

D


X

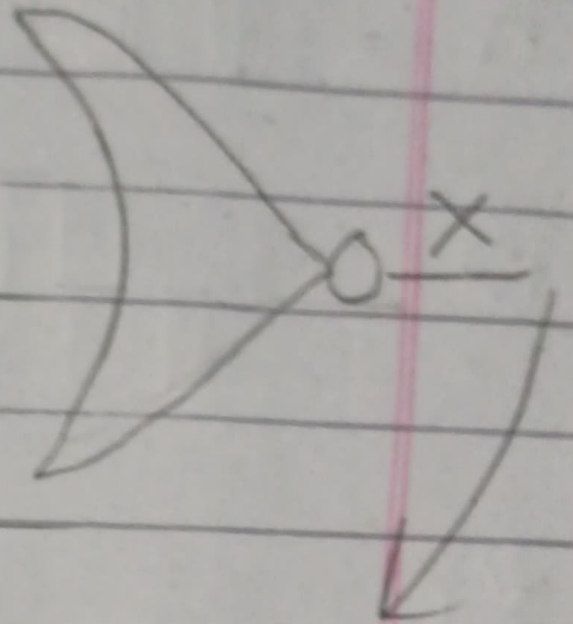


Q: 20

Answer: →


A

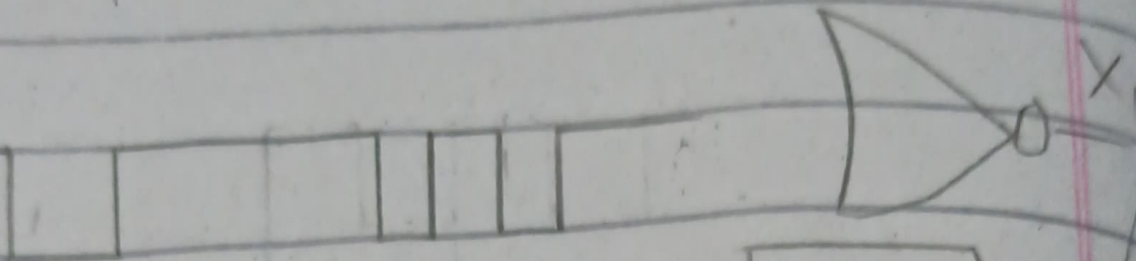


B

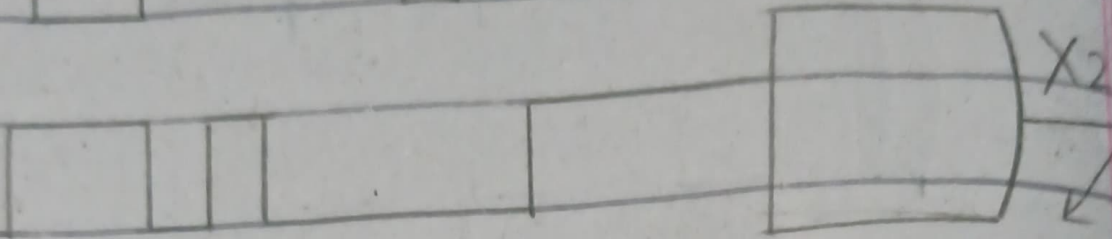

X_1

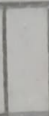


X_2

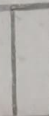

Q. 21

Answer: \rightarrow

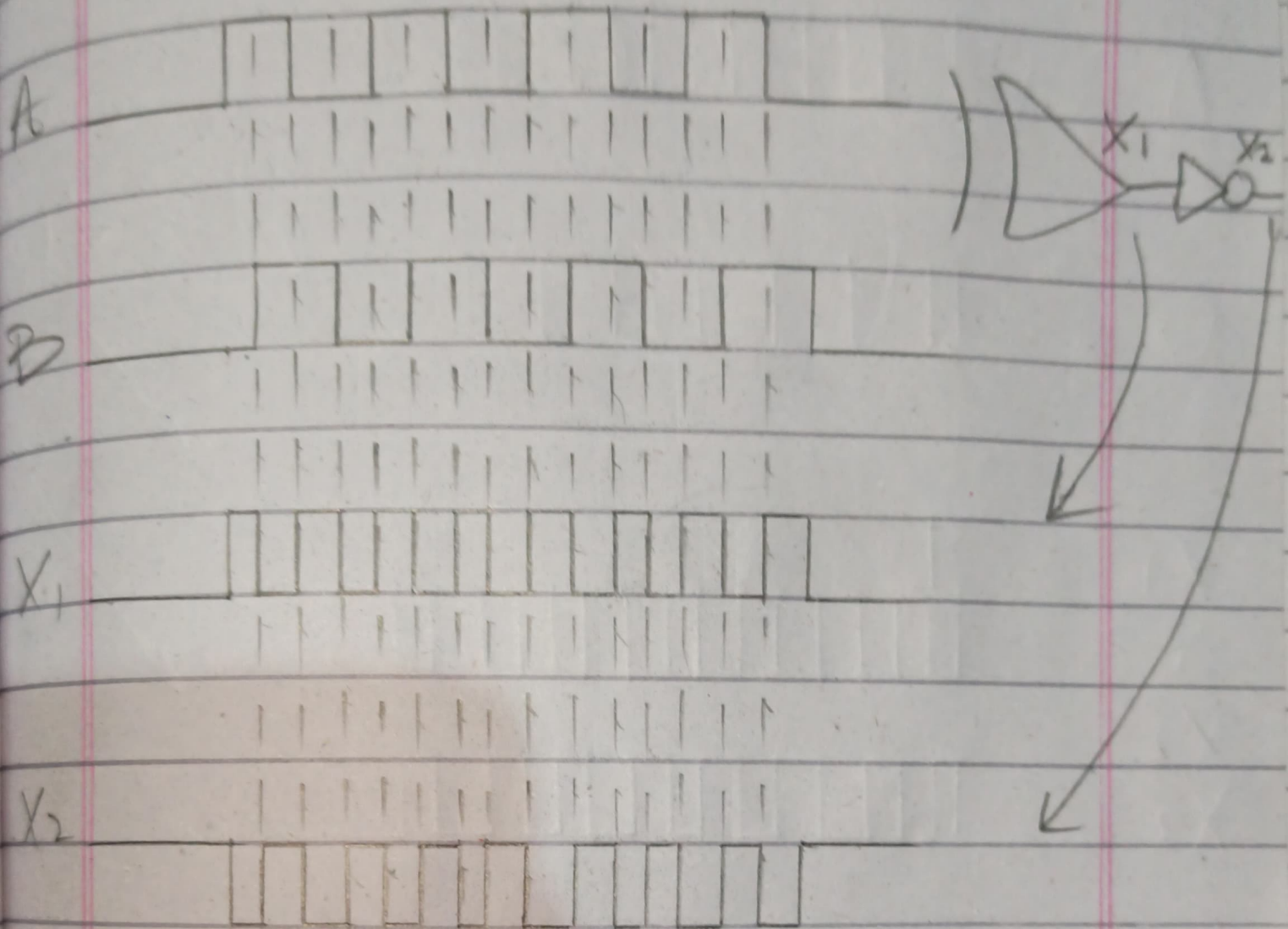

Q: 22

Answer: →

