

Department of Electrical Engineering

Assignment

Date: 14/04/2020

Course Details

Course Title: Power Electronics

Module: _____

Instructor: _____

Total 30

Marks: _____

Student Details

Name: Kiramat Ullah

Student ID: 13290

Note: Plagiarism of more than 20% will result in negative marking.

Similar answers of students will result in cancellation of the answer for all parties.


Q1	(a)	An appliance circuit has a R-L connected in series with a diode. After some time, modification is done to the circuit and a free-wheeling diode is added in parallel to the R-L. Will it have any impact on the performance and output of the circuit. Back your answer with before & after data, facts and figures. Does adding a free-wheeling diode in parallel to a R-C circuit have the same effect, different effect or no effect.	Marks 7
			CLO 1
	(b)	A Power Mosfet is connected in a circuit. The Drain to Source voltage, $V_{DS} = (\text{Last 2 digits of your student ID}) V$ and Threshold Voltage, $V_T = (\text{Last 1 digit of your student ID}) V$. What is the minimum Gate to Drain Voltage, V_{GS} required for the P.Mosfet to be in saturation mood.	Marks 3
			CLO 1
Q2	(a)	A Power Electronics appliance of 500W, 220V, 500KHz rating is using a Power Mosfet for switching purpose. If the P.Mosfet is replaced with a Power Bipolar Junction Transistor what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
	(b)	In the above appliance (Q2.a) if the P.Mosfet is replaced with a Silicon Controlled Rectifier what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
Q3	(a)	The bipolar transistor in the Figure below is specified to have β_F in the range of 8 to 40. The load resistance, $R_C = (\text{Last 2 digits of your student ID}) \Omega$.	Marks 10

The dc supply voltage, $V_{CC} = (\text{Last 3 digits of your student ID}) \text{ V}$ and the input voltage to the base circuit, $V_B = 10 \text{ V}$.

If $V_{CE} = (\text{First digits of your student ID}) \text{ V}$ and $V_{BE} = 1.5 \text{ V}$, find

- The mode of operation of the transistor
- the value of R_B that results in saturation with an ODF of 5,
- the β_{forced} ,
- the power loss, P_T in the transistor.

CLO 1

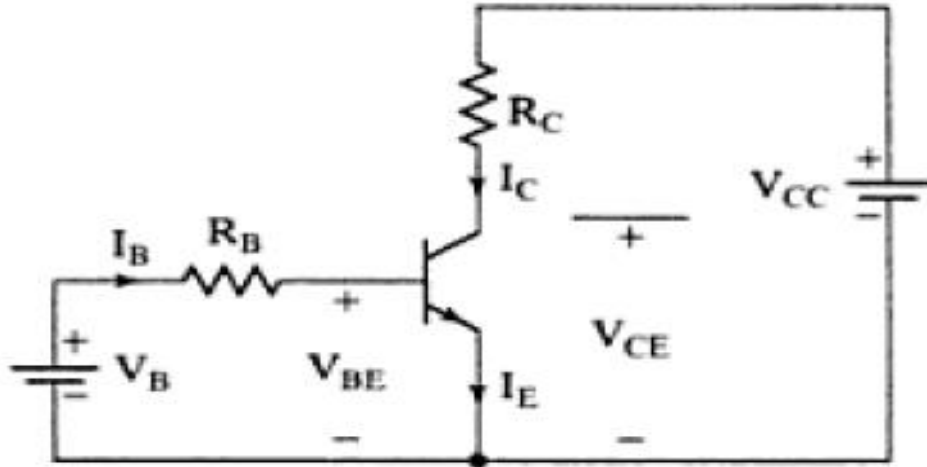

STUDENT NAME # KIRAMATULLAH

ID NO # 13290

COURSE TITLE # Power Electronics

DEPARTMENT # BEE

TEACHER NAME #

Engs. Shayan Tasiq


Jan

Question No 1

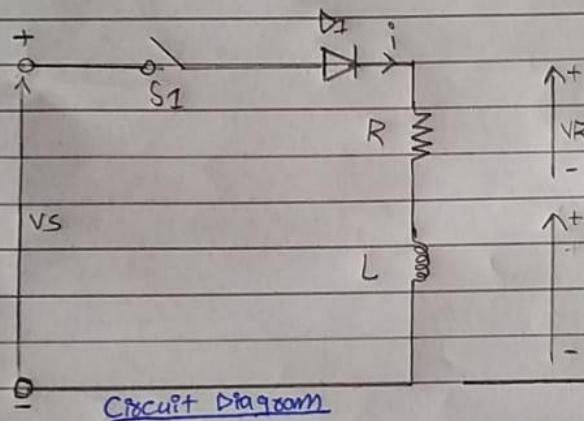Part (A)

Answer

↳ A circuit diagram of RL-connected in series with diode.



Circuit Diagram

When switch S_1 is closed at $t=0$ then current through the inductor increases and is expressed as,

$$V_S = V_L + V_R = L \frac{di}{dt} + Ri$$

When the initial condition $i(t=0) = 0$ and $i(t)$ is expressed as,

$$i(t) = \frac{V_S}{R} (1 - e^{-t/R_L})$$

When The rate of change

Kisamatullah

(2)

ID 13290

this current can be obtained from

$$\frac{di}{dt} = \frac{V_s}{L} e^{-tR/L}$$

The initial rate of rise of the current at ($t=0$) is obtained


$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_s}{L}$$

The voltage across the inductor is


$$V_L(t) = L \frac{di}{dt} = V_s e^{-tR/L}$$

where $\frac{L}{R} = \tau$ is the time

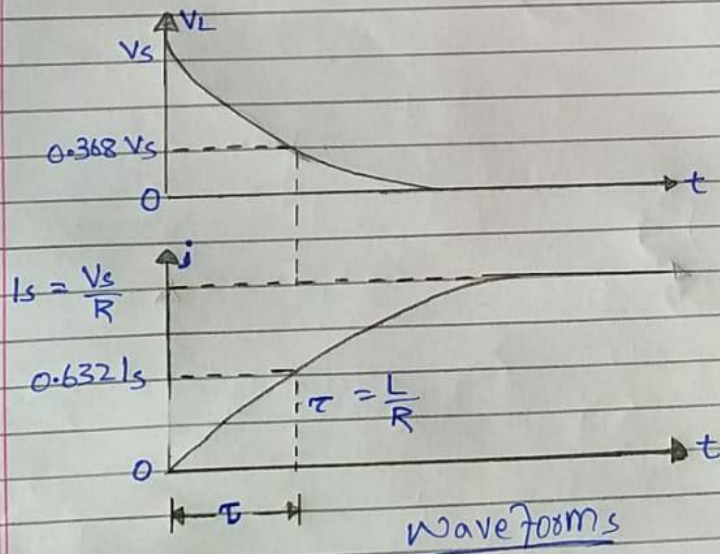constant of an RL load. The waveforms for the voltage and current are shown below.



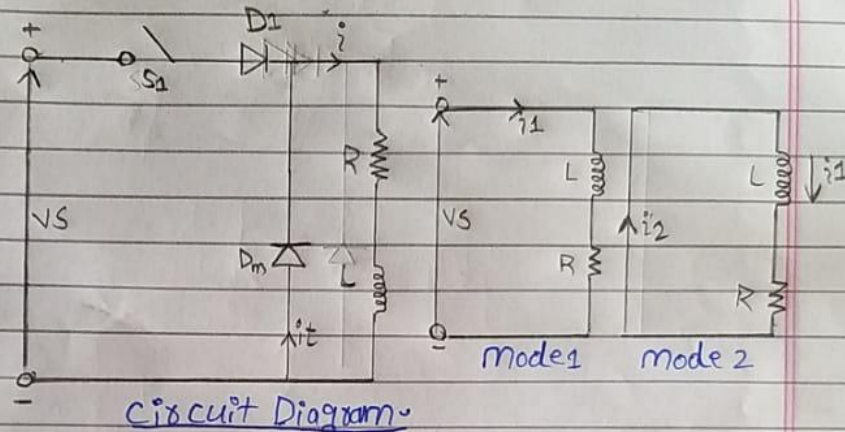
↳ A circuit diagram of RL-connected in parallel in free wheeling diode of D_m .



- 2) The inductor has property to store energy.
- 2) In AC current during positive half cycle the inductor stores energy.
- 3) At negative half cycle the inductor de-energies.
- 4) This may cause reverse damage to circuit.
- 5) To avoid energy dissipation free-wheeling diode is used.
- 6) In negative half cycle, the

Free wheeling diode becomes forward biased so that the current will flow through diode.

7) Therefore it de-energises inductor.

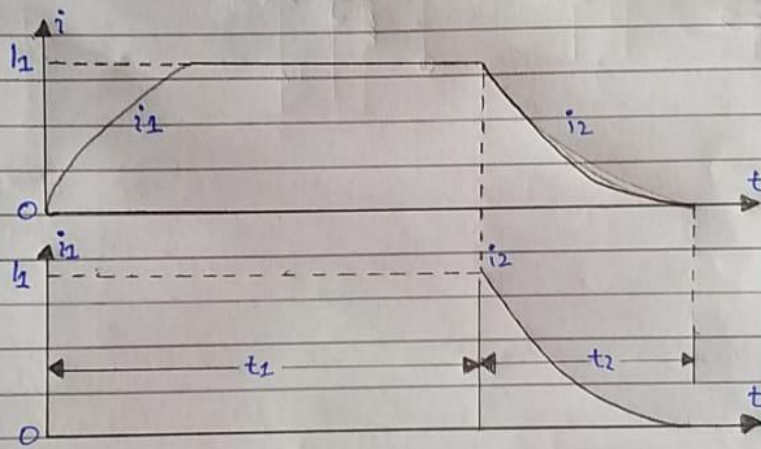

Waveforms

Circuit with free wheeling diode.

So, Now

\Rightarrow R-L Then it will only reduce in ripple and prevent in back current from leading to zero. And it has no impact on half wave rectification.

\Rightarrow Secondly if R-C is taken instead of R-L the the effect will be same. The only difference will be the load voltage and i_2 can be prevented from leading to zero.

X=====X=====X=====

Kizamatullah (5)

ID 13290

Question No 1

Part (B)

Answer

Given data:-

$$V_T = 1V$$

$$V_{DS} = 90$$

Find $V_{GS} = ?$ in saturation mode

Solution:-

In saturation mode.

$$\Rightarrow V_{DS} = V_{GS} - V_T$$

$$\Rightarrow V_{GS} = V_{DS} + V_T$$

$$V_{GS} = 90 + 1 = 91$$

As

$$\boxed{V_{GS} = 91 V}$$

Ans///

Question No 2

Part (A)

Answer

A) \Rightarrow When we replace a power mosfet with a power BJT there will be a high effect on its output and performance of the appliance.

BJT is a current control device for such high voltage rating. It recovers the power mosfet.

But the losses occur in the appliance becomes slightly lower because (BJT has lesser losses as compared to Mosfet). But

BJT has switching limits i.e. second Breakdown (SB). It

is a destructive phenomena results from current flow to a small portion of the base, producing localized hot spots.

If the energy these hot spots is sufficient, the excessive localized heating may damage the transistor.

But to avoid this problem the manufacture usually provide the Forward Biased safe operating Area (FBSOA) and Reverse Biased safe operating area (RBSOA) which works in turn-ON and turn-OFF conditions.

It indicates the i_c - V_{ce} limits of the transistor. For reliable operation the transistor must not be subjected to greater power dissipation than that shown by the FBSOA and RBSOA.

The BJT have high switching frequencies. since these turn-ON and turn-OFF times are low.

The MOSFET driver circuit is simple and easy to design, but the BJT driver circuit is complex. You can add a thyristor to circuit because both provides a good control range of current with small controlling current. Also for the operating frequency because the operating frequency of BJT is quite low as compare to MOSFET.

Question No 2

Part (B)

Answer

- B) The silicon controlled rectifier is a current controlled device. Single pulse to turn ON as BJT. The ON-state voltage drop is lower i.e. less than 2 volts as compare to power MOSFET.

Kisamatullah

(8)

ID 13290

The delay given in the
Question falls in the
category of SCR and
BJT as its maximum
V-I rating of SCR is
100KV and of BJT is
5000Amp

$\frac{2KV}{100Amp}$

But the operating frequency
of SCR is quite lower
than power Mosfet.
So it will damage the
efficiency and performance
of the appliance.

Question No 3

Part (a)

Answer

a) Given that:-

$$\Rightarrow V_{CC} = 290 \text{ V}$$

$$\Rightarrow R_C = 90 \text{ V}$$

$$\Rightarrow V_B = 10 \text{ V}$$

$$\Rightarrow V_{CE} = 1 \text{ V}$$

$$\Rightarrow V_{BE} = 1.5 \text{ V}$$

Find mode ?

Solution:-

The mode of operation of the transistor is an saturation mode.

Question No 3

Part (b)

Answer

Solution:-

$$\text{Find } R_B = ?$$

So,

$$I_{CS} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C}$$

$$\frac{290 - 1}{90} = \frac{289}{90}$$

$$I_{CS} = 3.2111 \text{ A} \rightarrow \text{Ampere}$$

Ans

Kizamatullah

(10)

ID 13290

⇒ We know that

So,

$$I_{B_s} = \frac{I_{C_s}}{\beta_F (\text{mini})}$$

$$I_{B_s} = \frac{3.2111}{8}$$

$$I_{B_s} = 0.40138 \text{ A}$$

Ans

⇒ Find $I_B = ?$

So,

$$I_B = ODF \times I_{B_s}$$

$$I_B = 5 \times 0.40138$$

$$I_B = 2.0069 \text{ A}$$

Ans

⇒ As we know,

When

$$R_B = \frac{V_B - V_{BE}}{I_B}$$

$$R_B = \frac{10 - 1.5}{2.0069} = \frac{8.5}{2.0069}$$

$$R_B = 4.2353 \Omega$$

Ans

Question No 3

Part (c)

Answers

Solution :-

We find $B_{force} = ?$
Now,

$$B_{force} = \frac{I_{cs}}{I_B}$$

$$= \frac{3.2111}{2.0069}$$

Now,

$$B_{force} = 1.600029 \Omega$$

Ans

Question No 3

Part (D)

Answers

Solution :-

Now we find $P_T = ?$

so,

$$P_T = V_{BE} I_B + V_{CE} I_{cs}$$

$$V_{BE} = 1.5 \text{ V}$$

$$I_B = 2.0069 \text{ A}$$

Kizamatullah

(12)

ID 13290

$$\Rightarrow V_{CE} = 1 \text{ V}$$

$$\Rightarrow I_{CS} = 3.2111 \text{ A}$$

Now

$$P_T = V_{BE} I_B = V_{CE} I_{CS}$$

$$= (1.5)(2.0069) + (1)(3.2111)$$

$$= 3.01035 + 3.2111$$

$$P_T = 6.22145 \text{ Watt}$$

Ans///

— X — X — X —