

ID# 13794

(1)


26/09/20

Final Paper

Digital Logic Design

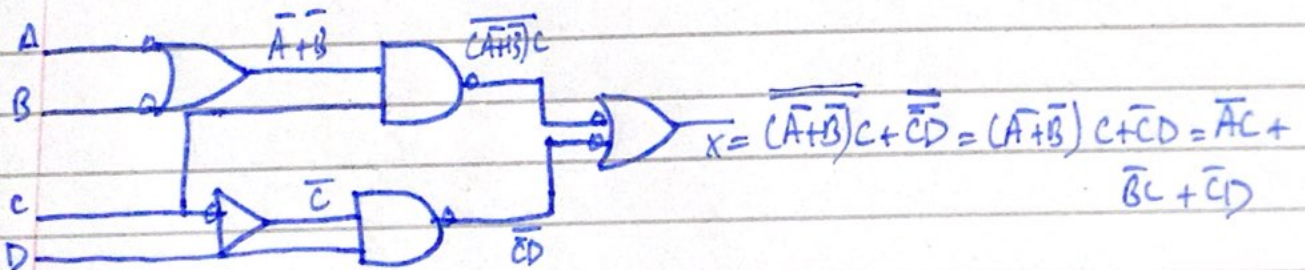Q1) Draw the logic circuit using the input (A, B, C, D) and output (x) waveforms in


SS1: The output expression for the circuit is developed in figure. The SOP form indicates that the output is High when A is Low and C is High or when B is Low & C is High or when C is Low or D is High



Q5) Show the logic required to convert a 4-bit Gray code to binary and use that logic to convert the following Gray code words to binary: 1011

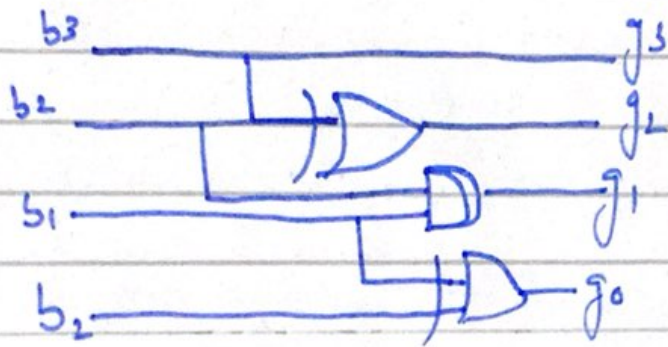
(2)

Ans: The conversion of binary to gray code can be done by using a logic circuit. The gray code is a non-weighted code because there is no particular weight ~~code~~ is assigned for the position of the bit.



Q6) Draw & explain the logic diagram?


Ans:

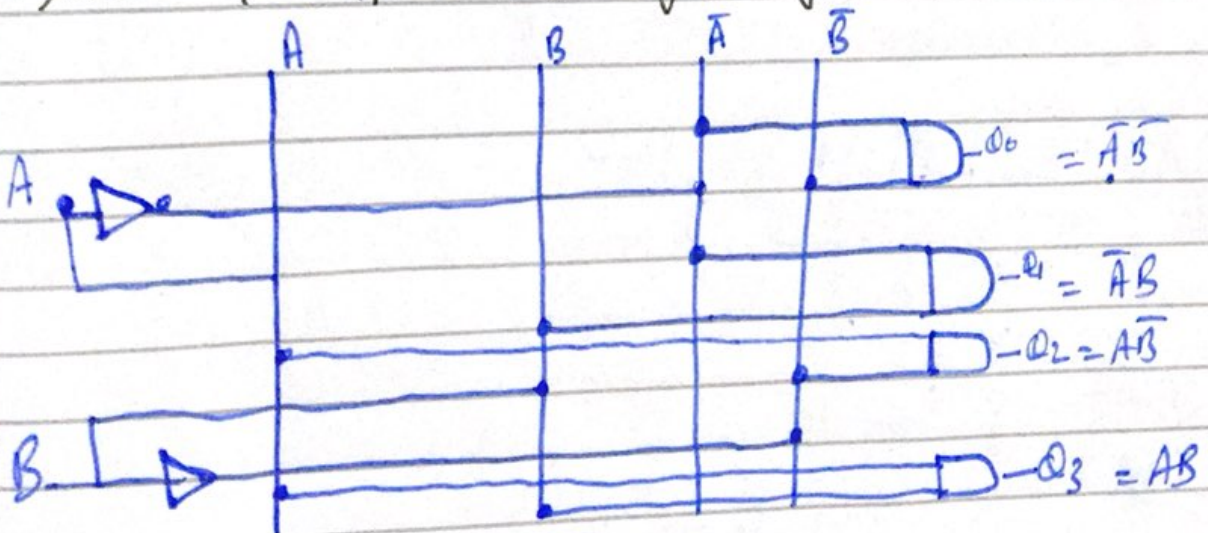

(3) 8

Q9) Draw the logic diagram and timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represents the proper binary number after each clock pulse.

sol: (logic 1)

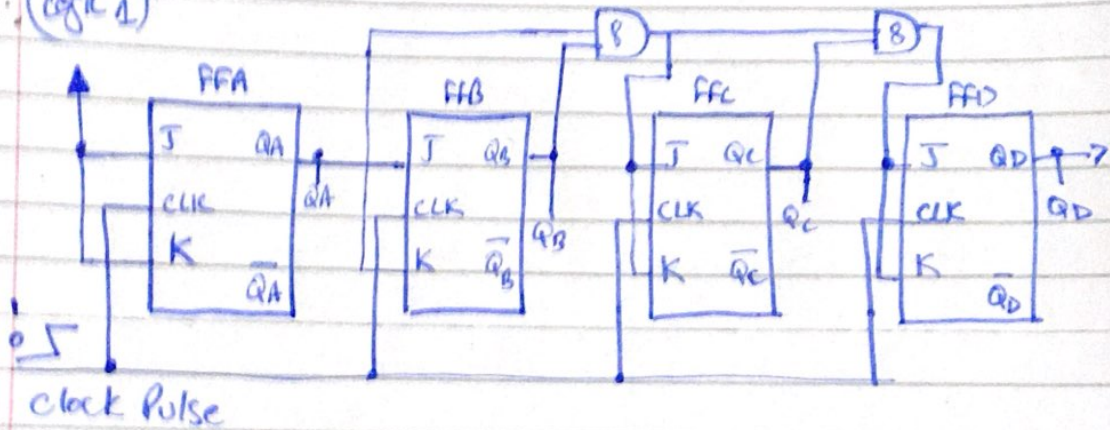


Binary 4-bit Synchronous Up Counter

Q4) Determine the  $A=B$ ,  $A>B$ , and  $A<B$  outputs for the input numbers shown on the comparator in figure.

Ans:

(4)

Ans:

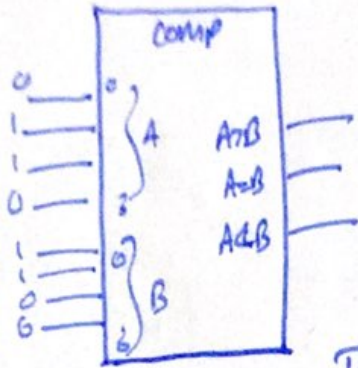

The number on the A input is 13 (0110) and the number on the B input is 11 (1011). The  $A > B$  output is HIGH & the other outputs are low.


Q2)

Sol:

select	data input	output
S1	S0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Q8)

Sol:

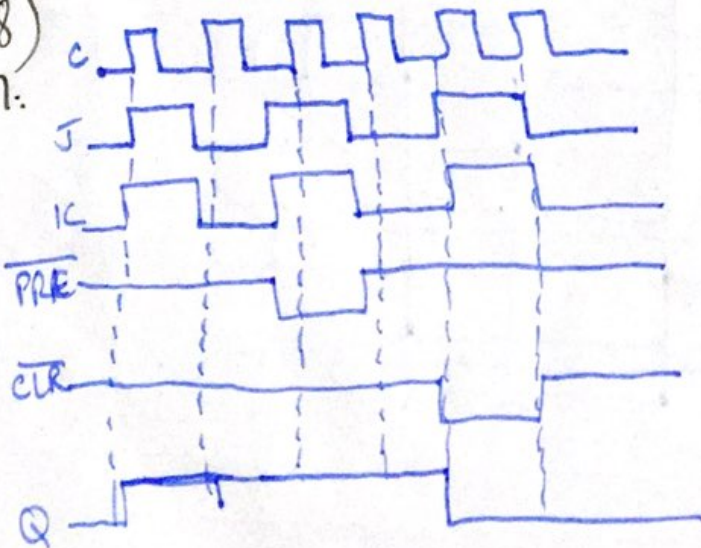

Q7)

Def: JK-Flip Flop: The flip flop is a basic building block of sequential logic circuits. It is a circuit that has two stable states & can store one bit of state info. The output changes state by signals applied to one or more control inputs.

The basic JK flip flop has J, K inputs & a clock input & outputs Q &  $\bar{Q}$  (the inverse of Q) optionally it may also include the  $\overline{PR}$  &  $\overline{CLR}$  control inputs.

Frequency divider:

