

Haroon Rashid

Reg#16549

Semester: 6th

Subject: DLD Lab-8

Submitted to: Sir MUHAMMAD AMIN

Lab 9: JK Flip Flop

Observation Table:

JK Flip Flop:- Input Variable: CLR, CLK, J, K

Output Variable: Q, Qbar

Control		Inputs		Outputs	
CLK BAR	CLK	J	K	Q	Qbar
1	1	0	0	Q ₀	Q ₀ ⁻
1	1	1	0	1	0
1	1	0	1	0	1
1	1	1	1	TOGGLE	

→ Memory State