

Name

AKIF HAYAT

ID

16016

Subject

LCA

Assignment

sessional

Submitted to

Engr. Shahid Jinnah

①

Q No 1:- Evaluate the determinants.
Solution:- (i) Given

$$\begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}$$

Solution:-

$$\begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}$$

$$= 6 - (-4)$$

$$= 6 + 4 = 10$$

(ii) Given:-

$$\begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

Solution:- Expand by Row 1

$$= 0 \begin{vmatrix} 4 & 1 \\ 3 & 5 \end{vmatrix} - 2 \begin{vmatrix} 6 & 1 \\ 3 & 5 \end{vmatrix} + 11 \begin{vmatrix} 6 & 4 \\ 3 & -1 \end{vmatrix}$$

$$= 0 - 2(30 - 3) + 11(-6 - 12)$$

$$= -2(27) + 11(-18)$$


$$= -54 - 198$$

$$= -252$$

Q No 2:-

Ans:-

Figure:-

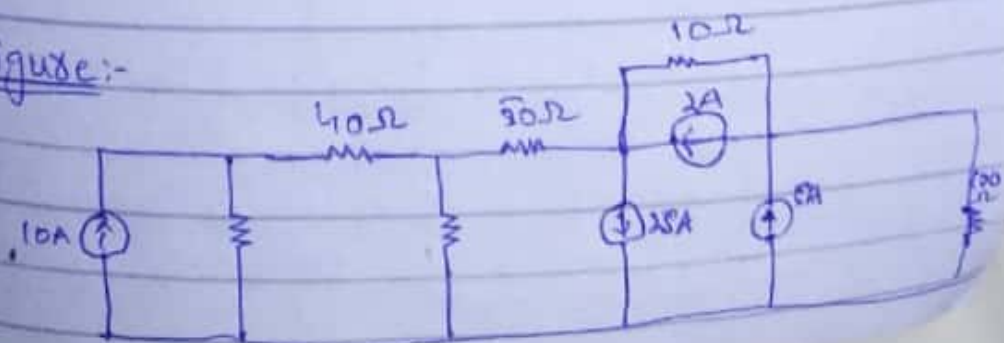

(2)

solutions-

All nodes in the above circuit is verified so we solve it through nodal analysis.

(i) Applying KCL on node 1:-

$$\frac{V_1}{20} + \frac{V_1 - V_2}{40} = 10$$

$$\frac{2V_1 + V_1 - V_2}{40} = 10$$

$$3V_1 - V_2 = 10 \times 40$$

$$3V_1 - V_2 = 400 \quad \text{--- (2)}$$

(ii) Applying KCL on node 2:-

$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{50} = 0$$

$$\frac{5V_2 - 5V_1 + 2V_2 + 4V_2 - 4V_3}{200} = 0$$

$$-5V_1 + 11V_2 - 4V_3 = 0$$

(iii) Applying KCL on node 3:-

$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_4}{10} = 2 - 2.5$$

$$\frac{V_3 - V_2}{50} + \frac{5V_3 - 5V_4}{10} = -0.5$$

(3)

$$\frac{V_3 - V_2 + 5V_3 - 5V_4}{50} = -0.5$$

$$-V_2 + 6V_3 - 5V_4 = -25 \quad \text{--- (1)}$$

Applying KCL on node 4:-

$$\frac{V_3 - V_2}{10} + \frac{V_3}{200} = 5 - 2$$

$$\boxed{\frac{20V_3 - 20V_2 + V_3}{200} = 3}$$

$$\frac{20V_3 - 20V_2 + V_3}{200} = 3$$

$$-20V_2 + 21V_3 = 600 \quad \text{--- (4)}$$

Solving further by using calculator:-

so we get

$$V_1 = 180.46 \text{ V}$$

$$V_2 = 141.3 \text{ V}$$

$$V_3 = 168.2 \text{ V}$$

$$V_4 = 172.5 \text{ V}$$

As from the figure we know that $V_2 = V_p$


Result:-

$$V_p = 141.3 \text{ V}$$

Q No 3:-

Ans:-

Figure:-

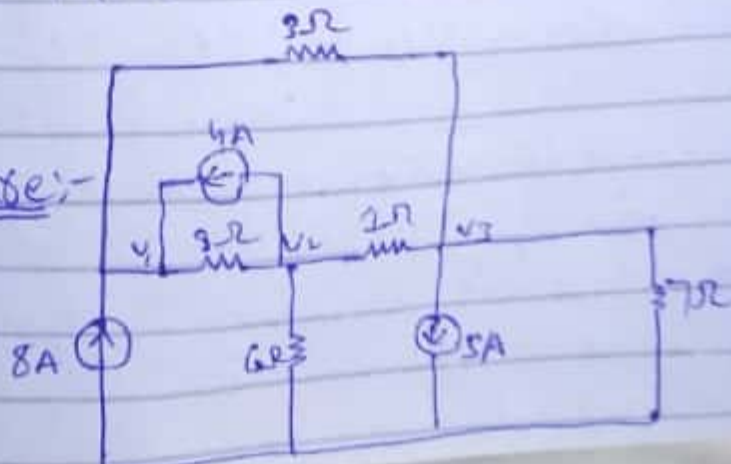

(4)

Solution:-

Solving by nodal analysis.

① Applying KCL on node 1:-

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{3} = 8 + 4$$

$$\frac{V_1 - V_2 + V_1 - V_3}{3} = 12$$

$$2V_1 - V_2 - V_3 = 36 \quad \text{--- (1)}$$

② Applying KCL on node 2:-

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + V_2 - V_3 = 4$$

$$\frac{5V_2 - 5V_1 + V_2 + 15V_2 - 15V_3}{15} = 4$$

$$-5V_1 + 23V_2 - 15V_3 = -60 \quad \text{--- (2)}$$

③ Applying KCL on node 3:-

$$V_3 - V_2 + \frac{V_3 - V_1}{3} + \frac{V_3}{7} = 5$$

$$\frac{21V_3 - 21V_2 + 7V_3 - 7V_1 + V_3}{21} = 5$$

$$-7V_1 - 21V_2 + 31V_3 = -105 \quad \text{--- (3)}$$

Now solving by Cramer's rule:-

(6)

$$V_2 = \begin{vmatrix} 2 & 36 & -1 \\ -5 & 4 & -15 \\ -7 & -105 & 31 \end{vmatrix}$$
$$= 2 \begin{vmatrix} 4 & -15 \\ -105 & 31 \end{vmatrix} - 36 \begin{vmatrix} -5 & -15 \\ -7 & 31 \end{vmatrix} - 15 \begin{vmatrix} -5 & 4 \\ -7 & -105 \end{vmatrix}$$
$$= -2902 - 9360 - 553$$
$$= \frac{-12815}{-786}$$

$$V_2 = 16.30$$

$$V_3 = \begin{vmatrix} 2 & -1 & 36 \\ -5 & 2 & 4 \\ -7 & -21 & -105 \end{vmatrix}$$
$$= 2 \begin{vmatrix} 2 & 4 \\ -21 & -105 \end{vmatrix} + 1 \begin{vmatrix} -5 & 4 \\ -7 & -105 \end{vmatrix} + 36 \begin{vmatrix} -5 & 2 \\ -7 & -21 \end{vmatrix}$$
$$= -35280 + 553 + 4284$$
$$= \frac{-30443}{-786}$$

$$V_3 = 38.73$$

Now we know that

$$V_{SR} = -V_2$$

$$V_{SR} = 16.30V$$

$$P = \frac{V^2}{i} = \frac{V_3^2}{7}$$


$$P = \frac{(38.73)^2}{7}$$

$$P = 214.28 \text{ W.}$$

(7)

Q No 4:-

Ans:-

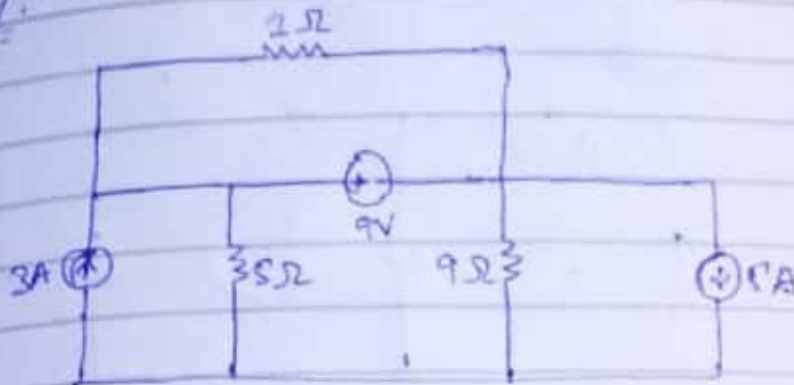

Solution:

considering V_1 & V_2 as a supernode.

Applying KCL on supernode

$$\frac{V_1 - V_2}{1} + \frac{V_1}{5} + \frac{V_2 - V_1}{1} + \frac{V_2}{9} = 3 - 5$$

$$45V_1 - 45V_2 + 9V_1 + 45V_2 - 45V_1 + 9V_2 = 2$$

45

$$9V_1 + 9V_2 = 90 \quad \text{--- (1)}$$

$$V_1 - V_2 = 9 \quad \text{--- (2)}$$

$$9V_1 + 9V_2 = 90$$

$$9V_1 - 9V_2 = 81$$

$$18V_1 = 171$$

$$V_1 = 171 / 18$$

$$V_1 = 9.5 \text{ V}$$

Putting in eq (2)

$$V_2 = V_1 - 9$$


$$V_2 = 9.5 - 9$$

$$V_2 = 0.5 \text{ V}$$

(8)

Q No 51-

Ans:- Figure:-

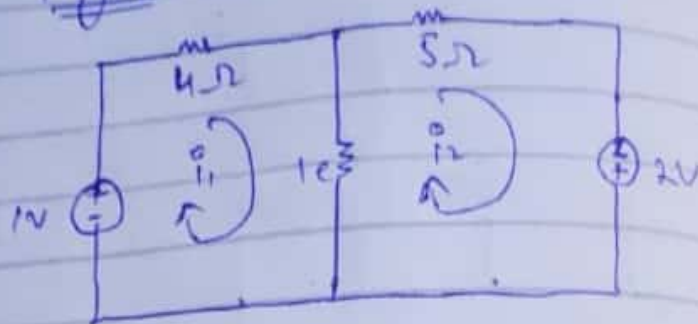

Solution:-

Solving by Mesh analysis

Applying KVL on i_1

$$4i_1 + 1(i_1 - i_2) = 1$$

$$5i_1 - i_2 = 1 \quad \text{--- (i)}$$

(ii) Applying KVL on i_2 :

$$1(i_2 - i_1) + 5i_2 = 2$$

$$-1i_1 + 6i_2 = 2 \quad \text{--- (ii)}$$

Multiplying 5 with eq (ii) & Add with eq (i)

$$5i_1 - i_2 = 1$$

$$\underline{-5i_1 + 30i_2 = 10}$$

$$29i_2 = 11$$

$$i_2 = 11/29$$

$$i_2 = 0.379 \text{ A}$$

Putting in eq (i)

$$5i_1 = 1 + 0.379 \text{ A}$$

$$i_1 = 0.275 \text{ A}$$

Result:-


$$i_1 = 0.275 \text{ A}$$

$$i_2 = 0.379 \text{ A}$$

(9)

Q No 6:-

Ans:- Figure:-

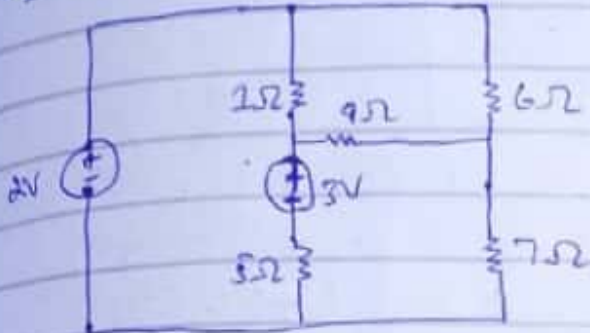

Sol:-

Applying KCL on i_2 / Mesh 2

$$1(i_2 - i_2) + 5(i_2 - i_3) = 3 + 2$$

$$i_2 - i_2 + 5i_2 - 5i_3 = 5$$

$$6i_2 - i_2 - 5i_3 = 5 \quad \text{--- (1)}$$

Applying KCL on i_2 / Mesh 3

$$1(i_2 - i_1) + 6i_2 + 9(i_2 - i_3) = 0$$

$$-i_2 + 16i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

Applying KCL on Loop 1:-

$$5(i_3 - i_1) + 9(i_3 - i_2) + 7i_3 = -3$$

$$-5i_2 - 9i_2 + 21i_3 = -3 \quad \text{--- (3)}$$

Solving by Cramer's rule

$$\begin{bmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ -3 \end{bmatrix}$$

$$|A| = \begin{vmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{vmatrix}$$

$$= 6 \begin{vmatrix} 16 & -9 & +1 & -1 & -9 \\ -9 & 21 & -5 & 21 & -5 \end{vmatrix} - 1 \begin{vmatrix} -5 & -1 & -5 \\ -5 & -9 & 21 \end{vmatrix} + 5 \begin{vmatrix} -1 & 16 & -9 \\ -5 & -9 & 21 \end{vmatrix}$$

$$= 6(235) - (-1)(-66) - 5(89)$$

$$= 1015$$

$$i_1 = \begin{vmatrix} 5 & -1 & -5 \\ 0 & 16 & -9 \\ -3 & -9 & 21 \end{vmatrix}$$

$$= 5 \begin{vmatrix} 16 & -9 \\ -9 & 21 \end{vmatrix} + 0 - 3 \begin{vmatrix} -1 & -5 \\ 16 & -9 \end{vmatrix}$$

$$= 5(386 - 81) + 0 - 3(+9 - (-75))$$

$$= 5(255) + 0 - 3(+9 + 75)$$

$$= 5(255) + 0 - 3(84) - 3(89)$$

$$= 1275 - 252 - 267$$

$$i_1 = \frac{1008}{1015} \text{ A}$$

$$i_1 = \frac{1008}{1015}$$

$$i_1 = 0.993$$

$$i_2 = \begin{vmatrix} 6 & 5 & -5 \\ -1 & 0 & -9 \\ -5 & -3 & 21 \end{vmatrix}$$

$$= 6 \begin{vmatrix} 0 & -9 \\ -3 & 21 \end{vmatrix} - 5 \begin{vmatrix} -1 & -9 \\ -5 & 21 \end{vmatrix} - 5 \begin{vmatrix} -1 & 0 \\ -5 & -3 \end{vmatrix}$$

$$= 6(0 - 27) - 5(-21 - 45) - 5(-3 - 0)$$

$$= 6(-27) - 5(-66) - 5(-3)$$

$$= -162 + 330 + 15$$

$$= -162 + 345$$

$$= 183$$

$$i_2 = \frac{183}{1015} = 0.18 \text{ A}$$

$$P_3 = \begin{pmatrix} 0 & -1 & 5 \\ -1 & 16 & 0 \\ -5 & -9 & 3 \end{pmatrix} \quad (11)$$

$$= 6 \begin{vmatrix} 16 & 0 & +1 \\ -9 & 3 & -5 \\ +5 & -1 & 16 \end{vmatrix} - 1 \begin{vmatrix} +1 & 0 & +5 \\ -5 & 3 & -5 \end{vmatrix} + 5 \begin{vmatrix} -1 & 16 \\ -5 & -9 \end{vmatrix}$$

$$= 6(48 - 0) + 1(-3 + 0) + 5(+9 + 80)$$

$$= 6(48) + 1(3) + 5(89)$$

$$= 288 + 3 + 445$$

$$= 736$$


$$P_3 = \frac{736}{1015}$$

$$i_3 = 0.72 \text{ A}$$

Q No 7:

Ans:

Figure:

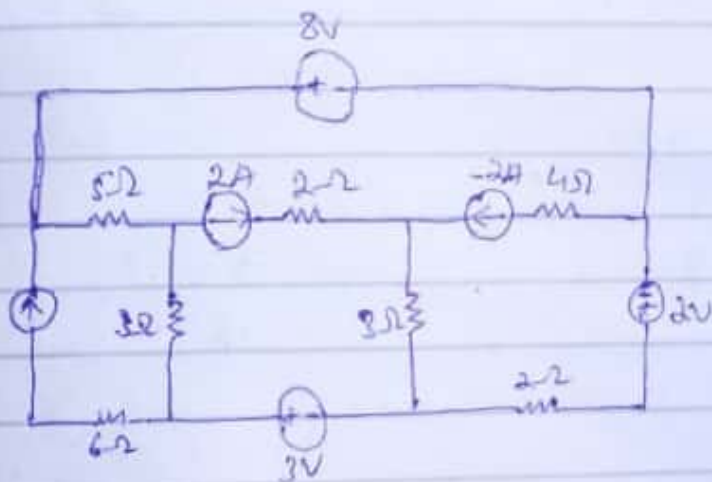

Considering i_1, i_2 & i_3 as a supermesh.
Applying KCL. supermesh.

$$5(i_1 - 3) + 3(i_2 - 3) + 2i_3 = 3 + 2 - 8$$

$$5i_1 - 15 + 3i_2 - 9 + 2i_3 = -3$$

$$5i_1 + 3i_2 + 2i_3 = 12 \quad \text{--- (1)}$$

we also know that

$$i_2 - i_1 = 1$$

$$\text{where } i_1 = 1 + i_2 \quad \text{--- (2)}$$

(12)

Q7

$$i_1 - i_3 = -2$$

$$i_3 = +2 + i_2 \quad \text{--- (b)}$$

Putting in eq (1)

$$5i_1 + 3(1 + i_2) + 2(-2 + i_2) = 12$$

$$5i_1 + 3 + 3i_2 - 4 + 2i_2 = 12$$

$$10i_1 - 1 = 12$$

$$i_1 = 11/10$$

$$i_1 = 1.1 \text{ A}$$

Putting in eq A & B

$$i_2 = 1 + 1.1$$

$$i_2 = 2.1 \text{ A}$$

Q8

$$i_3 = +2 + 1.1$$

$$i_3 = 3.1 \text{ A}$$

Result

$$i_1 = 1.1 \text{ A}$$


$$i_2 = 2.1 \text{ A}$$

$$i_3 = 3.1 \text{ A}$$

Q8:-

Ans:-

Figure:-

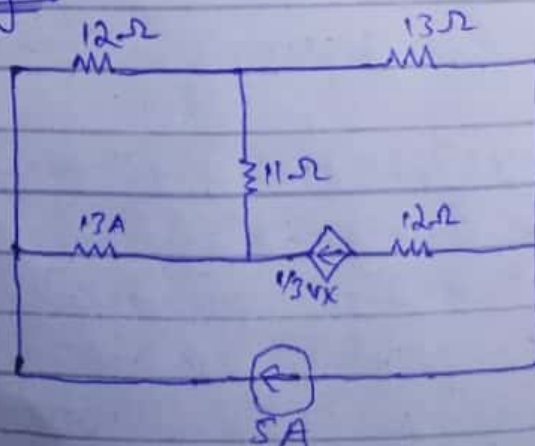

(13)

from the figure we know that 5A current is flowing through i_2 .
 $i_1 = 5A$

Now there is an independent source b/w i_2 & i_3 .
so

$$i_1 - i_3 = 1/3 \text{ Vx}$$

$$i_3 = \frac{13 i_3 + 5}{3}$$

$$i_3 = -1.5 A$$

Applying Mesh analysis on i_2 .

$$13(i_2 - i_1) + 11(i_2 - i_3) + 12i_2 = 0$$

$$13i_2 - 13i_1 + 11i_2 - 11i_3 + 12i_2 = 0$$

$$36i_2 - 13(5) - 11(-1.5) = 0$$

$$36i_2 = 65 - 16.5$$

$$i_2 = \frac{48.5}{36}$$

36


$$i_2 = 1.347 A.$$

Q NO 2:-

Chapter # 5


Ans:- (11)

Figure

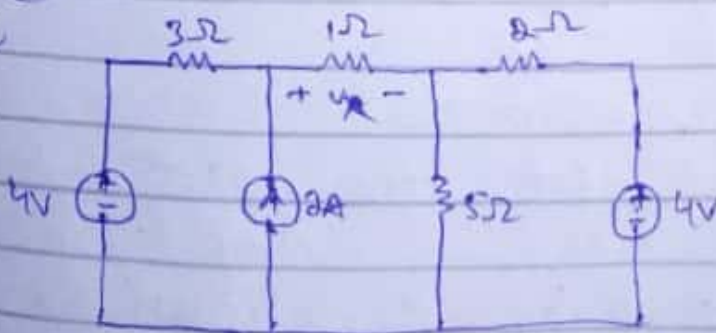


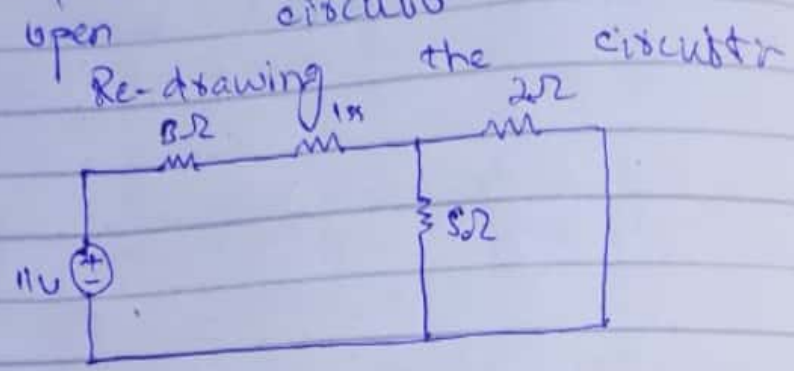(14)

Solution:
Setting the right-hand voltage as a short circuit & the current source as an open circuit.



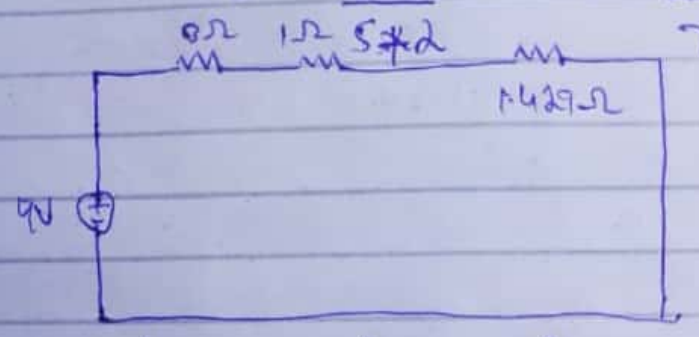As 5Ω & 2Ω are in parallel so combining both.
 $= \frac{5 \times 2}{5 + 2} = \frac{10}{7} = 1.429\Omega$



Apply mesh analysis


$$3i_1 + 1i_1 + 1.429 = 11$$

$$i_1 = \frac{11}{5.42}$$

$$i_1 = V_x = 0.736$$

Now let's set the left-hand side voltage as a short circuit & current source as an open circuit.


(15)

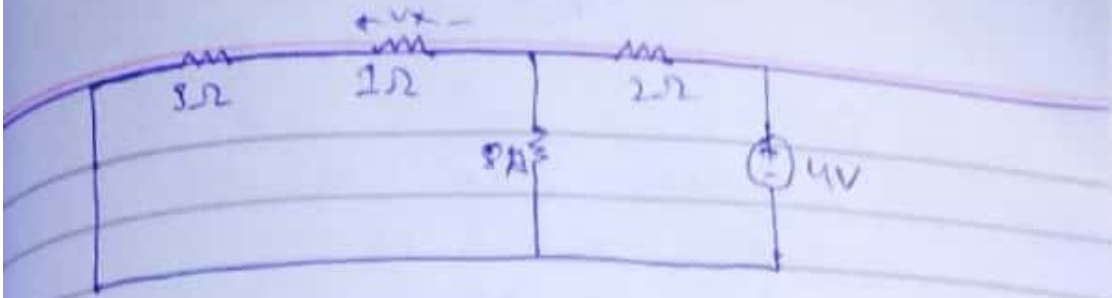

As 5Ω is in parallel with
 1Ω

$$R_{eq} = \frac{5 \times (3+1)}{5 + (3+1)} = \frac{20}{9}$$

$$= 2.222\Omega$$

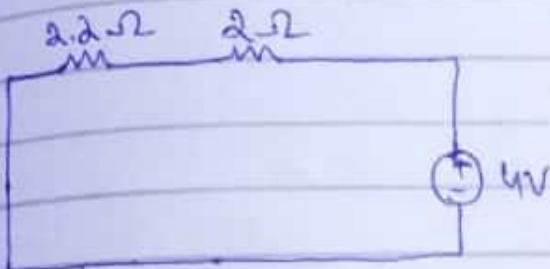

Now by mesh analysis.

$$i_1 = \frac{4}{4.2} = 0.95 \text{ A}$$

$$V_{2.2\Omega} = -2.10 \text{ V}$$


Now for 1Ω

$$V_{x2} = \frac{-2.10 (1)}{1+3}$$

$$V_{x2} = \frac{-2.10}{4}$$

$$V_{x2} = -0.525 \text{ V}$$

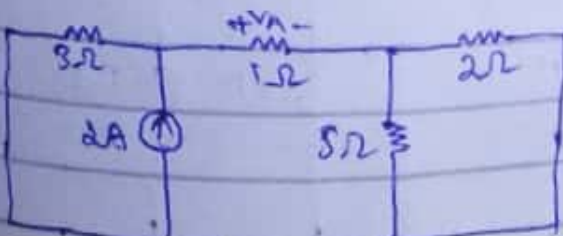
Now setting the two voltages
 as a short circuit and
 Redraw the circuit.



(16)

$$R_{eq} = 5 \parallel 2$$
$$= \frac{2 \times 5}{5+2} = \frac{10}{7} = 1.42 \Omega$$

Re-drawing the circuits

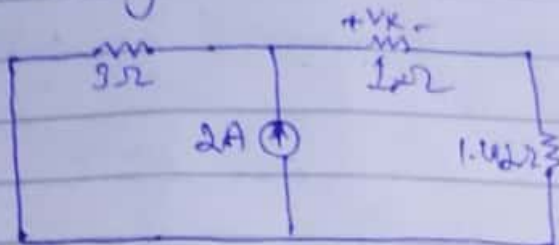

Applying current dividing rule.

$$I_{2\Omega} = \frac{2(3)}{3+1+1.4}$$

$$I_{2\Omega} = 1.105$$

Now

$$V_x = IR$$

$$V_{x1} = (1.105)(1)$$

$$V_{x2} = 1.105$$

Now

adding all the voltages

$$V_x = V_{x1} + V_{x2} + V_{x3}$$

$$= 0.73 + (-0.52) + 1.10$$

$$V_x = 1.31 \text{ V}$$


Q No 2

Ans: Figure:-



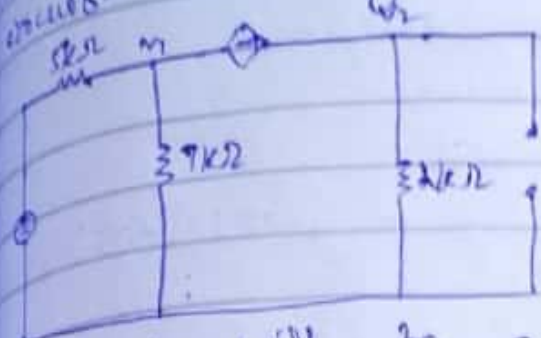(17)

Removing the current sources so
will be act on open
circuits - Redrawing the circuit.



At v_2 will be a supernode applying
kcl on a supernode.

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{v_2}{2000} = 0$$

Now $v_1 - v_2 = 0.2 I_{x1}$

$$v_2 = 0.2 I_{x1} + v_1$$

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{0.2 I_{x1} + v_1}{2000} = 0$$

But $v_1 = 7000 I_{x1}$


$$\frac{7000 I_{x1} - 1}{5000} + \frac{7000 I_{x1}}{7000} + \frac{7000 I_{x1} + 0.2 I_{x1}}{2000} = 0$$

$$1.4 I_{x2} = 0.2 + I_{x1} + 3.5 I_{x2} + 0.1 I_{x2} = 0$$

$$6 I_{x2} = 0.2$$

$$I_{x1} = 0.03 \text{ A}$$

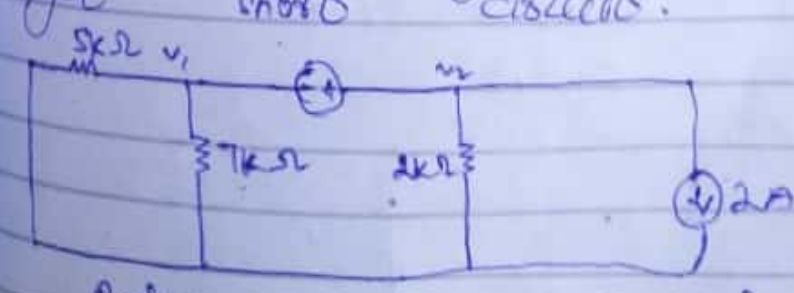Now the voltage source will be
get short circuits.



Applying kcl on supernode.

(18)

$$\frac{V_1}{5000} + \frac{V_1}{7000} + \frac{V_1}{2000} = -2$$

$$\therefore V_2 = V_1 + 0.2 I_{x2}$$

$$\frac{V_1}{5000} + \frac{V_1}{7000} + \frac{V_1 + 0.2 I_{x2}}{2000} = -2$$

$$\therefore V_1 = 7000 I_{x2}$$

$$\frac{7000 I_{x2}}{5000} + \frac{7000 I_{x2}}{7000} + \frac{7000 I_{x2} + 0.2 I_{x2}}{2000} = -2$$

$$1.4 I_{x2} + I_{x2} + 3.5 I_{x2} + 0.2 I_{x2} = -2$$
$$6 I_{x2} = -2$$

$$I_{x2} = -2/6$$

$$I_{x2} = -0.33 \text{ A}$$


$$I = I_{x1} + I_{x2}$$

$$I = 0.07 - 0.33$$

$$I = 0.3 \text{ A}$$

Q NO 3

Ans: Figure:-

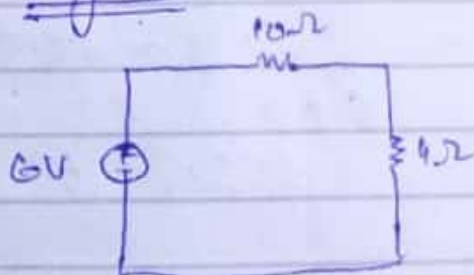


According to ohm's law

$$V = IR$$

$$I = V/R = 6/10$$


$$I = 0.6 \text{ A}$$

Re-drawing circuit

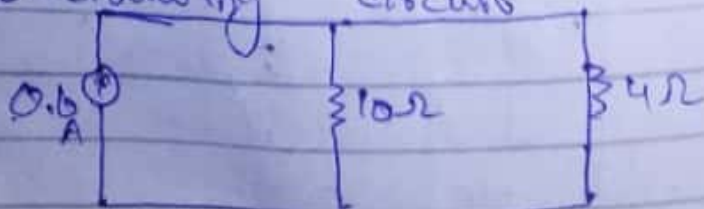

(19)

Figure 2:

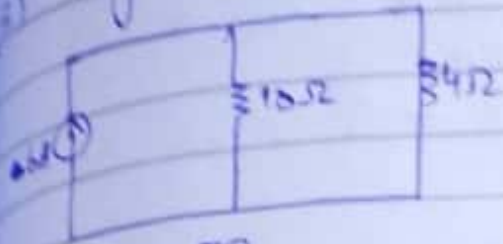

$$V = IR$$

$$V = (6)(10)$$

$$V = 60V$$


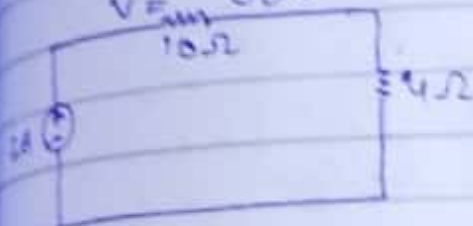


Figure 3:

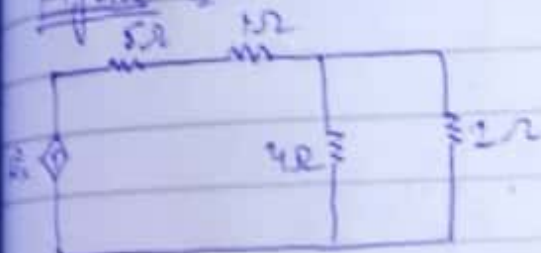


$$V = IR$$

$$I = V/R$$


$$= 2/5$$

$$I = 0.4A$$

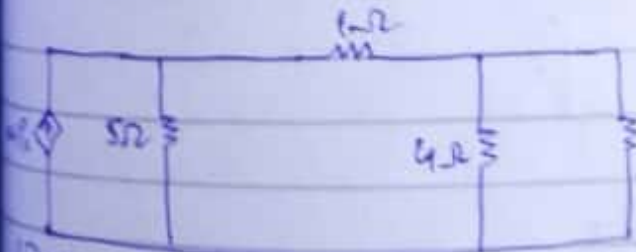

Q No 4:-

Ans:-

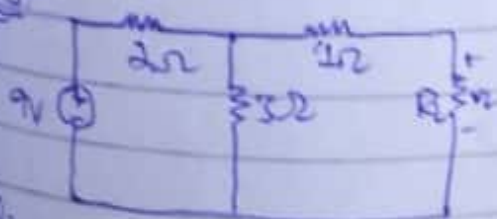

sol:-

(20)


To get R_{Th} we will add all the resistor accepts

$$R_{Th} = 2 \parallel 3 + 1$$
$$= \frac{6}{5} + 1$$


$$R_{Th} = 2.2 \Omega$$

Now solving by source transformation


$$I = V/R = \frac{9}{2} = 4.5$$

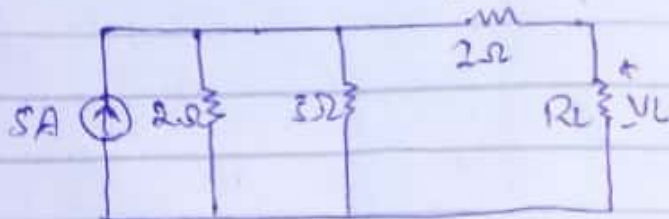
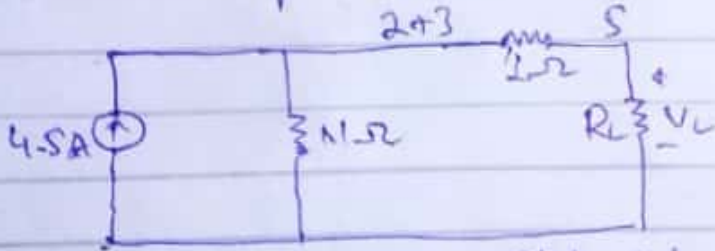
$$R_{eq} = \frac{2 \times 3}{2+3} = \frac{6}{5} = 1.2$$



$$V = R = (4.5)(1.5) = 5.4V$$

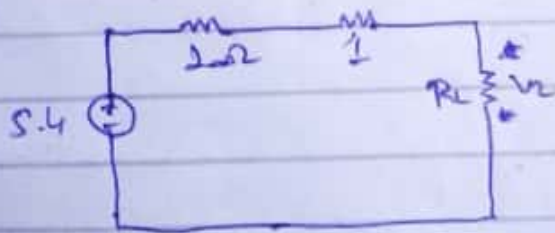

$$V_{Th} = 5.4V$$

$$R_{Th} = 2.2 \Omega$$

(21)

Now calculating each value of R_L

$$R_L = 1\Omega = \frac{5.4(1)}{1+2.2}$$

$$V_L = 1.68V$$

$$\begin{aligned} \text{(ii)} \quad R_L &= 3.5\Omega \\ &= \frac{(5.4)(3.5)}{3.5+2.2} \end{aligned}$$

$$V_L = 3.31V$$

$$\begin{aligned} \text{(iii)} \quad R_L &= 6.25\Omega \\ &= \frac{(5.4)(6.25)}{(6.25)(2.2)} \end{aligned}$$

$$V_L = 3.99V$$

$$\begin{aligned} \text{(iv)} \quad R_L &= 9.8\Omega \\ &= \frac{(5.4)(9.8)}{(2.2)+9.8} \end{aligned}$$

$$V_L = 4.41V$$

Q No 5:-

Ans:- Figure:-





$$R_{eq} = \frac{5 \times 5}{5+5} = \frac{25}{10} = 2.5$$


$$V = IR$$

$$= (1)(0.8) = 0.8$$

(22)

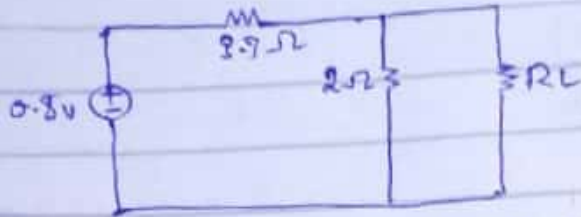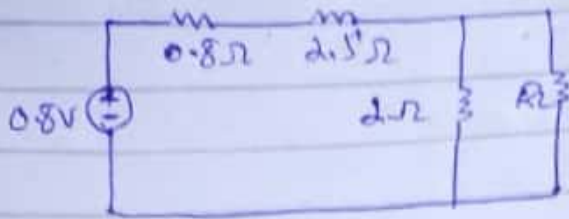

$$I = 0.8 / 3.3 = 0.24$$

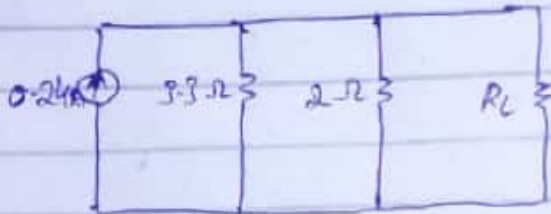

$$R_{eq} = \frac{3.3 \times 2}{2 + 3.3} = \frac{6.6}{5.3}$$

$$R_{eq} = 1.245$$



$$I_N = 0.24 \text{ A}$$

$$R_N = 1.245 \Omega$$

Now

$$V = IR$$

$$V_{Th} = I_N \cdot R_N$$

$$= (0.24)(1.245)$$

$$V_{Th} = 0.30 \text{ V}$$

Eq

$$R_N = R_{Th}$$

$$R_{Th} = 1.245$$

(23)

Find each value for R_L

$$R_L = 0 \Omega$$
$$= \frac{0.30 \Omega}{1.245 + 0}$$

$$I_L = 0.243 \text{ A}$$

$$R_L = 2 \Omega$$
$$= \frac{0.30 \Omega}{1.245 + 1} = 0.13 \text{ A}$$

$$I_L = 0.135 \text{ A}$$

$$R_L = 4.92 \Omega$$
$$= \frac{0.30 \Omega}{1.245 + 4.92}$$

$$I_L = 0.049 \text{ A}$$


$$R_L = 8.107 \Omega$$
$$= \frac{0.30 \Omega}{1.245 + 8.107}$$

$$I_L = 0.032 \text{ A}$$

Q No 6 Part (ii)

Ex 5.3

Figure 1

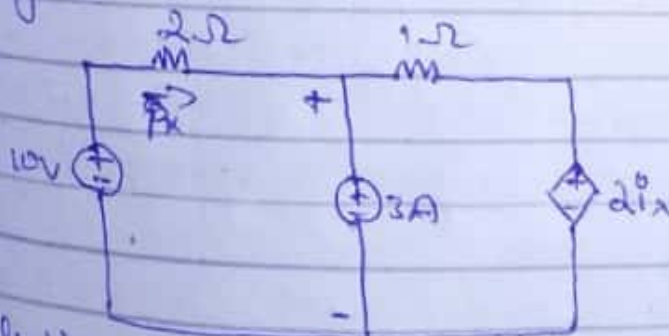


Solution:

First we will remove current source and will make it an open circuit

(24)

So the figure will be

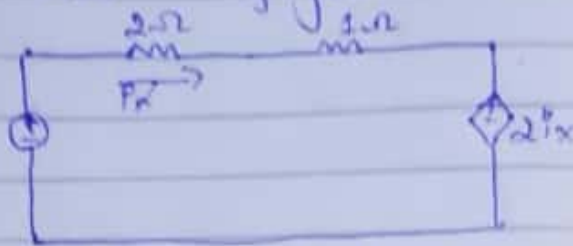


Applying KVL on Mesh

$$2ix' + 1ix' + 2ix' = 10$$

$$5ix' = 10$$

$$ix' = 2A$$

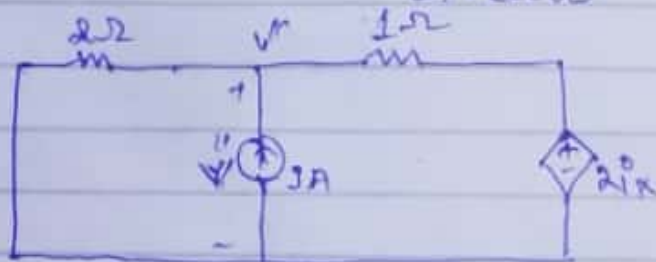Now will remove voltage source
for making it an open
circuit



Applying KCL on v''

$$\frac{v''}{2} + \frac{v'' - 2ix''}{1} = 3$$

$$v'' + 2v'' - 2ix'' = 3$$

$$3v'' - 4ix'' = 6$$

We know from the figure

$$v'' = -2ix''$$

$$3(-2ix'') - 4ix'' = 6$$

$$-10ix'' = 6$$

$$ix'' = -6/10$$


$$ix'' = -0.6A$$

(25)

$$P_x = P_{x'} + P_{x''}$$
$$= 2 + (-0.6)$$

$$P_x = 1.4 \text{ A}$$

Example

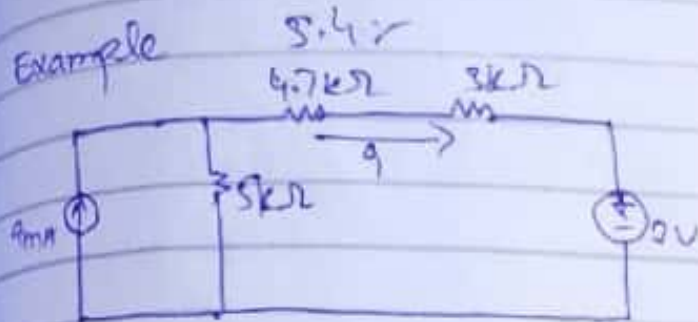

Soln

We know that


$$V = IR$$

$$V = (9 \times 10^{-3}) (5000)$$

$$= (0.009) (5000)$$

$$V = 45$$

Redrawing the circuit

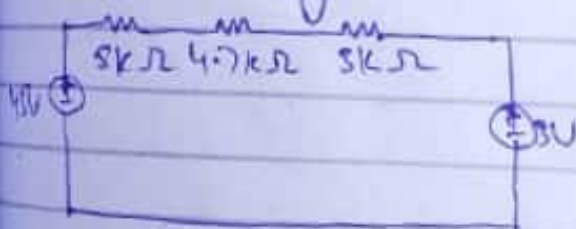

Applying KVL on Mesh

$$5000i + 4700i + 3000i = 45 - 3$$


$$12700i = 42$$

$$i = 0.003 \text{ A}$$

Example

5.5

Figure 1

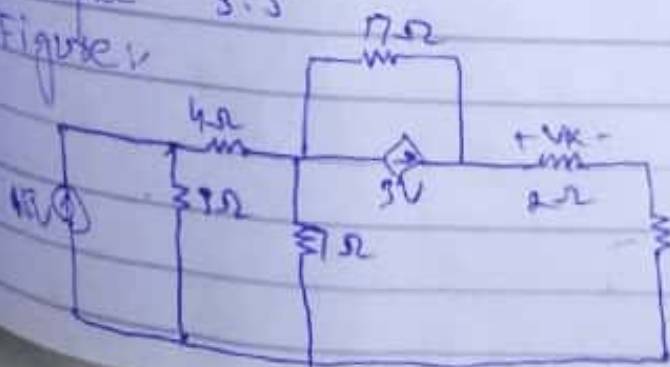

(26)


$$V = IR$$

$$V = 5(3) = 15V$$

$$V_x = 3(17)$$

$$V_x = 51$$

Redrawing a circuit

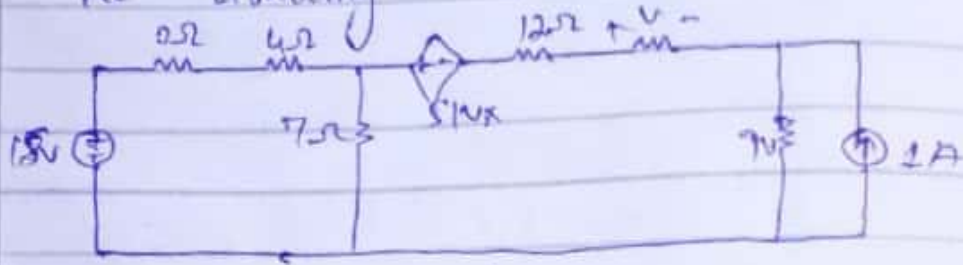


$$R = 5 + 4$$
$$= 9\Omega$$

$$I = \frac{V}{R} = \frac{15}{9} = 1.67A$$

$$V = IR = (1.67)(9) = 15V$$

$$V = 15V$$

Redrawing a circuit

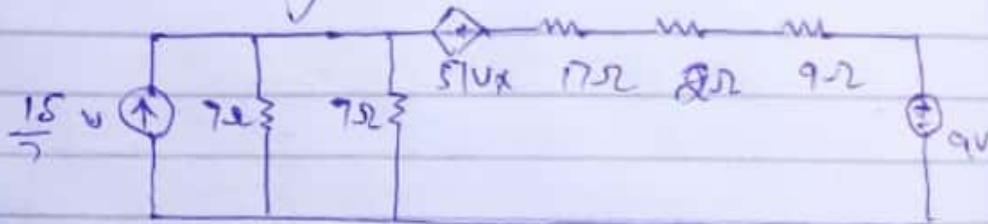


$$V = IR = \left(\frac{15}{9}\right)(9)$$

$$V = 15$$

$$R = 7 + 17 + 9$$

$$R = 26\Omega$$

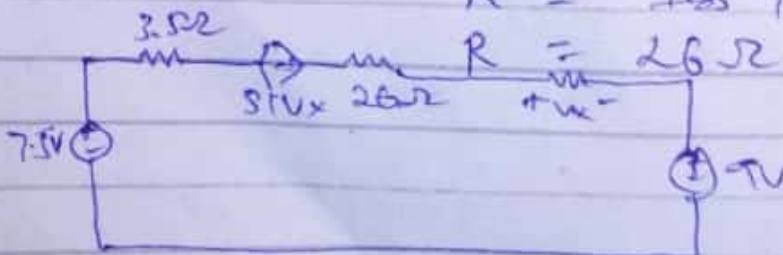

Applying KVL on Mesh

(27)

$$3.5i - 51v_x + 28i = 7.5 - 7$$

$$v_x = 21$$

$$3.5i - 51(21)i + 28i = 1.8$$

$$-1039.5i = -1.5$$

$$i = \frac{-1.5}{-1039.5}$$

$$i = 0.0014 \text{ A}$$

Example 5.6




Solution:

$$I = V/R = 12/3 = 4 \text{ A}$$



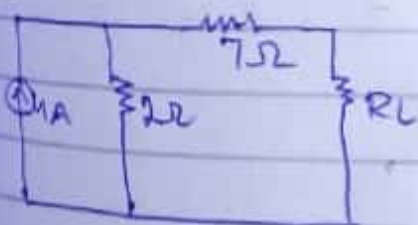
$$R_{eq} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2 \Omega$$




$$V = IR = (4)(2)$$

$$V = 8 \text{ V}$$

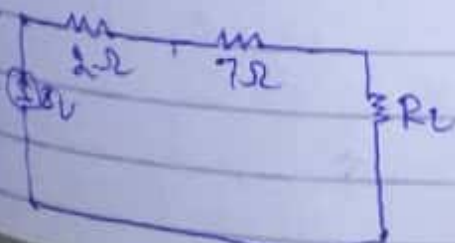

(28)

$$R = 2 + 7 = 9$$

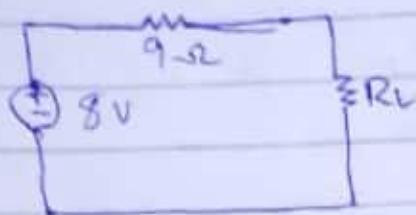

$$V_{TH} = 8V$$

$$R_{TH} = 9\Omega$$

$$R.P = \left(\frac{8}{9 + R_L} \right)^2 R_L$$


For any value of R_L with
different solution.

Example: 57

Figure:



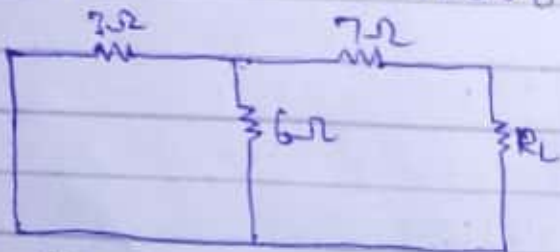For finding R_{TH} we will
remove voltage source & make
it a short circuit.



For R_{TH} we will add
all the resistor except R_L


$$R_{TH} = 3 \parallel 6 + 7$$

$$= \frac{18}{8} + 7$$

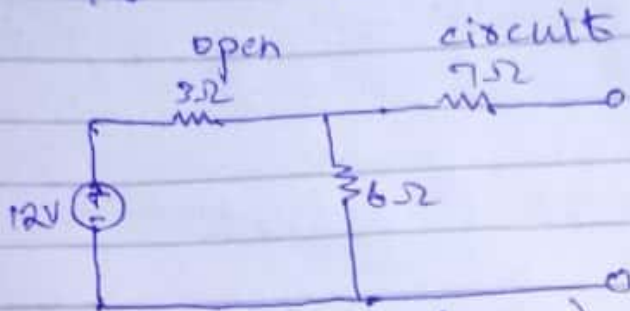(27)

$$R_{TH} = 9$$

For V_{OC} we will remove R_L and make it as an open circuit




$$V_{OC} = 12 \left(\frac{6}{3+6} \right)$$

$$V_{OC} = 8V$$

Q No 3

Ans Figure

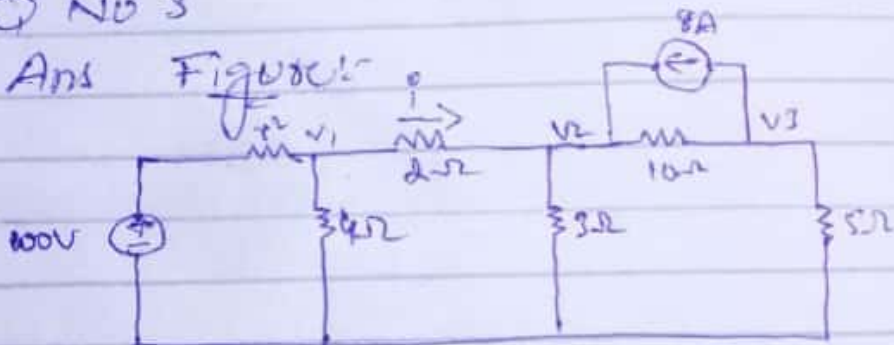

Applying KCL on node 1:

$$\frac{V_1 - 100}{3} + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Applying KCL on node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_1 - V_3}{10} = 8$$

$$30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3 = 80$$

(30)

$$-30V_2 + 53V_2 - 3V_3 = 480 \quad (2)$$

Applying KCL on node 3-

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 8$$

$$V_3 - V_2 + 2V_3 = 80$$

$$-V_2 + 3V_3 = 80 \quad (3)$$

Taking eq (1)

$$9V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{9} \quad (a)$$

Taking eq (2)

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad (b)$$

Putting eq (a) & (b) in eq (2)

$$-30(0.57)V_2 + 14.28 + 53V_2 - 3(0.33V_2 - 26.67) = 480$$
$$-17.1V_2 - 425.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

$$V_1 = 20.31$$

Putting in eq (a)


$$V_1 = \frac{4(20.31) + 100}{9} = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

(31)

Q2 Solving by mesh analysis:

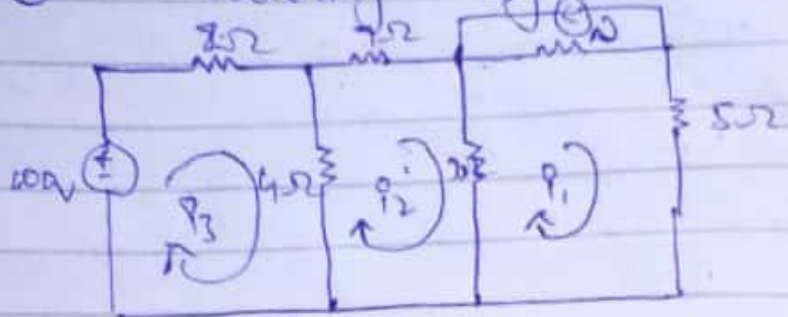

Applying KVL on Loop 1

$$8i_1 + 4(i_2 - i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Applying KVL on Loop 2

$$2i_2 + 4(i_2 - i_1) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Applying KVL on Loop 3

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_2 = \frac{11i_3 - 100}{12} \quad \text{--- (4)}$$

Taking eq (3)

$$3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (5)}$$

Putting eq (4) & (5) in eq (2)

(32)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$
$$\Rightarrow -1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$
$$7.2i_2 = +20 = 20/7.2$$

$$i_2 = 2.77 \text{ A}$$

$$i_L = i_x$$

$$i_A = 2.77 \text{ A}$$

Applying KCL on node (3)

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = 0$$

$$\frac{v_3 - v_2 + v_3}{10} = 0 \quad \text{--- (3)}$$

Now Taking eq (1) & (2)

$$7v_1 - 4v_2 = 100$$

$$v_1 = \frac{4v_2 + 100}{7} \quad \text{--- (4)}$$

Now

$$-v_2 + 3v_3 = 0$$

$$v_3 = 1/3 v_2 \quad \text{--- (5)}$$

Putting in eq (2)

$$-30(0.57v_2 + 14.28) - 4v_2 + 2(0.33v_2) = 0$$
$$-17.1v_2 - 428.4 - 4v_2 + 0.66v_2 = 0$$

$$20.44v_2 = 428.4$$

$$v_2 = -20.95$$

Putting in eq (4)

$$v_1 = 2.31$$


$$i_1 = \frac{2.31 + 20.95}{2} \Rightarrow i_1 = 11.63$$

(33)

Applying KCL on node ④:-

Now Removing voltage source making it short circuit

Redrawing circuit:-

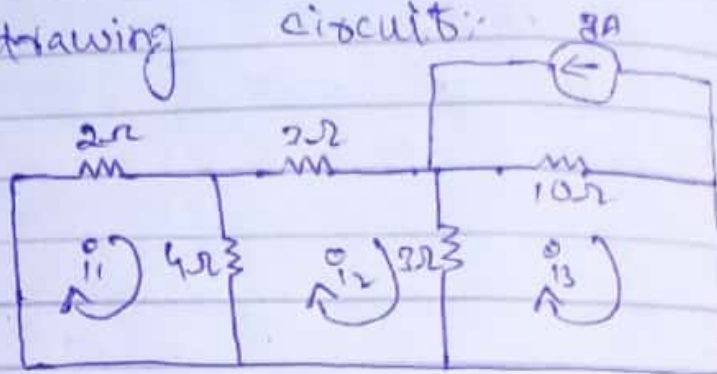

$$i_4 = 2A$$

Applying KVL on loop 1

$$8i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Applying KVL on loop 2

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + 5i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3

$$10i_3 + 3i_3 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80$$

Taking eq (1)

$$i_1 = i_2$$

$$i_1 = 0.33i_2 \quad \text{--- (3)}$$

(34)

$$-3P_2 + 18P_3 = -80$$

$$P_3 = \frac{3P_2 - 80}{18} \quad \text{--- (b)}$$

$$4(0.33P_2) + 9P_2 - 3(0.16P_2 - 4.44) = 0$$

$$1.32P_2 + 9P_2 - 0.48P_2 + 13.32 = 0$$

$$P_2 = 1.354$$

Now

$$I = I_1 + I_2$$

$$I = 1.44 + 1.35$$

$$I = 2.79 \text{ A}$$

Result

$$I = 2.79 \text{ A}$$