

Haroon Rashid

Reg# 16549

Semester 6<sup>th</sup>

Assignment: DLD Lab

Submitted to: Sir MUHAMMAD AMIN

# Lab:- 1

Table 1.1: Output Observation Table

S.No	Inputs		Outputs							
	A	B	NOT		AND	OR	NAND	NOR	XOR	XNOR
			A	B						
1	0	0	1	1	0	0	1	1	0	1
2	0	1	1	0	0	1	1	0	1	0
3	1	0	0	1	0	1	1	0	1	0
4	1	1	0	0	1	1	0	0	0	1

Not is According to be A & B