

Haroon Rashid


Reg# 16549

Semester: 6th

Final Paper: **DIGITAL LOGIC AND
DESIGN (THEORY)**


Submitted to: Sir MUHAMMAD AMIN

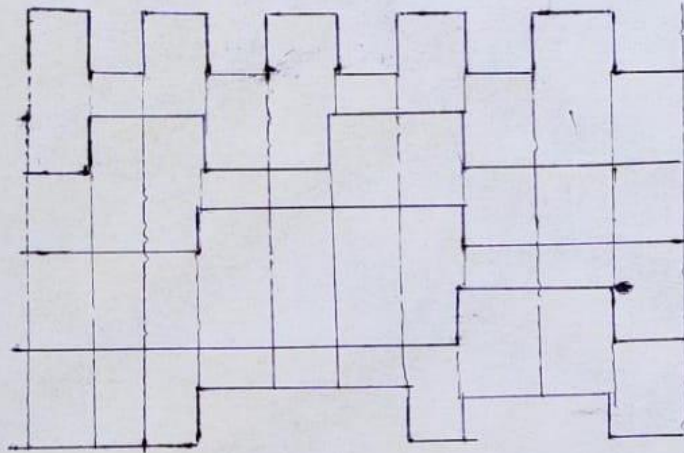Q1:- Draw the logic circuit using the input (A, B, C, D) and output (X) waveforms in Figure 01.



Answer:-

Solution.

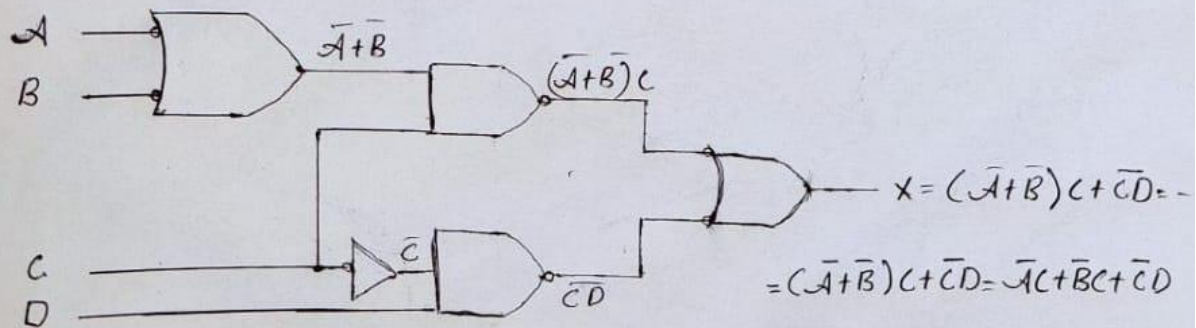

Q2: For the 4-Input multiplexer, data inputs are given as

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

Find the Output Y if the select inputs are given as


a) $S_0 = 1, S_1 = 0$

$$S_0 = 0, S_1 = 1$$

$$S_0 = 1, S_1 = 1$$

$$S_0 = 0, S_1 = 0$$

Answer:-

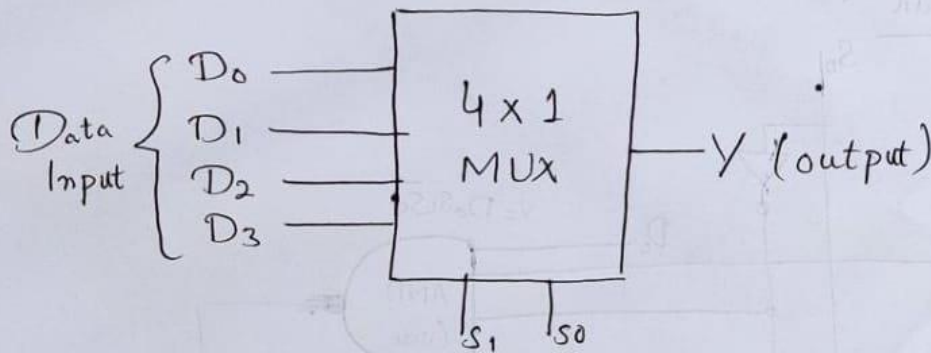

Find Select lines:-

$$n = 4$$

$$m = \log_2 n$$

$$m = \log_2 4$$

$$= \log_2 2^2 \quad \because \log_a a = 1$$


$$m = 2 \log_2 2 = 2 \cdot 1 = 2 \rightarrow \text{Select lines}$$

S_0	S_1	Data
1	0	D_0
0	1	D_1
1	1	D_2
0	0	D_3

Output (Y)

$$Y = D_0 S_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 S_0 + D_3 \bar{S}_1 \bar{S}_0$$

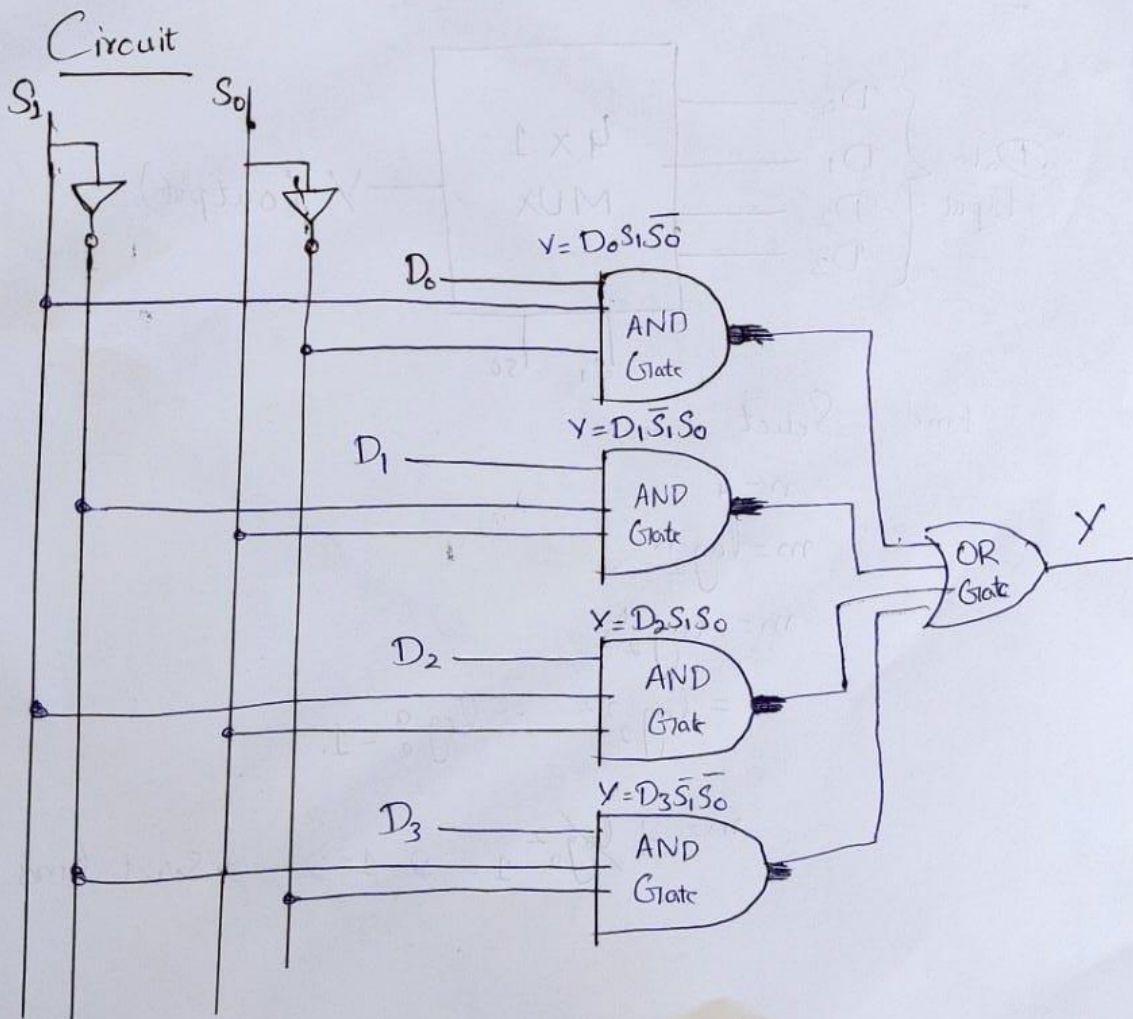Output = $Y = D_0 S_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 S_0 + D_3 \bar{S}_1 \bar{S}_0$



Q3. For the Circuit in Figure 02, assume the inputs are $\overline{\text{Add/Subt}}=1$, $A=1010$, & $B=1101$. What is the Output

Answer-


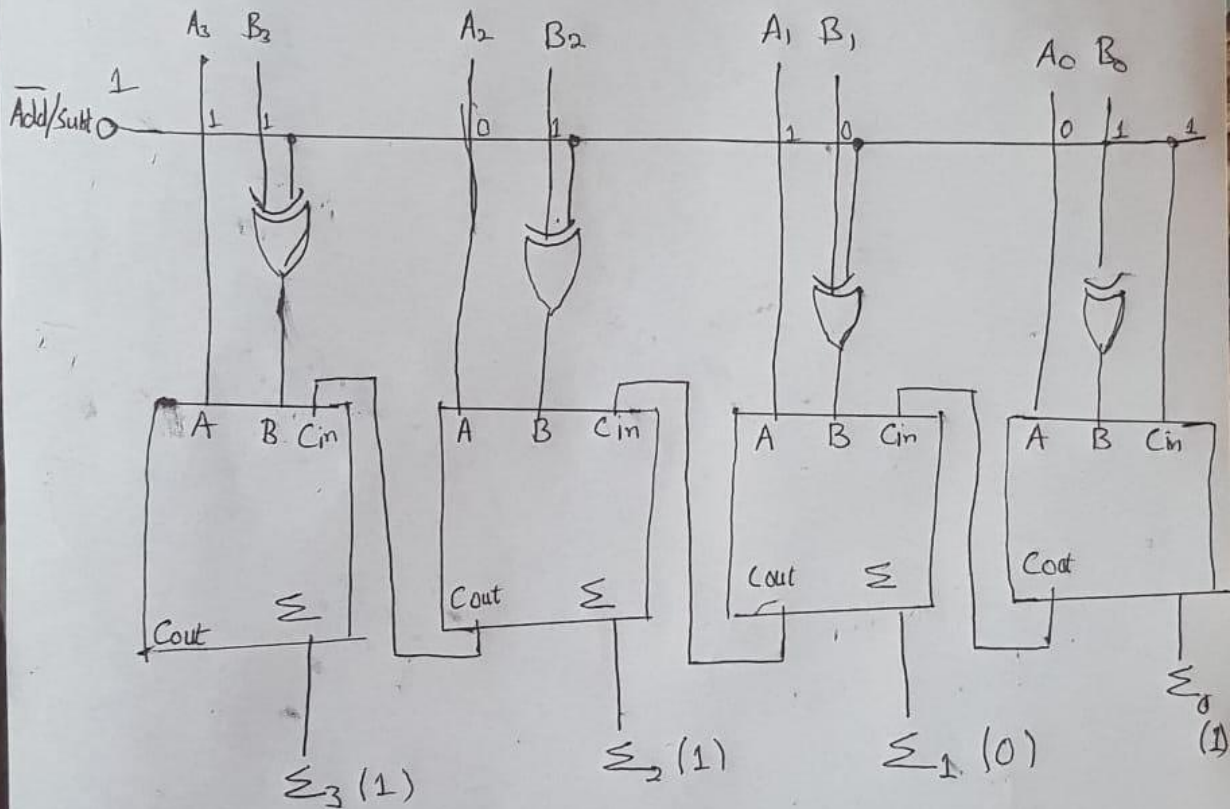


Figure 02

The Output of the

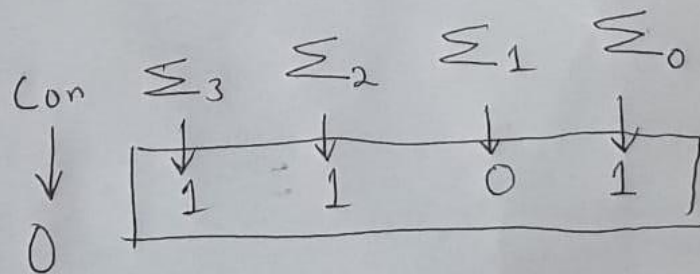

Q4:- Determine the $A=B$, $A>B$, and $A<B$ outputs for the Input numbers shown on the comparator in Figure 03.

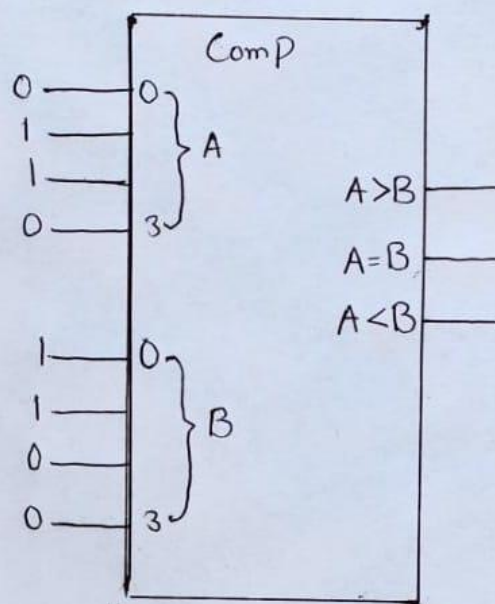


Figure 03

Answer:- The Number on the A Inputs is 0110 and the number on the B inputs is 0011. The $A>B$ output is HIGH and the other outputs are LOW.

Q5:-> show the logic required to convert a 4-bit Gray code to binary and use that logic to convert the following Gray words to binary: 1011.

Answer:-> Solution

convert Gray code to binary code 1011

Method-1: (Gray code to Binary)


$$b_3 = g_3 = 1$$

$$b_2 = b_2 \oplus g_2 = 1 \oplus 0 = 1$$

$$b_1 = b_2 \oplus g_1 = 1 \oplus 1 = 0$$

$$b_0 = b_1 \oplus g_0 = 0 \oplus 1 = 1$$

\therefore Binary : 1101

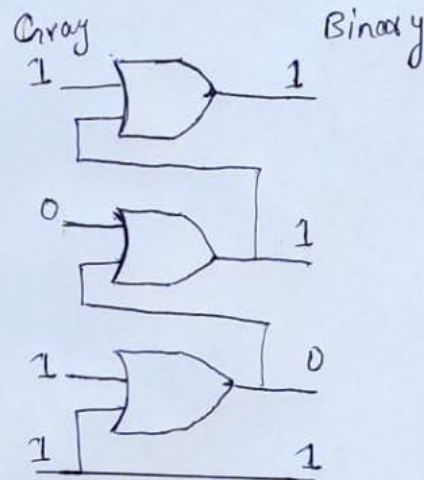

Method 2:-> (Gray code to Binary)

g_3	g_2	g_1	g_0	Gray code
1	0	1	1	
↓	↓	↓	↓	
1	→ 1	→ 0	→ 1	
b_3	b_2	b_1	b_0	


$= g_3 = b_3 \oplus g_2 = b_2 \oplus g_1 = b_1 \oplus g_0$ Binary code.

Binary 1101

Q6. Draw a circuit of 4-bit active low decoder


4-bit Decoder for Active low

Binary Inputs A_0, A_1, A_2, A_3

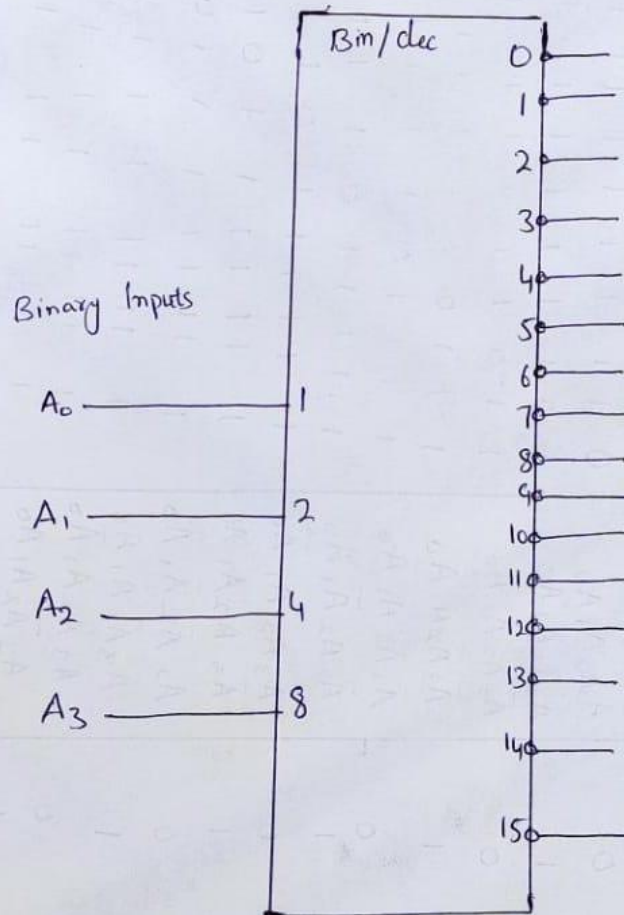


In an active-low output is required for each decoded number the entire decoder can be implemented with NAND gates & inverters.

Q6:- Circuit of 4-bit active low


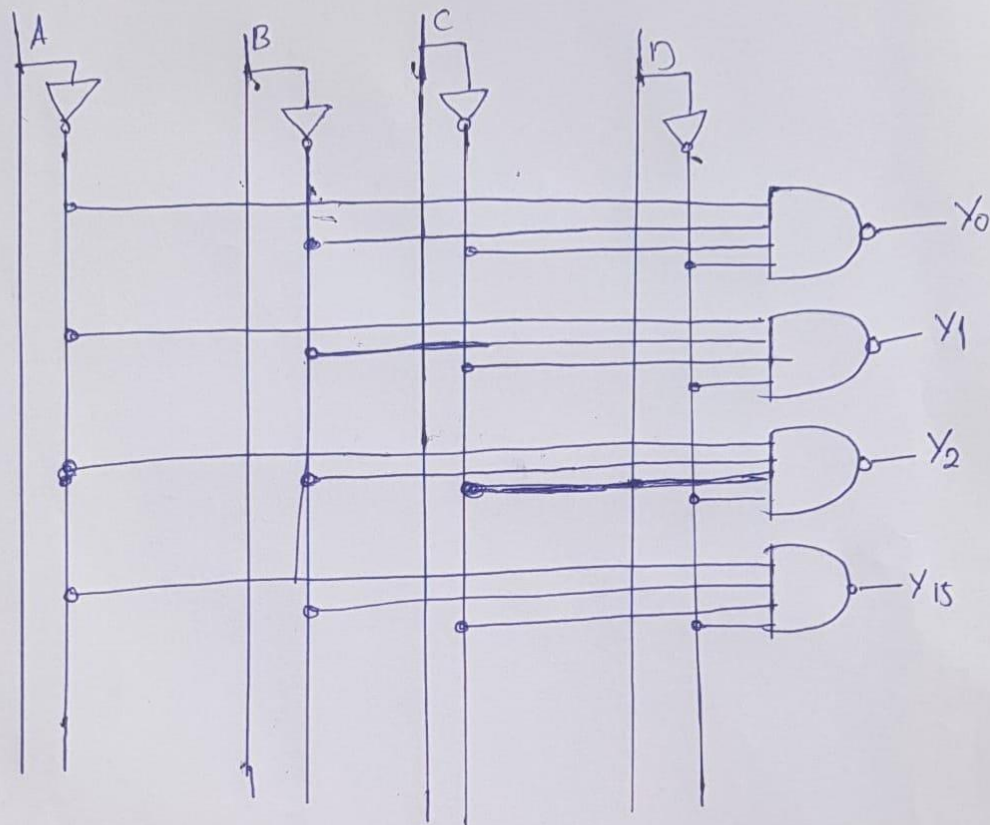


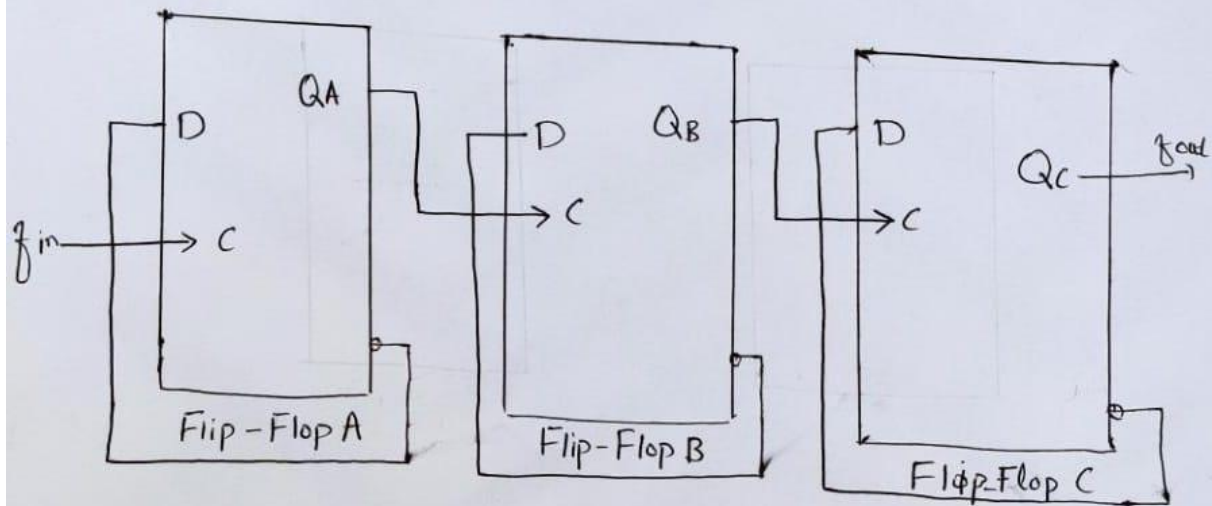Q7. Frequency divider (Use 3-JK flip flop & assume 16 KHZ frequency of the initial wave form)




Q8:- Determine the Q waveform relative to the clock if the signals shown in Figure 04 are applied to the ~~Output~~ inputs of the J-K flip-flop. Assume that Q is initially Low.

Ans:-

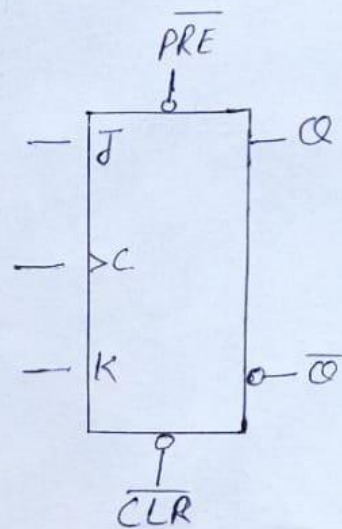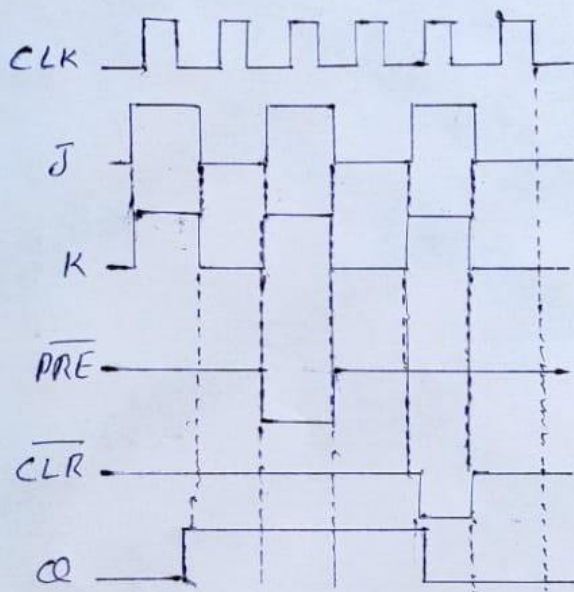


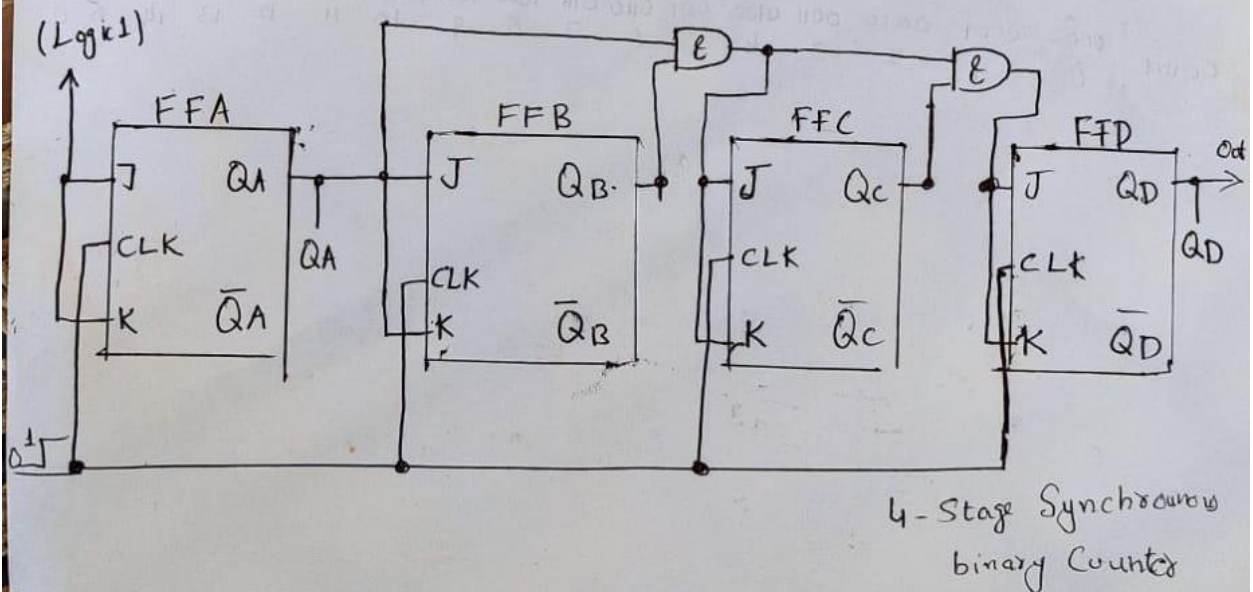Q9:-
 Draw the logic diagram & timing diagram for the 4-stage Synchronous binary Counter. Verify that the waveforms of the Q outputs represent the Proper binary number after each clock pulse.


Ans:- Logic Diagram of 4 Stage Synchronous



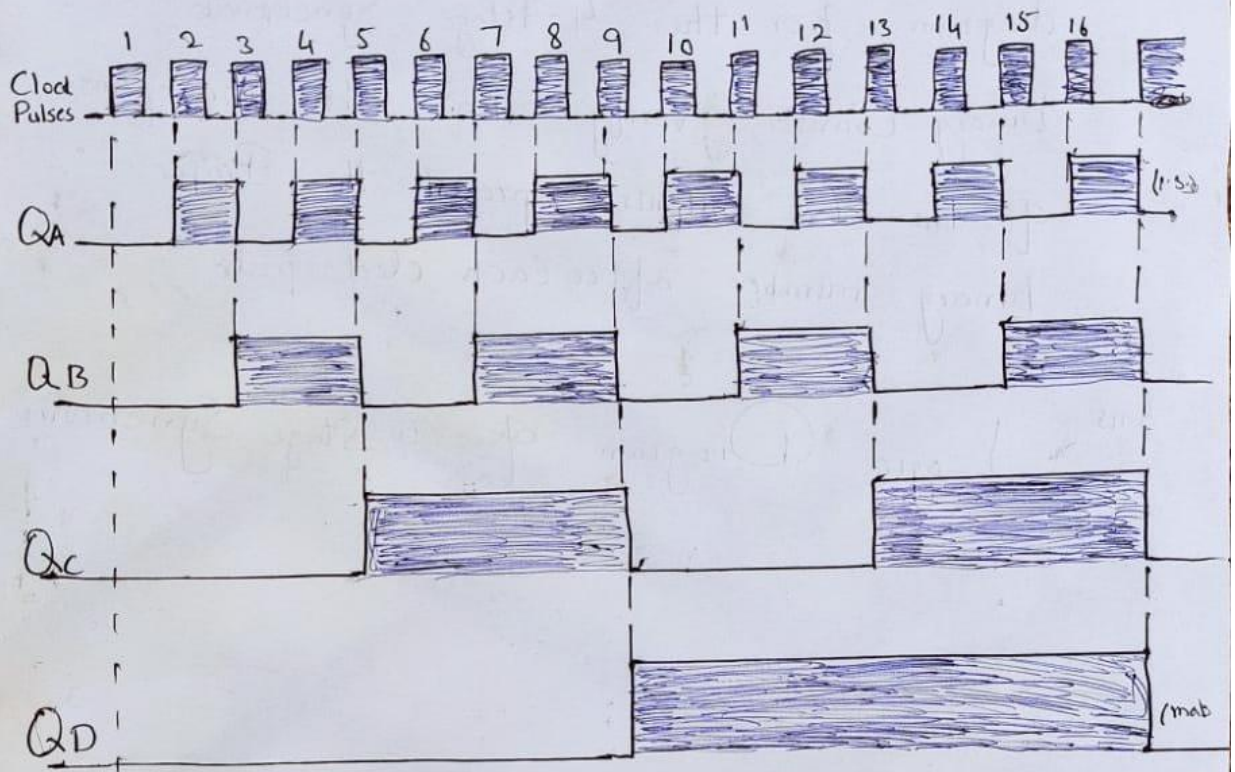4-Stage Synchronous Counter Waveform Timing Diagram



Count	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111	0000
	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	0

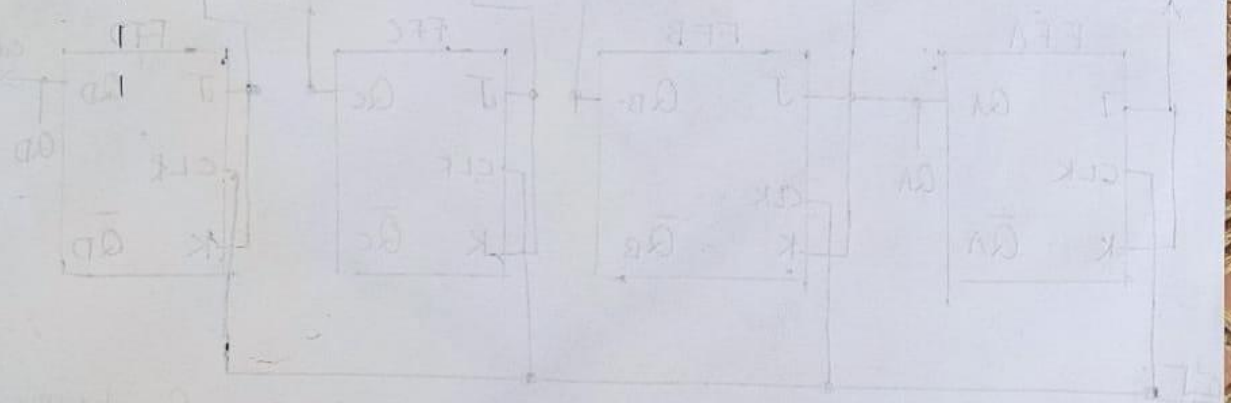

4-Stage Synchronous Counter
 Circuit Diagram