

Department of Electrical Engineering

Midterm Exam

Date: 29/09/2020

Course Details

Course Title: Electronic Devices and Circuits
Instructor: Dr shehryar


Module: 4th semester
Total Marks: 50

Student Details

Name: M.Salman shahid

Student ID: 15006

Student Signature: _____

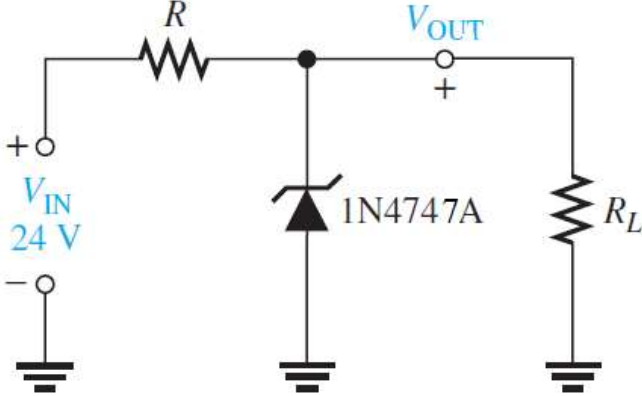Q1.	<p>The 1N4747A zener used in the regulator circuit of Figure 1 is a 15 V diode, determine the following:</p> <p>(a) Determine V_{OUT} at I_{ZK} and at I_{ZM}. (b) Calculate the value of R that should be used. (c) Determine the minimum value of R_L that can be used.</p> <p>The electrical characteristics and values of V_Z, I_Z, I_{ZK}, Z_Z can be found in diode datasheet Fig 3-7 (in course reference book) and online.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 1</p>	<p>Marks 10 CLO 02</p>
Q2.	<p>Determine I_B, I_C, I_E, V_{BE}, V_{CE} and V_{CB} in the circuit shown in Figure 2.</p>	<p>Marks 05 CLO 02</p>

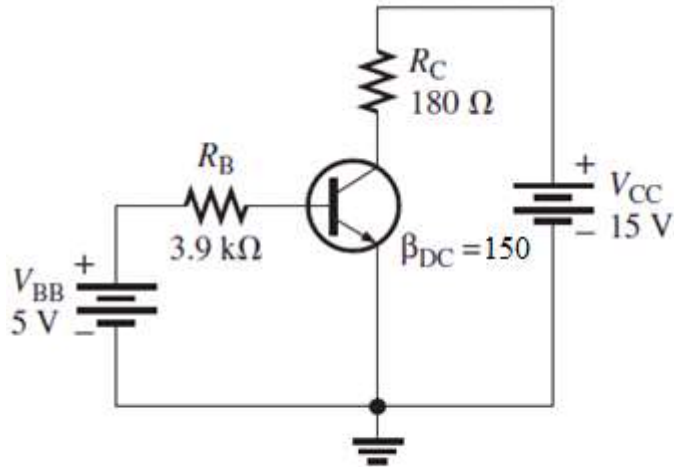


Figure 2

Q3.	<p>Discuss how is BJT used as an amplifier with the help of schematic diagram for a basic BJT amplifier? Which basic configurations are required for it? Consider input AC and DC values as $5\mu\text{A}$ and $15\mu\text{A}$ respectively, assume $\beta = 200$.</p>	<p>Marks 10 CLO 03</p>
Q4.	<p>For a transistor to act as a “switch”, you need to join each of the following conditions on the left to “ON” or “OFF” state.</p> <p>Transistor fully ON Transistor fully OFF Input and base are at 0V Collector current $I_c = 0$ $V_{CE} = V_{CC}$ BE junction is reverse bias BC junction is forward bias Maximum of saturation current I_c flows</p> <p style="text-align: right; font-size: 2em;">OFF</p> <p>BE junction is forward bias BC junction is forward bas $V_{CE} = 0\text{V}$ BE junction is less than 0.7V</p> <p style="text-align: right; font-size: 2em;">ON</p>	<p>Marks 05 CLO 02</p>
Q5.	<p>Discuss that how JFET (n-channel) can be used as voltage control device when the value of $V_{GS} < 0\text{V}$ and $V_{DS} > 0\text{V}$. Draw schematics with polarity conventions and explain the operation in detail.</p>	<p>Marks 10 CLO 03</p>
Q6.	<p>For the transistor circuit given in Fig. 3, calculate the following:</p> <ol style="list-style-type: none"> What is V_{CE} when $V_{IN} = 0\text{V}$? Determine the minimum value of I_B is required to saturate this transistor if β_{DC} is 125 and $V_{CE(\text{sat})}$ is 0.4V. 	<p>Marks 10 CLO 03</p>


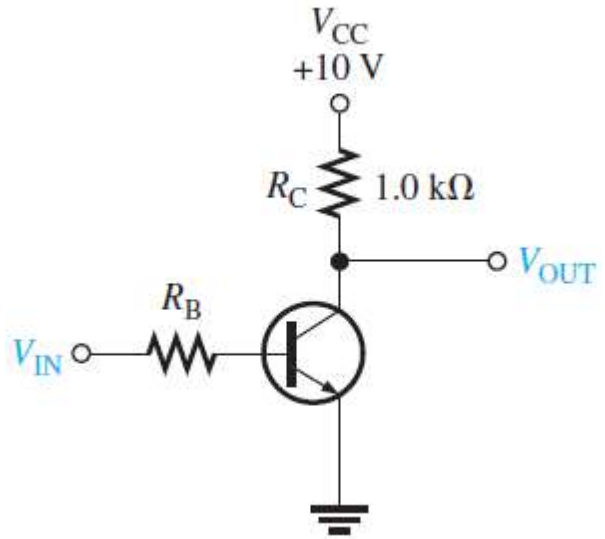


Figure 3

Q 1.	The 1N4747A zener used in the regulator circuit of Figure 1 is a 15 V diode, determine the following:	Marks 10 CLO 02
	(a) Determine V_{OUT} at I_{ZK} and at I_{ZM} . (b) Calculate the value of R that should be used. (c) Determine the minimum value of R_L that can be used.	
	The electrical characteristics and values of V_Z , I_Z , I_{ZK} , Z_Z can be found in diode datasheet Fig 3-7 (in course reference book) and online.	
	Figure 1	

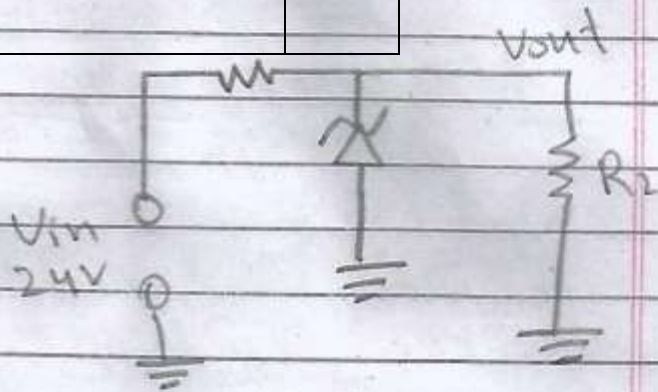

a) for I_{ZK}

$$V_{OUT} = V_Z - \Delta I_Z Z_Z$$

$$= 20 - (12.25 \text{ mA}) (220\Omega)$$

$$= 19.7305 \text{ V.}$$

Now for Zener max current
Power dissipation 1W

$$I_{ZM} = \frac{P_{O(max)}}{V_Z} = \frac{1}{20} = 0.05$$

$$I_{ZM} = 50 \text{ mA}$$

for I_{ZM} :-

$$V_{out} = V_Z + \Delta I_Z Z_Z$$

$$= 20V + (I_Z - I_Z) Z_Z$$

$$= 20V + (0.0542)(20)$$

$$= 21.1924V$$


b) Calculating value of R for Max zener current that occurs when there is no load.

$$R = \frac{V_{in} - V_{out}}{I_{ZM}}$$

$$= \frac{24V - 21.1924V}{50mA} = \underline{2.8076}$$

$$= 56.152 \Omega$$

$$R = 56 \Omega$$

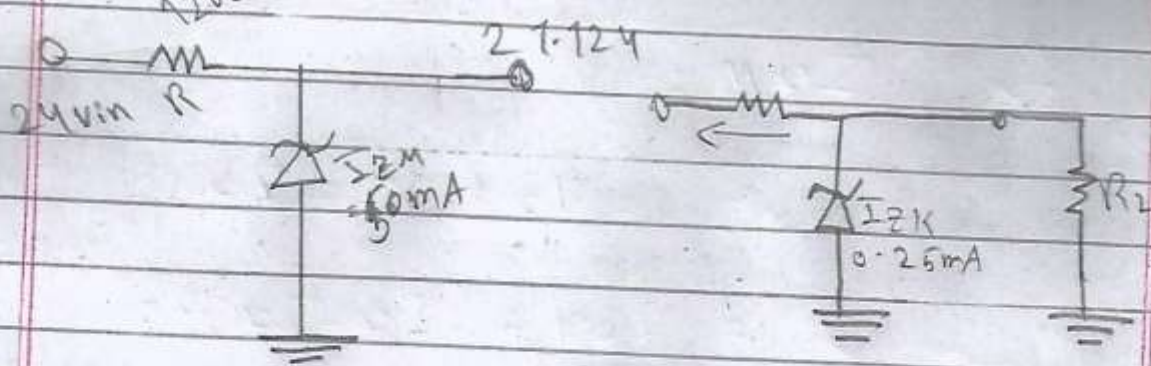

c) For the minimum load resistance (max load current) the Zener current is $I_{ZK} = 0.25\text{mA}$

$$I_T = \frac{V_{in} - V_{out}}{R} = \frac{24 - 19.07306}{60\Omega}$$

$$= 0.0749167$$

$$= 74.9166\text{ mA}$$

$$I_L = I_T - I_{ZK}$$

$$= 74.9166 - 0.25$$

$$= 74.666\text{ mA}$$

$$R_L (\text{min}) = \frac{V_{out}}{I_L} = \frac{19.7306}{74.666\text{ mA}}$$

$$= \text{~~264.0\Omega~~}$$


$$= 264\Omega$$

Q2.

Determine I_B , I_C , I_E , V_{BE} , V_{CE} and V_{CB} in the circuit shown in Figure 2.

Marks 05

CLO 02

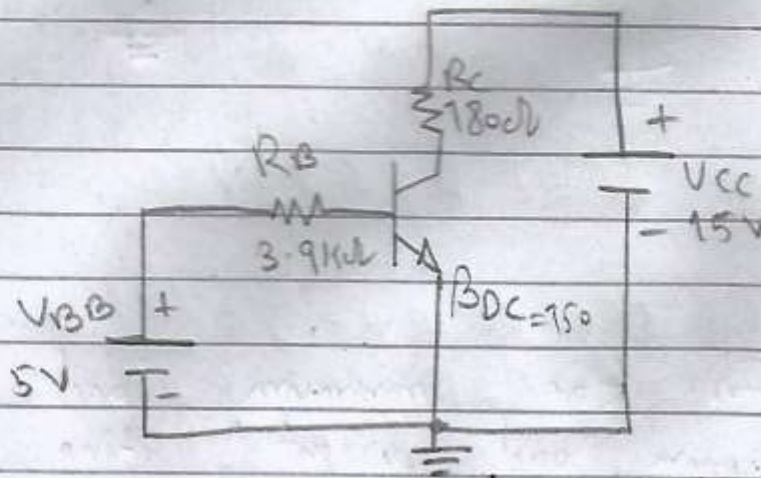

Soln As we know from
Base to emitter voltage drop
is equal to $V_{BE} = 0.7V$

So Base current

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7}{3.9k\Omega}$$

$$= 0.0011025A$$

$$= 1102.564\mu A$$

$$I_C = \beta_{DC} I_B = (150)(1102.564\mu A)$$

$$= 165384$$

$$= 165.384mA$$

$$I_E = I_C + I_B$$

$$= 165.384mA + 1102.564\mu A$$

$$= 1267.948mA$$

Now for V_{CE} & V_{CB}

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 15 - (165.384 \text{ mA})(180 \Omega)$$

$$= 15 - (0.0655)(180)$$

$$= 15 - (11.79)$$

$$V_{CE} = 3.21$$

$$V_{CB} = V_{CE} - V_{BE}$$

$$3.21 - 0.7 = 11.79$$

Q3.

Discuss how is BJT used as an amplifier with the help of schematic diagram for a basic BJT amplifier? Which basic configurations are required for it? Consider input AC and DC values as $5\mu\text{A}$ and $15\mu\text{A}$ respectively, assume $\beta = 200$.


Marks 10

CLO 03

Ans:-
 For using BJT as an amplifier we need to set them in Active region because BJT working as an amplifier when use is active region.

Transistor has three Basic configuration for using it in Amplification mode.

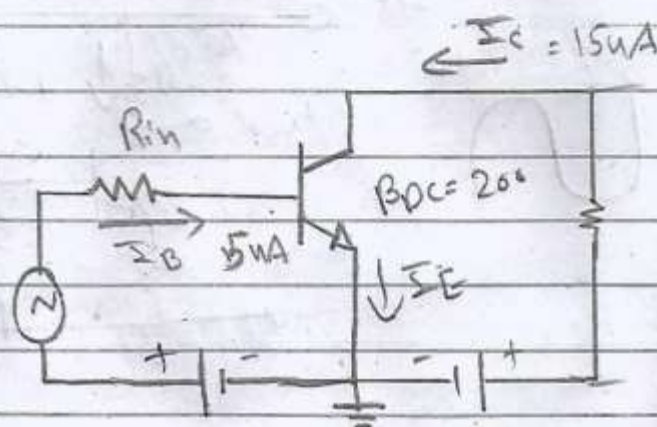Common Base : - Voltage Gain no Current
 Common Emitter Both gain
 Common Collector Current gain no voltage



So this is common emitter configuration of transistor for which has both voltage & current amplification.

$$I_C = \beta \cdot I_B$$

$$= 200 + 5\mu A$$

$$I_C = 200.00005\mu A$$

$$I_E = I_C + I_B$$

$$I_E = 200.00005\mu A + 15\mu A$$

$$I_E = 200.00002$$

Q4.

For a transistor to act as a "switch", you need to join each of the following conditions on the left to "ON" or "OFF" state.

Marks 05

CLO 02

Q4-

(Transistor fully on)

: BE junction is ~~reverse~~ forward Biased

: Max Saturation Current I_c flows

(Transistor fully off)

: Input V_{in} Base are at 0V

: Collector Current $I_c = 0$

: $V_{CE} = V_{CC}$

: BE junction is reverse Biased

: BC junction is forward Biased.

: $V_{CE} = 0V$

: BE junction is less than 0V


Q5.

Discuss that how JFET (n-channel) can be used as voltage control device when the value of $V_{GS} < 0V$ and $V_{DS} > 0V$. Draw schematics with polarity conventions and explain the operation in detail.


Marks 10
CLO 03

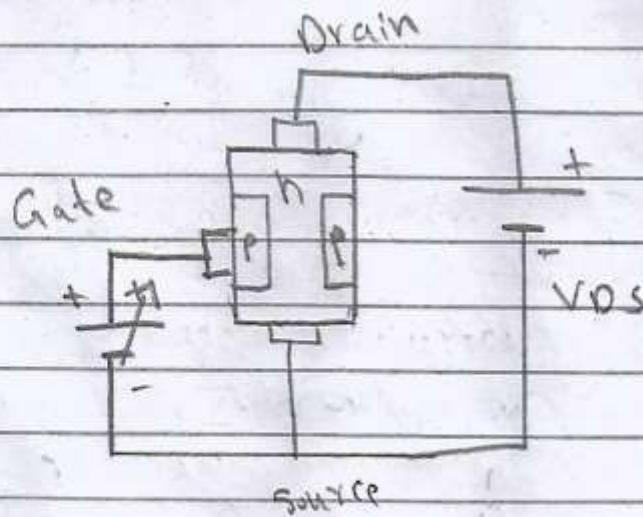Q5:-


Ans:- JFET is a type of junction field effect transistor which is voltage controlled device as differ from BJT which is current controlled.



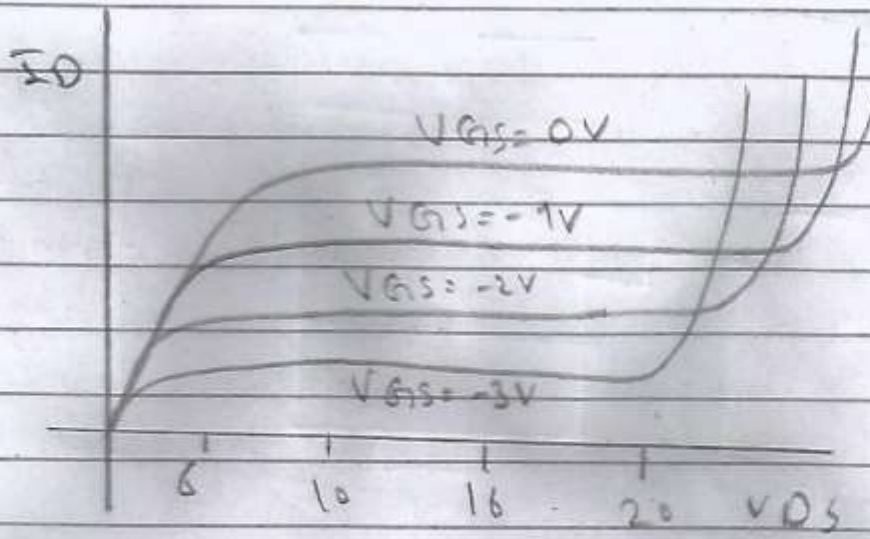Actually in FET the drain to source current is controlled by the width of the channel. The electric field is produced by the gate to source voltage.




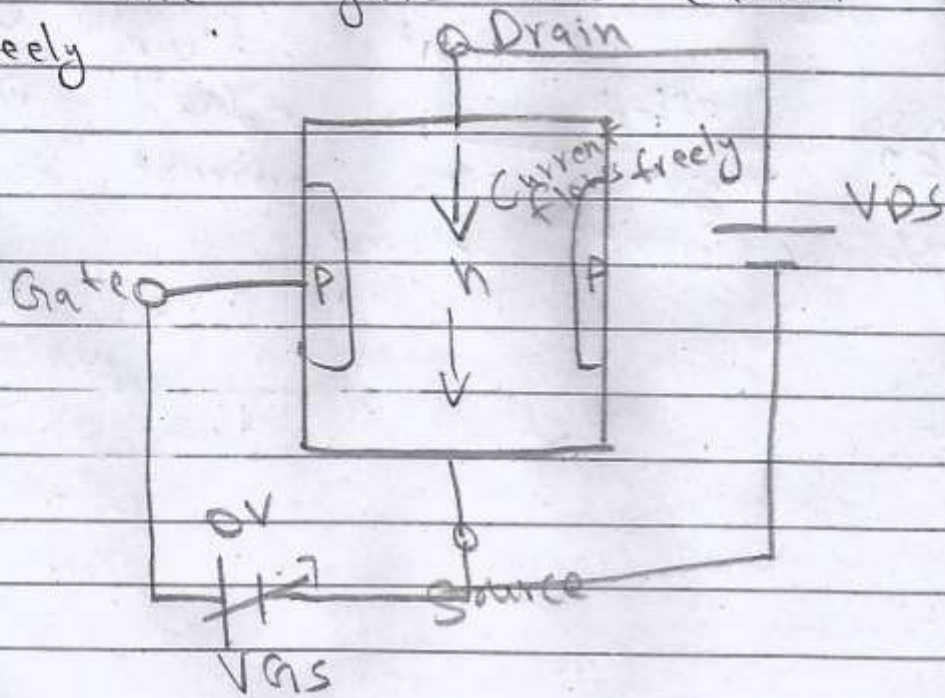So if we see to the graph which the no voltage applied to the gate the current flows freely.



the channel are wider and Drain current moves freely

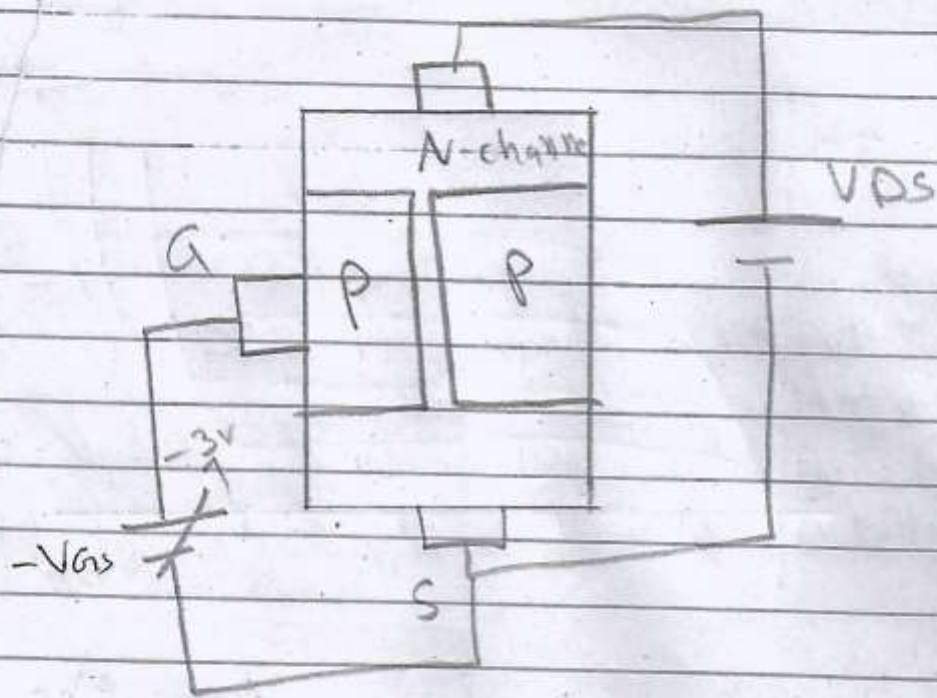if we move V_{GS} to negative value the channel width start to decrease and current cannot move.



so V_{GS} is more negative
 so no current flows and
 this effect is called pinch
 off
 less current flows.

Q6.	For the transistor circuit given in Fig. 3, calculate the following: a) What is V_{CE} when $V_{IN} = 0V$? b) Determine the minimum value of I_B is required to saturate this transistor if β_{DC} is 125 and $V_{CE(sat)}$ is $0.4V$.	Marks 10 CLO 03
-----	--	-----------------------

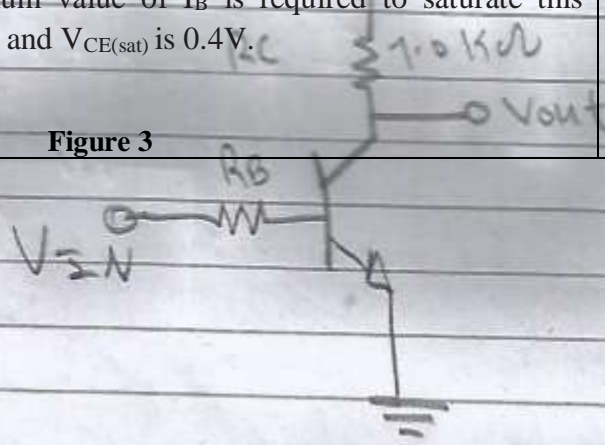


Figure 3

Sol - a) When $V_{IN} = 0V$ the transistor is in cutt off so act like open switch
 $V_{CE} = V_{CC} = 10V$

b) Minimum value of I_B to saturate the transistor.

$$I_B(\text{min}) = \frac{I_C(\text{sat})}{\beta_{DC}}$$

So required I_C
 $V_{CC} = 10V$ $R_C = 1.0k\Omega$

$$I_C(\text{sat}) = \frac{V_{CC}}{R_C} = 0.01$$

$$\begin{aligned}
 \text{So } I_B(\text{min}) &= \frac{I_C(\text{sat})}{\beta_{DC}} \\
 &= \frac{0.01}{125} = 0.00008 \\
 &= 0.08 \text{ mA}
 \end{aligned}$$