

NAME = ABDUL - Haseeb



ID = 6988


Subject = Power - System Analysis

Submitted to = Engr - muhammad - Amir - Aman

Assignment No = 1

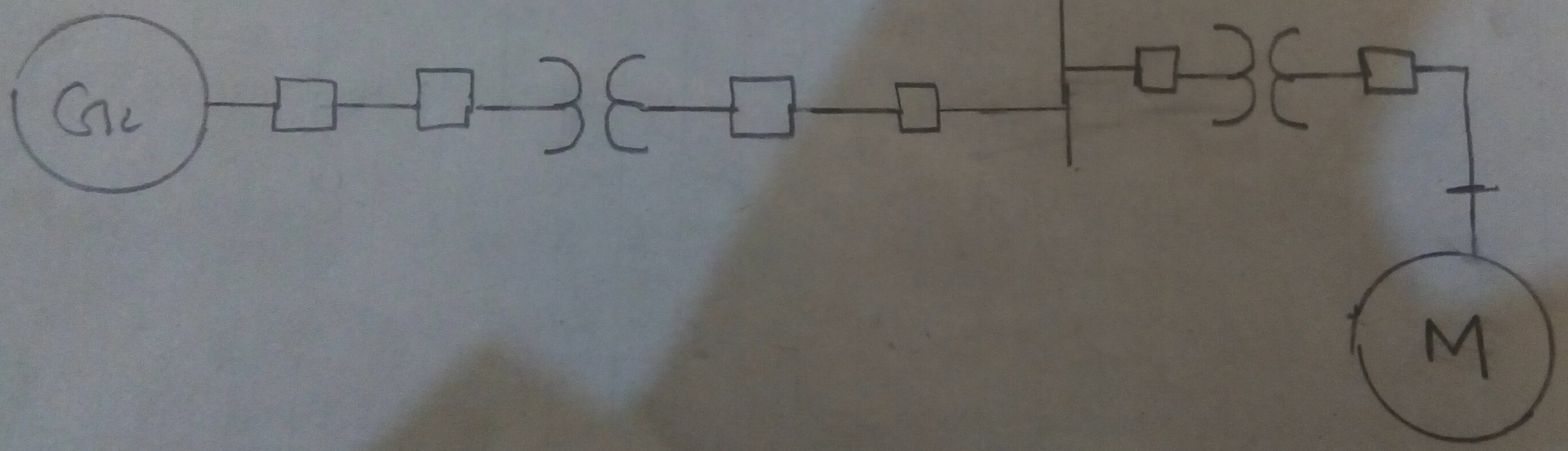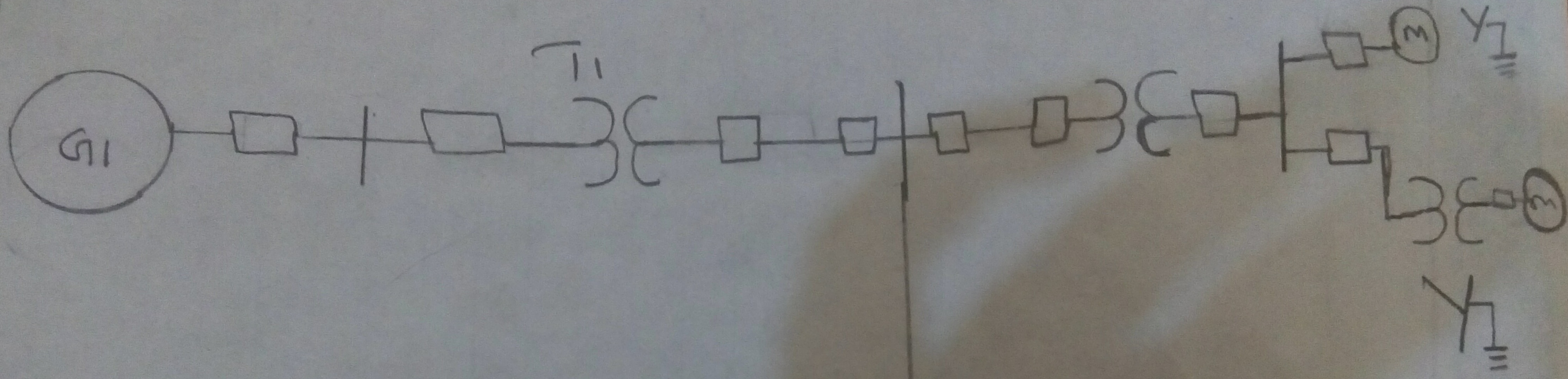
Q = 1 Single line Diagram = Convert into Redance & Impedance



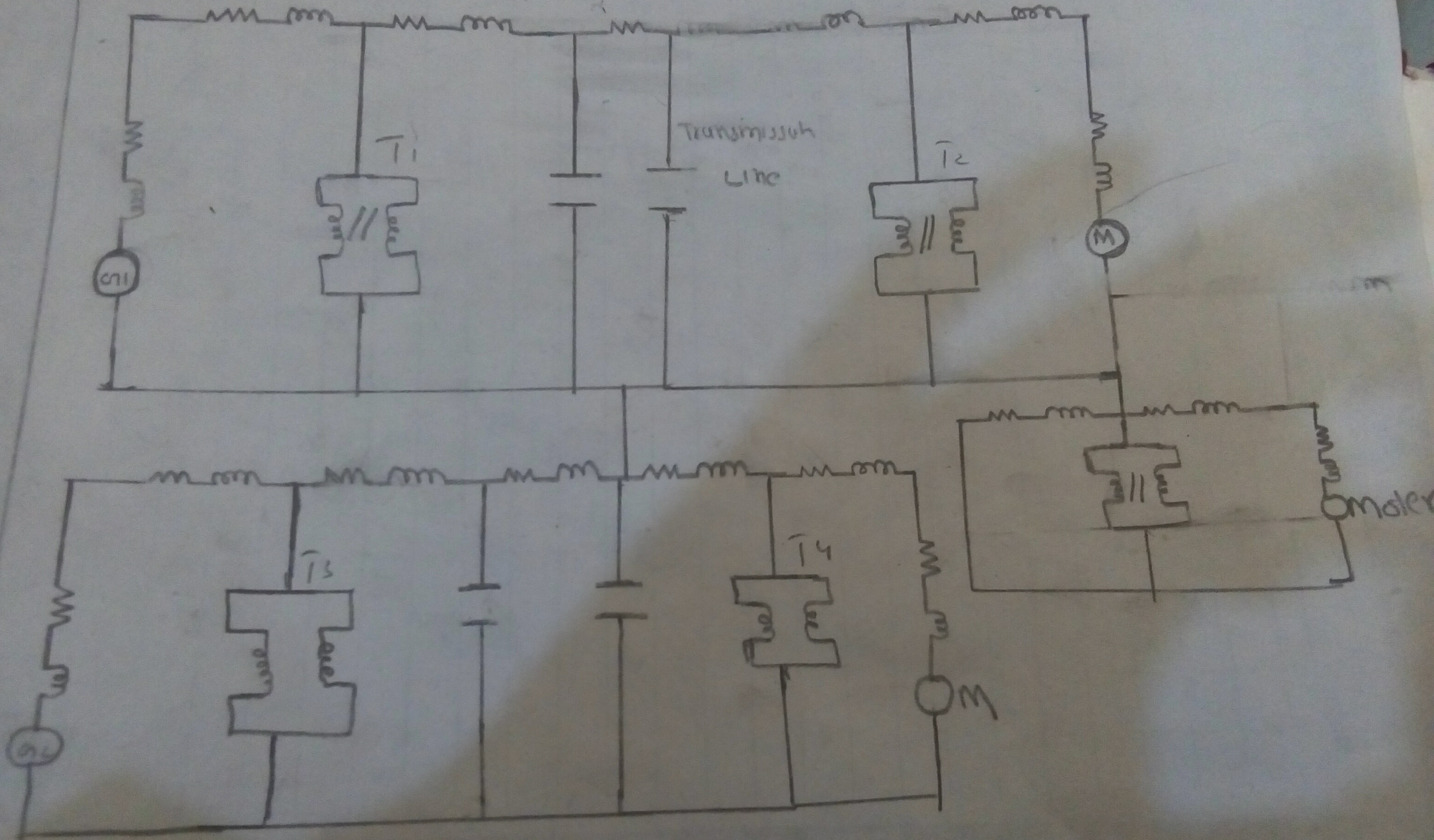

Page = 3

ID 6988

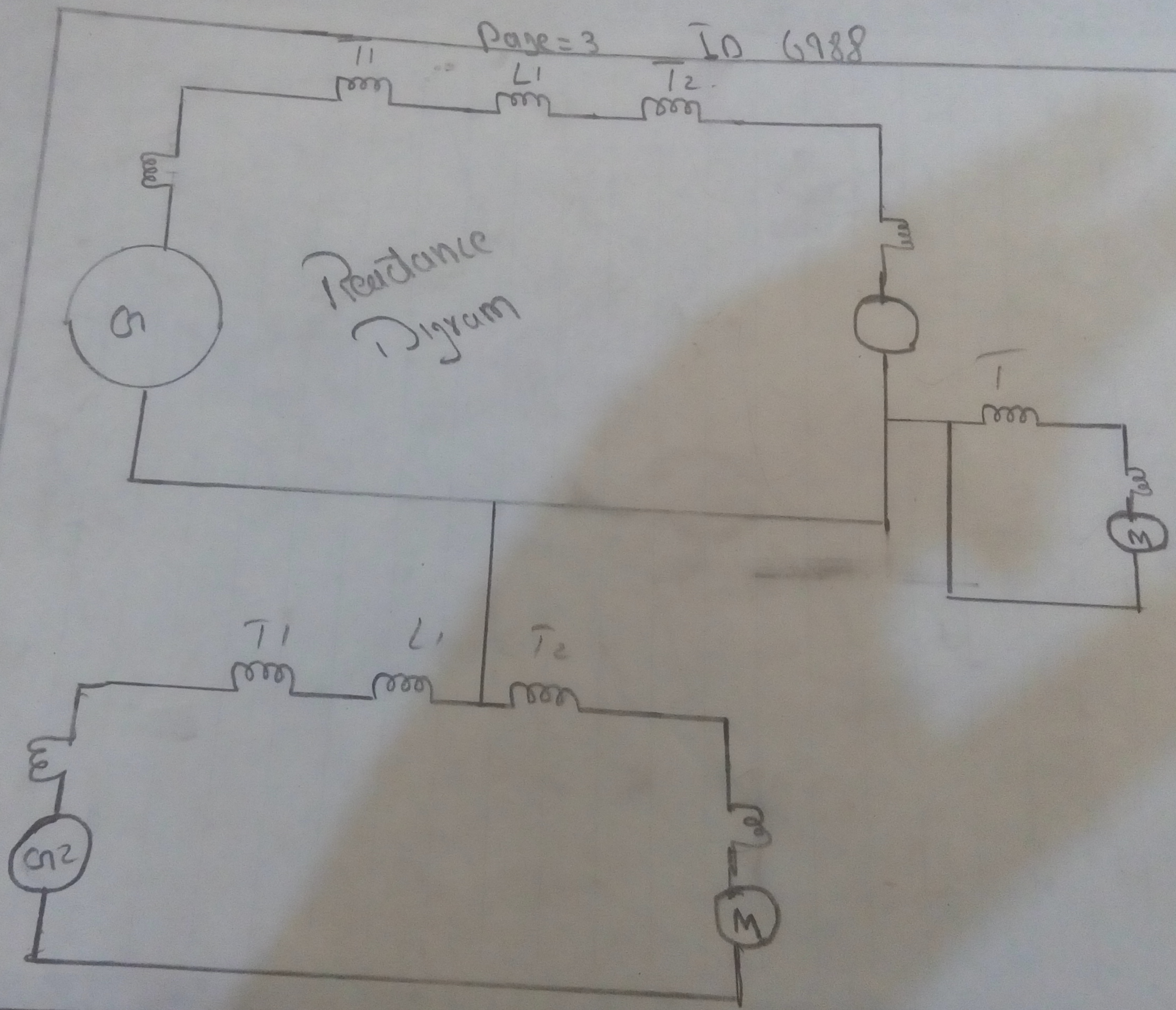

Q

Question Number = 2

A transformer is rated 20kV/220kV 300 MVA and has internal impedance of 6.4Ω seen from the low voltage side 22kV, 400 MVA. a) base show V_{pu} , S_{pu} and Z_{pu} .

$$\begin{aligned} \rightarrow V_{pu} &= Z_p \times I_{pu} \\ &= 6.4 \times 350 = 2.240 \end{aligned}$$

$$Z_{pu} = \frac{V \times I}{S}$$

$$\frac{2.24 \times 350}{7700}$$


$$S = 7700$$

$$Z_{base}^{pu} = \frac{V_{base}^2}{S_{base}}$$

$$\frac{(22)^2}{7700}$$

$$\frac{484}{7700}$$

$$0.0628$$

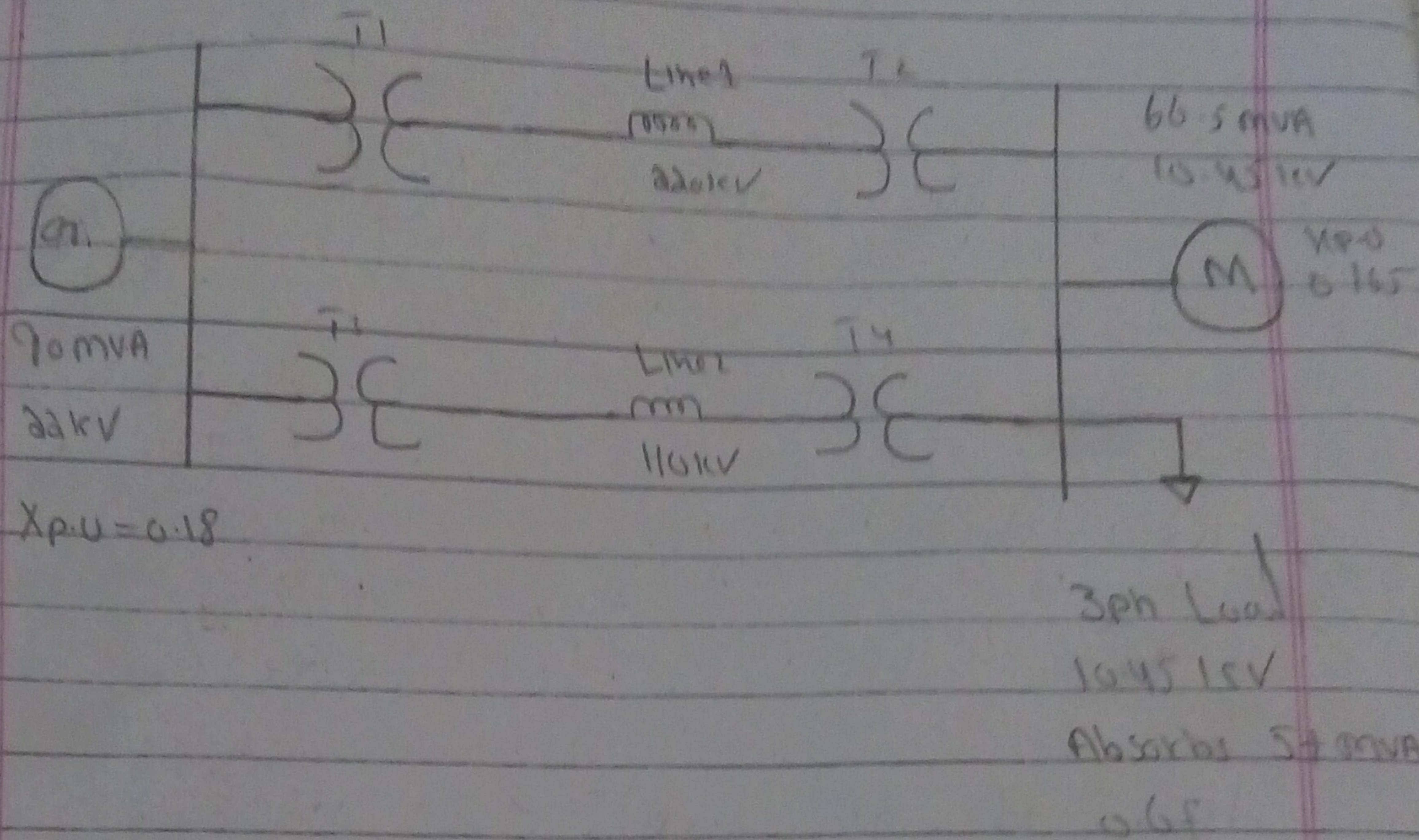

$T_1 = 50 \text{ MVA}, 22/220 \text{ kV}, X_{p.u} = 0.18$

$T_2 = 40 \text{ MVA}, 22/110 \text{ kV}, X_{p.u} = 0.06$

$T_3 = 40 \text{ MVA}, 22/110 \text{ kV}, X_{p.u} = 0.064$


$T_4 = 40 \text{ MVA}, 110/110 \text{ kV}, X_{p.u} = 0.008$

Line 1 48.4 ohm (total)

Line 2 65.43 ohm (total)

\Rightarrow The equivalent impedance Diagram of the above system.

Impedance Diagram

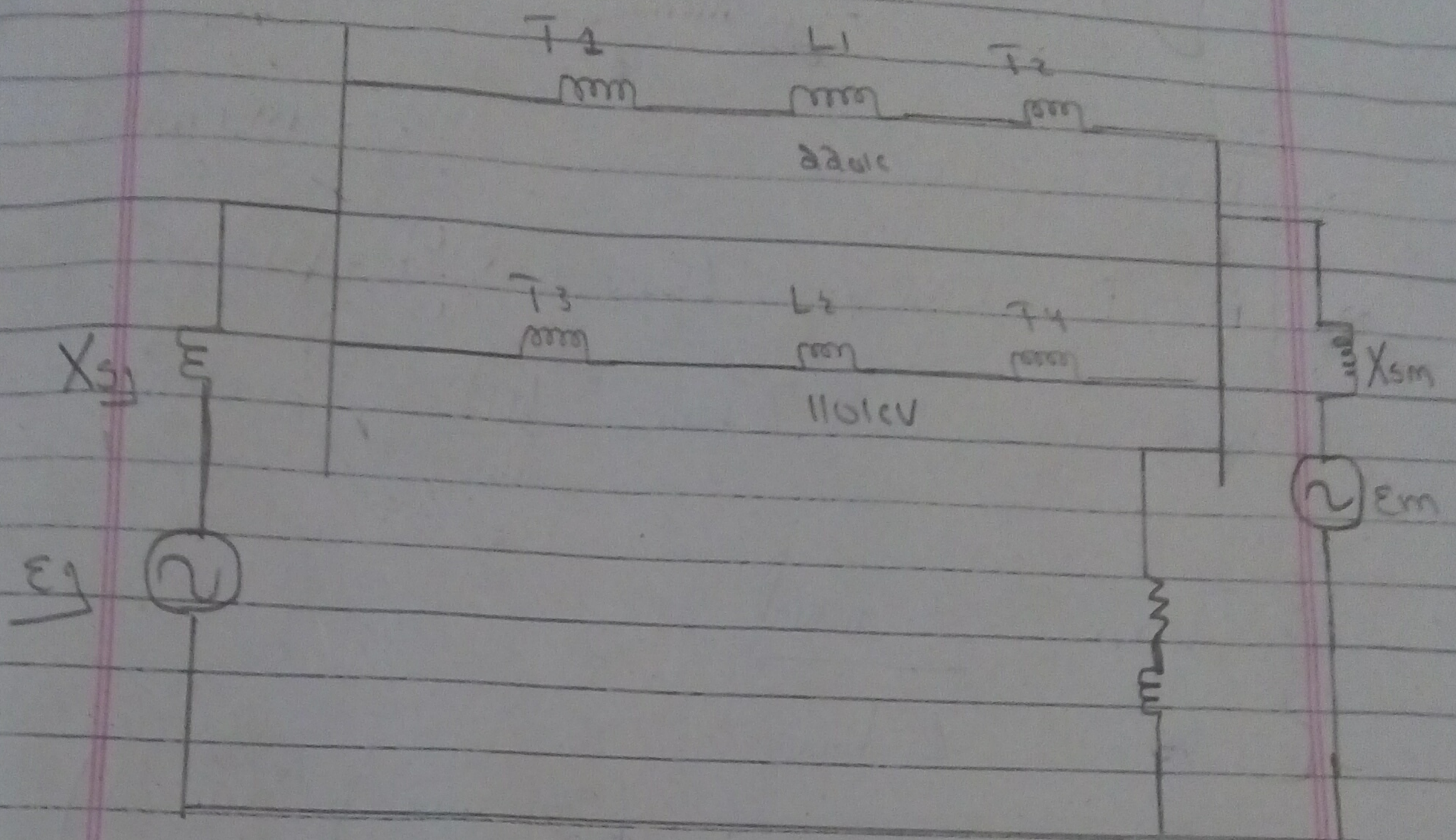

Assume a system base of 100

100 MVA. This is random assumption

and chosen to make a calculation

easy when per unit impedance,

So, $S_{base} = 100 \text{ MVA}$

=> Calculation

$$Z_{base} = \frac{kV_{base}^2}{Z_{base} \text{ MVA}}$$

=> For T-Line 1 $Z_{base} = \frac{(220)^2}{100} = 484 \text{ ohm}$

=> For T-Line 2 $Z_{base} = \frac{(110)^2}{100} = 121 \text{ ohm}$

For 3-phase Load $Z_{base} = \frac{(11)^2}{100} = 1.21 \text{ ohm}$

=> $Z_{p.u.} = \frac{Z_{actual}}{Z_{base}}$

$$Z_{p.u. \text{ new}} = Z_{p.u. \text{ old}} \left(\frac{S_{base \text{ new}}}{S_{base \text{ old}}} \right) \left(\frac{V_{base \text{ old}}}{V_{base \text{ new}}} \right)^2$$

~~The voltage ratio in equation~~

The ratio of the transformer voltage rating on the primary side and secondary side to the system nominal voltage on the same side

$$\text{For T-Line 1 wing } X_{L1} \text{ pu} = \frac{48.4}{484} = 0.1 \text{ pu}$$

0.1 pu

$$\text{For T-Line 2, wing (a) } X_{L2} \text{ pu} = \frac{65.43}{131}$$

0.5 pu

for 3-phase load.

$$\text{Power factor } \cos^{-1}(0.6) = 53.13$$

$$\text{Thus } S_{3\phi} (\text{Load}) = 57 \angle 53.13$$

~~$$Z_{ad} = \frac{(V_{rated})^2}{S^*}$$~~

$$Z_{ad} = \frac{(V_{rated})^2}{S^*} = \frac{10.45^2}{57 \angle -53.13}$$

$$\Rightarrow 1.1495 + j1.53267 \text{ ohm}$$

$$1.1495 + j1.5326$$

1.21

$$0.95 + j1.2667 \text{ pu}$$

Page = 9 = ID = 6988

For generator the new per unit

reactance expression

$$X_{sg} = 0.18 \left(\frac{100}{90} \right) \left(\frac{22}{22} \right)^2$$

$$= 0.2 \text{ p.u.}$$

For Transformer T_1 : $X_{t1} = 0.1 \left(\frac{100}{50} \right) \left(\frac{22}{22} \right)^2 = 0.2 \text{ p.u.}$

// // T_2 : $X_{t2} = 0.06 \left(\frac{100}{40} \right) \left(\frac{220}{220} \right)^2 =$

$$0.15 \text{ p.u.}$$

~~// // T_3~~

// // T_3 : $X_{t3} = 0.064 \left(\frac{100}{40} \right) \left(\frac{220}{220} \right)^2 =$

$$0.16 \text{ p.u.}$$


// // T_4 : $X_{t4} = 0.08 \left(\frac{100}{40} \right) \left(\frac{110}{110} \right)^2 =$


$$0.2 \text{ p.u.}$$

For motor. $X_{sm} = 0.185 \left(\frac{100}{66.5} \right) \left(\frac{10.45}{11} \right)^2$

$$= 0.25 \text{ p.u.}$$

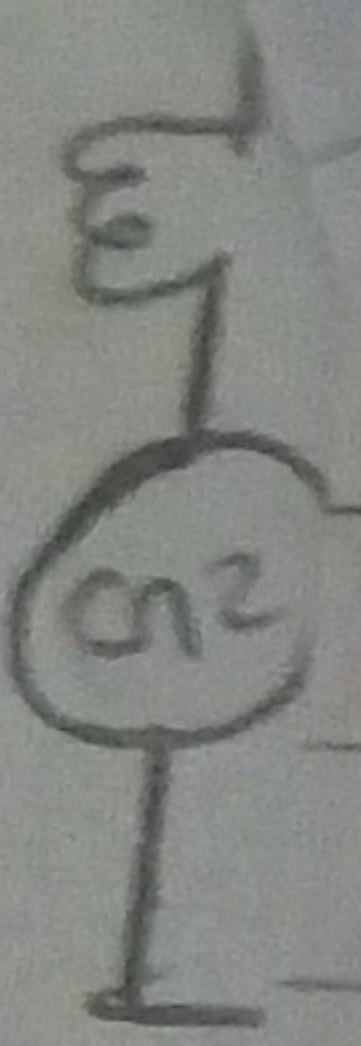Page = 4
Question n.
300 mva
of G.
Voltage
base



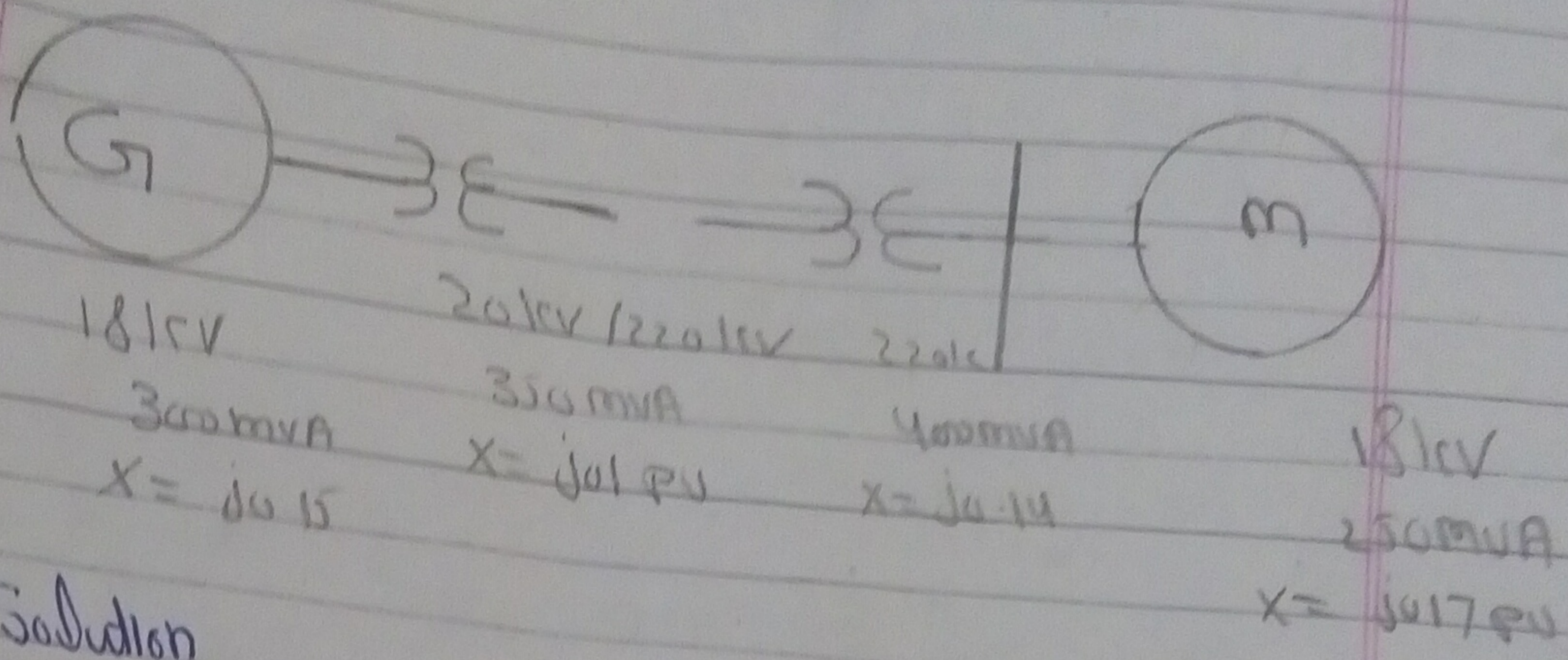

Solution =

$$I_0 = \frac{\text{Per fault } 17.81 \text{ kV}}{12.66} = 0.140$$

All resistance are given in base 20 mva and apparent voltage

Load = 200 mva, 0.80 power factor leading.

$$\frac{200}{10} = 10 \text{ p.u.}$$

=> Per fault current




$$I_0 = \frac{10}{0.140 \times 0.80}$$

~~10~~

$$\Rightarrow \frac{10}{0.112}$$

89.2857

Per-fault equivalent ckt

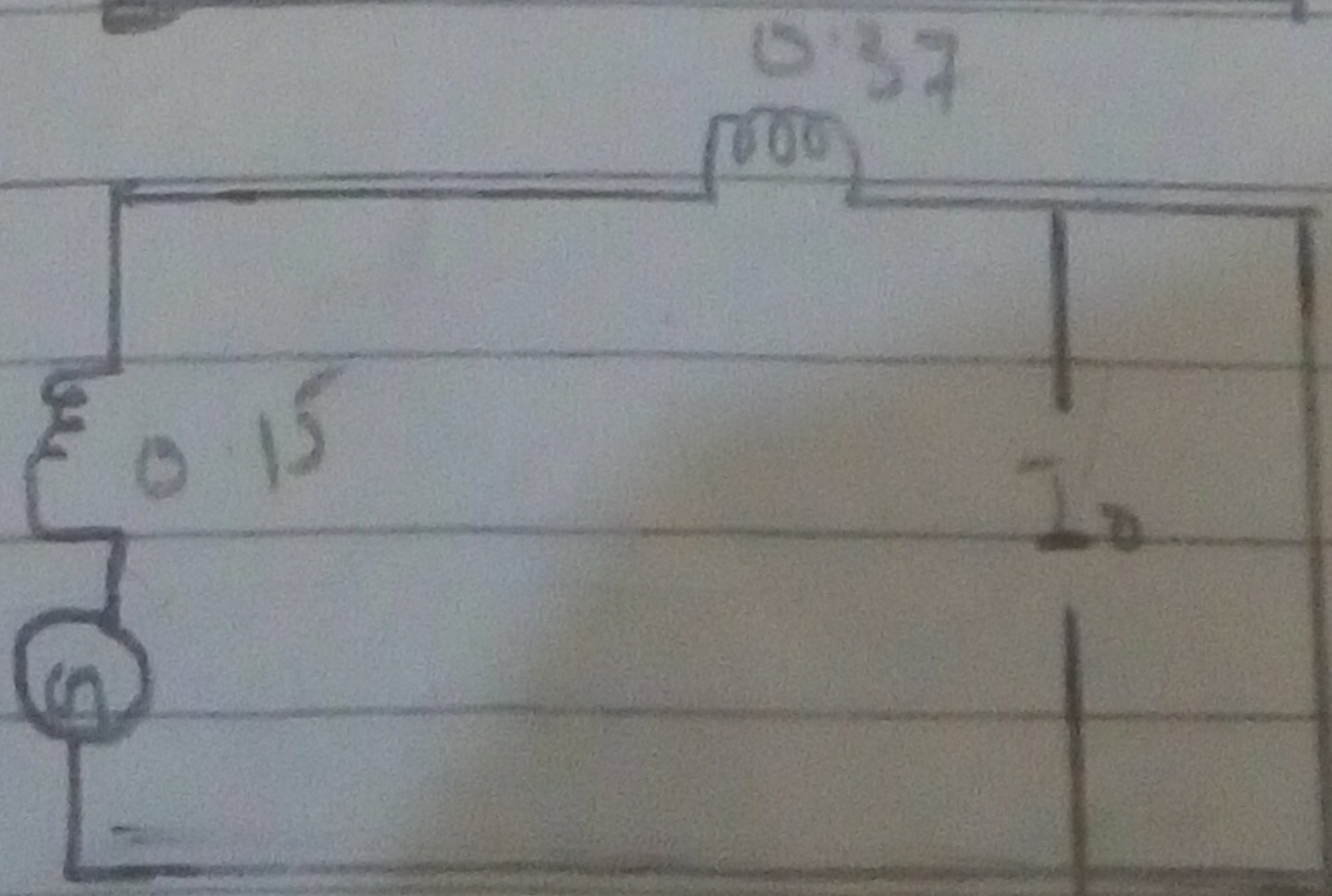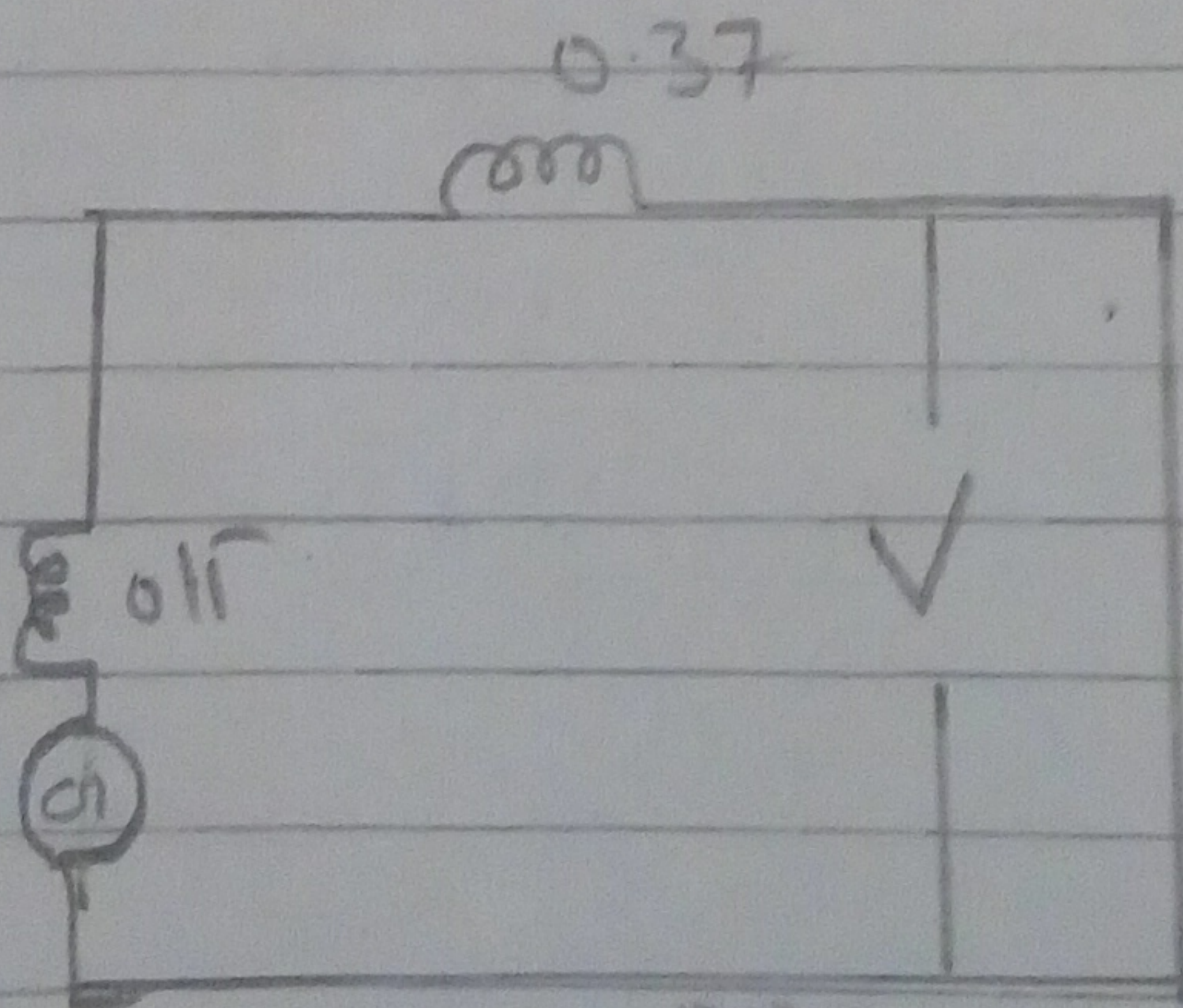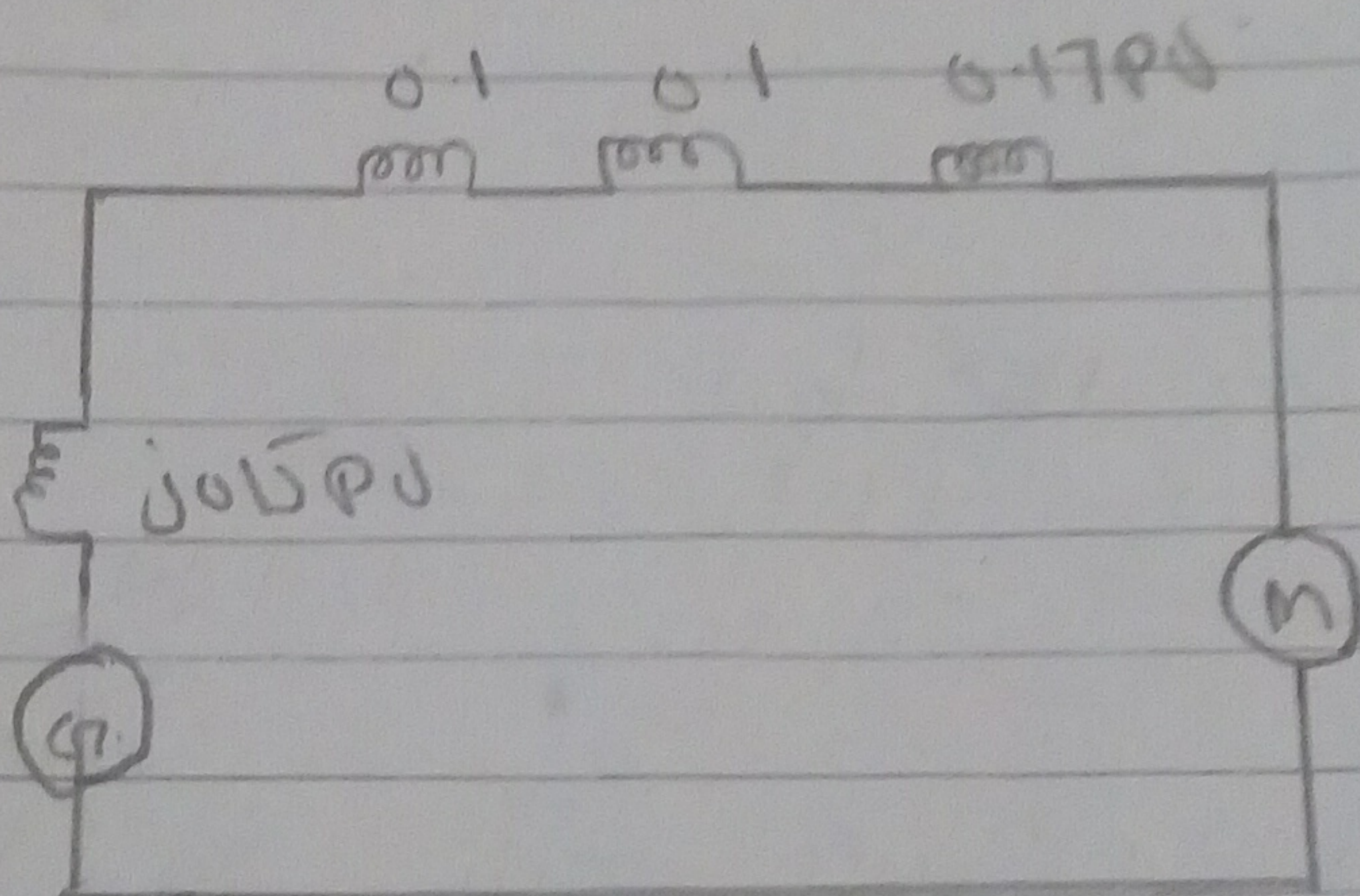

Q Question No = "6"

Ans =

overcurrent protective devices must operate to isolate short circuit fault safely minimize damage to circuit element and avoid if possible, shut down of plant. An accurate knowledge prospective fault current through out the system is essential for the correct application of protective devices and the design busbar and terminal arrangement to withstand consequential mechanical and thermal stresses.

