



Industrial Electronics
Assignment

Question No 1. Multiple choice Questions

1. Does the severity of an electric shock increase or decrease with each of the following changes?
 - a. A decrease in the source voltage
 - b. An increase in body current flow
 - c. An increase in body resistance
 - d. A decrease in the length of time of exposure

2. State the piece of electrical safety equipment that should be used to perform each of the following tasks:
 - a. A switching operation where there is a risk of injury to the eyes or face from an electric arc
 - b. Using a multimeter to verify the line voltage on a 3-phase 480 volt system
 - c. Opening a manually operated high-voltage disconnect switch.

3. In which industrial revolution the use of IT and Electronic systems further automated the production of industrial sector
 - a. First
 - b. Second
 - c. Third
 - d. Fourth

4. Industrial safety is primarily a management activity which is concerned with _____, Controlling, Eliminating hazards from the industries.
 - a. Reducing
 - b. Increasing
 - c. Suppressing

5. The _____ is defined as the device which convert the one form of energy into another form of the energy.
 - a. Sensor
 - b. Transducer
 - c. Resistor
 - d. Capacitor



Industrial Electronics
Assignment

Question No 2


10

- A. Draw digital logic circuit and ladder diagram that is equivalent to the following Boolean Function that will initiate a motor “M” to start? (10) **CLO-2**
 $M = B'CD' + B'CE + B'CF$

Question No 3

10

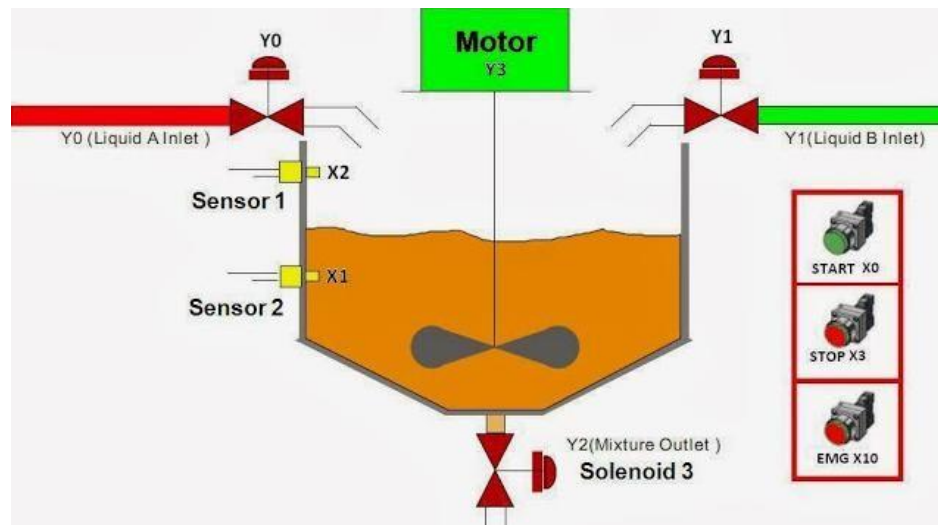- A. Describe and draw ladder diagram for the below given process having a container infused with liquids A and B in order when START is pressed. When it reaches the set level, mix the two liquids evenly then open the valve to let out the mixture? **CLO-2**



.Good Luck.

name = Raham Zeb (1) solution paper.

Question no 1:- Multiple choice questions.


- (1) An increase in body resistance.
- (2) opening a manually operated high voltage disconnector switch
- (3) Third
- (4) Reducing
- (5) Transducer

Q no 2:- Draw digital logic circuit and ladder diagram that is equivalent to the following Boolean function that will initiate a motor "M" to start?


Ans: $M = (\bar{B} \cdot C \cdot \bar{D}) + (\bar{B} \cdot C \cdot E) + (\bar{B} \cdot C \cdot \bar{F})$

Logic Diagram - $M = \bar{B}'C'D + \bar{B}'C'E + \bar{B}'C'\bar{F}$

Logic Diagram

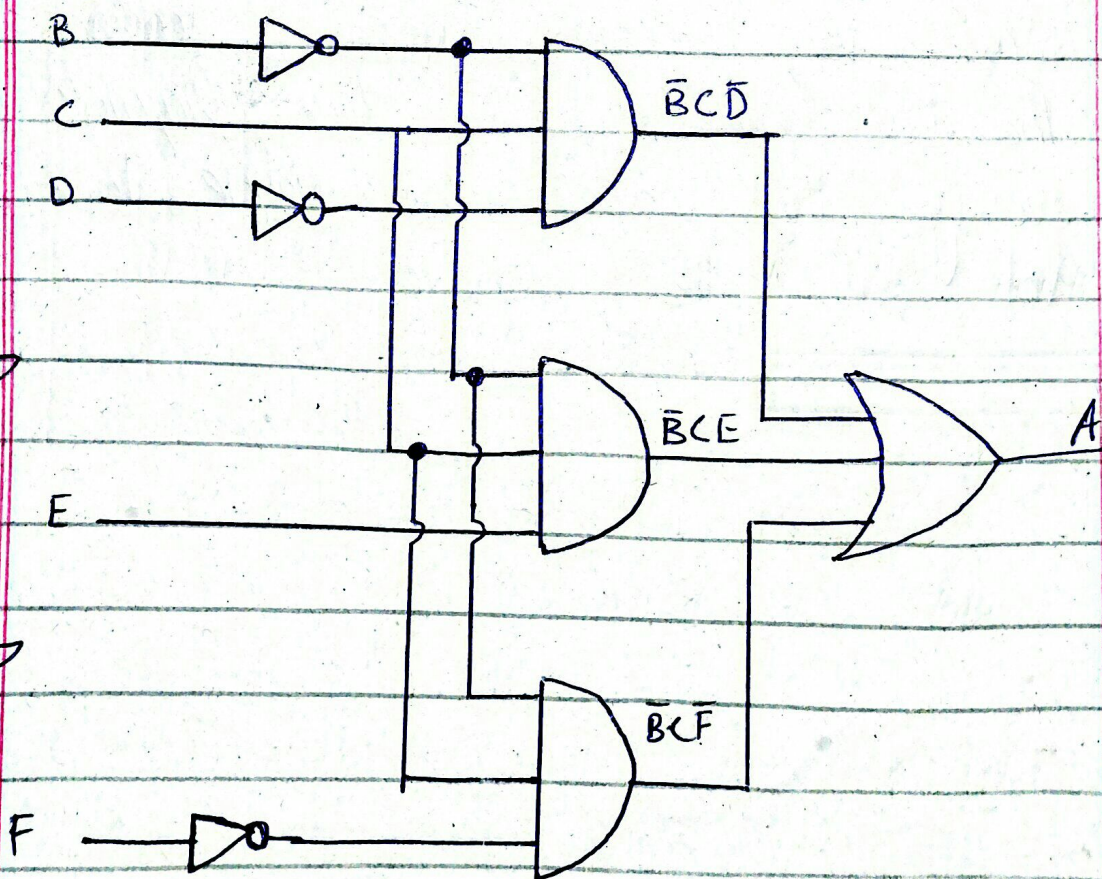

Ladder Diagram

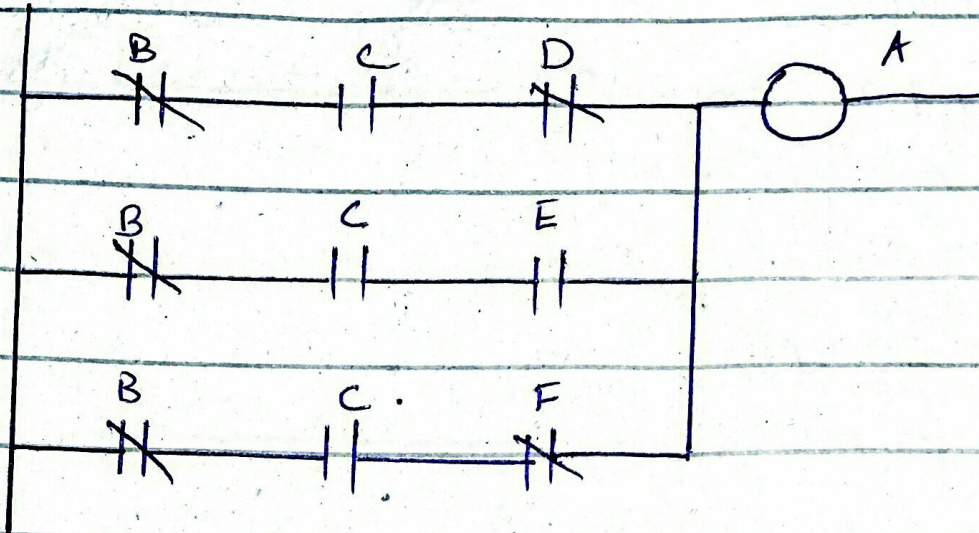Question no 3:


A. Describe and draw ladder for the below given process having a container infused with liquids A and B in order when start is pressed. when it reaches the set level, mix the two liquids evenly then open the valve to let out the mixture?

NAME = ~~Raham~~ ~~Feb~~

(3)

IO = 13074

Ans:

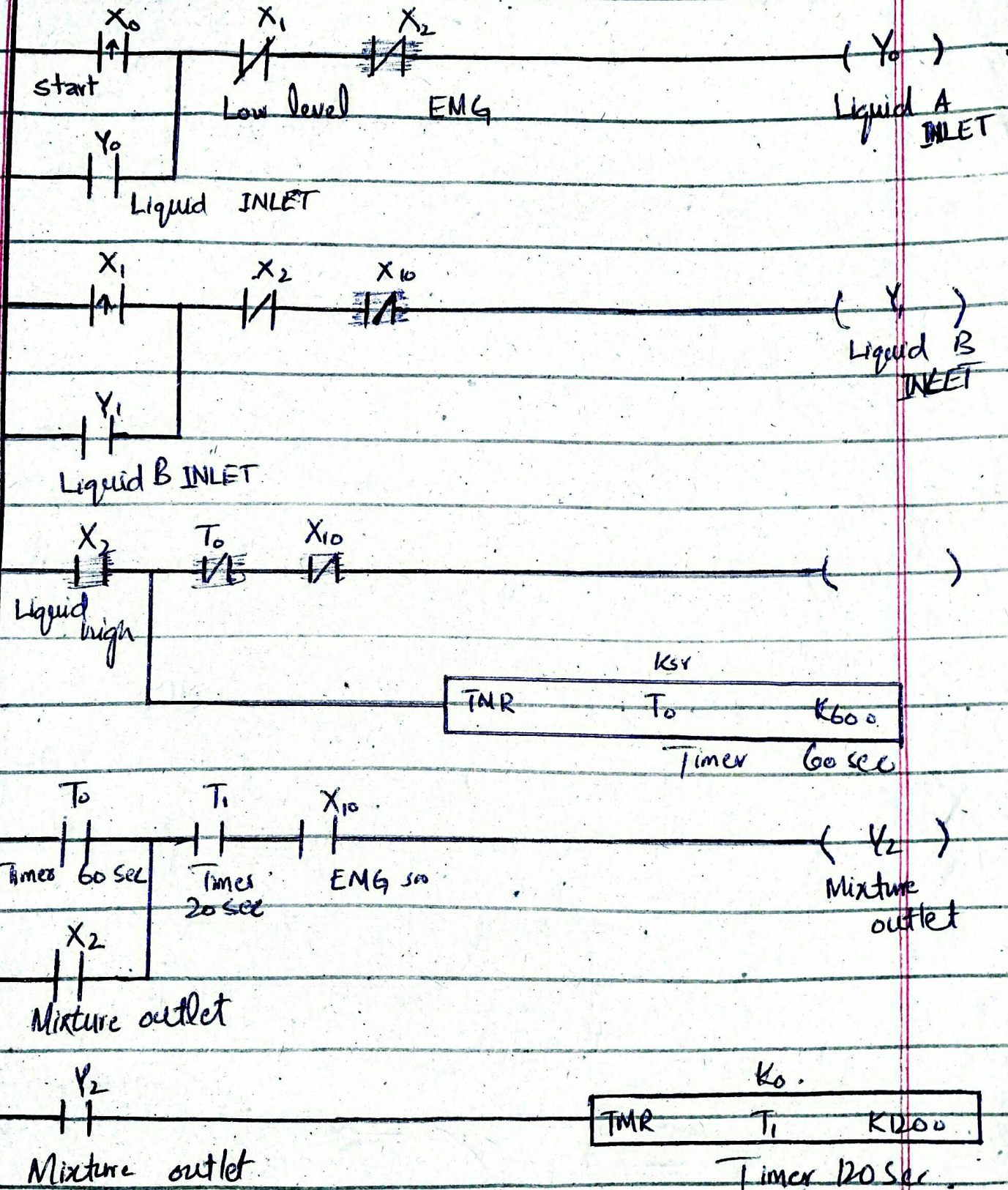

Number of PLC Inputs

X_1 - Start Switch

X_1 - Low level float Sensor.

$X_1 = ON$ when the level reaches X_2 .

X_2 - High level float Sensor.

$X_2 = ON$ when the button is pressed.

$X_3 =$ Stop Switch

$X_{10} =$ Emergency stop button.

$X_{10} = ON$ when the button is pressed.

Number of PLC Outputs

Y_0 - Liquid A inlet.

Y_1 - Liquid B inlet.

Y_2 - Mixture outlet.

Y_3 - Agitator / stirrer.

Number of PLC Timers Required.

~~T_0~~ sec, 100ms

T_0 - 60 second Timer, 100 ms Time Base. 60K present value timer

T_1 - 120 second Timers, 100 ms Time Base. 1200 present value timers

Ladders Program Description.

- * $X_0 = ON$ when start is pressed. Y_0 will be ON and latched and the valve will be opened for infusing Liquid A until the level reaches the low float sensor.
- * $X_1 = ON$ when the level reaches the low-level float sensor. Y_1 will be on and latched and the valve will be opened for infusing Liquid B until the level reaches the high level float sensor.
- * $X_2 = ON$ when the level reaches the high-level float sensor. Y_3 will be ON and activates the agitator. Also timers.
T₀ will start to ~~count~~ count for 60 sec.
T₀ will stop working. Y_2 will be ON and latched and the mixture will drain out of the container.

Raham zeb (6)

13074

* When $Y_2 = ON$ timer T_2 will start to count for 120 sec. After 120 sec T_1 will be ON and Y_2 will be off the draining process will be stopped