

Department of Electrical Engineering
Sessional Assignment
Course Details

Course Title: Instrumentation and Measurement **Module:** 6th (BE)

Student Details

Name: Talha Khan **Student ID:** 13845

Q1: A wattmeter has 2 current coils connected in parallel, each having a resistance of 0.7Ω . The wattmeter is connected in a circuit to measure power with its potential coil on the supply side. The reading on the wattmeter is $100W$ and the reading on the ammeter connected in series with the current coil is $3A$. Calculate:

- a) Power loss in the wattmeter
 - b) True load power
 - c) Percentage error due to wattmeter connection
-

Q2: Two voltmeters have the same range $0-500V$. The internal resistances are $30K\Omega$ and $20K\Omega$ respectively. If they are connected in series and $700V$ be applied across them, what will be their readings?

Answers:

Q 1:-

Sol:- Given Data:-

Two current coils Resistance =

$$R_1 = 0.7\Omega$$

connected in
Parallel.

$$R_2 = 0.7\Omega$$

wattmeter $P = 100\text{w}$


current $I = 3\text{A}$

Required:-

(a) Power loss in the wattmeter.

(b) True load power.

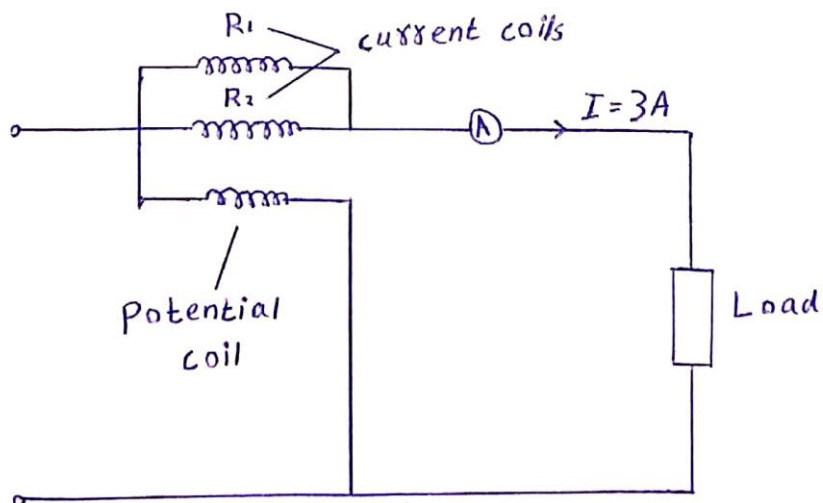(c) Percentage error due to wattmeter connection.



Sol:-

Effect low Resistance of current coils.

$$R_c = \frac{R_1 R_2}{R_1 + R_2} = \frac{0.7 \times 0.7}{0.7 + 0.7} = 0.35 \Omega$$

(i) Power loss in wattmeter

$$I^2 R_c = 3^2 (0.35) \\ = 3.15 \text{ w}$$

$$(ii) \text{ True load power} = 100 - 3.15 \\ = 96.85 \text{ w}$$

$$(iii) \text{ \% age error} = \frac{100 - 96.85}{96.85} \times 100 \\ = 3.25 \%$$

Q (2)

Given data:-

$$V = 0-500V$$

$$R_1 = 30k\Omega$$


$$R_2 = 20k\Omega$$

$$V_T = 700V$$

Required:

$$V_1 = ?$$

$$V_2 = ?$$

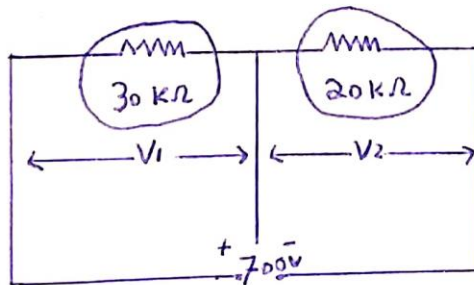

voltage divider rule, the readings of the two voltmeter are:

Page (4)

$$V_1 = \frac{30k\Omega}{30k\Omega + 20k\Omega} \times 700$$

$$V_1 = 420V$$

$$V_2 = \frac{20k\Omega}{30k\Omega + 20k\Omega} \times 700$$

$$V_2 = 280V$$
