



NAME: Farhan shah

ID: 13180

Department:

B.Electrical Engineering

Semester:

8th

Subject:

power electronic

Submitted to:

Engr.shahyan tariq sir

Date:

19/4/2020

Department of Electrical Engineering
Assignment

Date: 14/04/2020

Course Details


Course Title:	<u>Power Electronics</u>	Module:	<u>8th</u>
Instructor:	<u>Engr.shahyan triq sir</u>	Total	<u>30</u>
		Marks:	

Student Details



Name:	<u>farhan shah</u>	Student ID:	<u>13180</u>
--------------	--------------------	--------------------	--------------

Note: Plagiarism of more than 20% will result in negative marking.
Similar answers of students will result in cancellation of the answer for all parties.

Q1	(a)	An appliance circuit has a R-L connected in series with a diode. After some time, modification is done to the circuit and a free-wheeling diode is added in parallel to the R-L. Will it have any impact on the performance and output of the circuit. Back your answer with before & after data, facts and figures. Does adding a free-wheeling diode in parallel to a R-C circuit have the same effect, different effect or no effect.	Marks 7
			CLO 1
	(b)	A Power Mosfet is connected in a circuit. The Drain to Source voltage, $V_{DS} = (\text{Last 2 digits of your student ID}) \text{ V}$ and Threshold Voltage, $V_T = (\text{Last 1 digit of your student ID}) \text{ V}$. What is the minimum Gate to Drain Voltage, V_{GS} required for the P.Mosfet to be in saturation mood.	Marks 3
			CLO 1
Q2	(a)	A Power Electronics appliance of 500W, 220V, 500KHz rating is using a Power Mosfet for switching purpose. If the P.Mosfet is replaced with a Power Bipolar Junction Transistor what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
	(b)	In the above appliance (Q2.a) if the P.Mosfet is replaced with a Silicon Controlled Rectifier what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
Q3	(a)	The bipolar transistor in the Figure below is specified to have β_F in the range of 8 to 40. The load resistance, $R_C = (\text{Last 2 digits of your student ID}) \Omega$.	Marks 10

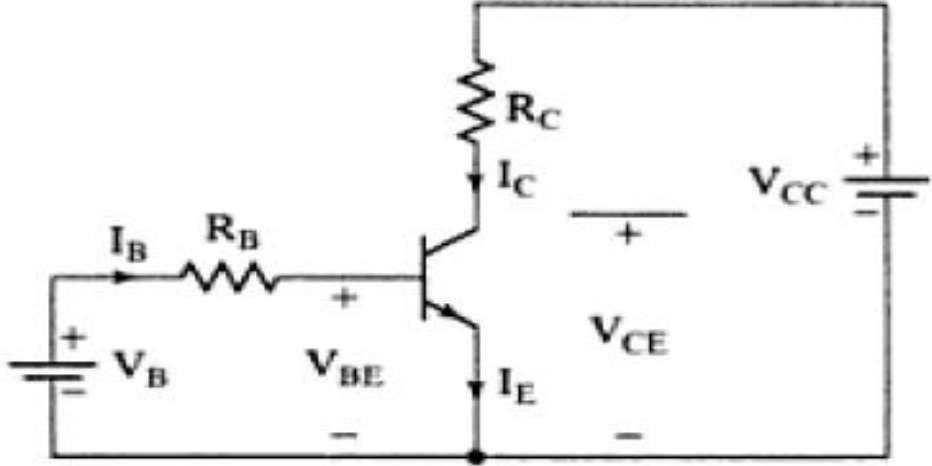	<p>The dc supply voltage, $V_{CC} = (\text{Last 3 digits of your student ID}) \text{ V}$ and the input voltage to the base circuit, $V_B = 10 \text{ V}$.</p> <p>If $V_{CE} = (\text{First digits of your student ID}) \text{ V}$ and $V_{BE} = 1.5 \text{ V}$, find</p> <ol style="list-style-type: none"> The mode of operation of the transistor the value of R_B that results in saturation with an ODF of 5, the β_{forced}, the power loss, P_T in the transistor. 	CLO 1
		

⇒ RL Connected in Series with Diode:-

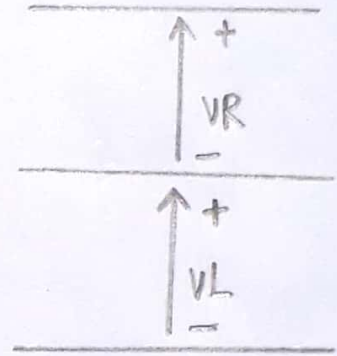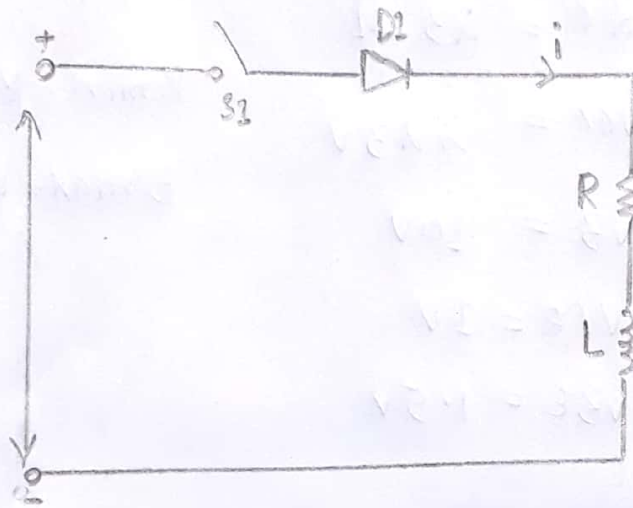

⇒ When S_1 is closed at $t=0$, the current through the inductor increases and is expressed as:

$$v_s = v_L + v_R = L \frac{di}{dt} + Ri$$


⇒ With the control initial condition $i(t=0) = 0$ $i(t)$ is expressed as

$$i(t) = \frac{v_s}{v_R} (1 - e^{-tR/L})$$


⇒ The Rate of change of this circuit can be obtained from.

$$\frac{di}{dt} = \frac{v_s}{L} e^{-tR/L}$$

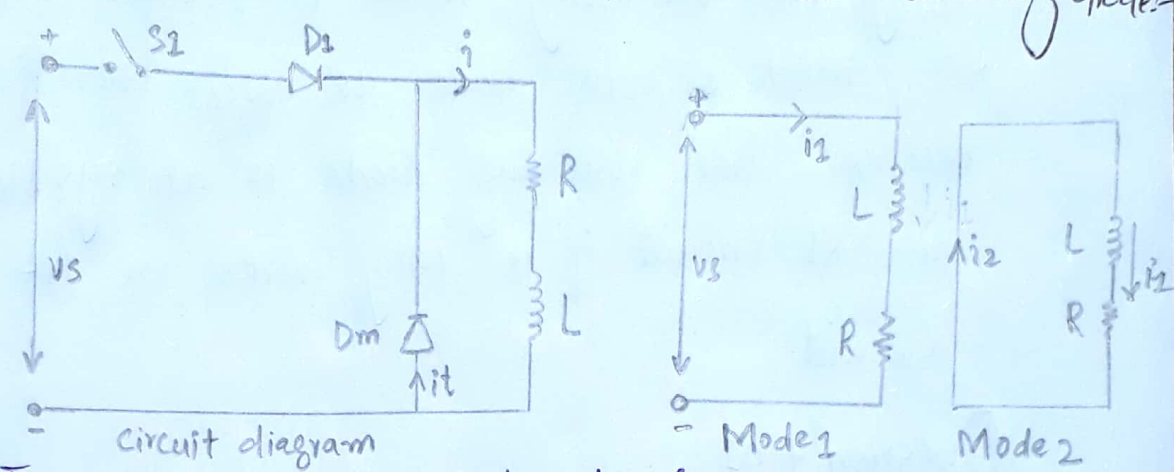⇒ RL Circuit Connected in parallel with free wheeling diode.



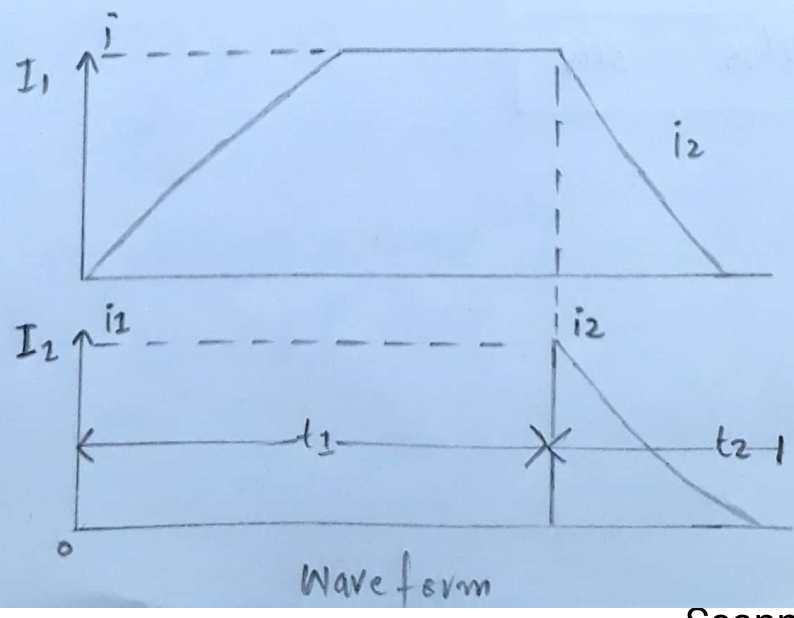- ⇒ The Inductor has property to store energy.
- ⇒ In AC current during positive half cycle the Inductor stores energy.
- ⇒ At Negative half cycle the Inductor de-energises.
- ⇒ This may cause reverse damage to circuit.
- ⇒ To avoid energy dissipation free wheeling diode is used.
- ⇒ In negative half cycle the free-wheeling diode because forward bias so the current will flow through diode.




⇒ The initial rate of rise of the current (at $t=0$) is obtained:

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_S}{L}$$

The voltage across the inductor is

$$V_L(t) = L \frac{di}{dt} = V_S e^{-t/RL}$$

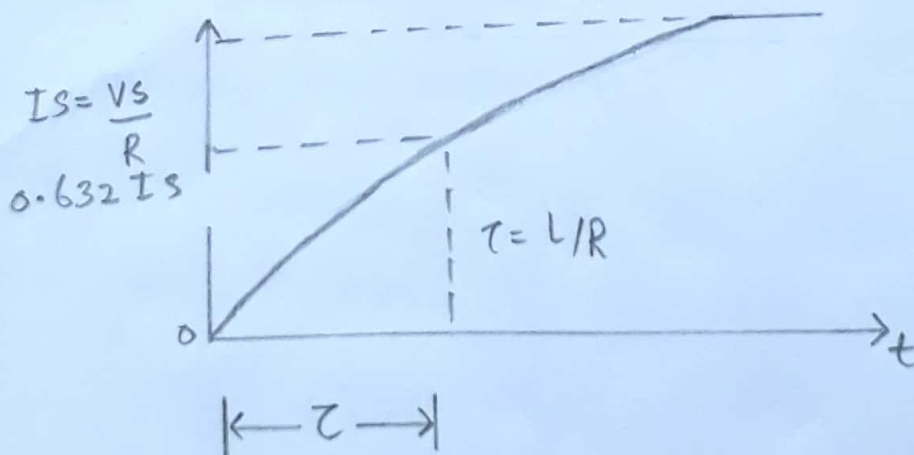where $L/R = \tau$ is the time constant of RL load. The waveforms for the voltage & current are shown.



⇒ Adding free wheeling diode in parallel with RC circuit will have no effect because free wheeling diode is always placed in RL circuit & it only works in RL circuit.

Question # 01

(Part b)

Data:-

$$V_{DS} = 80V$$

$$V_T = 2V$$

Solution:-

For Saturation

$$V_{DS} \gg V_{GS} - V_T$$

$$V_{DS} = V_{GS} - V_T$$

$$V_{GS} = V_{DS} + V_T$$

$$V_{GS} = 80 + 2$$

$$V_{GS} = \cancel{80V} + 2V = 82V$$

Question # 02 part(A)

Given Data:-

appliance of 500W, 220V, 500KHz rating using a power Mosfet for switching purpose.

→ Reason:-

IF the power Mosfet is replaced with a power Bipolar Junction Transistor what effect will it have on the performance, losses and efficiency of the appliance.

- 1) ⇒ BJTs and Mosfets are mainly used in power Electronic circuits.
- 2) ⇒ The Switching speed of a BJT is many times slower than that of a Mosfet of similar size and rating.
- 3) ⇒ A BJT is a current controlled device, and a large base current is required to keep the device in the on state. In addition to obtain fast turn off a higher reverse base current is required.


4) \Rightarrow Power Mosfet are voltage controlled devices. They are preferable to BJT in high frequency applications where switching power loss is important. However the on state voltage drop of power mosfets higher than that of BJT of similar size and rating. Therefore in high voltage application where on state losses are to be minimized a BJT is preferred.

5) \Rightarrow High power BJT are commonly power converters at a frequency below 10KHz and are effectively applied in the power rating upto 1200V, 400A.

6) \Rightarrow Power Mosfets are used in high speed power converts. these are available at relatively low power rating i-e in the range of 1000V, 100A.

\rightarrow Power Bipolar Junction transistors:-

\Rightarrow Power transistor are available in both NPN and PNP. However we will connected on the NPN device since it has a higher current and voltage rating than the PNP device.

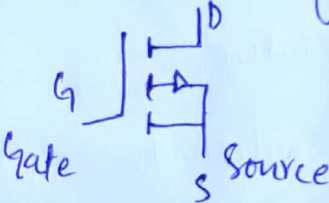- ⇒ application: AC motor control SMPS.
- ⇒ Maximum VI Rating: 600V/200A
- ⇒ This is voltage controlled.
- ⇒ Type of device: majority carrier.
- ⇒ Communication circuit:- Not necessary.
- ⇒ Blocking capacity: Asymmetrical
- ⇒ Temperature :- Positive
- ⇒ Parallel operation:- Easy to parallel
- ⇒ symbol:- 

The above effect on the performance losses and efficiency of the appliance.

⇒ Efficient:-

Mosfet is usually more efficient switches for power supplies. BJT will consume more power because its wasting current when it switches on. Also the BJT generally has 0.3V voltage drop in the input pin and it takes a lot of base current to do that.

⇒ Mosfet:-

is more tolerant to heat and it can simulate a good resistor. and Mosfet is used for power supplies and is efficient whereas BJT is used in low power consuming devices like LED. BJT consumes more as it is a device.

⇒ LOSSES:-

losses due to BJT will be low and due to mosfet will be higher because mosfet is voltage controlled device and BJT is current control.

Switching of Mosfet is higher than BJT.

Question # 03

Given Data:-

$$R_c = 23 \Omega$$

$$V_{CC} = 223V$$

$$V_B = 10V$$

$$V_{CE} = 1V$$

$$V_{BE} = 1.5V$$

$$B_{min} = 8$$

$$B_{max} = 40$$

To Find:-

(a) Mode of operation of transistor

$$CDF = 5$$

(b) $R_B = ?$

(c) B Force

(d) power loss PT in the transistor.

Solution:-

(a) Saturation mode

$$(b) I_{CS} = \frac{V_{CC} - V_{CE}(\text{Sat})}{R_C}$$

$$= \frac{223 - 1}{23}$$

$$I_{CS} = 9.6A$$

$$I_{BS} = \frac{I_{CS}}{B_{min}}$$

$$= \frac{9.6}{8}$$

$$I_{B_s} = 1.2 \text{ A}$$

$$CDF = \frac{I_B}{I_{B_s}}$$

$$I_B = CDF \times I_{B_s}$$

$$= 5 \times 1.2$$

$$I_B = 6 \text{ A}$$

$$R_B = \frac{V_B - V_{BE}}{R_i \cdot I_B}$$

$$= \frac{10 - 1.5}{6}$$

$$R_B = 1.41 \Omega$$

$$B_{force} = 1.6$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$= \frac{223 - 1}{23}$$

$$I_C = 9.6 \text{ A}$$

$$P_T = V_{BE} I_B + V_{CE} I_C$$

$$= 1.5 \times 6 + 1 \times 9.6$$

$$9 + 9.6$$

$$P_T = 18.6 \text{ W}$$