

Department of Electrical Engineering
Assignment
Date: 23/06/2020

Course Details

Course Title: Instrumentation and Measurement Module: 6th (BE)
 Instructor: _____ Total Marks: 50

Student Details

Name: _____ Student ID: _____

Note: Draw neat diagrams where necessary. Assume missing details if required.

Q1.	A student has connected two voltmeters in series and have applied 500V across them. Both voltmeters have the same range of 0-300V. What will be their readings if their internal resistances are 25kΩ and 15 kΩ respectively?	Marks 10
		CLO 2
Q2.	A dynamometer type wattmeter has two current coils each having a resistance of 0.5Ω. Both of the coils are connected in parallel. The wattmeter voltage coil is connected to the supply side. The wattmeter shows a reading of 200W while the reading on the ammeter is 4A which is connected in series with the current coil of the wattmeter. Calculate the following parameters: a) Power dissipated in the wattmeter b) True load power c) Percentage error due to the connection of wattmeter	Marks 10
		CLO 2
Q3.	(a) What is the difference between Kelvin's bridge and Wheatstone Bridge? Explain briefly.	Marks 05
		CLO 3
	(b) Explain how the potential on the upper (top) node in a DC bridge is equal to the potential on the lower (bottom) node?	Marks 05
		CLO 3

Q4.	(a) Why the energy meters designed for DC circuits cannot be used for AC circuits?	Marks 05
		CLO 03
	(b) What will happen if the phase difference between two alternating fluxes in an induction type energy meter is zero degrees?	Marks 05
		CLO 03
Q5.	(c) Why the series magnet is wound with a wire of few turns as compared to shunt magnet in an induction type energy meter?	Marks 05
		CLO 03
	(d) What is the significance of meter constant in an energy meter?	Marks 05
		CLO 03



Name ≈ Rafiqat Ullah Khan

ID ≈ 14107

Date = 23-06-2020

Subject = EMI

Submitted to ≈

Sir walled Jan

(i)

Question: 01

Sol:-

Given data:-

Two voltmeter in series range = 0-300V

Applied voltage across them = 500V


Internal resistance of $V_1 = 25\text{K}\Omega$

Internal resistance of $V_2 = 15\text{K}\Omega$

Required:-

we have to find readings in both voltmeters.

Diagram:-

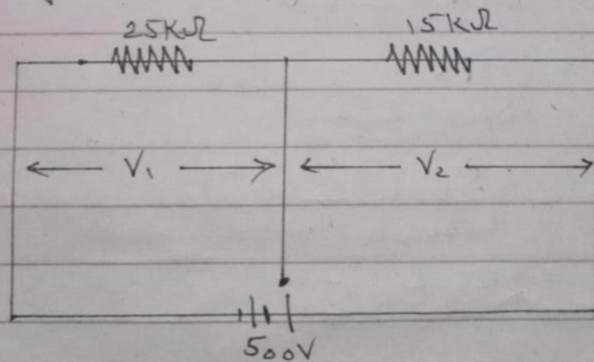

Formula:-

$$V_1 = \frac{R_1}{R_1 + R_2} \times V$$

Solution:-

(2)

Solution:-

$$V_1 = \frac{R_1}{R_1 + R_2} \times V$$

$$V_1 \Rightarrow \frac{25 \times 10^3}{25 \times 10^3 + 15 \times 10^3} \times 500$$

$$\text{"} \Rightarrow \frac{25000}{25000 + 15000} \times 500$$

$$\text{"} \Rightarrow \frac{25000}{40000} \times 500$$

$$\text{"} \Rightarrow 312.5 \text{ V}$$

$$V_2 \Rightarrow \frac{R_2}{R_2 + R_1} \times V$$

$$\text{"} \Rightarrow \frac{15 \times 10^3}{15 \times 10^3 + 25 \times 10^3} \times 500$$

$$\text{"} \Rightarrow \frac{15000}{15000 + 25000} \times 500$$

$$\text{"} \Rightarrow \frac{15000}{40000} \times 500$$

$$\text{"} \Rightarrow 0.375 \times 500$$

$$V_2 \Rightarrow 187.5 \text{ V}$$



(3)

Question = 2 :-

Given data:-


Coil resistance = $R = 0.5 \Omega$

Power = $P = 200 \text{ W}$

Current = $I = 4 \text{ A}$

Required:- a):- Dissipated power = ?
b):- True load power, c):- % error = ?

Diagram:-

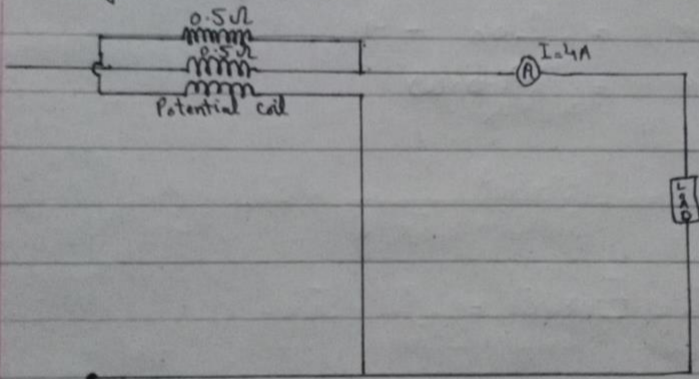

Solution:-

$$R_c = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$= \frac{(0.5) \times (0.5)}{0.5 + 0.5}$$

$$= \frac{0.25}{1}$$

$$R_c = 0.25 \Omega$$

(4):-

a):- Power dissipated in resistor

$$P \Rightarrow I^2 R$$

$$\Rightarrow (4)^2 (0.25)$$

$$\Rightarrow 4 \text{ W}$$

b):-

True load power = ?

$$\text{T.L.P} = \text{Total power} - \text{Dissipated power}$$

$$\text{"} = 200 - 4$$

$$\text{"} = 196 \text{ W}$$

c):-

$$\% \text{ Error} = ?$$

$$\text{"} = \frac{P_T - \text{Load Power}}{\text{Load Power}} \times 100$$

$$\text{"} = \frac{200 - 196}{196} \times 100$$

$$\text{"} = 2.04\%$$



-(5):-

Question - 3 :- (a) :-

i) :- Difference between Kelvin Bridge and wheatstone bridge :-
Kelvin Bridge :-

The Kelvin bridge is more advance and helps in measuring resistance less than one ohm while it has more resistors. The w.B.

Wheatstone Bridge :-

It measure electrical resistance by balancing them a bridge circuit. The circuit has two legs in which one contain a resistance between 1 ohm to 10 ohms.

It can also measure impedance, Capacitance and inductance.

∴ (6) :-

Question: (3) :- (b) :-

This part is known as balance condition when $I_3 = 0$ A.

Now as

$$V_{BD} = V_B - V_D \Rightarrow I_3 G$$

So $V_{BD} = I_3 G$ ∴ Now put I_3 value

$$V_{BD} = \Delta(G) \Rightarrow \Delta V \quad \text{OR}$$

$$V_B - V_D = 0 \quad \text{OR} \quad V_B = V_D$$

Now in eq (i) and eq (ii)

$$i) :- V_{AB} = V_A - V_D = I_1 P \rightarrow \text{new eq (i)}$$

$$V_{BC} = V_D - V_D = I_1 Q \rightarrow \text{new eq (ii)}$$

Now new eq (i) and eq (iii)

$$= I_1 P \Rightarrow I_2 R \quad (\text{OR}) \quad \frac{I_1}{I_2} = \frac{R}{P} \rightarrow (5)$$

Compare eq (2) with eq (iv)

$$I_2 x = I_1 Q$$

$$\frac{I_1}{I_2} = \frac{x}{Q} \rightarrow (6)$$

So compare eq (5) and (6)

$$\frac{R}{P} = \frac{x}{Q}$$

OR

$$x = \left(\frac{R}{P}\right) Q$$



(7):-
Question-4:-(a):-


Energy meter designed for DC circuit is not AC.

Because AC energy works due to involvement of two alternating magnetic fields produced by AC quantities (voltage and current) that interacts with an aluminium disk causing eddy current to induce in the disk. In DC such induction effect and eddy current not produced.

Part:- (b):-

It should be noted that when $\theta = 0^\circ$ then deflecting torque is zero or no torque can be produced.

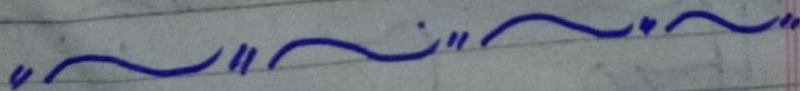Torque will be maximum when $\theta = 90^\circ$



(8):

Question (5):-(a)

A series magnetic is wound with a wire of few turns and connected in series with load so that it carries the load current. The coil of this magnetic is highly non-conductive.

Question:-(5):-(b):

Meter constant:-

$N \propto \text{Energy}$, $N = K \times \text{energy}$
where K is called meter constant
Meter constant:- $K = \frac{N}{\text{energy}} \Rightarrow \frac{\text{no. of revolution}}{\text{Kwh}}$

Hence the no. of revolution made by the disc for 1 Kwh of energy consumption is called meter constant. For example, if meter constant of energy meter is 1500 rev/kwh. It means that for consumption of 1 Kwh the disc will make 1500 revolution.

~~~~~  
The End