

**Department of Electrical
Engineering Sessional
Assignment Date: 04/05/2020
Course Details**

Course Title: Electronic Circuit Design **Module:** 04 **Instructor:** Sir Mujtaba Ihsan
Total Marks: 20

**Student
Details**

Name: Mansoor Jadoon **Student ID:** 16637

Q1. **Explain** the trans conductance curve for n-channel JFET given below Marks 04 CLO 1

Q2. **State** the characteristics of a practical operational amplifier. Marks 04 CLO 1

Q3. **Calculate** output voltage for summing amplifier if $V_1 = 0.2V$, $V_2 = 0.5V$ and $V_3 = 2V$ and
 $R_1=R_2=R_3=R_f =$ not consider for your work?

6k Ω

Justify your answer with
reason.

Mark
s 05

Mark
s 04

CLO

CLO

2

Q4. (a) You are working on an audio circuit in the lab. Which class of power amplifier will


2

(b) **Outline** the differences between an amplifier and a rectifier. Marks 03 CLO 2

(1)

Q1:

Ans:

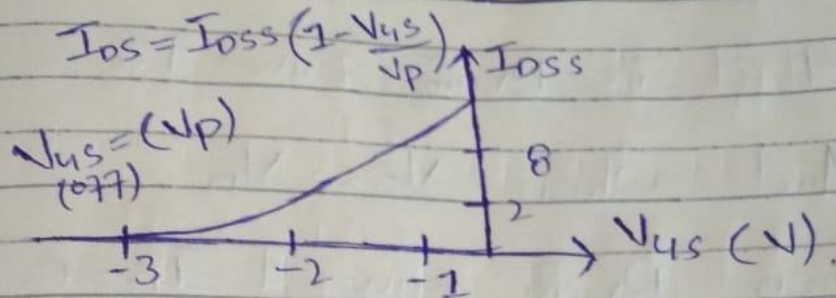

Given graph give us the transfer characteristics of N-channel JFET.

In the graph drain current (I_D) and voltage source to gate (V_{GS}) is shown. and curve is between voltage gate and source (V_{GS}) to drain current (I_D) and also drain to source current decrease with increase in negative gate source bias.

when $V_{GS} = 0$.

$$I_{DS} = I_{DSS} \left(1 - \frac{0}{V_p} \right)^2$$

(2)

$$\boxed{I_D = I_{DSS}}$$

that is Drain current.

And when $V_{GS} = V_D$

Then Drain current $I_D = 0$

" — " — " — " — " — "

Q2 Ans:

Practical Op Amp

characteristics:

- 1) It is voltage gain of the op-amp when no feedback is practically it is several thousands.
- 2) It is finite and typically greater than $1M\Omega$. But using FETs for the input stage it can be increased upto several hundred M.
- 3) The bandwidth of is

(3)

open loop configuration is very small by application of negative feedback.

4) It is typically few hundred ohm with the help of negative feedback. it can be reduced to very small value like 1 to 2 ohm.

" — " — " — " — "

Q3 Ans:

Given:

$$V_1 = 0.2V$$

$$V_2 = 0.5V$$

$$V_3 = 2V$$

$$R_1 = R_2 = R_3 = R_7 = 6K\Omega$$

As:

$$V_{out} = \left(\frac{R_7}{R_1} V_1 + \frac{R_7}{R_2} V_2 + \frac{R_7}{R_3} V_3 \right)$$

↳ equ (i)

(4)

As:

$$A_1 = \frac{R_7}{R_1} \Rightarrow \frac{6 \text{ k}\Omega}{6 \text{ k}\Omega} \Rightarrow 1$$

$$A_2 = R_7 / R_2 \Rightarrow \frac{6 \text{ k}\Omega}{6 \text{ k}\Omega} \Rightarrow 1$$

$$A_3 = R_7 / R_3 = \frac{6 \text{ k}\Omega}{6 \text{ k}\Omega} \Rightarrow 1$$

And also equ (i) written as:

$$V_{\text{out}} = (A_1 \times V_1) + (A_2 \times V_2) + (A_3 \times V_3)$$

$$V_{\text{out}} = (1 \times 0.2) + (1 \times 0.5) + (1 \times 2)$$

$$V_{\text{out}} = (0.2) + (0.5) + 2$$

$$V_{\text{out}} = 2.7 \text{ V}$$

(5)

Q4 (a) Ans:

In Lab class 'C' amplifier are not used because:

- i) class 'C' amplifier have lowest linearity.
- ii) class 'C' amplifier are not suitable in audio applications.
- iii) For these amplifiers it is difficult to obtain ideal inductors and coupling transforms.
- iv) These amplifier reduce dynamic range.

(b)

Q4 (b) Ans

Difference between rectifier and amplifier:

Amplifier

Rectifier

is used to increase the strength of electric signal

Allow current to pass in only one direction.

It convert AC signal to DC

Convert AC voltage of 100V or greater to DC voltage.

Amplifier also increase the power of weak signal

By using single diode convert AC signal to DC.

