


Digital Logic & Design (Lab)

Name: Changaiz khan

ID: 13206

Q.1 Design and verify the logic circuit for the following:


(a) Half adder using logic gates

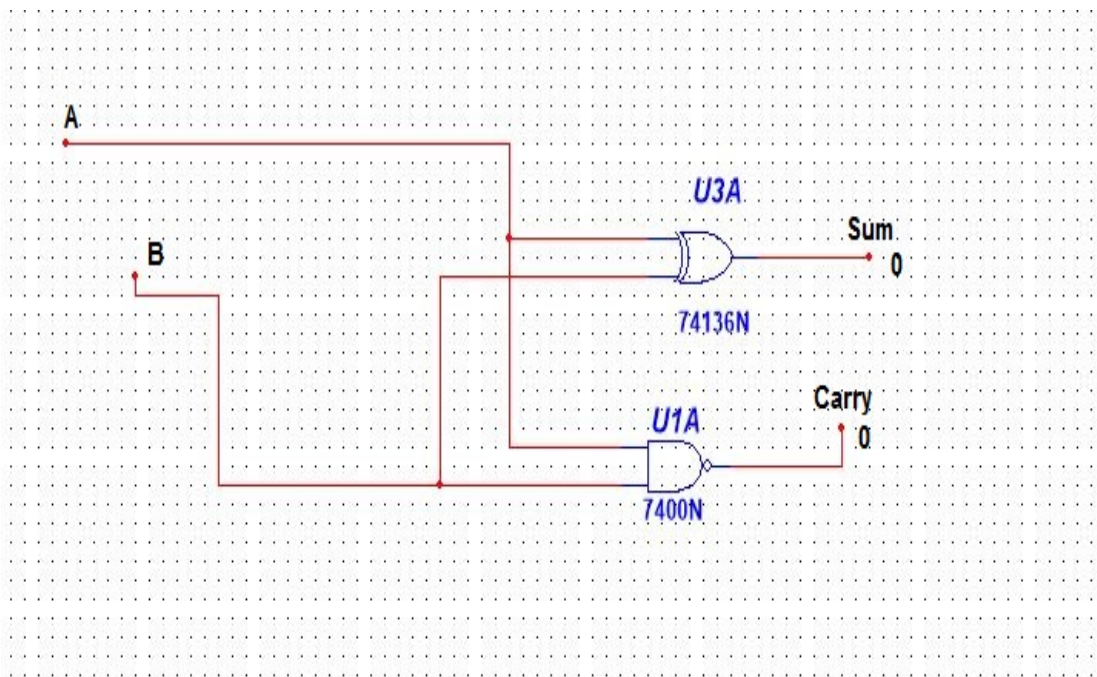

INPUTS		OUTPUTS	
A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the equation, it is clear that this 1-bit adder can be easily implemented with the help of EXOR Gate for the output 'SUM' and an AND Gate for the carry. Take a look at the implementation below

(b) Half-subtract or using logic gate

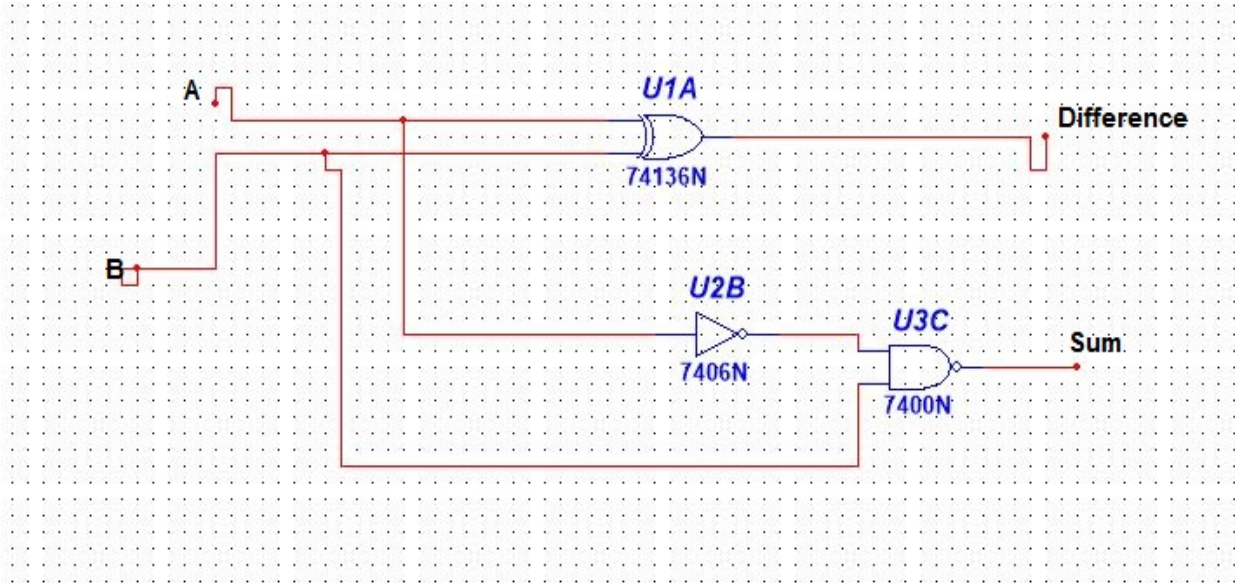


Truth Table

The half subtractor truth table explanation can be done by using the logic gates like EX-OR logic gate and AND gate operation followed by NOT gate.

First Bit	Second Bit	Difference (EX-OR Out)	Borrow (NAND Out)
0	0	0	0
1	0	1	0
0	1	1	1
1	1	0	0


(c) J K Flip flop

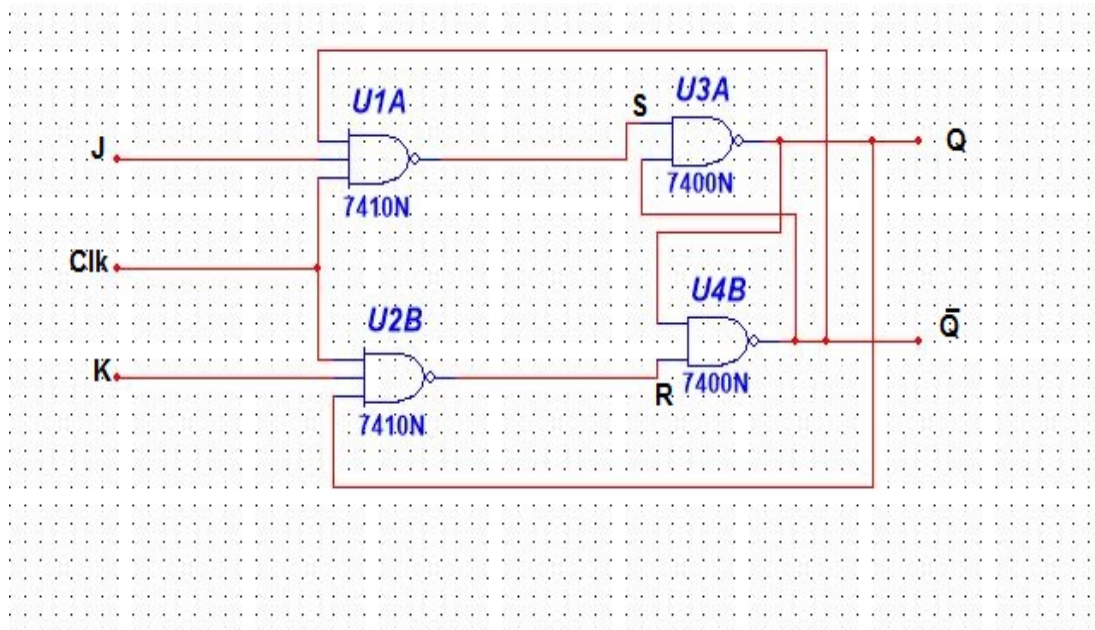

The Truth Table for the JK Function

	Clock	Input		Output		Description
	Clk	J	K	Q	Q	
same as for the Jk Latch	X	0	0	1	0	Memory no change
	X	0	0	0	1	
	$\bar{\downarrow}$	0	1	1	0	Reset Q » 0
	X	0	1	0	1	
	$\bar{\downarrow}$	1	0	0	1	Set Q » 1
	X	1	0	1	0	
toggle action	$\bar{\downarrow}$	1	1	0	1	Toggle
	$\bar{\downarrow}$	1	1	1	0	

(d) Serial in-serial Out shift register

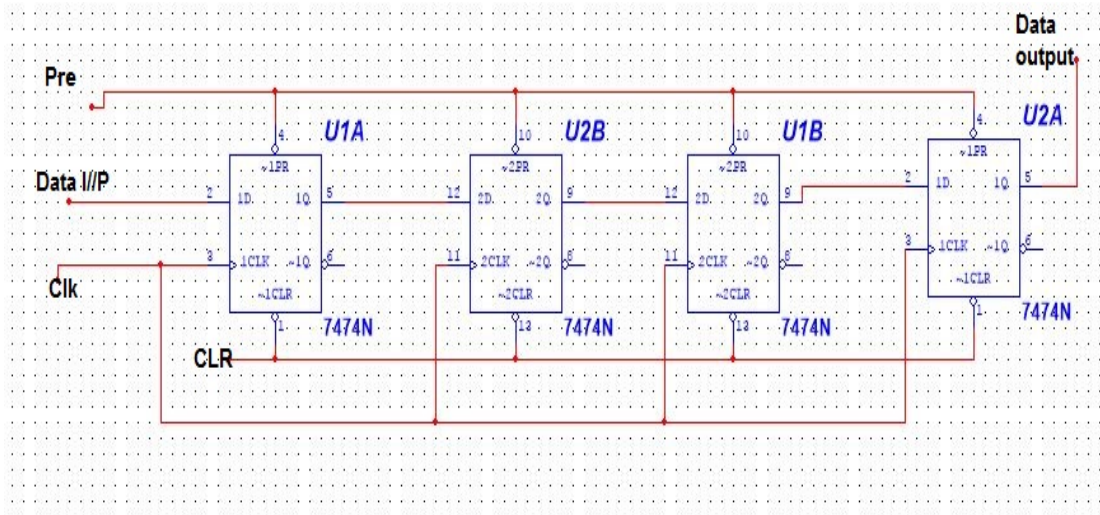

TRUTH TABLE:

CLK	Serial in	Serial out
1	1	0
2	0	0
3	0	0
4	1	1
5	X	0
6	X	0
7	X	1

(e) Synchronous BCD Counter

