

(2)

NAME : HAMEED KHAN  
Department : BS (CS)  
Semester : 1~~st~~ 4th  
ID : 15066  
Subject : Basic electronics  
Submitted To : KHANID HAMEED  
Date : 25/6/2020

(Q5)

(9)

advantages of BJT :-

- ① it has a large gain bandwidth.
- ② it shows better performance at high frequency.
- ③ it has a better voltage gain
- ④ it has high current density.
- ⑤ it can be operated in low or high power applications.

disadvantages of BJT :-

- ① The BJT is more an effect or reading
- ② it has a very complex base control so it may lead to confusion



(2)

- and requires a skilful handling
- ③ it is more noise produced.
  - ④ it has a low thermal stability.
  - ⑤ The switching frequency of a BJT is low.

### advantages of FET:-

- ① FETs have better thermal stability.
- ② FET are voltage controlled devices.
- ③ FETs are less ~~FET~~ affected by ~~reading~~ reddiation.
- ④ FETs produce less noise.

### disadvantages of FET:

- ① FETs have a poor frequency response due to its high input capacitance.
- ② FETs can be damaged due to the static electricity.
- ③ FETs have a very poor linearity and generally they are less linear than Bipolar Junction Transistor.



(3)

(Q5)

(b)

When the <sup>drain</sup> voltage is increased, the positive drain potential opposes the gate voltage bias and therefore reduces the surface potential in the channel. The channel inversion layer charge decreases with increasing drain-source voltage and ultimately it becomes zero when the drain-source voltage equal to

$$(V_{GS} - V_{GS(th)})$$

This point is called the channel pinch-off voltage where the drain current becomes saturated.

---

---

---

---



(Q No 2)




(\*) As the magnitude of  $V_{CE}$  decrease there comes a point when the collector voltage becomes less than the base voltage. When this happens the transistor region which is highly non-linear and is not usable for amplification.

(\*) The cut off region of operation occurs for base currents near zero. In the cutoff region the collector current approaches zero in a non linear manner and is also avoided for communication application.

(\*) The linear region is where we want to be for an



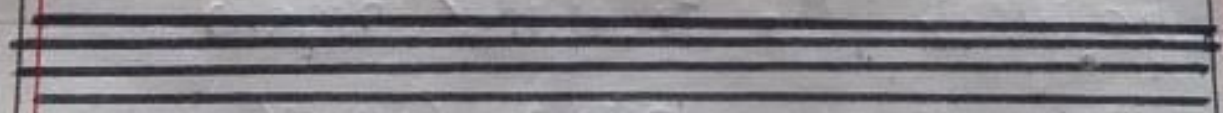Complications in the linear  
 for active regions the  
 course would ideally be  
 to indicate the normally  
 off condition as we  
 know that for  $V_{GS}$  exceeding  
 the threshold voltage.  
 $V_{GS}$  on N-Type inversion  
 layer connecting the source  
 to drain is created





(03)




(6)

(1)


# Common emitter:-

When the emitter terminal is common to both the input and the output circuit the mode of operation is called the common emitter or the ground emitter configuration of the transistor.

(a)

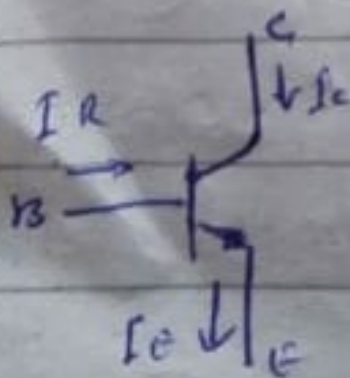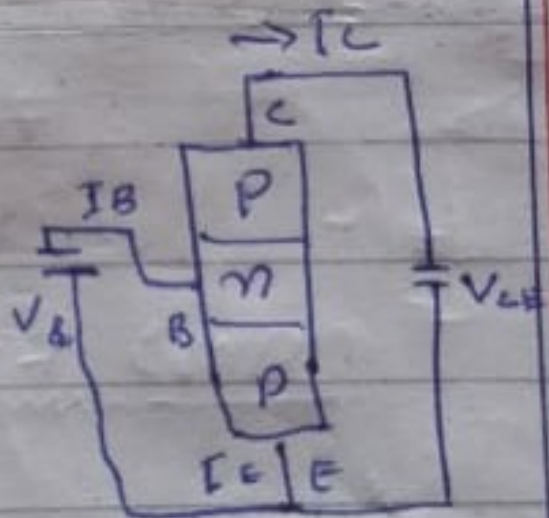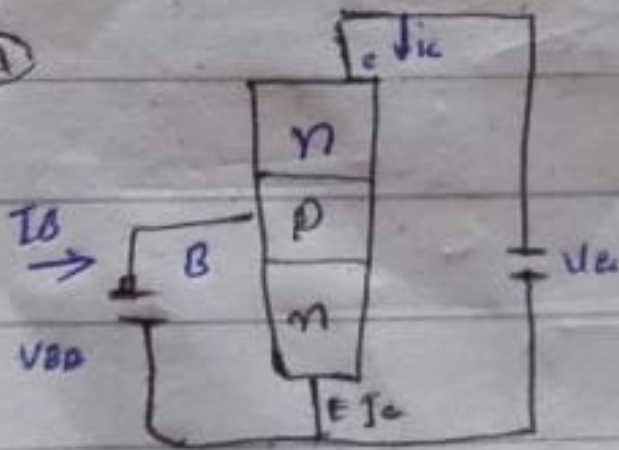

(n-p-n transistor)

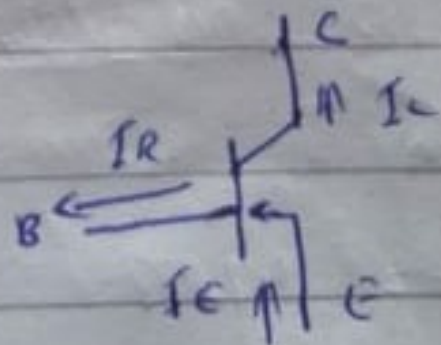

(p-n-p transistor)





(7)

## ② Common Collector:-

When the collector terminal of the transistor is common to both the input and the output terminals the mode of operation is known as the Common Collector mode or the ground collector configuration.

Configuration:-

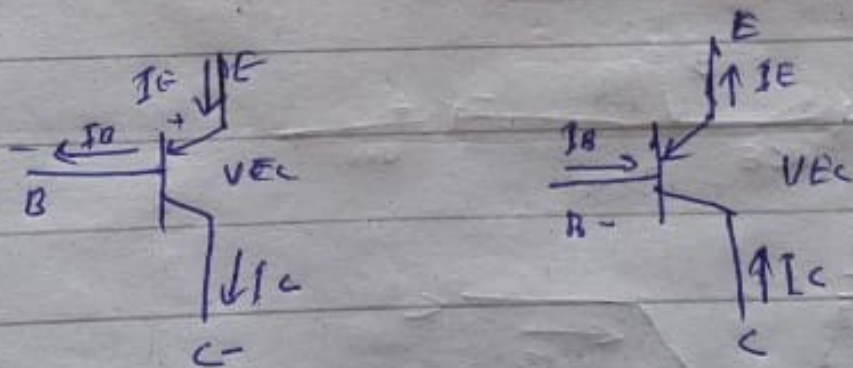
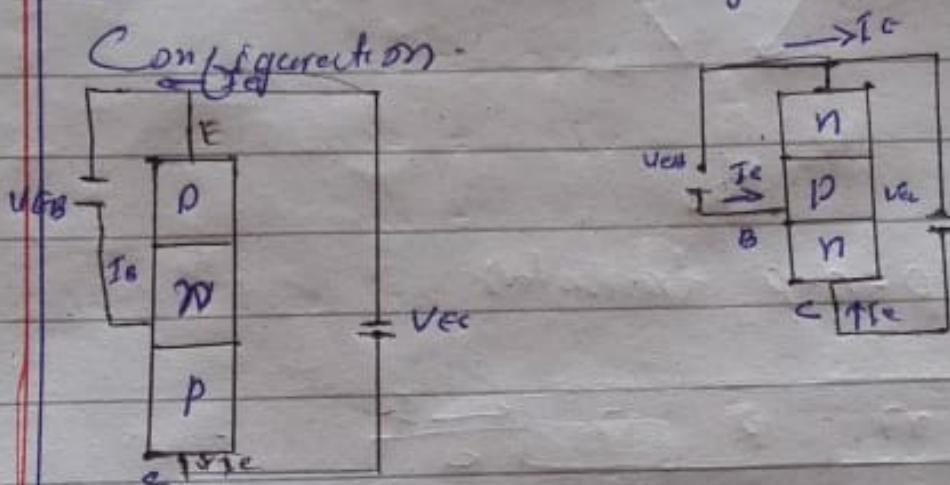


## ③ Common Base:-



In this mode the base terminal is common to both the input and the output circuits. This mode is also

8

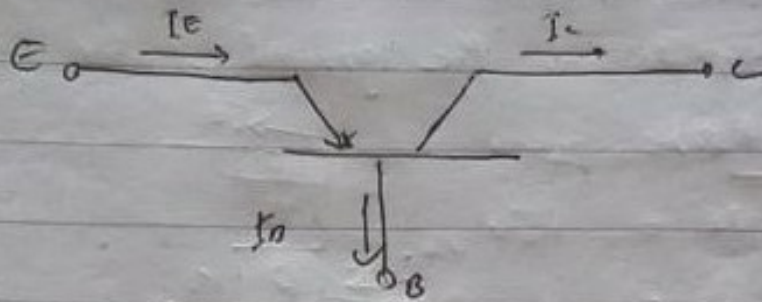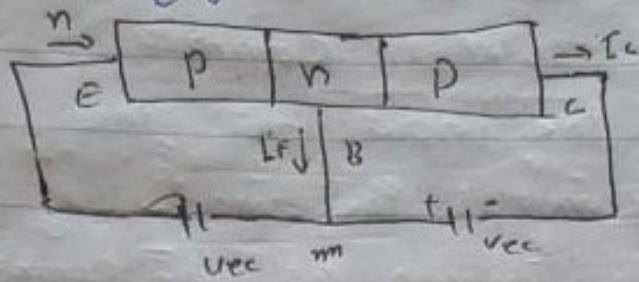referred to as the grounded base configurations.



(p-n-p transistor)

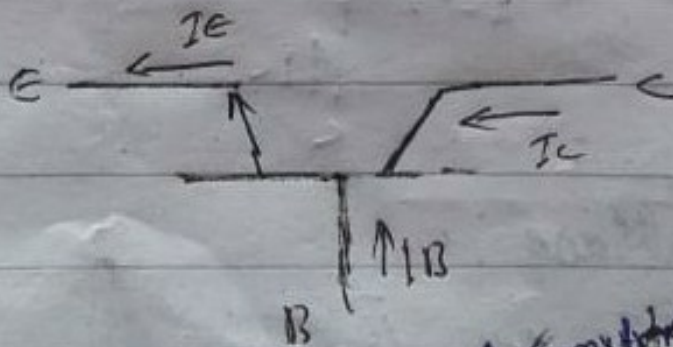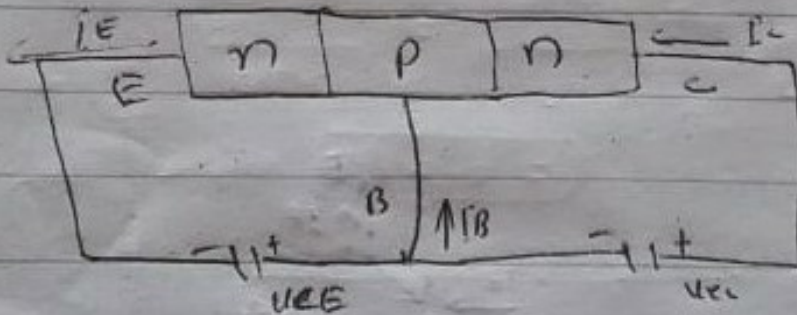

(n-p-n transistor)



(9)

Q1

Part (b)

Given data:→

$$\text{Load Resistance } R_L = 1500 \Omega$$

$$\text{Input Current} = E_i = 24$$

$$\text{Resistance} = R = 470 \Omega$$

Required data:→

$$\text{load voltage} = V_L = ?$$

Sol:→ As we know that

$$V_L = \frac{R_L E_i}{R + R_L}$$

putting values

$$\Rightarrow V_L = \frac{1500 \times 24}{470 + 1500}$$

$$\Rightarrow V_L = \frac{36000}{1970}$$

$$\Rightarrow \boxed{V_L = 18.27 \text{ V}}$$

Result:→

$$\boxed{V_L = 18.27 \text{ V}}$$



(10)

Q1 part (a)

Given

$$I_1 = \frac{24V}{470\Omega}$$

$$51.06 \text{ mA}$$

Special purpose diode

Since the load voltage is 15V

$$I_2 = \frac{15V}{1.5K\Omega}$$

$$I_2 = 10 \text{ mA}$$


The zener current is the diff  
b/w total current

$$I_z = 51.06 \text{ mA} - 10 \text{ mA}$$

$$I_z = 41.06 \text{ mA} \quad \text{Ans}$$



(11)  
(Q4)

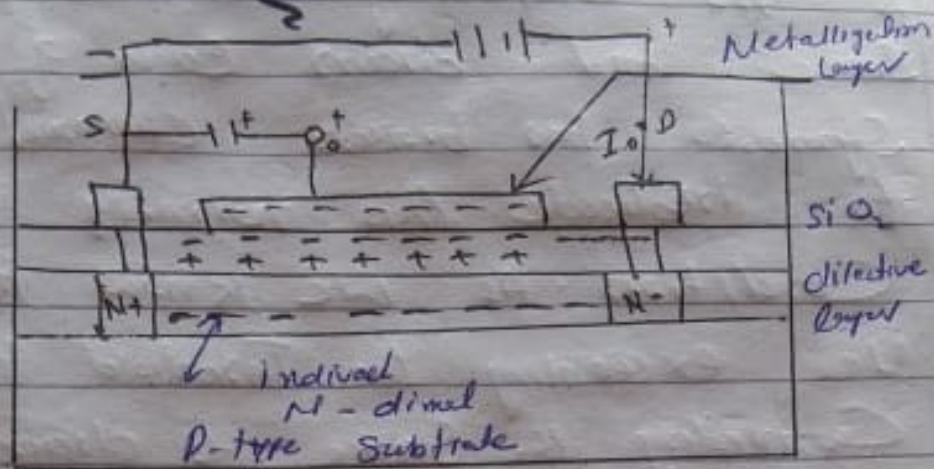

The current  $I_{DS}$  at  $V_{GS} = 0$  is very small being of the order of a few nano-amps when the  $V_{GS}$  is made positive the drain current  $I_D$  increases slowly at first and then much more rapidly with the drain current  $I_D$  attain some definite small value say  $10 \mu A$ . A current  $I_{D1}$  ON corresponding approximately to the maximum value given on the drain characteristics and the value of  $V_{GS}$  required to give this current  $I_{D1}$  ON are also usually given on the manufacturer's data



(12)

Sheet for zero value of  $V_{GS}$  the E-MOSFET is so off because there is no conducting channel between source and drain. Each of schematic symbols has broken channel line to indicate this normally off condition. As we know that for  $V_{GS}$  exceeding the threshold layer connecting the source to drain is created.

The END