

(1)

ABDUL MOEZ

Id : 12371

Electronic Devices & Circuits

BE(E) Mid Exam.

25 August, 2020.

Instructor: Dr. Shahriyar.

Q⁵

A) What is Power Supply filter?
Discuss its operation with help of a Circuit diagram.

Ans:- A Power Supply filter ideally eliminates the fluctuations in the output voltage of a half wave or full wave rectifier & produces a constant level dc-voltage.


The filter is simply a capacitor connected from the rectifier output to ground.

The output of a filter is nearly smooth dc output voltage.

The small amount of fluctuation in the filter output voltage is called ripple.

(2)

Operation of Power Supply filter.

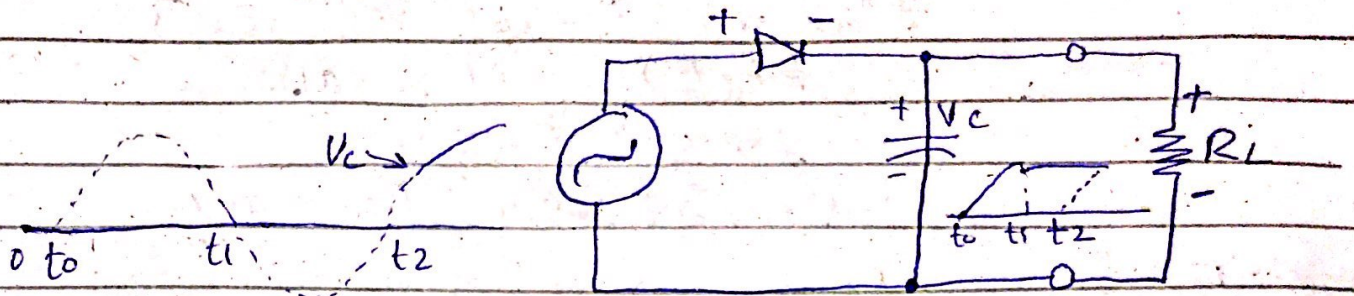

- Initial charging of the capacitor (diode is forward-biased) happens only once when power is turned on.
- The capacitor discharges through R_L after the peak of positive alternation when the diode is reverse-biased. The discharging occurs during the portion of the input voltage indicated by the solid dark blue curve.
- The capacitor charges back to peak of input when the diode becomes forward-biased. This charging occurs during the portion of the input voltage indicated by the solid dark blue curve.

(3)

Q⁵ b) How are n-type and p-type Semiconductors formed?

Ans: N-type & P-type Semiconductors are formed through a process called doping - which exist in extrinsic (impure) Semiconductor materials.

Doping is a process of controlled addition of impurities to intrinsic (pure) Semiconductor material so their conductivity can drastically increased.

N-type Semiconductors are formed by adding a pentavalent impurity atom in a Silicon Crystal Structure. For example antimony (Sb) is added & its extra electron becomes a free electron.

P-type Semiconductors are formed by adding a trivalent impurity to increase the no. of holes. For Silicon (Si), Boron (B), trivalent impurity is added.

(4)

Q⁵ c) What is a diode limiter? What is difference B/w a positive limiter & Negative limiter?

Ans:- Diode Circuit called limiters or clippers are sometimes used to clip off portions of signal voltage above or below certain levels.

There are two types of basic diode limiter/clippers positive limiter or negative limiter.

Diode Positive limiter limits or clips off the positive part of the input voltage whereas diode negative limiter limits or clips of a certain negative part of these input voltage just by turning around the diode of the circuit.

Q⁵ d) What component in a clamping circuit effectively act as battery?

Ans:- Capacitor is the component in a clamping circuit that effectively act as a battery.

(5)

Q⁵ e) When a 60 Hz Sinusoidal Voltage is applied to the input of a half wave rectifier what is output frequency?

Ans:- When a 60 Hz Sinusoidal Voltage is applied to the input of a half wave rectifier the output frequency remain same that is 60 Hz.

Q⁵ f) If the load resistance connected to a filtered power supply is decrease what happens to ripple voltage?


Ans:- If the load resistance connected to a filtered power supply is decrease then the ripple voltage is increased.

Q⁵ g) Discuss how Diode limiters & diode clampers differ in term of their function?


Ans:- Diode limiters are used to clip off portions of signal voltages above or below certain levels whereas clampers are circuits used to add a DC offset or a DC level to an AC voltage.
→ limiters are also called as clippers & clampers are also called as DC restorers.

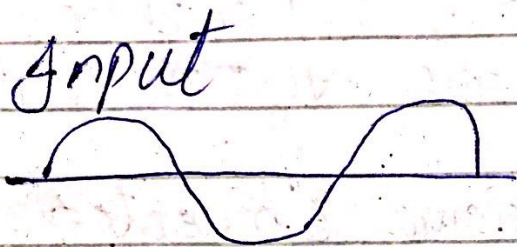(6)



→ Diode limiters are of two types. positive clippers or negative clippers & clampers are of two types; positive clammers or negative clammers.




Positive limiter output.

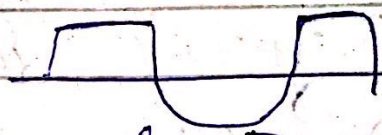


negative limiter output

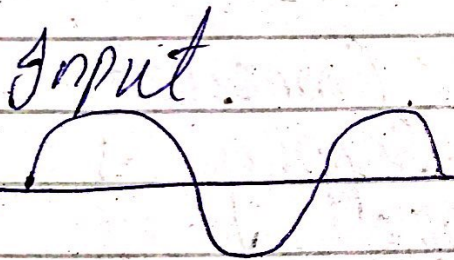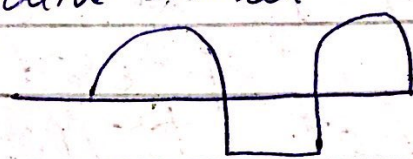

Positive clamper

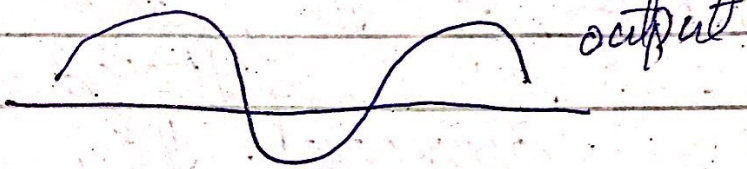

negative clamper

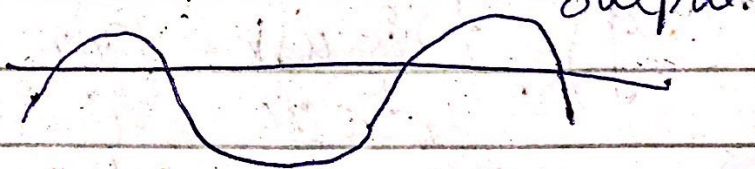

(7)

Q¹ a) What type of Circuit is this?

Ans: It is called Center-tapped full wave rectifier.

b) What is total Peak Secondary Voltage?

$$\text{Ans: } \frac{V_P}{V_S} = \frac{V_P(P)}{V_P(S)}$$


$$\frac{4}{1} = \frac{50}{V_P(S)}$$

$$V_P(S) = \frac{50}{4} = V_P(S) = 12.5$$

$$V_P(S) = 12.5V$$

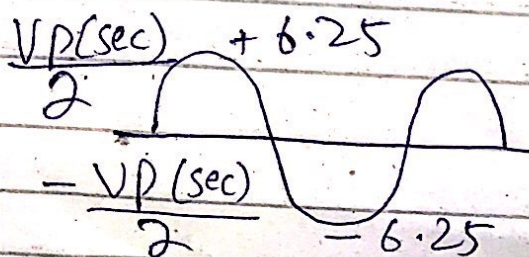c) Find the peak Voltage across each half of the Secondary?


As we know from above
Show that $V_P(\text{sec}) = 12.5V$ so we can
can be given



$$\frac{V_P(\text{sec})}{2} = \frac{12.5}{2} = 6.25V$$

(8)

Find Voltage across each half after rectification.
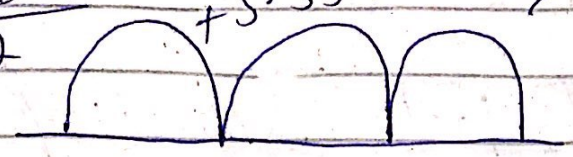
$$\frac{V_p(\text{sec}) - 0.7}{2} + 5.55\text{V} \Rightarrow \frac{V_p(\text{sec}) - 0.7}{2} = \frac{12.5 - 0.7}{2} = 5.55\text{V}$$


d) What is the peak current through each diode?

Let I_{D1} & I_{D2} be the current through diode D_1 & D_2

$$\text{Let } I_{D1} = I_{D2} = I_D$$

from the figure in the question

$$I_D = \frac{V_D}{R_L} = \frac{V_p(\text{sec}) - 0.7}{2 R_L}$$

Putting the values

$$= \frac{\left(\frac{12.5 - 0.7}{2}\right) \text{V}}{10\text{K}\Omega}$$

$$= \frac{5.55\text{V}}{10 \times 10^3 \Omega}$$

$$= 0.555 \times 10^{-3} \text{ A}$$

$$I_D = 0.555 \text{ mA}$$

(9)

e) What minimum PIV rating must the diodes have?

Each diode must have a minimum PIV rating of

$$PIV = 2 \left(\frac{V_P(\text{sec})}{2} - 0.7 \right) + 0.7V$$


$$PIV = 2 \left(\frac{12.5}{2} - 0.7 \right) + 0.7V$$

$$PIV = 2(5.55) + 0.7$$

$$PIV = 11.8V$$

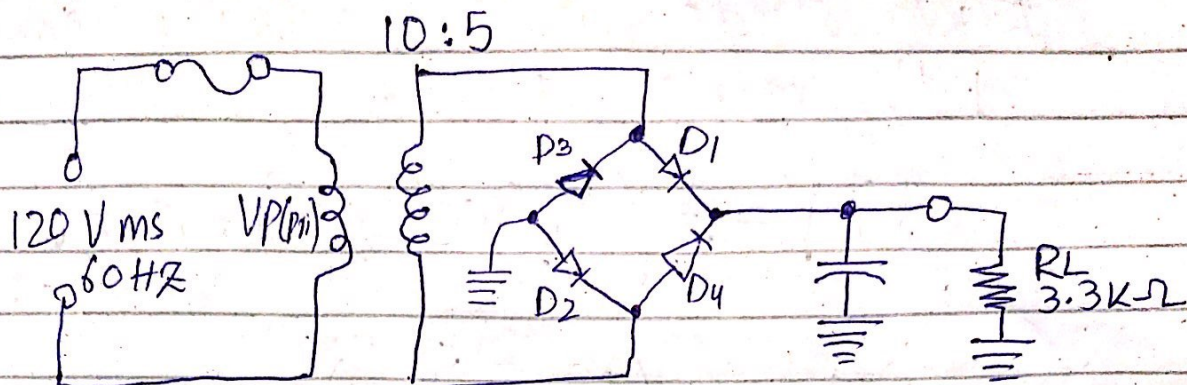(10)

Q² Determine the ripple factor for the filtered bridge rectifier with a load as indicated



As from turn ratio we know

$$n = \frac{N_s}{N_p} = \frac{5}{10} = 0.5$$

We also know that

$$V_p(\text{pri}) = \sqrt{2} \times V_{\text{rms}}$$

$$= 1.414213 \times 120$$

$$= 169.705 \approx 170\text{V}$$

$$V_p(\text{pri}) = 170\text{V}$$

Also for peak Secondary Voltage

$$\frac{N_s}{N_p} = \frac{V_p(\text{sec})}{V_p(\text{pri})}$$

$$\Rightarrow V_p(\text{sec}) = \frac{N_s}{N_p} (V_p(\text{pri}))$$

$$= \frac{5}{10} (170\text{V}) = 0.5 \times 170$$

$$V_p(\text{sec}) = 85\text{V}$$

The rectified Voltage before filter will be:

$$V_p(\text{rect}) = V_p(\text{sec}) - 1.4V$$

$$= 85V - 1.4 = 83.6V$$

As we know the output frequency of a full wave rectifier is twice as of the input i.e.: $60 \times 2 = 120 \text{ Hz}$.

So the approximate output peak to peak ripple Voltage will be:

$$V_r(\text{pp}) \cong \left(\frac{1}{fR_{\text{LC}}} \right) V_p(\text{rect})$$

$$= \left(\frac{1}{(120 \text{ Hz})(3.3 \text{ k}\Omega)(100 \mu\text{F})} \right) 83.6V$$

$$V_r(\text{pp}) = (0.0252525) 83.6V$$

$$V_r(\text{pp}) = 2.1110$$

The approximate output Voltage.

$$V_{\text{DC}} = \left(1 - \frac{1}{2fR_{\text{LC}}} \right) V_p(\text{rect})$$

$$V_{\text{DC}} = \left(1 - \frac{1}{2(120 \text{ Hz})(3.3 \text{ k}\Omega)(100 \mu\text{F})} \right) 83.6V$$

12

$$V_{DC} = (1 - 0.012626) 83.6 \text{ V}$$

$$V_{DC} = (0.987373) 83.6 \text{ V}$$

$$V_{DC} = 82.5444 \text{ V}$$

Now atleast we can calculate ripple factor

$$\gamma = \frac{V_r(\text{PP})}{V_{DC}}$$

Putting values.

$$\gamma = \frac{2.1111 \text{ V}}{82.5444 \text{ V}}$$




$$\gamma = 0.02557544$$

The Percent ripple will be

$$2.557\%$$

Answer

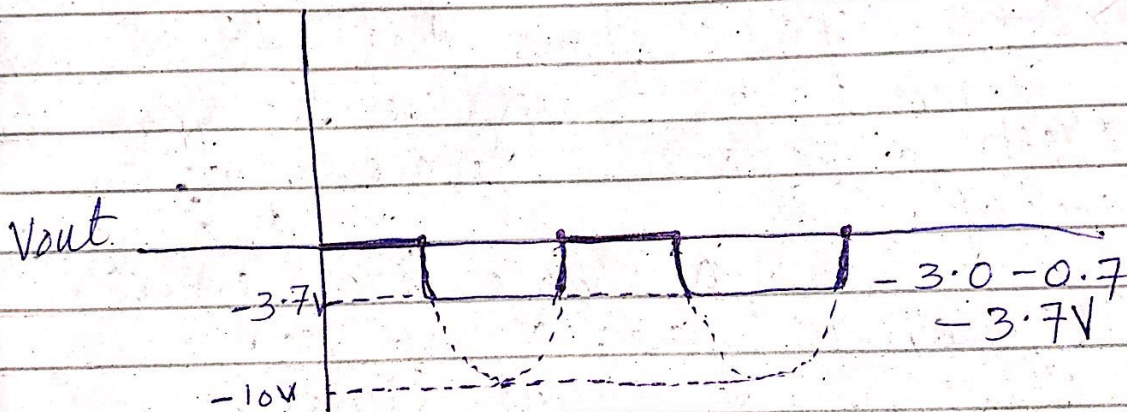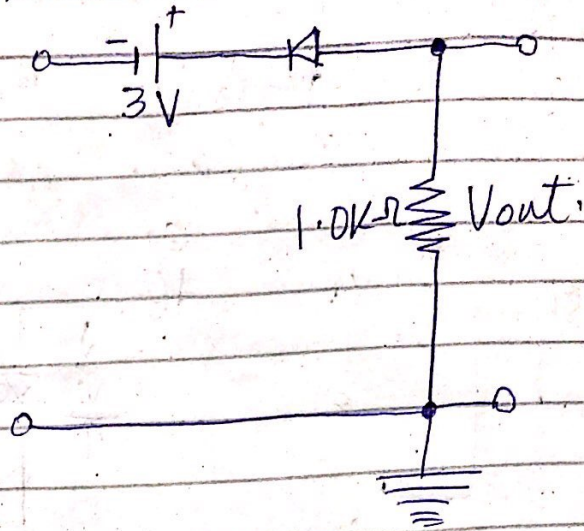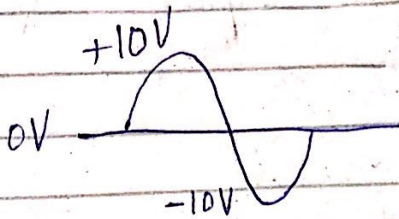Q³ Determine the output Voltage Wave form for the Circuit.




→ As from the figure we can see that there will be no output Voltage for the positive cycle as it is completely clipped as shown in V_{out} graph

AND for the negative half the wave form holds a negative value of $-V_{BIAS} - 0.7$

$$= -3.0 - 0.7 = -3.7V$$

Ans

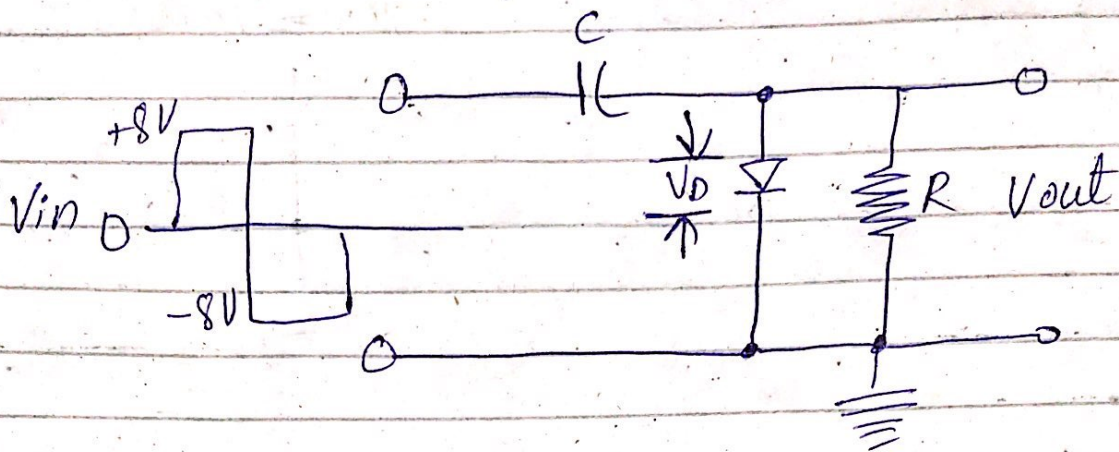Q. Determine the output Voltage Waveform for the Circuit. Assume RC time Constant is much greater than the period of the input.



→ The figure shows that the circuit is a negative clamper with a square wave input voltage. So, as a whole the negative clamper will add a -ve dc offset to the input signal.

