
IQRA NATIONAL UNIVERSITY



Linear circuit analysis (LAB)

NAME:	abdullah
ID NO:	16194
DATE:	may 11 th , 2020
SUBMITTED TO:	Sir Waleed Jan
ASSIGNMET :	Open ended lab




IQRA NATIONAL UNIVERSITY
DEPARTMENT OF ELECTRICAL ENGINEERING

Linear Circuit Analysis (LAB)

Open Ended Lab

Consider a DC circuit in which two lamps, one DC motor and one DC fan are connected in series-parallel combination to a 12V DC power supply as shown in the figure below. Resistances of two lamps are denoted by R_1 and R_2 respectively. Resistance of the coil of DC motor is denoted R_3 and resistance of the coil of DC fan is denoted by R_4 . Using any of the circuit analysis techniques, compute the below given parameters:

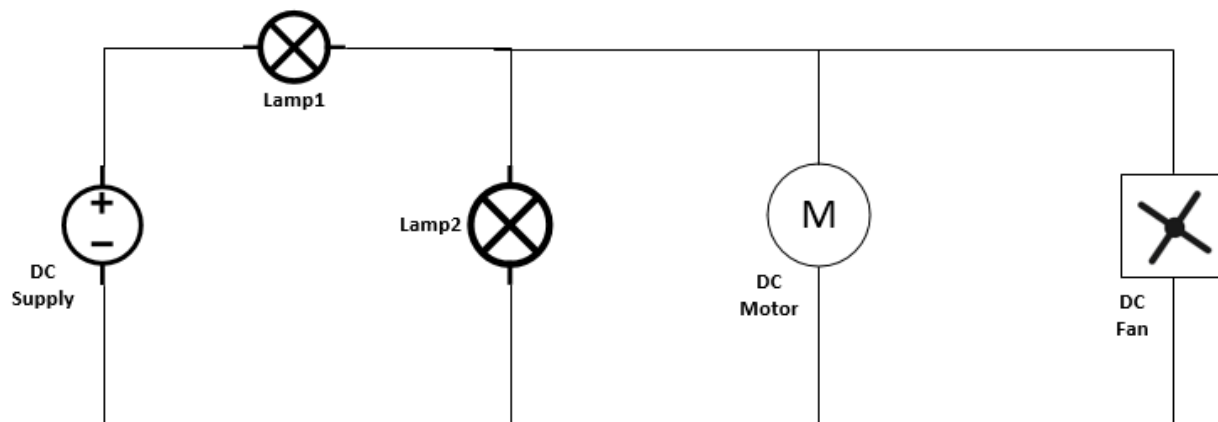
- 1) Current flowing through each lamp, DC motor and DC fan.
- 2) Voltage across each lamp, DC motor and DC fan.
- 3) Power loss in each lamp, DC motor and DC fan



Note:

- a) Each student should take different value of R_1 , R_2 , R_3 , and R_4 .
- b) Verify the result practically through a circuit simulation software.

Q no 12
ANSW figure

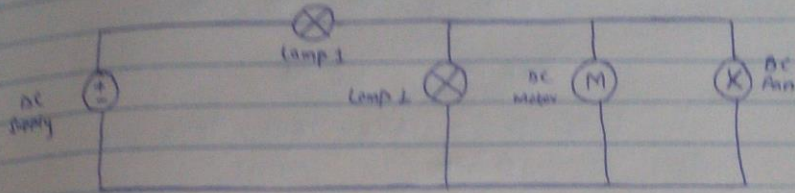


Required

- Current across each resistor = ?
- voltage across each resistor = ?
- Power absorbed by each = ?

Soln

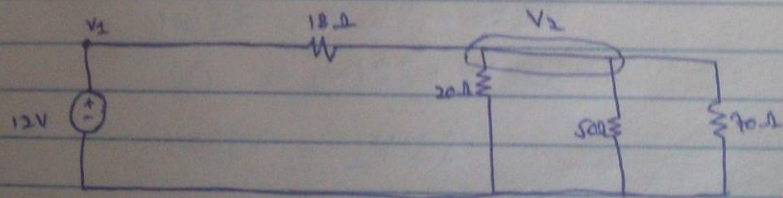Find Current through node 1
analysis for this identifying nodes.



Applying KCL on node 1

$$\frac{V_1 - V_2}{18} = 12$$

$$V_1 - V_2 = 216$$

Date: / /

Applying KCL on node 2.

$$\frac{V_2 - V_1}{18} + \frac{V_2}{20} + \frac{V_2}{50} + \frac{V_2}{20} = 0$$

Taking LCM

$$\frac{350V_2 - 350V_1 + 315V_2 + 126V_2 + 90V_2}{6300} = 0$$

$$-350V_1 + 881V_2 = 0$$

Taking eq ① $\times 350$

$$V_1 - V_2 = 216$$

$$350V_1 - 350V_2 = 75600 \quad \text{--- (a)}$$

adding eq (a) with eq ②

$$\cancel{350V_1} - 350V_2 = 75600$$

$$-350V_1 + 881V_2 = 0$$

$$531V_2 = 75600$$

$$V_2 = 142.4 \text{ V}$$

Putting V_2 in eq ①

$$V_1 - 142.4 = 216$$

$$V_1 = 358.4 \text{ V}$$

Date: / /

Current across resistor (1)

$$I = \frac{V_1}{R}$$

$$I = \frac{358.4}{18}$$

$$I_{10\Omega} = 19.9 \text{ A}$$

Current across resistor (2)

$$I_{20\Omega} = \frac{V_2}{R}$$

$$= \frac{142.4}{20}$$

$$I_{20\Omega} = 7.12 \text{ A}$$

Current across resistor (3)

$$I_{50\Omega} = \frac{142.4}{50}$$

$$I_{50\Omega} = 2.84 \text{ A}$$

Current across resistor (4)

$$I_{70\Omega} = \frac{142.4}{70}$$

$$I_{70\Omega} = 2.03 \text{ A}$$

Result:

$$\text{Current across bulb 1} = 19.9 \text{ A}$$

$$\text{Current across bulb 2} = 7.12 \text{ A}$$

$$\text{Current across fan} = 2.84 \text{ A}$$

$$\text{Current across Motor} = 2.03 \text{ A}$$

Date: / /

(ii) Finding voltage across each

voltage across R_1 :

$$V = IR$$

$$= (19.9)(18)$$

$$V = 358.2 \text{ V}$$

voltage across R_2 :

$$V = IR$$

$$= (9.12)(20)$$

$$V = 182.4$$

voltage across R_3

$$V = (2.84)(50)$$

$$V = 142$$

voltage across R_4

$$V = IR$$

$$= (2.03)(70)$$

$$V = 142.1$$

Result:

$$V \text{ across Bulb 1} = 358.2 \text{ V}$$

$$V \text{ across Bulb 2} = 142.4 \text{ V}$$

$$V \text{ across Motor} = 142 \text{ V}$$

$$V \text{ across Fan} = 142.1 \text{ V}$$

Date: / /

Finding Power across each resistor:

$$\begin{aligned}P(R_1) &= (I_1)(V_1) \\ &= (358.2)(19.9) \\ &= 7.6 \text{ mW}\end{aligned}$$

Power for

$$\begin{aligned}P(R_2) &= (I_2)(V_2) \\ &= (9.12)(142.4) \\ &= 0.403 \text{ mW}\end{aligned}$$

$$\begin{aligned}P(R_3) &= (I_3)(V_3) \\ &= (2.84)(141) \\ &= 0.403 \text{ mW}\end{aligned}$$

$$\begin{aligned}P(R_4) &= I_4 V_4 \\ &= (2.03)(142.1) \\ &= 0.288 \text{ mW}\end{aligned}$$

Results

$$P_1 = 7.6 \text{ mW}$$

$$P_2 = 0.403 \text{ mW}$$

$$P_3 = 0.403 \text{ mW}$$

$$P_4 = 0.288 \text{ mW}$$

Circuit by simulation:

