
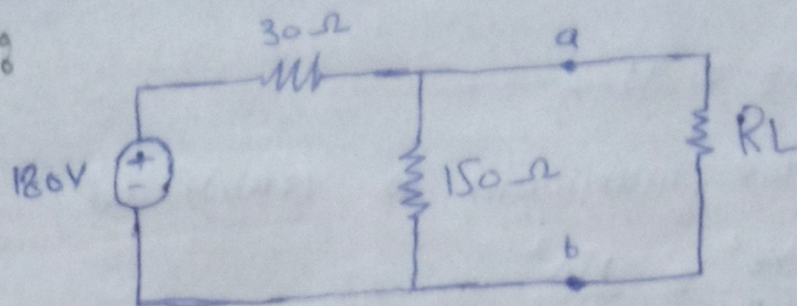


Ans (4) \therefore

Sol:

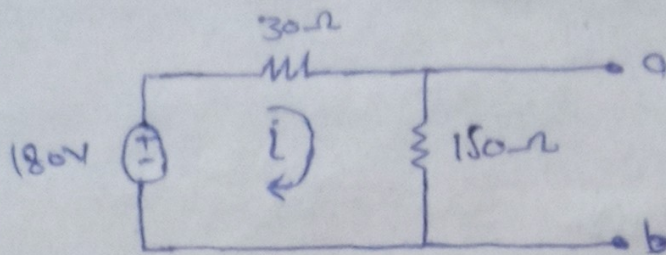

let us determine thevenine equivalent ckt as seen from a-b




$$I = \frac{180}{30+150} \Rightarrow \frac{180}{180} \Rightarrow \boxed{1A}$$

$$V_{an} = V_{oh} = 150 \times 1 \Rightarrow \boxed{150V}$$

To find R_t , deactivate 180V source,

$$R_t = \frac{30 \times 150}{30+150} \Rightarrow \boxed{25\Omega}$$

The thevenine equivalent

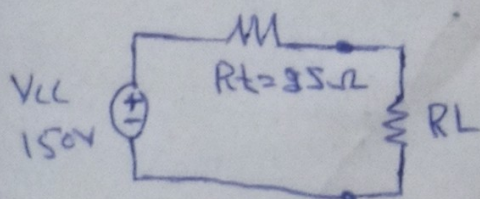

The maximum is transferred when

$$R_L = R_t = 25 \Omega$$

Then the maximum is transferred

$$P_{\max} = \frac{V_t^2}{4R_L} = \frac{150^2}{4 \times 25}$$

$$P_{\max} = 2.25 \text{ Watts.}$$

The thevenin source V_t provide total power of

$$P_t = 150 \times i = 150 \left(\frac{150}{25+25} \right)$$

$$P_t = 450 \text{ Watts} \Rightarrow \text{Ans}$$

Q1

Ans

Part (A): Star to Delta Transformation.

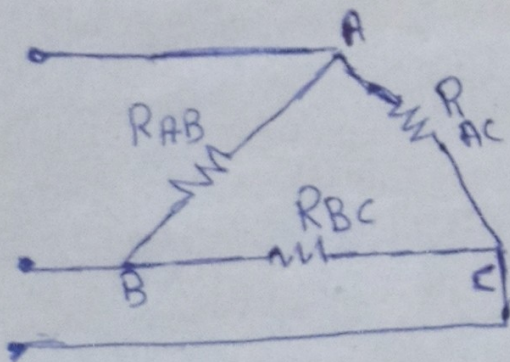


Fig = A

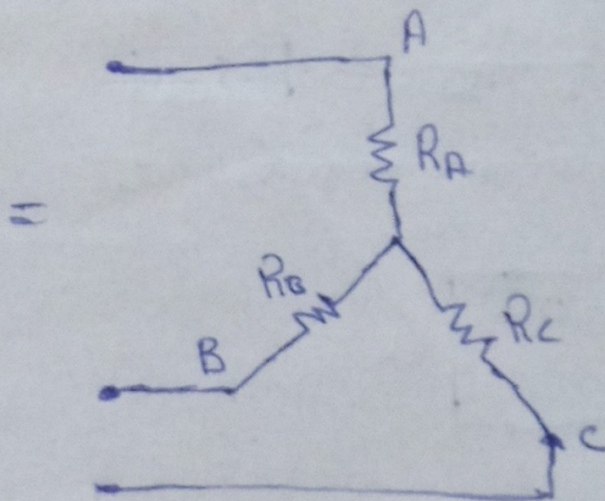


Fig B.

Let R_{AB} , R_{BC} and R_{AC} be the three resistance as connected to delta as shown in fig (a) R_A , R_B and R_C are the three equivalent resistance as connected in star as shown in fig (b)

The equivalent resistance between A and B

$$\therefore R_A + R_B = \frac{R_{AB}(R_{BC} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (1)}$$

Between B and C

$$R_B + R_C = \frac{R_{BC}(R_{CA} + R_{AB})}{R_{AB} + R_{BC} + R_{AC}} \quad \text{--- (2)}$$

Between C and A

$$R_C + R_A = \frac{R_{AC}(R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{AC}} \quad \text{--- (3)}$$

eq (1) & (2)

$$2R_A = \frac{2R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{AC}} \quad \text{--- (4)}$$

In similar way $\boxed{R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{AC}}} \Rightarrow \textcircled{7}$

and $\boxed{R_C = \frac{R_{BC} R_{AC}}{R_{AB} + R_{BC} + R_{AC}}} \Rightarrow \textcircled{8}$

② Star to delta Transformation

From eq ⑤, ⑦ and ⑧ we write

$$R_{AB} + R_{BC} + R_{CA} = \frac{R_{AB} R_{BC} R_{CA} (R_{AB} + R_{BC} + R_{CA})}{(R_{AB} + R_{BC} + R_{CA})^2}$$

Sub eq ⑤

$$= \frac{R_{BC}}{\sum R_{AB}} \times R_A \sum R_{AB}$$

$$= R_A R_{BC}$$

$$\therefore R_{BC} = \frac{R_A R_{AB} + R_{BC} + R_{CA} R_A}{R_A} \quad \text{--- } \textcircled{10}$$

In similar way.


$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C} \quad \text{--- } \textcircled{11}$$

In A circuit:

$$Z_A = \frac{Z_{AB} Z_{CA}}{\sum Z_{AB}}, \quad Z_B = \frac{Z_C Z_{AB}}{\sum Z_{AB}}$$

$$Z_C = \frac{Z_{CA} Z_{CB}}{\sum Z_{AB}}$$

Ans ③

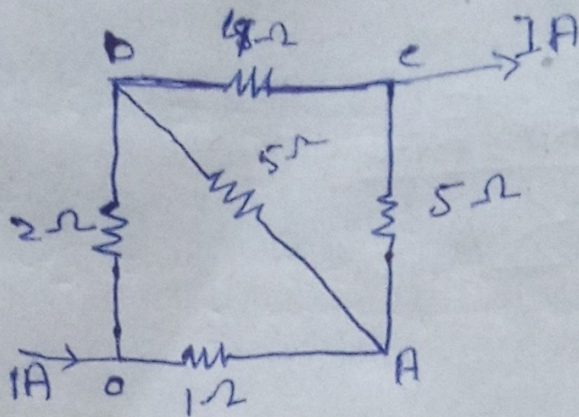


\Rightarrow Junction Rules

① $I = I_1 + I_2$

$I_1 = I_3 + I_4$

$I_2 + I_3 = I_5$

$I_4 + I_5 = I$

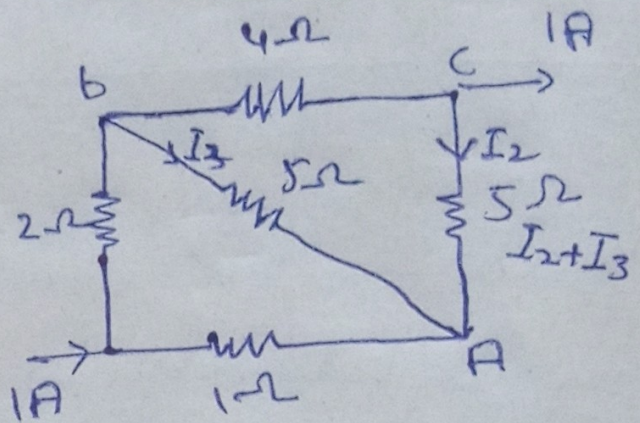

Now

1) $I_5 - I(1) - (I_1 - I_3)(1) = \phi$

2) $I_3 - I_3(1) - (I_2 + I_3)(2) = \phi$

3) $-I_1(1) = I_3(1) + I_2(1) = \phi$

3) $I_2 = I_1 + I_3$

$I_3 = 2I_1 - I_3$ ←

$I_3 = 3(I_1 + I_3) + 2I_3$

$I_3 = 3I_1 + 5I_3$ ←

Ans (2)


 \Rightarrow Laplace transform of impulse function

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$$= \int_0^{\infty} 1 \cdot e^{-st} dt = -\frac{1}{s} [e^{-st}]_0^{\infty}$$

$$= -\frac{1}{s} [0 - 1]$$

$$= \frac{1}{s}$$

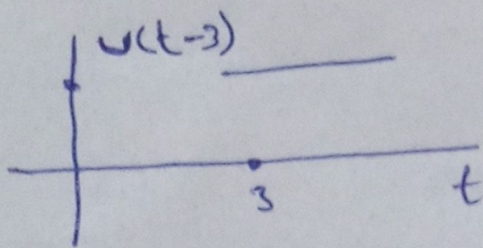 \Rightarrow Laplace transform of unit function.

$$u(t) = 1 \text{ if } t \geq 0$$

$$u(t-3) = 1 \text{ if } t-3 \geq 0$$

$$\rightarrow t \geq 3$$

$$u(t) = 0 \text{ if } t < 0$$

$$u(t-3) = 0 \text{ if } t-3 < 0$$

$$\rightarrow t < 3$$

⇒ Laplace transform of Ramp function

$$r(t) = t u(t)$$

$$R(s) = \int_0^{\infty} \underbrace{t e^{-st}}_{dv} dt \quad \underbrace{=}_{\text{parts}} \quad \frac{t e^{-st}}{-s} \Big|_0^{\infty} - \int_0^{\infty} \frac{e^{-st}}{-s} dt$$

$$\underbrace{=}_{\text{parts}} \frac{1}{s} \int_0^{\infty} e^{-st} dt = \frac{1}{s} \cdot \left(\frac{e^{-st}}{-s} \Big|_0^{\infty} \right)$$

$\text{Re}[s] > 0$

$$\underbrace{=}_{\text{parts}} \frac{1}{s} \cdot \left(0 + \frac{1}{-s} \right) = \frac{1}{s^2}$$

$\text{Re}[s] > 0$