


Course Title: Electrical Network Analysis

Module: 4th

Instructor: Dr. Shahryar Shafique

Name: Danish Hayat

Student ID: 14566

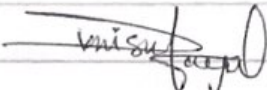
Student Signature: 

Date: 13th April, 2020

## Question No: 1

The switch in figure has been in position A for a long time. At  $t=0$  the switch moves to B. Determine  $v(t)$  for  $t > 0$  & calculate its value at  $t = 2s$  &  $8s$ .

Figure:

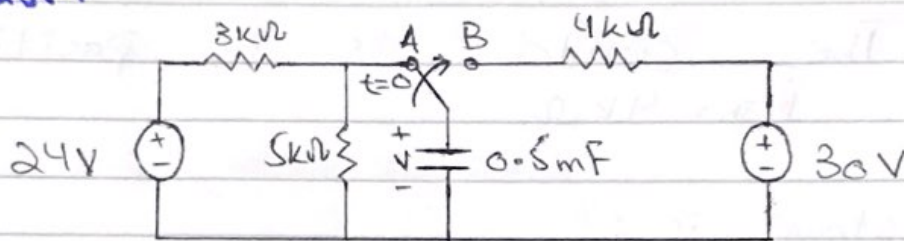

Solution:

For  $t < 0$ :

The switch is at position A. The capacitor acts like an open circuit to dc, but  $v$  is the same as the voltage across  $5k\Omega$  resistor. Hence the  $v$  across the capacitor just before  $t=0$  is obtained by voltage division as;

$$v(0^-) = \frac{5}{5+3} (24) = 15 \text{ V}$$

As the capacitor can't change instantaneously.

$$v(0) = v(0^+) = 15 \text{ V.}$$

For  $t > 0$ :

The switch is in position B. The  $R_{th} = 4 \text{ k}\Omega$

Time constant is;

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\tau = 2 \text{ s}$$

Since the capacitor acts like an open circuit to dc at steady state;

$$v(\infty) = 30 \text{ V.}$$

Thus

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$= 30 + (15 - 30) e^{-t/2}$$

$$= (30 - 15 e^{-0.5t}) \text{ V}$$

At  $t = 2$ :

$$V(2) = 30 - 15e^{-\frac{2}{2}}$$

$$= 30 - 15e^{-1}$$

$$V(2) = 24.48 \text{ V}$$

At  $t = 8$ :

$$V(8) = 30 - 15e^{-\frac{8}{2}}$$


$$= 30 - 15e^{-4}$$

~~$$V(8) = 29.7$$~~

$$V(8) = 29.72$$

**Question No: 2:**

Determine the inductor current for both  $t > 0$  &  $t < 0$  for the circuit.

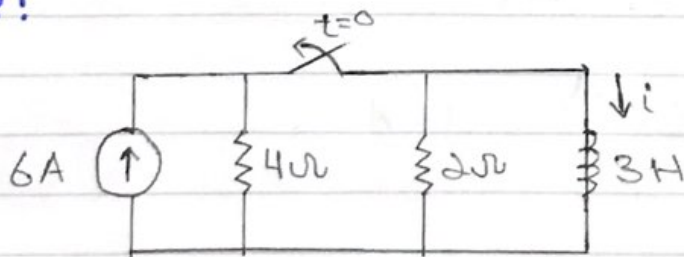**Figure:**

Solution:

For  $t < 0$ :

The switch is closed & the inductor acts as short circuit

Therefore inductor current

$$i = 6A$$

For  $t > 0$ :

The switch is opened & the time constant  $\tau = \frac{L}{R}$

$$\tau = \frac{3}{2}$$

Now the inductor current  $i(t) = \frac{-t}{\tau}$


$$i(t) = 6e^{-\frac{t}{3/2}}$$

$$i(t) = 6e^{-2t/3} \text{ (A)}$$

## Question No 5:

Find  $v(t)$  &  $i(t)$  in the circuit in figure.

Figure:

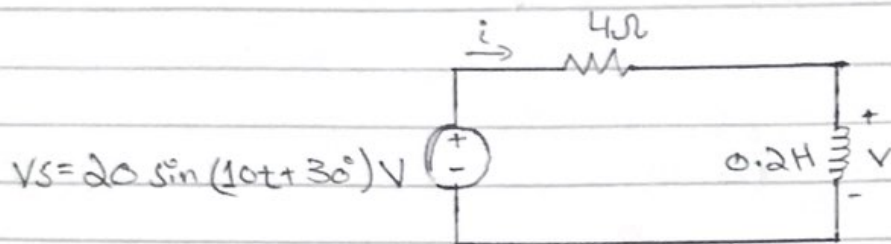

Solution:

For  $i(t)$ 

From the voltage source

$$v_s = 20 \sin(10t + 30^\circ) \text{ V}$$

$$v_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V}$$

$$v_s = 20 \cos(10t - 60^\circ) \text{ V}$$

$$v_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 10 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 10 \times 0.2$$

$$0.2 \text{ H} = j2 \Omega$$

Given circuit can be represented as;

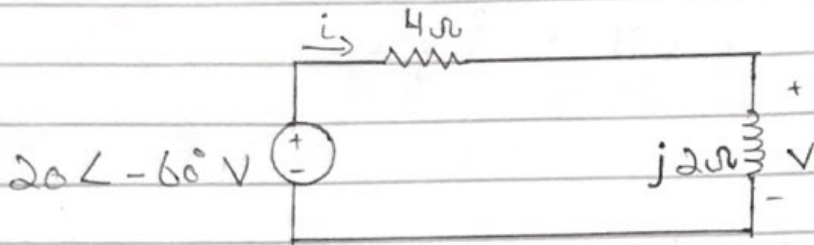

from the above circuit,

$$Z = 4 + j2\Omega$$

Hence, the current is,

$$i = \frac{20\angle -60^\circ}{4 + j2}$$

$$i = \frac{20\angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$

$$i = \frac{20\angle -60^\circ}{4.472 \angle 26.57^\circ}$$

$$i = 4.472 \angle -86.57^\circ$$

(converting) this into time domain.

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

For  $v(t)$  :

From the circuit

Voltage across the inductor is,

$$V = j\omega \times i$$

$$V = j2 \times (4.472 \angle 86.57^\circ)$$

(converting polar form to rectangular form we get;

$$V = j2 \times (0.26756 - j4.464)$$

$$V = 8.928 + j0.53512$$

(converting rectangular form to polar form



$$V = \left( \sqrt{(8.926)^2 + (6.53512)^2} \right) \angle \tan^{-1} \left( \frac{6.5312}{8.928} \right)$$

$$V = 8.944 \angle 3.4^\circ$$

Converting this into time domain

$$V(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$V(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$V(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$

### Question No 3:

A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

find the response when  $L = 0.5 \text{ H}$ ,

$R = 4 \Omega$  &  $C = 0.2 \text{ F}$ ,

Let  $i(0) = 1 \text{ A}$ ,  $\frac{di(0)}{dt} = 0$

**Solution:**

The step response of the branch voltage of the given RLC circuit is described by;

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by  $L$ ;

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{10}{L}$$

ming by  $\frac{C}{C}$

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{10C}{LC}$$

As  $C = 0.2F$ , thus;

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{2}{LC}$$

Substitute;

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \dots (i)$$

The general form for source-free RLC is given by.

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC} \dots (2)$$

Comparing 1 & 2 we get,

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \rightarrow (4)$$

$$\frac{I_s}{LC} = 20 \rightarrow (5)$$

From (3),  $\alpha$  is given by;

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/sec} \rightarrow (6)$$

The natural frequency  $\omega_0$  is given by;

$$\omega_0 = \sqrt{\frac{1}{LC}} \rightarrow \text{⊗}$$

From (4),

$$\omega_0 = \sqrt{10} \text{ rad/sec} \rightarrow (7)$$

From (6) & (7):

$$\because \alpha > \omega_0$$

$\therefore$  The circuit is <sup>is</sup> overdamped

The roots of characteristic equation are given by;

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 + \sqrt{4^2 - 10}$$

$$= -4 + \sqrt{6} \text{ rad/s}$$

And,

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 - \sqrt{4^2 - 10}$$

$$= -4 - \sqrt{6} \text{ rad/s}$$

From (5), the steady current is given by

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2 = 2 \text{ A} \rightarrow (8)$$

The current for overdamped is given by;

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

Substitute  $t=0$ :

$$i(0) = I_s + A_1 + A_2$$

Substitute:

$$1 = 2 + A_1 + A_2$$

Thus,

$$A_1 + A_2 = -1 \rightarrow (10)$$

From 9, find  $\frac{di(t)}{dt}$ ,

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute  $t=0$ :

$$\frac{di(0)}{dt} = A_1 s_1 e^{s_1 \cdot 0} + A_2 s_2 e^{s_2 \cdot 0}$$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute the values;

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0 \rightarrow (11)$$

Solving (10) & (11) simultaneously

$$A_1 = -1.316$$

$$A_2 = 0.316$$

Substitute in (9)

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t} \text{ A}$$

### Question No 4:

A series RLC circuit has

$$R = 100 \Omega$$

$$L = 240 \text{ H}$$

$$C = 10 \text{ mF}$$

if the input voltage is  $v(t) = 10 \cos 2t$ ,  
find the current flowing through  
the circuit.

Solution:

The input voltage is,

$$v(t) = 10 \cos 2t \text{ V}$$

$$\text{Amplitude} = V_m = 10 \text{ V}$$

$$\text{Angular frequency} = 2 \text{ rad/s}$$

$$\text{Phase angle, } \phi = 0^\circ$$

So

Phasor for the voltage  $v(t)$ :

$$v(t) = 10 \angle 0^\circ \text{ V}$$

Now for inductive reactance.

$$X_L = \omega L$$

$$\text{So } \omega = 2 \text{ rad/s, } L = 240 \text{ H}$$

$$X_L = (2)(240)$$

$$X_L = 480 \Omega$$

Now for capacitive Reactance

$$X_c = \frac{1}{\omega C}$$

$$\omega = 2 \text{ rad/s}, \quad C = 10 \text{ mF}$$

$$\frac{1}{2(10 \times 10^{-3})}$$

$$\frac{1}{2 \times 10^{-2}}$$

$$\frac{1 \times 10^2}{2}$$

$$X_c = 50 \Omega$$

Now for impedance;

$$Z = R + jX_L - jX_c$$

$$R = 100 \Omega, \quad X_L = 480 \Omega, \quad X_c = 50 \Omega$$

putting in equation



$$Z = (100 + 480 - 50) \Omega$$

$$Z = (100 + j430) \Omega$$

Represent "Z" in phasor form

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left( \frac{430}{100} \right)$$

$$= \sqrt{10,000 + 184,900} \angle \tan^{-1} (4.3)$$

$$= \sqrt{194,900} \angle \tan^{-1} (4.3)$$

$$Z = 441.47 \angle 76.9^\circ \Omega$$

Now for current flowing in the circuit;

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ, \quad Z = 441.47 \angle 76.9^\circ \Omega$$

putting in equation

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.9^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.9^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.9^\circ \text{ A}$$

$$= 22.6 \angle -76.9^\circ \text{ mA}$$

So,

The general expression for " $i$ "

$$i = 22.6 \cos(\omega t - 76.9^\circ) \text{ mA.}$$

