

NAME

M. SALMAN NASIR

ID

16664

LCA (Lab)

OPEN ENDED
LAB


SUBMITTED TO

"SIR WALID
JAN"

DATED

27-June-2020

* _____ *

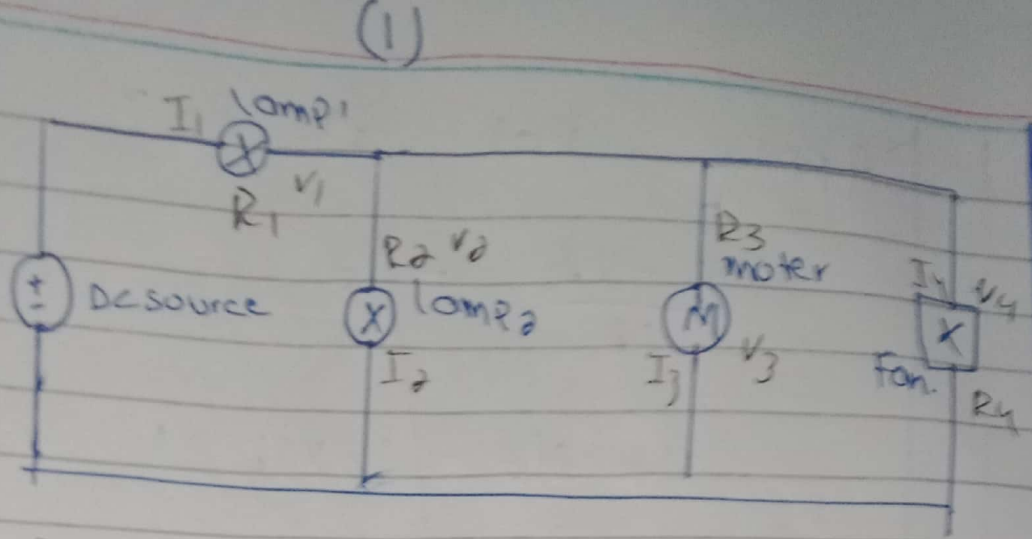

find
 current flow through
 each component
 voltage across each
 component
 power loss in each
 if source = 12V

Solution :-
 Let


$$R_1 = 10 \text{ ohm}$$

$$R_2 = 4 \text{ ohm}$$

$$R_3 = 50 \text{ ohm}$$

$$R_4 = 25 \text{ ohm}$$

Re draw Fig & Identify nodes.

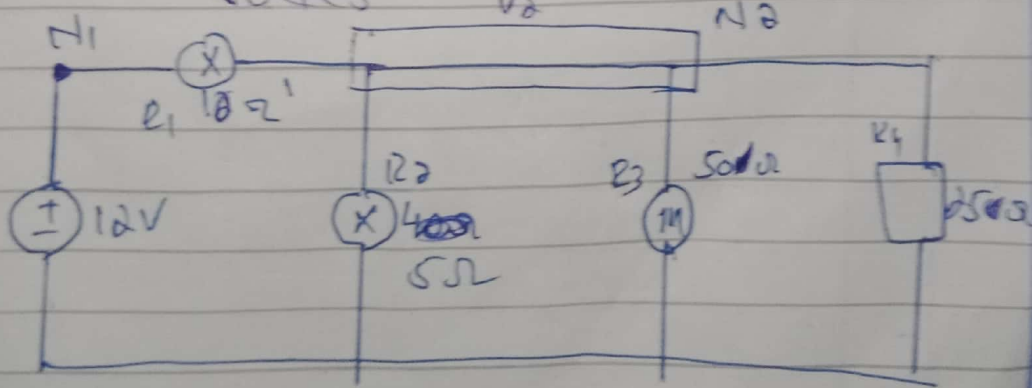

P-T-O

(2)

Apply KCL on V_1

$$\frac{V_1 - V_2}{10} = 12$$

$$V_1 - V_2 = \frac{120}{1} \rightarrow \text{(i)}$$

at node 2:-

$$\frac{V_2 - V_1}{10} + \frac{V_2}{5} + \frac{V_2}{50} + \frac{V_2}{25} = 0$$

Taking LCM:-

$$\frac{5V_2 - 5V_1 + 10V_2 + V_2 + 2V_2}{50} = 0$$

$$-5V_1 + 18V_2 = 0 \rightarrow \text{(ii)}$$

multiply eq (i) by 5 &
Add

$$\begin{aligned} 5V_1 - 5V_2 &= 600 \\ -5V_1 + 18V_2 &= 0 \end{aligned}$$

$$23V_2 = 600$$

$$V_2 = 26.08 \rightarrow \text{A}$$

(3)

put $V_2 = 26.8$ in ①

$$V_1 - V_2 = 120$$

$$V_1 - 26.8 = 120$$

$$V_1 = 120 + 26.8$$

$$V_1 = 146.8 \text{ V} \rightarrow \star \star$$

Current through each component

\star Current through lamp R_1 -

as $V = IR$

$$V/R = I$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{146.8}{10}$$

$$I_1 = 14.68 \text{ A}$$

(4)

Current through R_2 :-

$$I_2 = \frac{V_2}{R_2}$$

$$I_2 = 26/50$$

$$I_2 = 0.52 \text{ A}$$

Current through R_3

$$I_3 = \frac{V_3}{R_3}$$

$$I_3 = 26/50$$

$$I_3 = 0.5 \text{ A}$$

Current through R_4

$$I_4 = \frac{V_4}{R_4}$$

$$I_4 = 26/25$$

$$I_4 = 1.04 \text{ A}$$

(5)

Voltage across each
Component :-

From eq * & **

$$V_1 = 146 \text{ V}$$

$$V_2 = 26 \text{ V}$$

From Fig

V_1 voltage across lamp

& V_2 voltage across
lamp -

$$V_4 = 146 \text{ V}$$

$$V_2 = 26 \text{ V}$$

Also

lamp & motor and fan
are in parallel hence
voltage will be same

$$V_2 = V_3 = V_4 = 26 \text{ volt}$$

(6)

power loss :-

power loss at L_{ami} :

$$P = I \cdot V$$

$$P_1 = I_1 \cdot V_1$$

$$P_1 = 14.6 \times 146$$

$$P_1 = 2131 \text{ watt}$$

P at lamp :-

$$P_2 = I_2 \cdot V_2$$

$$= 5.2 \times 26$$

$$P_2 = 135.2 \text{ watt}$$

P at motor :-

$$P_3 = I_3 \times V_3$$

$$= 0.5 \times 26$$

$$P_3 = 13 \text{ watt}$$

$$P_4 = I_4 \times V_4$$

$$P_4 = 27.04 \text{ watt}$$

(7)

Result :-

Voltage	across	lamp 1	$V_1 = 146V$
//	//	lamp 2	$V_2 = 28V$
//	//	motor	$V_3 = 28V$
//	//	Fan	$V_4 = 28V$

Current	through	lamp 1	$I_1 = 14.6A$
//	//	lamp 2	$I_2 = 5.2A$
//	//	motor	$I_3 = 0.5A$
//	//	Fan	$I_4 = 1.04A$

power loss :-

power	loss at	lamp 1	$P_1 = 2131W$
//	//	lamp 2	$P_2 = 135.2W$
//	//	Motor	$P_3 = 13W$
//	//	Fan	$P_4 = 27.04W$

