

HASEEB ULLAH

ID# 16314

SUBJECT : LCA

TEACHER : Sir Sohail ABBAS

2ND Semester (final paper)

QUESTION #01


find the value of i_x for the circuit using

i) Nodal Analysis

ii) Mesh Analysis

iii) superposition theorem

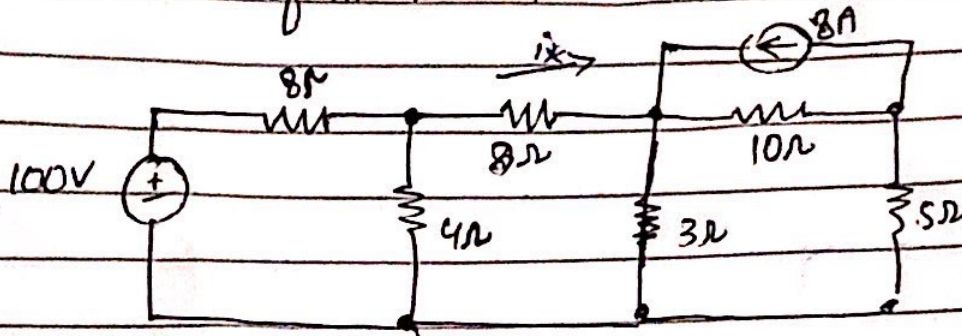iv) compare the number of steps and degree of easiness of all the three methods with each other.



Solution:- (i) Nodal analysis

Apply KCL on node 1

$$v_1 \frac{-100}{8} + v_1 \frac{1}{4} + v_1 \frac{-v_2}{2} = 0$$

$$v_1 - 100 + 2v_1 + 4v_1 - 4v_2 = 0$$

$$7v_1 - 4v_2 = 100 \quad \text{--- (1)}$$

Apply KCL on Node 2:

$$v_2 \frac{-v_1}{2} + v_2 \frac{1}{3} + v_2 \frac{-v_3}{18} = 8$$

$$30v_2 - 30v_1 + 20v_2 + 3v_3 - 3v_3 = 8$$

60

Page # L

$$-30V_1 + 53V_2 - 3V_3 = 480 \quad \text{--- (2)}$$

Apply KCL on node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (4)}$$

Taking eq (2)

$$-V_2 + 3V_3 = -80$$

$$\frac{V_3 - V_2 - 80}{3} \quad \text{--- (5)}$$

putting eq (4) and (5) in eq (2)

$$-30(0.57V_2 + 14.28) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.01V_2 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

putting in eq (a)


$$V_2 = \frac{4(20.31) + 100}{7}$$

$$V_2 = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

Mesh analysis:

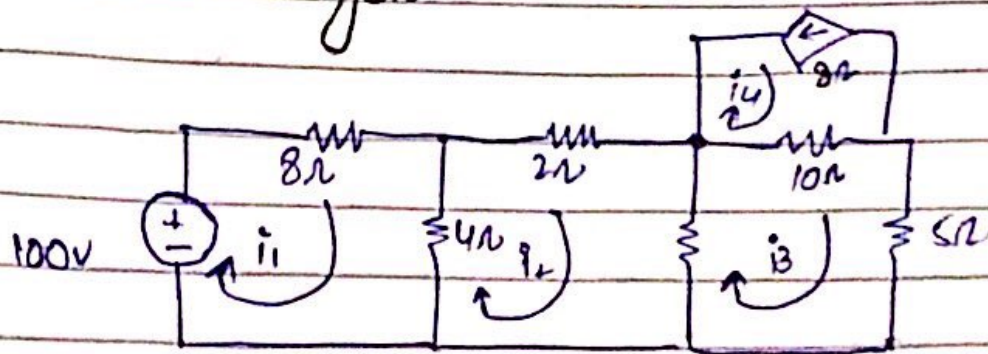

Apply KVL on loop 1

$$8i_1 + 4(i_2 - i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_2 - 4i_2 = 100 \quad \text{--- (1)}$$

Applying KVL on loop 2

$$0i_2 + 4(i_2 - i_2) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_2 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop (3)

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (b)}$$

putting eq (a) and (b) on eq (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

$$7.2i_2 = -100$$

$$\Rightarrow i_2 = 20/7.2$$


$$\Rightarrow i_2 = i_x$$

$$\Rightarrow i_2 = 2.79 \text{ A}$$

$$\Rightarrow \boxed{i_x = 2.79 \text{ A}}$$

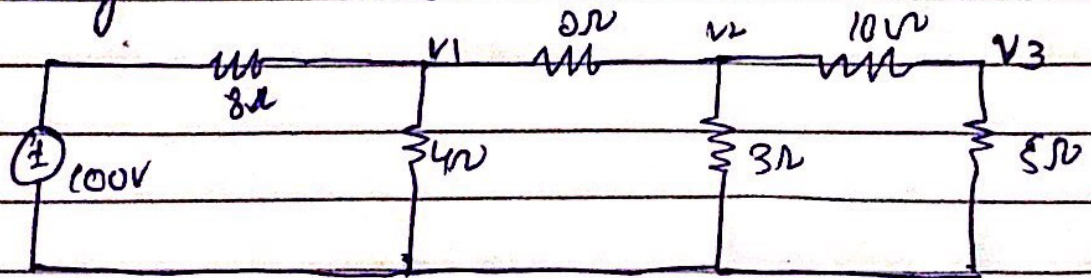iii) Superposition Theorem:-

first we remove the current source and then making it an open circuit Re drawing the circuit.



Apply KCL on node 1

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$\frac{V_1 - 100 + 4V_1 - 4V_2 + 2V_3}{8} = 0$$

$$7V_1 - 4V_2 + 100 = 0 \quad \text{--- (1)}$$

Apply KCL on node 2:-

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 + 53V_2 - 3V_3 = 0$$

Apply KCL on node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + V_3}{10} = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) and (3)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (4)}$$

$$\text{Now } -V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3}V_2 \quad \text{--- (5)}$$

putting an eq (4)

$$-30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 428.4 - 4V_2 + 0.66V_2 = 0$$

$$V_2 = -20.95$$


putting in eq (a)

$$v_2 = 2.31$$

$$i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = 11.63$$

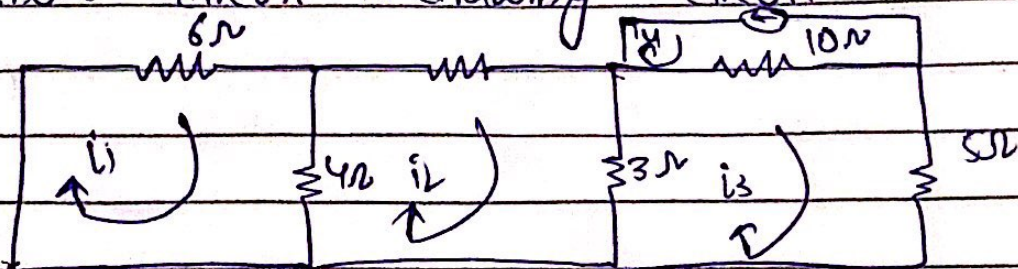now removing voltage source and making it short circuit re-drawing circuit.



$i_1 = 8A \Rightarrow$ Apply KVL on loop 1

$$8i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Apply KVL on loop 2

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop 3

$$10i_3 + 5i_3 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33 i_2 \quad \text{--- (a)}$$

Taking eq (b)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (b)}$$

$$-4(0.33 i_2) + 9i_2 - 3(0.16 i_2 - 4.44) = 0$$

$$1.32 i_2 + 9i_2 - 0.48 i_2 + 13.32 = 0$$

$$i_2 = 1.35 \text{ A}$$


$$\text{Now } i_x = i_1 + i_2$$

$$i_x = 1.44 + 1.35$$

$$i_x = 2.79 \text{ A}$$

$$\text{Result} = \boxed{i_x = 2.79 \text{ A}}$$

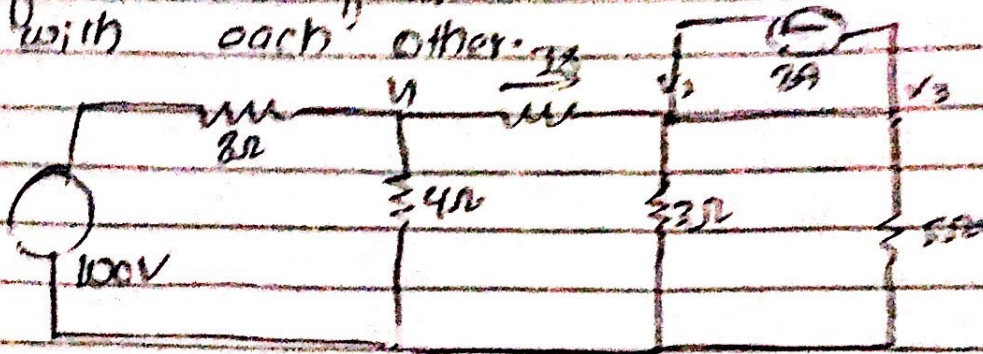compare the number of steps and degree of easiness of all the different methods with each other.



The number of steps in nodal and mesh analysis are almost equal but in superposition the number of mesh and nodal analysis.


Degree of easiness:

According to opinion mesh analysis is easier than nodal analysis and superposition theorem.

(12)

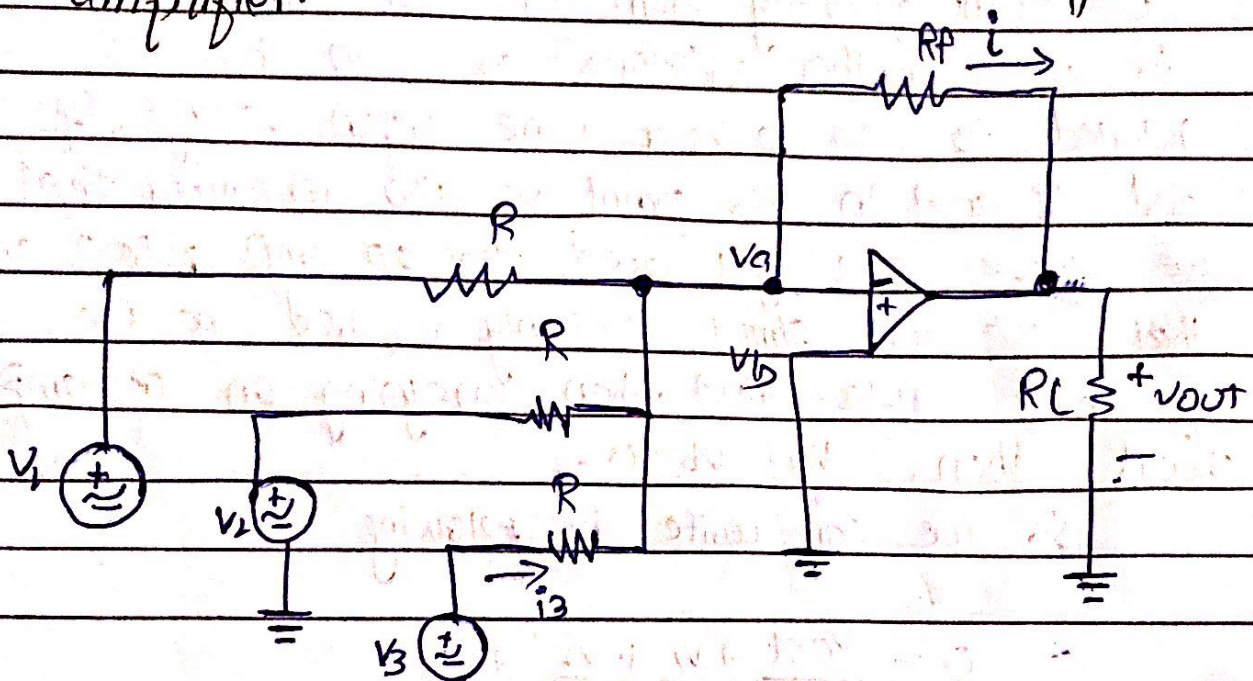Question #03

Obtain an expression for V_{out} in terms of V_1 , V_2 and V_3 for the op amp circuit in figure, also known as a summing amplifier.



In this simple summing amplifier circuit, the output voltage (V_{out}) now becomes proportional to the sum of input voltages V_1 , V_2 , V_3 etc.

Now,

$$i = i_1 + i_2 + i_3$$

So we can write the following equation at the node labeled V_a :

$$0 = \frac{V_a - V_{out}}{R_f} + \frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - V_3}{R}$$

This all equation contains both input voltages and V_{out} voltage. ~~but~~ also contain another voltage that is nodal voltage V_a . To remove this unknown quantity from our expression, we need to write another additional equation that is related to V_a to V_{out} & the input voltage, R_f and R and I_n . In this point we also remember that we have not yet used ideal op amp rule 2, and that we will almost certainly required the use of both rules. And when analyzing an op amp circuit then, $V_a = V_b = 0$.

So we can write the following

$$0 = \frac{V_{out}}{R_f} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

from Rearranging, we obtain the following expression for V_{out} :


$$V_{out} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

In this special case $V_2 = V_3 = 0$ we see that this equation was derived essentially the same circuit.

Question #02

Consider the $200\ \Omega$ resistor in figure as load resistor and develop.

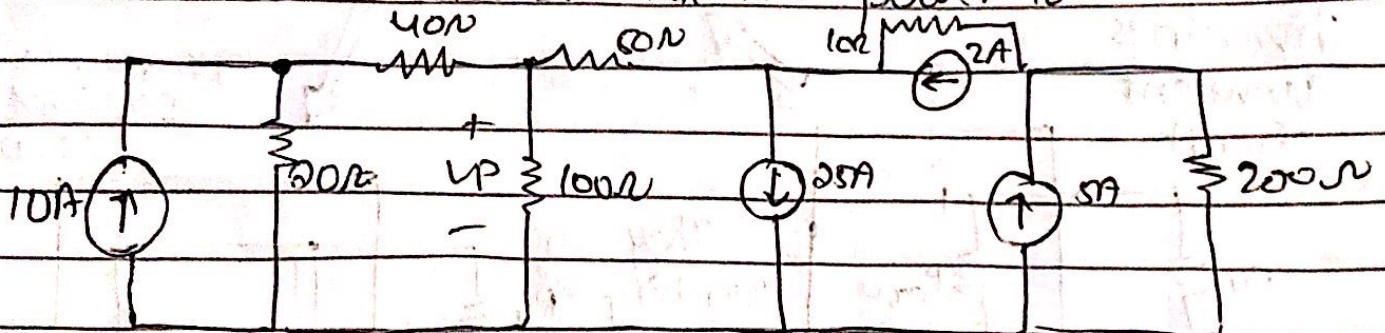
- i) Thevenin equivalent circuit
- ii) Norton equivalent circuit
- iii) find out what value of thevenin resistance should be used deliver maximum power to the load.




THEVENIN'S AND NORTON'S EQUIVALENT TUTORIAL:

Thevenin's theorem states that we can replace entire network by an equivalent circuit is an independent current source in parallel with an impedance (resistor).

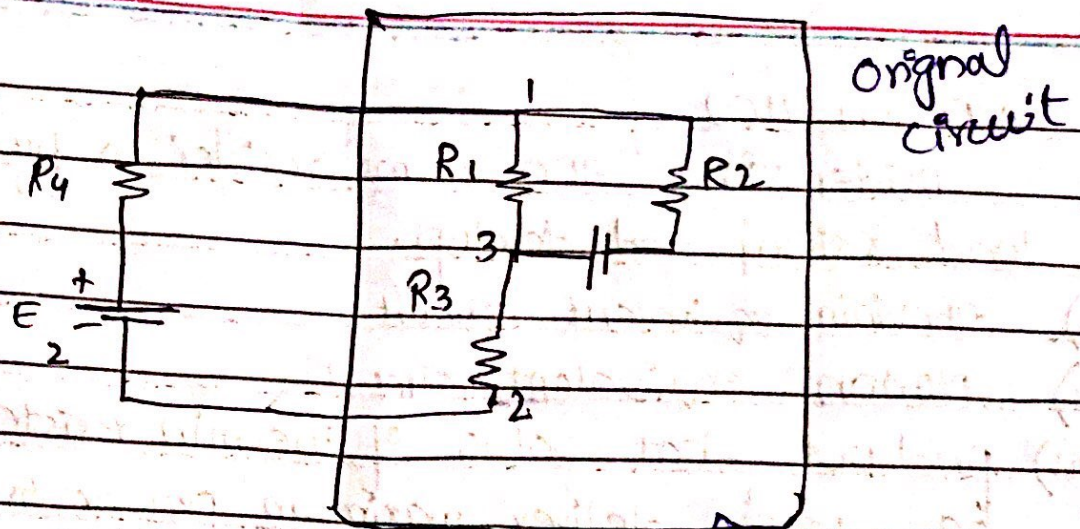
Therefore, the Norton equivalent circuit is a source transformation of the thevenin equivalent circuit.



Thevenin's equivalent circuit

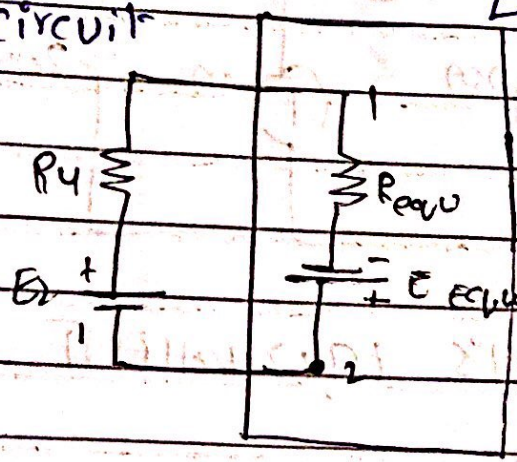

Norton's equivalent circuit

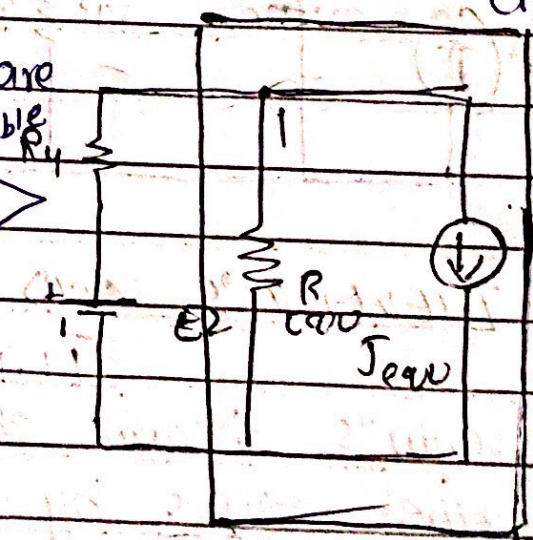

They are interchangeable

How to find Thevenin's equivalent circuit.

If the circuit contains

you should do

Resistors and independent sources.

1) connect an open circuit b/w a and b.

2) find the voltage across the open circuit which is $V_{oc} = V_{th}$.

3) Deactivate the independent sources
voltage source \rightarrow open circuit.
current source \rightarrow short circuit.

Resistors and dependent sources or independent sources.

1) connect an open circuit b/w a and b

2) find the voltage across the open circuit which $V_{oc} = V_{th}$.

If there are both dependent and independent sources-

3) connect a short circuit b/w a and b.

4) determine the current b/w a and b.

5) $R_{th} = V_{oc} / I_{ab}$

If there only dependent sources

3) connect \uparrow Ampere current source flowing from terminal b to a. ($I = 1[A]$)

4) Then $R_{th} = V_{oc} / I = V_{oc} / 1$