



Programs: BC (CS), BS(SE), BS(TELC)

Subject: Digital Logic Design
Major Assignment Final-Term

Course Code: CSC-201

EDP Code: 102007016

Summer Semester 2020

Name Shabban khan ID 12994

Q.1 Draw and explain the logic diagram for each of the following:

- A circuit for adding or subtracting two 4-bit numbers
- 4-bit active low decoder
- Decimal to BCD encoder
- Frequency divider (Use 3 J-K flip-flops and assume 16 kHz frequency of the initial wave-form.)

Q.2 For the 4-input multiplexer, data inputs are given as:

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

Find the output Y if the select inputs are given as:

- $S_0 = 1, S_1 = 0$
- $S_0 = 0, S_1 = 1$
- $S_0 = 1, S_1 = 1$
- $S_0 = 0, S_1 = 0$



Q.3 Timing diagram in Figure 01 shows inputs to a 9-bit parity checker. Draw the Σ Even and Σ Odd output for the even parity checking.

Q.4 The waveforms in Figure 02 are applied to the J, K, CLK, \overline{PRE} , and \overline{CLR} inputs as indicated. Determine the Q output, if the flip-flop is initially RESET.


Q.5 Use the waveforms in Figure 03 to draw the timing diagram for the parallel outputs (Q_1, Q_2, Q_3, Q_4) for the shift register. Assume that register is initially cleared.

Q.6 Draw the logic diagram and timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

Q6

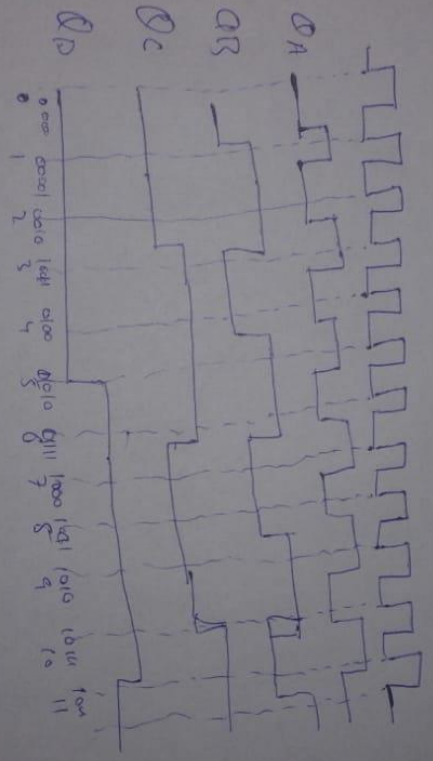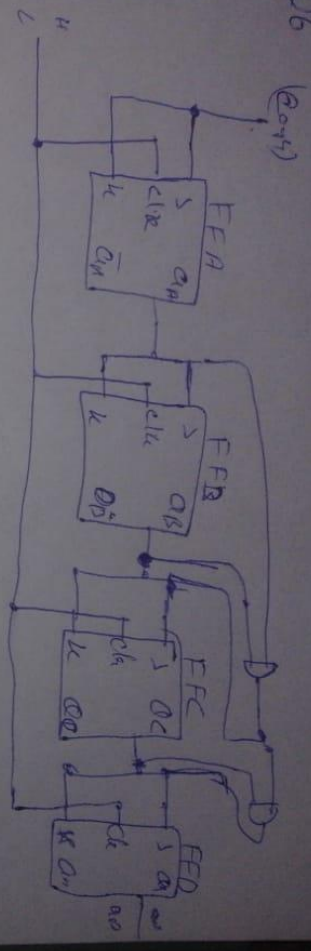

Q4

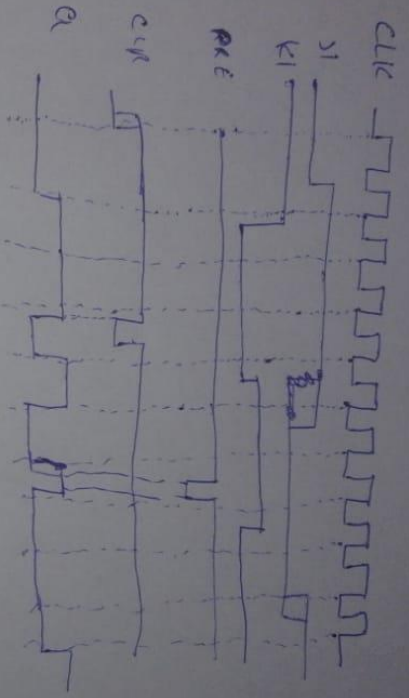

~~When the clock is applied to the input,~~
When the clock is applied to the input,
The flip-flop is set or reset regardless of
The state of the data input.

Q2

$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$

a) $S_0 = 1, S_1 = 0, Y = 0$


b) $S_0 = 0, S_1 = 1, Y = 1$

c) $S_0 = 1, S_1 = 1, Y = 0$

d) $S_0 = 0, S_1 = 0, Y = 1$

(Ans)

Q3

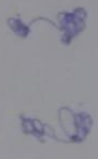


Even



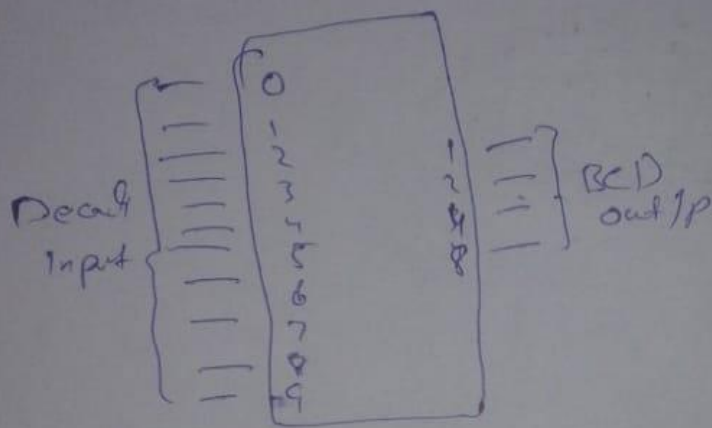
Q8e

encoder has ten inputs - one for each decimal digit and for outputs the output indicates the BCD code that represents the actual input.




Q1

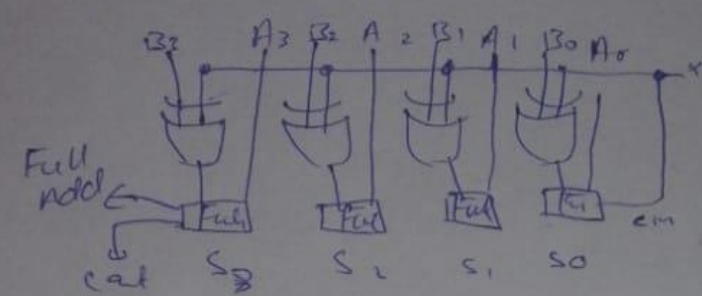Q1a In Digital circuit, A binary adder subtractor is one which is capable of both addition and subtraction of binary number is one circuit its 24 it is one of the component of ALU



Q1b

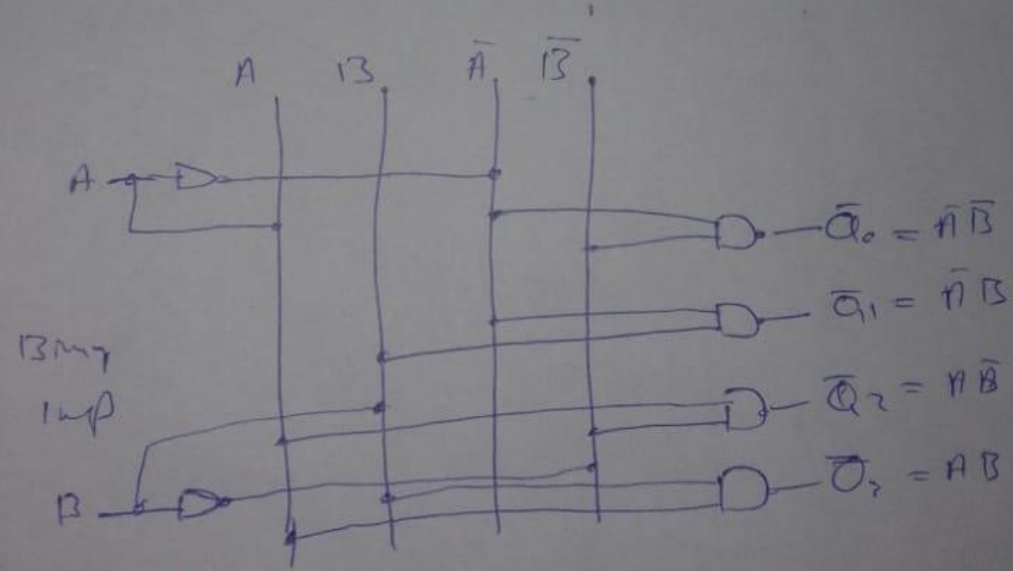

A	B	Q_0	Q_1	Q_2	Q_3
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0