

Name

Abdullah

ID NO

18194

Date

24/june/2020

Submitted to


Sir Sohail Inram

Subject

LC.A

Q NO 1

ANS:- Figure:-

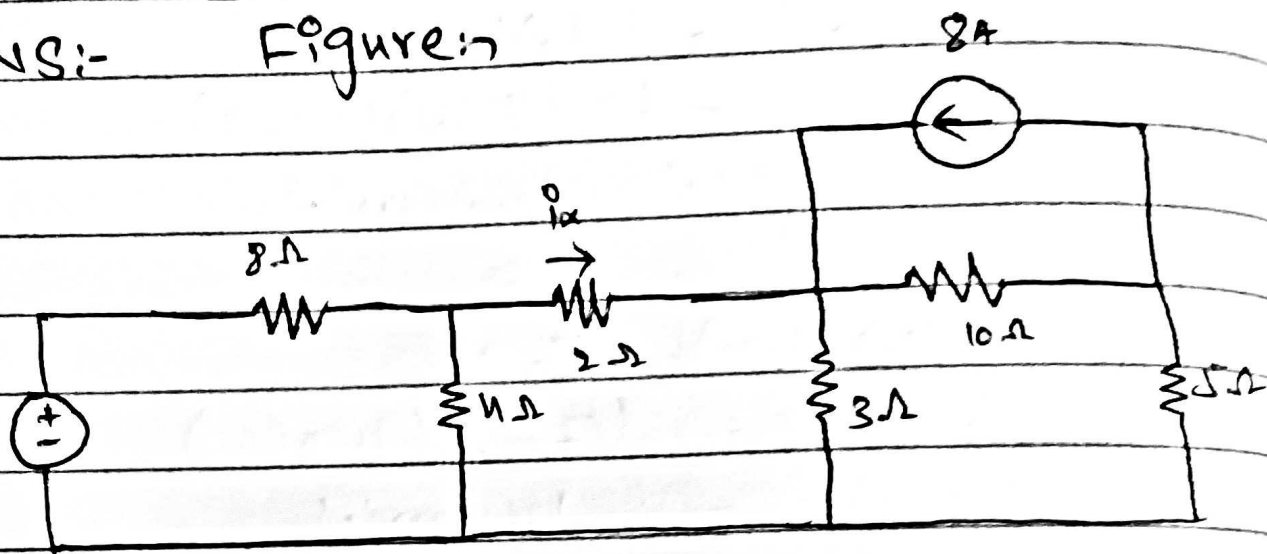

Required :-

- (i) Nodal analysis
- (ii) Mesh analysis
- (iii) Superposition Theorem
- (iv) Compare the number of steps & degree of easiness of all the three methods with each.


Solution :-

(i) Nodal analysis :-

For nodal analysis we will first identify nodes in the circuit.

Identifying nodes:

(2)

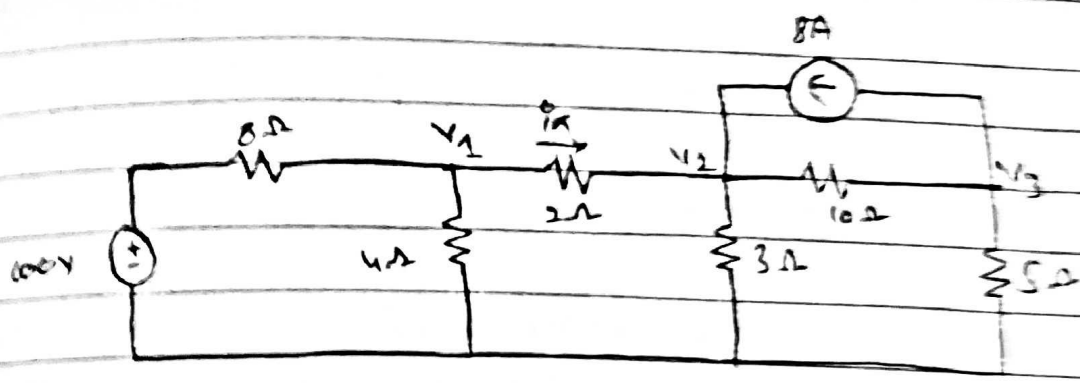

① Applying KCL on node 1

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$\frac{7V_1 - 4V_2 - 100}{8} = 0$$

$$0.875V_1 - 0.5V_2 = 12.5 \quad \text{--- (1)}$$

② Applying KCL on node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = -8$$

$$\frac{15V_2 - 15V_1 + 10V_2 + 3V_2 - 3V_3}{30} = -8$$

$$\frac{-15V_1 + 28V_2 - 3V_3}{30} = -8$$

$$-0.5V_2 + 0.933V_2 - 0.1V_3 = 8 \quad \text{--- (2)}$$

② Applying KCL on node (3),

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$-0.1V_2 + 0.3V_3 = -8 \quad \text{--- (3)}$$

Taking eq (1)

$$0.875V_1 - 0.5V_2 = 12.5$$

$$V_1 = \frac{12.5 + 0.5V_2}{0.875}$$

$$V_1 = 14.286 + 0.571V_2 \quad \text{--- (4)}$$

Taking eq (3)

$$-0.1V_2 + 0.3V_3 = -8$$

$$V_3 = \frac{0.1V_2 - 8}{0.3}$$

$$V_3 = 0.33V_2 - 26.67 \quad \text{--- (5)}$$

Putting eq (a) & (b) in eq (c)

$$-0.5(0.57V_2 + 14.286) + 0.933V_2 - 0.1(0.33V_2 + 2.667) = 8$$

$$-0.285V_2 - 7.143 + 0.933V_2 - 0.03V_2 + 2.667 = 8$$

~~$$0.618V_2 = 12.476$$~~

$$0.618V_2 = 12.476$$

$$V_2 = 20.18V$$

Putting V_2 in eq (a)

$$V_1 = 14.286 + 0.571(20.18)$$

$$V_1 = 25.80V$$

$$V_2 = 20.18V$$


for $i_x = \frac{V_1 - V_2}{2}$

$$= \frac{25.80 - 20.18}{2}$$

$$i_x = 2.79A$$

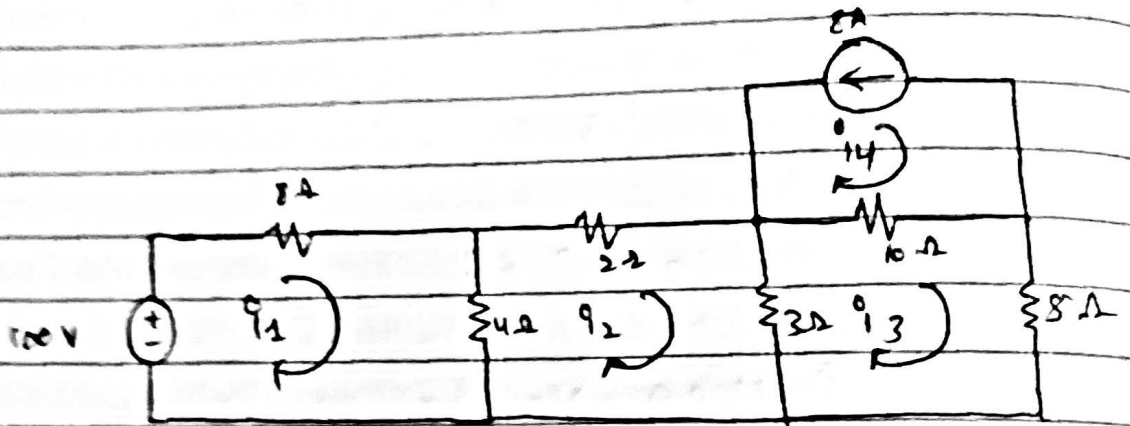(ii) Mesh analysis:

In mesh analysis first we have to identify a loop in the circuit



(i) Applying KVL on loop 1:

$$8i_1 + 4(i_1 - i_2) = 100$$

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

(ii) Applying KVL on loop 2:

$$2i_2 + 4(i_2 - i_1) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_1 + 9i_2 - 5i_3 = 0 \quad \text{--- (2)}$$

loop III

Applying KVL on loop 3:

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 - 10(8) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

iv

AND we know from the circuit that 8 A a current is flowing in loop 4

So

$$i_4 = 8 \text{ A}$$

Now Taking eq (1)

$$12i_1 - 4i_2 = 100$$

$$i_1 = \frac{100 + 4i_2}{12}$$

$$i_1 = 8.33 + 0.33i_2$$

(7)

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-80 + 3i_2}{18}$$

$$i_2 = -4.44 + 1.67i_2 \quad \text{--- (8)}$$

Putting in eq (2) the eq (8)

$$-4(8.33 + 0.33i_2) + 9i_2 - 3(-4.44 + 1.67i_2) = 0$$

$$-33.32 - 1.32i_2 + 9i_2 + 13.32 - 5.01i_2 = 0$$

$$-7.167i_2 = 20$$

$$i_2 = 2.790 \text{ A}$$

$$\text{AS } i_2 = i_x$$

So


$$i_x = 2.790 \text{ A}$$

Date: / /

8

By Superposition theorem

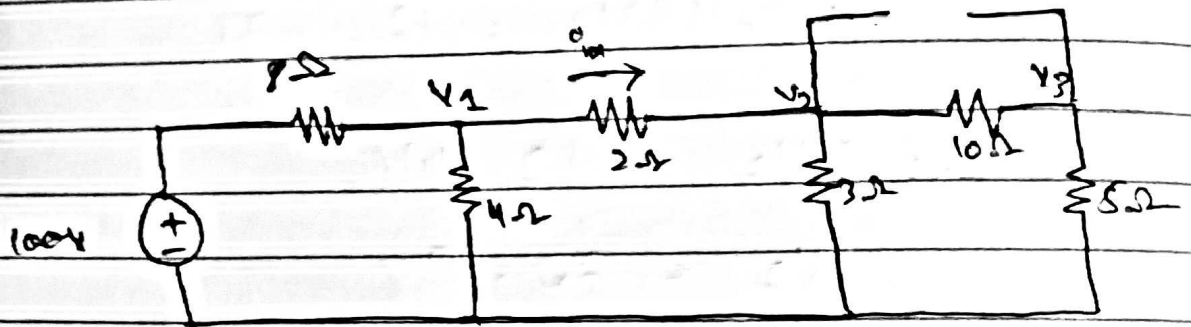removing the current source I_1 will make it as open circuit
 I_2 the voltage will be active
 drawing circuit & identifying node



applying KCL on node 1:

$$\frac{V_1 - 100}{8\Omega} + \frac{V_1}{4} + \frac{V_2 - V_1}{2} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$\frac{7V_1 - 4V_2 - 100}{8} = 0$$

$$0.875V_1 - 0.5V_2 = 12.5 \quad \text{--- (1)}$$

(ii) Applying KCL on node ①

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$\frac{15V_2 - 15V_1 + 10V_2 + 3V_2 - 3V_3}{30} = 0$$

$$\frac{-15V_1 + 28V_2 - 3V_3}{30} = 0$$

$$-0.5V_1 + 0.933V_2 - 0.1V_3 = 0 \quad \text{--- (2)}$$

(iii) Applying KCL on node ③:

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + 2V_3}{10} = 0$$

$$\frac{-V_2 + 3V_3}{10} = 0$$

$$-0.1V_2 + 0.3V_3 = 0 \quad \text{--- (3)}$$

AS WE know from ~~nodal~~
nodal analysis part that

eq (1) is ~~14.286 + 0.571V₂~~

$$V_1 = 14.286 + 0.571V_2$$

Taking eq (2)

$$-0.1V_2 + 0.3V_2 = 0$$

$$V_3 = \frac{0.1V_2}{0.3}$$

$$V_3 = 0.33V_2 \quad \text{--- (3)}$$

putting eq (1) & (3) in eq (2)

$$-0.5(14.286 + 0.571V_2) + 0.933V_2 - 0.1(0.33V_2) = 0$$

$$-0.285V_2 - 7.143 + 0.933V_2 - 0.033V_2 = 0$$

$$0.618V_2 = 7.143$$

$$V_2 = 11.56$$

Putting in eq A

$$V_2 = 14.286 + 0.57(11.56)$$


$$V_2 = 20.87$$

$$i_1 = \frac{V_1 - V_2}{R}$$

$$i_1 = \frac{20.87 - 11.56}{2}$$

$$i_1 = 4.65 \text{ A}$$

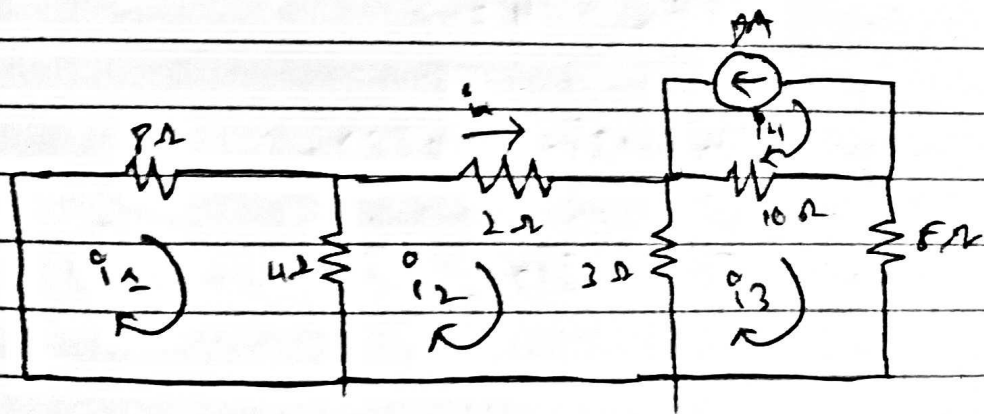Now making current source active and removing voltage source making as short circuit



① Applying KCL on loop 2

$$8i_2 + 4(i_2 - i_2) = 0$$

$$8i_2 + 4i_2 - 4i_2 = 0$$

$$12i_2 - 4i_2 = 0 \quad \text{--- ①}$$

Applying KVL on loop 2:

$$2i_2 + 4(i_2 - i_1) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_1 + 3i_3 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 - 10(8) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Now taking eq (2)

$$12i_2 - 4i_2 = 0$$

$$i_2 = \frac{4i_2}{12}$$

$$i_1 = 0.33 i_2$$

Date: / /

13

And from mesh analysis
Part we know that

eq (8) is

$$i_1 = -4.44 + 1.67i_2 \quad \text{--- (6)}$$

Putting eq (6) in eq (2)

$$-4(0.33i_2) + 9i_2 - 3(-4.44 + 1.67i_2) = 0$$

$$-1.32i_2 + 9i_2 - 5.07i_2 + 4.96 = 0$$

$$2.67i_2 = -4.96$$

$$i_2 = -1.867$$

Now

$$i_x = i_1 + i_2$$

$$= 4.65 - 1.867$$

$$i_x = 2.783 \text{ A}$$

Date: / /

14


(iv) The number of steps in nodal and mesh analysis are almost equal but in superposition the number of steps are almost of mesh and nodal analysis.

Degree of easiness


According to my opinion mesh analysis is easier than nodal analysis \therefore superposition theorem.

Q NO 2

ANSWER Figure:-

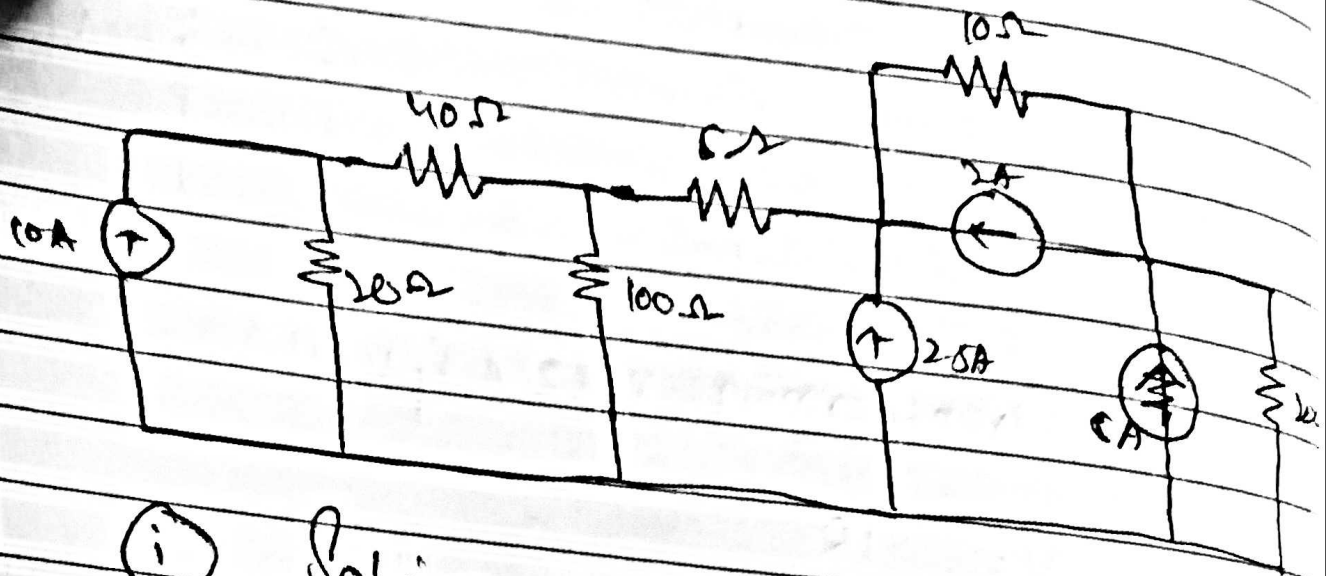


(i) Solving for thevenin:-

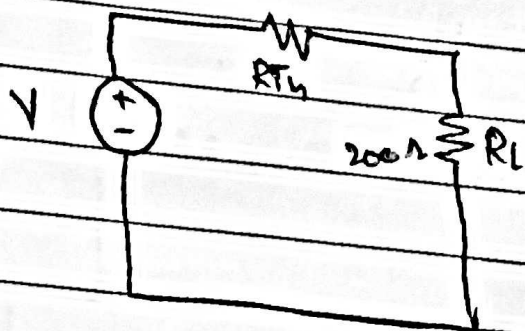

we will find R_{TH} for which we will remove all the current source & short circuit the load resistor.

Redrawing the circuit

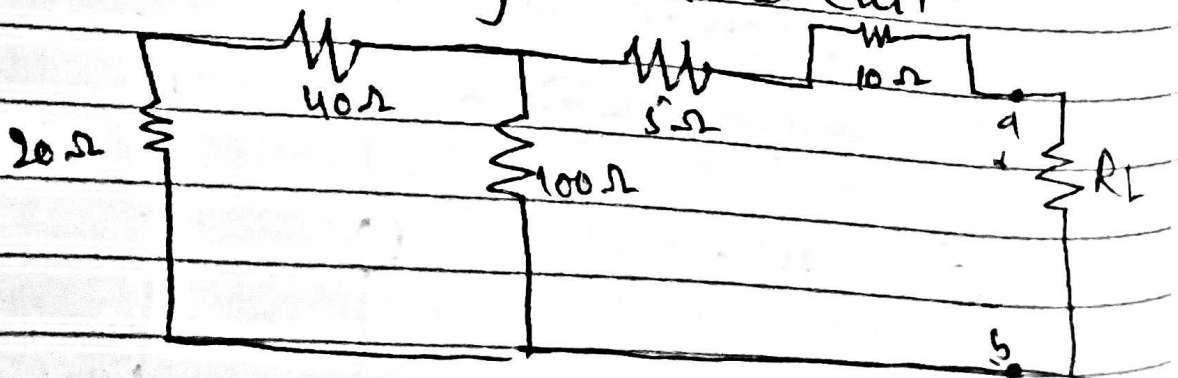

18

adding all resistor.

$$20 + 40 \parallel 100 + 5 + 10$$


$$60 \parallel 100 + 15$$

$$\frac{60 \times 100}{60 + 100} + 15$$

$$37.5 + 15$$

$$R_{Th} = 52.5$$

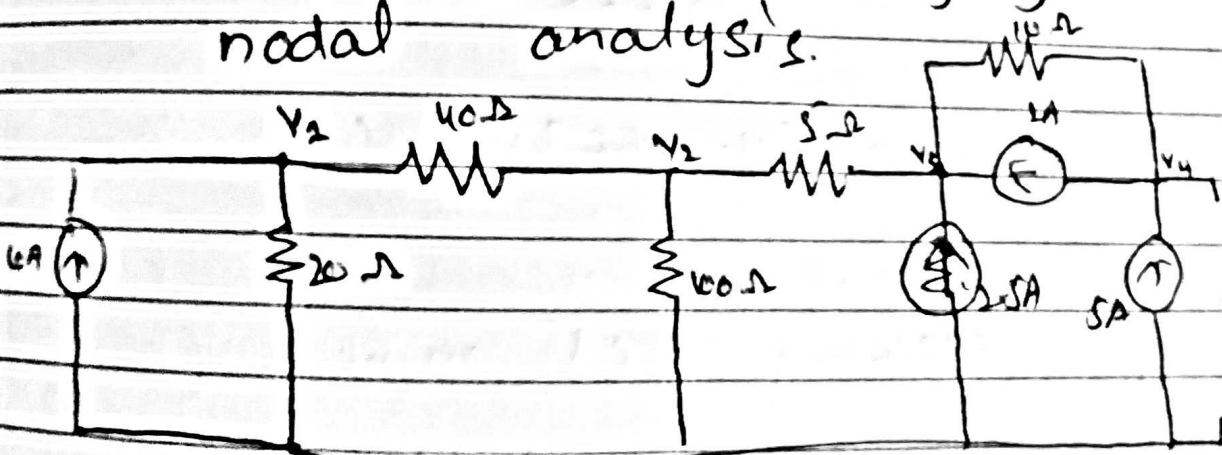for finding V_{Th} applying nodal analysis.



applying KCL on V_1


$$\frac{V_1 - V_2}{40} + \frac{V_1}{20} = 10$$

$$\frac{V_1 - V_2 + 2V_1}{40} = 10$$

$$V_1 - V_2 = 400 \quad \text{--- (1)}$$

Applying KCL on node 1
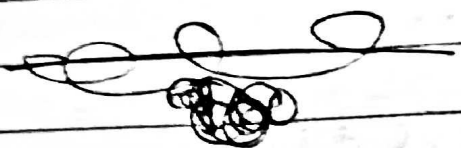
$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{5}$$



$$\frac{50V_2 - 50V_1 + 20V_2 + 400V_2 - 400V_3}{2000}$$

$$\frac{50V_1 + 70V_2 - 400V_3 = 0}{2000}$$

$$0.05V_1 + 0.035V_2 - 0.2V_3 = 0 \quad \text{--- (1)}$$

Applying KCL on node 3

$$\frac{V_3 - V_2}{5} + \frac{V_3 - V_4}{10} = 2.5 + 2$$

$$\frac{2V_3 - 2V_2 + V_3 - V_4 = 4.5}{10}$$

$$-2V_2 + 3V_3 - V_4 = 4.5 \quad \text{--- (2)}$$

Applying KCL on node (4)

$$\frac{V_4 - V_3}{10} = 5 - 2$$

$$V_4 - V_3 = 30 \quad \text{--- (4)}$$

Solving by using calculator.

$$V_1 = 275$$


$$V_2 = -124.9$$

$$V_3 = -87.5$$

$$V_4 = -57.5$$

$$V_{TH} = 275 - 124.9 - 87.5 - 57.5$$

$$V_{TH} = 5.1$$

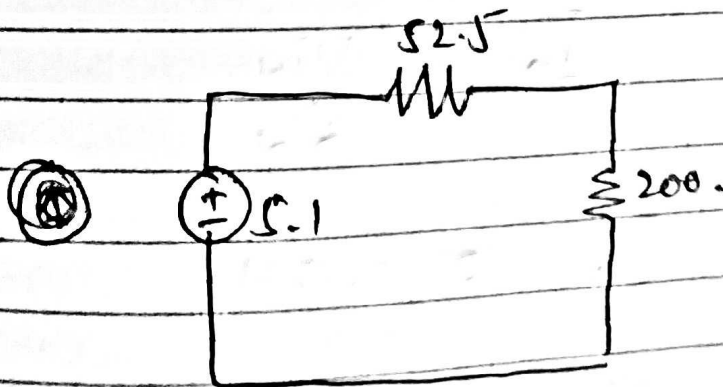


$$I_{TH} = \frac{V_{TH}}{R_{TH} + R_L} = 0.0204$$

$$I_{TH} = \frac{5-1}{5 \cdot 5 + 200}$$

$$I_{TH} = 0.02$$

(ii)

For Norton theorem

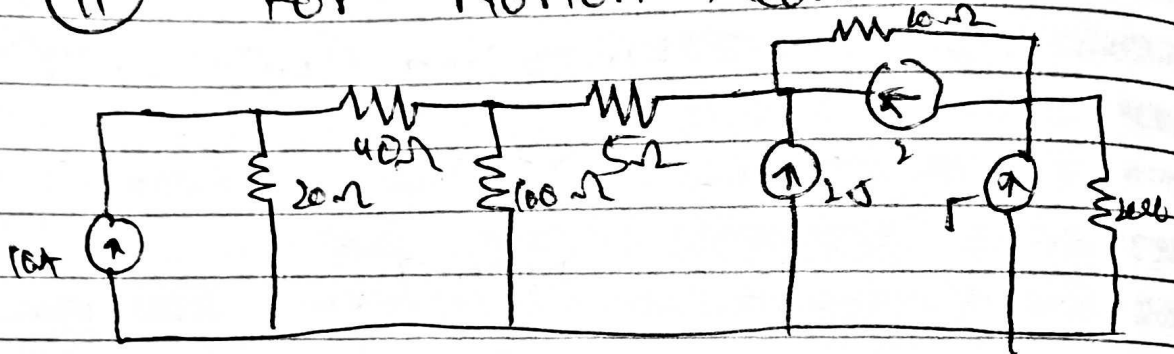

for R_N will be
the same

$$R_N = R_{TH}$$



$$R_N = 5\Omega$$

find $I_N = \frac{V_{TH}}{R_N}$

$$I_N = 0.09$$

As the circuit are same
so we find it
directly.

As for the Norton

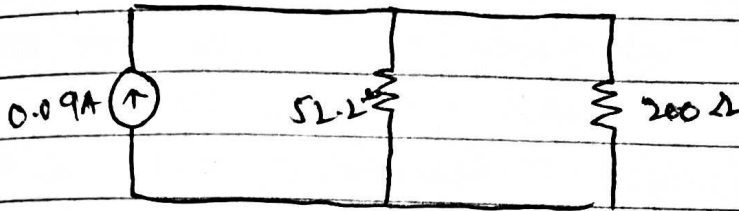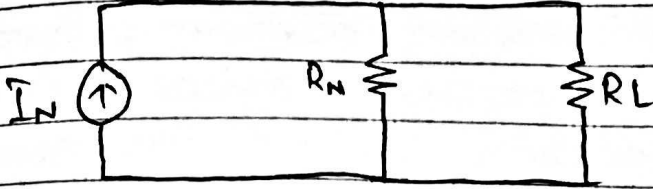

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$V_{TH} = I_N R_N$$

$$= (0.09)(52.2)$$

$$V_{TH} = 4.7 \text{ V}$$

$$R_{TH} = R_N = 52.2$$

Putting in eq

~~$$I_L = \frac{4.7}{52.2 + 200}$$~~

$$I_L = \frac{4.7}{52.2 + 200}$$

$$I_L = 0.019 \text{ A}$$

Date: / /

(22)

(iii)

Using theorem for finding power:

We know that


$$P = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

$$= \left(\frac{5.1}{52.5 + 200} \right)^2 200$$

$$P = 0.08W$$

Q NO 3

ANS: Figure

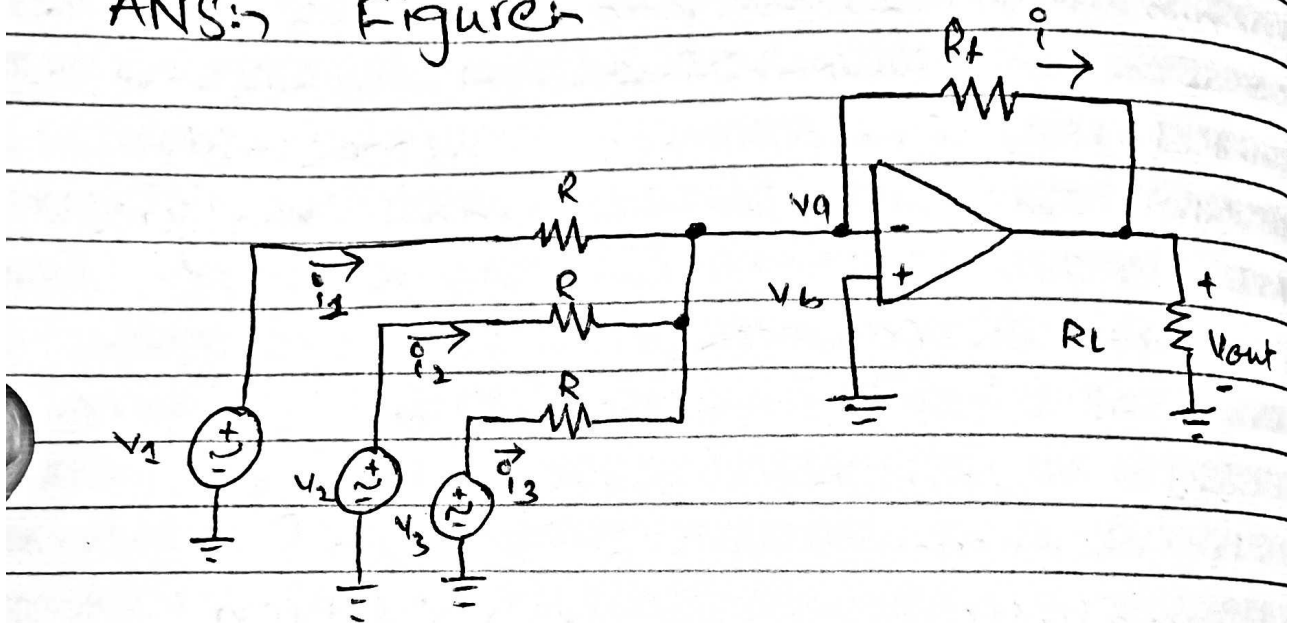

Solution:

We know that all the current is entering to the inverting terminal of the op-amp. We know that the current entering to inverting or non-inverting are virtually zero.

$$\therefore i = i_1 + i_2 + i_3 = 0$$

Therefore we are taking node V_a as mentioned in the circuit above.

AS Current I is flowing from V_a to V_{out} as V_a will be at high potential writing equation

$$0 = \frac{V_a - V_{out}}{R_f} + \frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - V_3}{R}$$

Now know that the potential of inverting & non-inverting terminal is zero so

$$V_a = V_b = 0$$

$$V_a = 0$$

So the equation will become

$$0 = \frac{V_{out}}{R_f} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

$$\frac{-V_{out}}{R_f} = \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

$$-V_{out} = R_f \left(\frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R} \right)$$

$$V_{out} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$