

Assignment

Name

=

Khalid Ichan

ID

=

13880

Programme

=

B-Tech (E)

Subject

=

network analysis (I)

Semester

=

5th


Submitted

=

TO = Engr. Muhammad

Aamir Aman


Q(1)

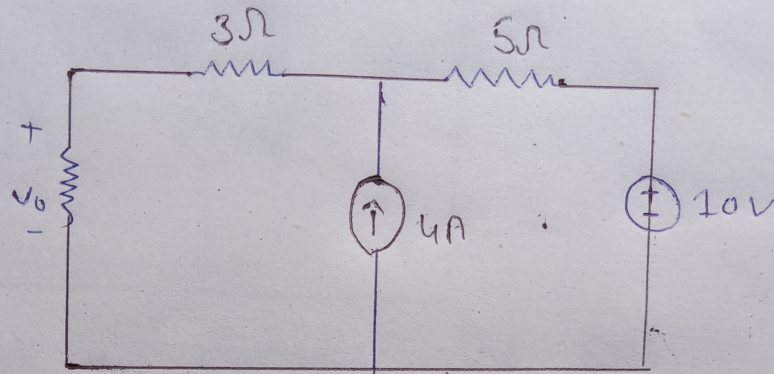

Solution \Rightarrow

Let $V_0 = V_1 + V_2$

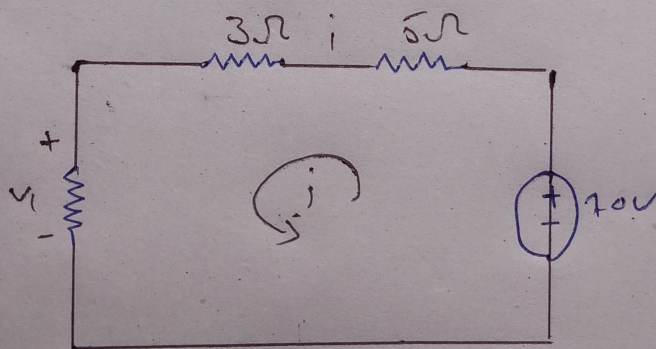where V_1 and V_2 are contribution to the 10V and 4A sources respectively



(a)

Apply ohm Law


To get V_1 consider the ckt

$$(2+3+5)i = 10$$

$$i = 10 / (10) = 1A$$

$$V_1 = 2i = 2V$$

(P.T.O)

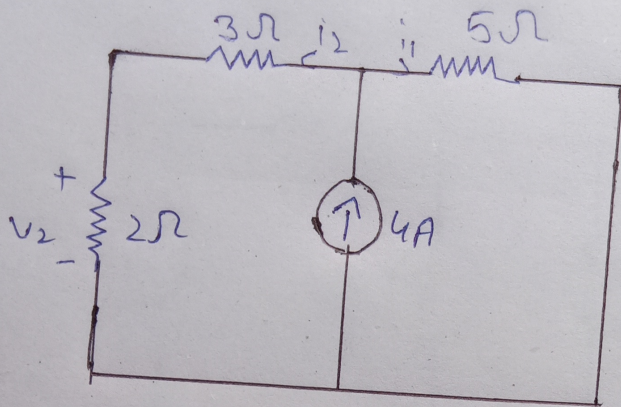


To get v_2 consider the circuit

$$i_1 = i_2 = 2A, \quad v_2 = 2i_2 = 4V$$

Thus

$$v = v_1 + v_2 = 2 + 4 = 6V$$

(002)

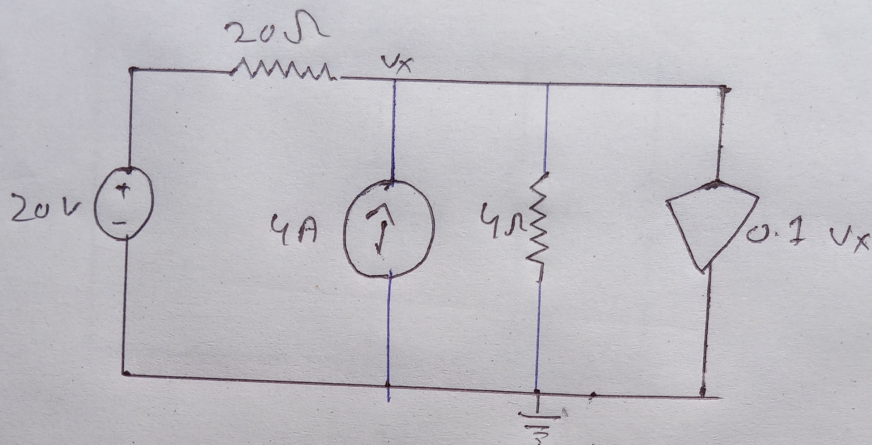


Solution:-

// - //

$$\text{Let } V_x = V_1 + V_2$$

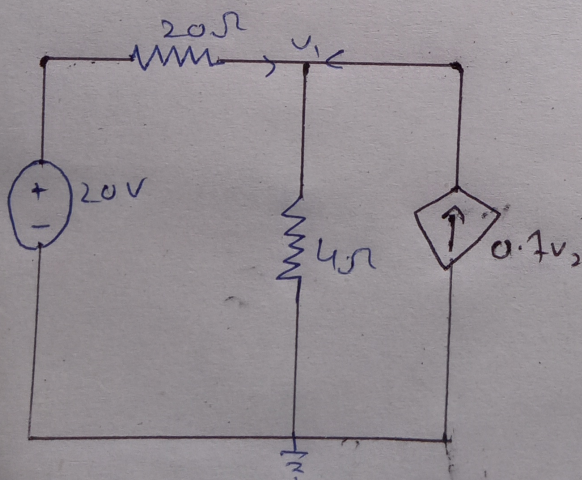where V_1 and V_2 are due to the 20V and 4A source respectively




Apply KCL

To obtain V_1 consider

$$\frac{20 - V_1}{20} + 0.1V_1 = \frac{V_1 - 0}{4}$$

$$V_1 = 5V$$

P.T.O

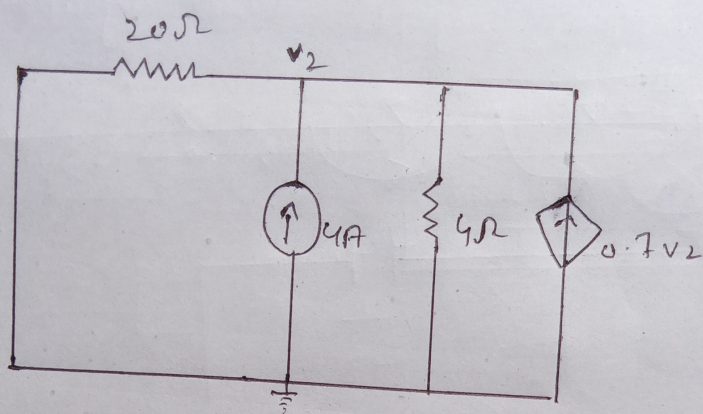

(b)

Apply KCL

For v_2 consider

$$4 + 0.7v_2 = \frac{v_2 - 0}{20} + \frac{v_2 - 0}{4}$$

$$v_2 = 20$$

Thus,

$$v_x = v_1 + v_2 = 25V$$