

NAME :- Naeem ulah

IO :- 6873

Subject :- Power Transmission
and Distribution

Instructor :- Sir Sajid Nawaz

Date :- 25-09-2020

Page (1)

Q No 1: Explain two generator method of obtaining 3-wire DC system.


Ans: There are several methods obtaining 3-wire DC system. However, the most important ones are:

1) Two generator method:

In this method, two shunt wound DC generator G_1 and G_2 are connected in series and the neutral is obtained from the common point b/w generator as shown in fig. 12.6(i). Each generator


supplies the load on its own side. Thus generator G_1 supplies a load current of I_a , whereas generator G_2 supplies a load current of I_a .

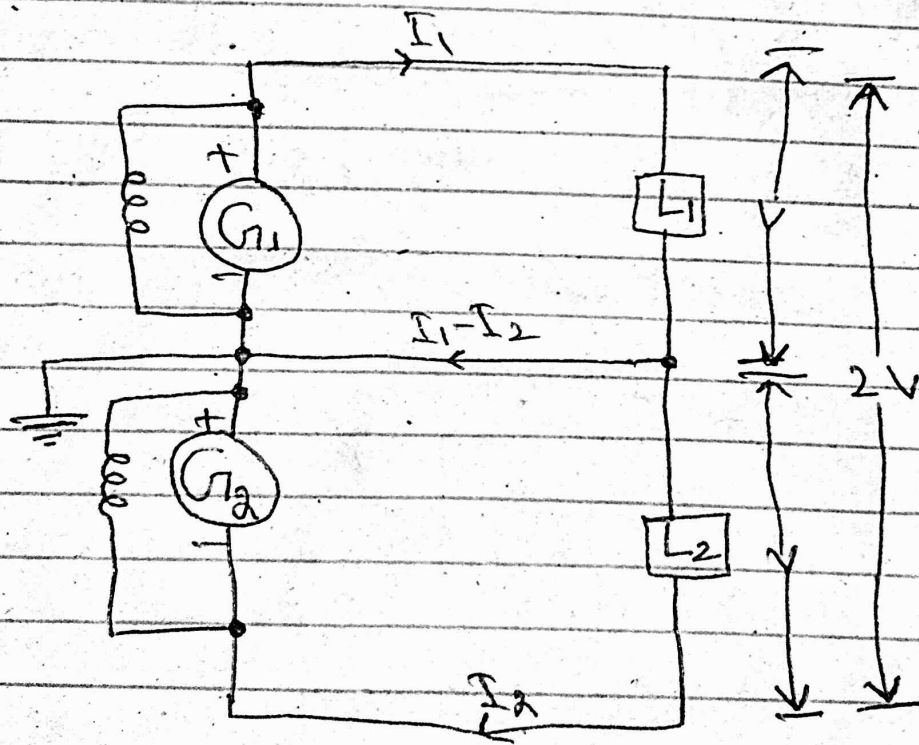The difference of load current on the two sides, known as out of balance current ($I_1 - I_2$) flows through the neutral wire. The principal disadvantages of this method is that two separate generators are required.



(i)

Fig 12.6

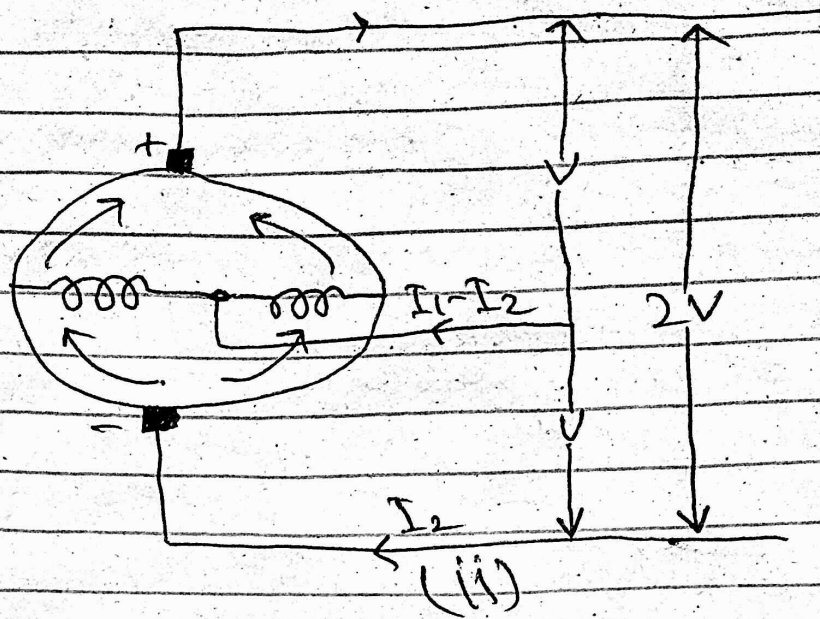


(2) three wire Dc. Generator :

⇒ The above method is costly on account of the necessity of two generators for this reason, 3-wire Dc generator was developed as shown in fig 12.6(ii). It consists of a standard 2 wire machine with one or two coils of high

reactance and low resistance, connected permanently to diametrically opposite points of the armature winding.

The neutral wire is obtained from the common point as

shown.

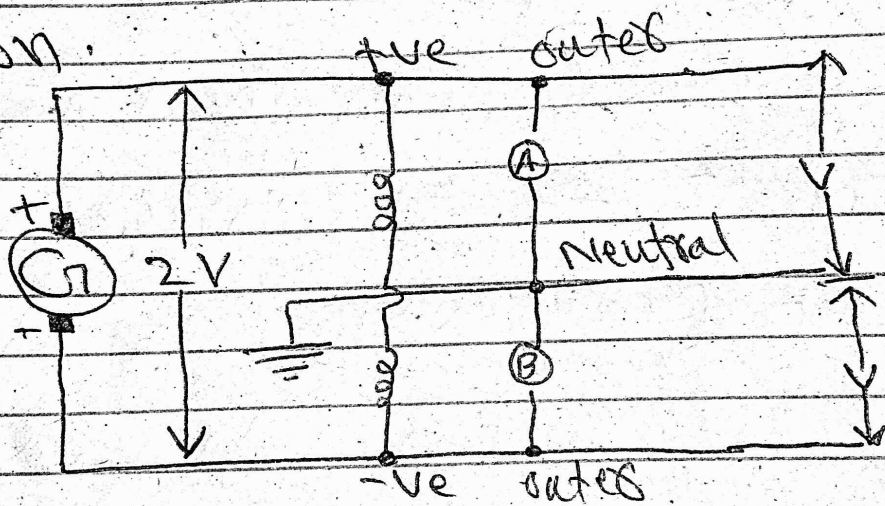

12.7

(3) Balancer set: The three wire system can be obtained from wire DC system by the use of balancer set as shown in fig 12.7. G is the main 2-wire DC generator and supplies to the whole system. The balancer set consist of two identical DC shunt machines A and B coupled mechanically with their armatures and field winding joined in series across the outers. The junction of their armature is earthed and neutral wire is taken

Page (6)

out from here. The balance set has the additional advantage that it maintains the ~~P.E~~ P.D on two sides of neutral equal to each other.

Q No 2: (A) write down the types of DC distributor. Also explain any one type.


Ans:- there are four types of DC Distributor which are given below.

- (1) distributor fed at one end
- (2) distributor fed at both ends.
- (3) distributor fed at centre end
- (4) Ring distributor.

⇒ Distributor fed at the centre.
In this type of feeding, the centre of the distributor is connected to the supply mains.

Page(8)

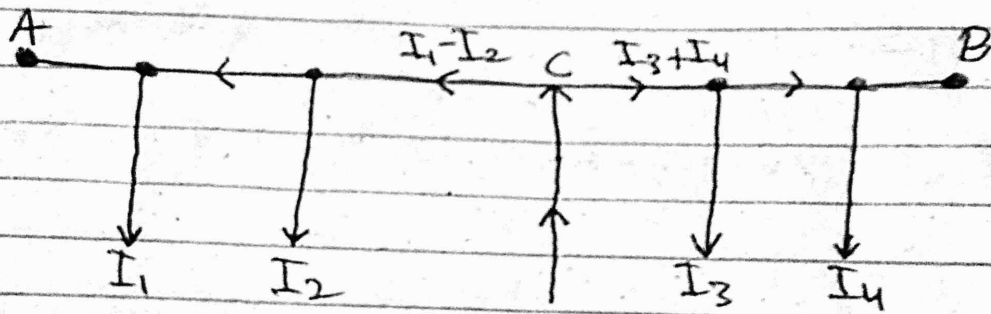as shown in fig. it is equivalent to two singly fed distributors, each distributor having a common feeding point and length equal to the half of the total length.



Page (9)

Q No 2 :-

(B) Explain Ground detector :-

Ans! The ground detector is an instrument which is used to detect conductor insulation, resistance to ground. An ohm meter, or a series of lights, can be used to detect the insulation strength of an ungrounded distribution system. Most power distribution system in use today use of the

Page(10)

grounded variety; However, some
ungrounded system still exist.

*

page(11)

Q No 38 -


Solution:-

fig 14.21(i) shows the lamp connection. The Lamp L_1 of 100 watts is connected b/w phase R and neutral whereas lamp L_2 of 150 watts is connected b/w phase Y and the neutral.


$$\begin{aligned} \text{Resistance of Lamp } L_1, R_1 &= \frac{(230)^2}{100} \\ &= \frac{52900}{100} \\ &= 529 \Omega \end{aligned}$$

$$\begin{aligned} \text{Resistance of Lamp } L_2, R_2 &= \frac{(230)^2}{150} \\ &= 352.67 \Omega \end{aligned}$$

Page (12)

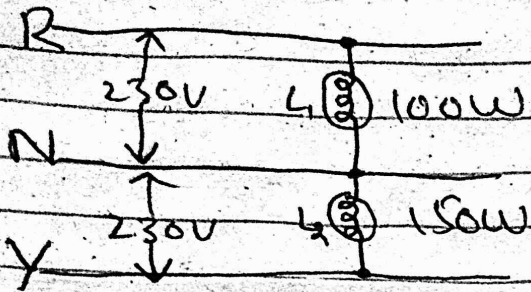

B (i)

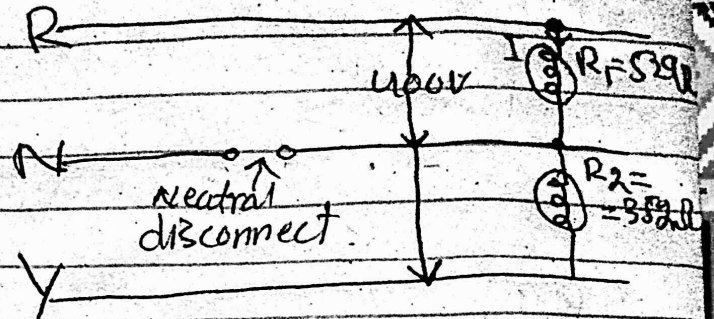

B (ii)

current through lamps,

$$I = \frac{\Sigma L}{R_1 + R_2} = \frac{400}{529 + 352.67} = 0.454 \text{ A}$$

$$I = 0.454 \text{ A}$$

⇒ voltage across Lamp $L_1 =$

$$V_{L_1} = IR_1 = 0.454 \times 529$$

$$= 240 \text{ V}$$

⇒ voltage across Lamp $L_2 =$

$$V_{L_2} = IR_2 = 0.454 \times 352.67$$

$$V_{L_2} = 160 \text{ V}$$

Page (13)

comments:- The voltage across 100 watt lamp is increased to 240V whereas that across 150 watt is decreased to 160V. therefore, 100 watt lamp becomes brighted and 150 watt lamp becomes dim. it may be noted here that if 100 watt lamp happens to be rated at 230V, it may burn out due to 240V coming across it.

Page(14)

Q No 4:- A two wire dc-distributor ABCDEA in the form of a

ring main is fed at point A at 220V and is loaded as under:
10A at B; 20A at C; 30A at D; and 10A at E. The resistance of various section (go and return) are:

$$AB = 0.1\Omega; BC = 0.05\Omega; CD = 0.01\Omega$$

$$DE = 0.025\Omega \text{ and } EA = 0.075\Omega.$$

Determine

(1) The point of minimum potential

(2) current in each section of distributor.

Solution:-

(i) According to KVL, the voltage drop in the closed loop ABCDEA is zero i.e.

$$I_{AB}R_{AB} + I_{BC}R_{BC} + I_{CD}R_{CD} + I_{DE}R_{DE}$$

$$+ I_{EA}R_{EA} = 0$$

OR

$$0.1I + 0.05(I-10) + 0.01(I-30) + 0.025(I-60) + 0.075(I-70) = 0$$

OR


$$0.26I = 7.55$$

$$I = \frac{7.55}{0.26} = 29.04 \text{ A}$$

$$I = 29.04 \text{ A}$$

the actual distribution of current is as shown in fig. 2(ii) from where it is clear that C is the point of minimum potential.

C is the point of minimum potential.

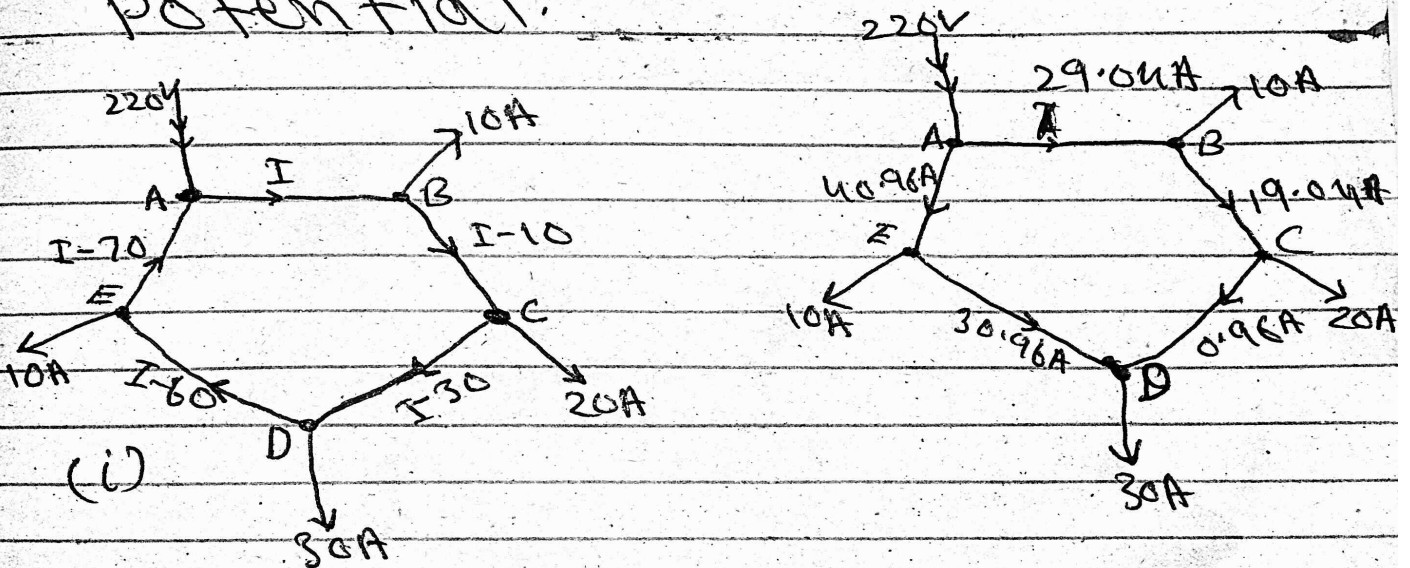

Page(16)

(ii) current in section AB = $I = 29.04 \text{ A}$ from
A to B

current in section BC = $I - 10 = 29.04 - 10 =$
 $= 19.04 \text{ A}$ from
B to C.

current in section CD = $I - 30 = 19.04 - 30 =$
 $= -0.96 \text{ A} = 0.96 \text{ A}$ from
D to C.

current in section DE = $I - 60 = 19.04 - 60$
 $= -30.96 \text{ A} = 30.96 \text{ A}$ from E to D

current in section EA = $I - 70 =$
 $= 29.04 - 70 = -40.96 \text{ A} = 40.96 \text{ A}$
from A to E.

*


Q No 5th -

(A) Explain 2-wire DC system.

Ans:

As the name suggests, this system uses two conductors, one is positive conductor and the other one is negative conductor. The energy is transmitted at only one voltage level to all the consumers using this system.

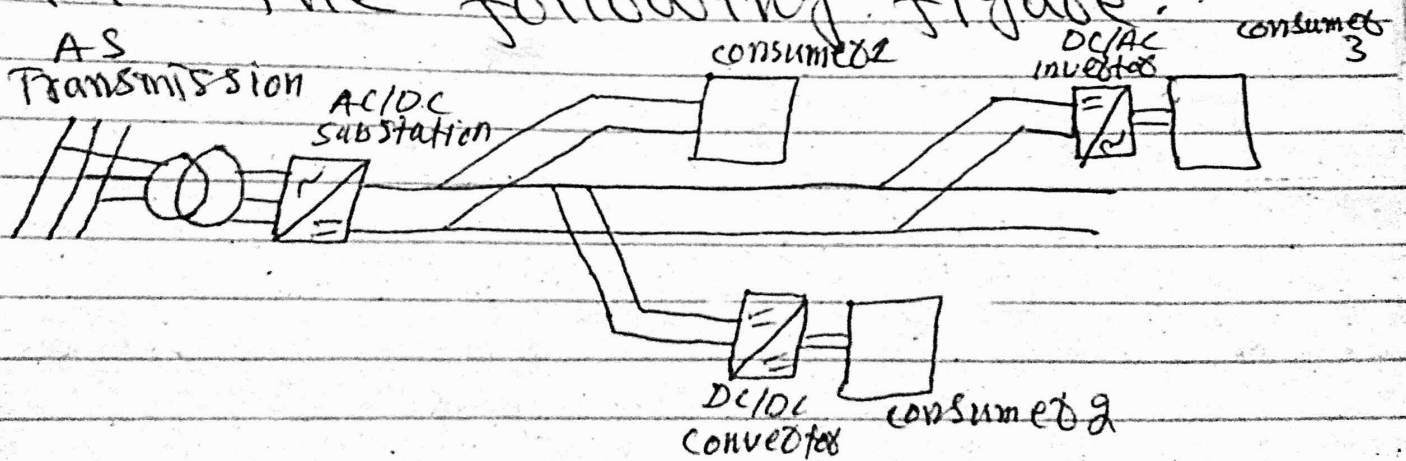A typical unipolar dc power distribution system is as shown in the following figure.



Q No 5 :-

(B) Booster :-

(1) A device for increasing electrical voltage or signal strength.

(2) The first stage of a rocket or spacecraft, used to give initial acceleration and then jettisoned.

End