

Name . Abid Khan

ID = 11445

Paper . Power Transmission and Distribution

Sir = Engr. Saadullah Ahmad

Date = 24 Sep 2020.

Question no = 1

a part

Solution.

Spacing of conductors, $d = 2\text{m} = 200\text{cm}$ Radius of conductor, $r = 1.2/2 = 0.6\text{cm}$ Loop inductance Per meter length of the
line.

$$= 10^{-7} (1 + 4 \log_e d/r) \text{ H}$$

$$= 10^{-7} (1 + 4 \log_e 200/0.6) \text{ H}$$

$$= 24.23 \times 10^{-7} \text{ H}$$

 \Rightarrow Loop inductance per km of the line

$$= 24.23 \times 10^{-7} \times 1000 = 24.23 \times 10^{-4} \text{ H} = 2.423 \text{ mH}$$

$$= \boxed{2.423 \text{ mH}}$$

Answer.

x x x x

Question no = 1

B Part.

Solution.

Load power factor, $\cos \theta_R$

= 0.8 Lagging



Total line impedance, $\vec{Z} = R + jX_L = 10 + j15$

$$|R| = |I_s| = |I|$$

 \Rightarrow Receiving end voltage, $V_R = 33 \text{ kV} = 33,000 \text{ V}$

$$\therefore \text{Line current, } I = \frac{\text{kW} \times 10^3}{\sqrt{R} \cos \phi_R} = \frac{1100 \times 10^3}{33000 \times 0.8} = 41.67 \text{ A}$$

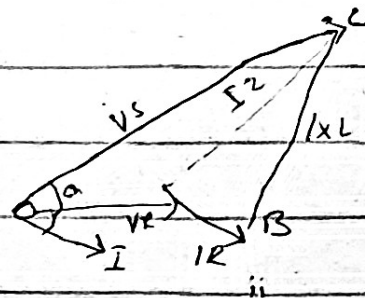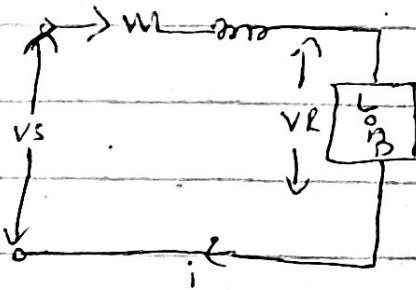As $\cos \phi_R = 0.8 \quad \therefore \sin \phi_R = 0.6$



The equivalent circuit and phasor diagram of the line are shown in fig (i) and (ii)

Taking receiving voltage \vec{V}_R as the Reference Phasor

$$\vec{V}_R = V_R + j0 = 33000 \text{ V}$$

$$\vec{I} = I (\cos \phi_R - j \sin \phi_R)$$

$$= 41.67 (0.8 - j0.6) = 33.33 - j25$$

(i) Sending end voltage

$$\vec{V}_S = \vec{V}_R + \vec{I} \vec{Z}$$

$$= 33000 + (33.33 - j25.0) (10 + j15)$$

$$= 33000 + 333.3 - j250 + j500 + 375$$

$$= 33708.3 + j250$$

$$\therefore \text{Magnitude of } V_S = \sqrt{(33708.3)^2 + (250)^2}$$

$$= 33709 \text{ V}$$

(ii) Angle b/w \vec{V}_S and \vec{V}_R is $\alpha = \tan^{-1} \frac{260}{33708.3} = \tan^{-1}$

$$0.0074 = 0.42^\circ$$

\therefore Sending end power factor angle is

$$\phi_S = \phi_R + \alpha = 36.87^\circ + 0.42 = 37.29^\circ$$

\therefore Sending end P.F

$$\cos \phi_S = \cos 37.29^\circ = 0.7956 \text{ Lagging}$$

(iii) Line losses $= I^2 R = (41.61)^2 \times 10 = 17364 \text{ W} = 17.364 \text{ kW}$
output delivered = 1100 kW

$$\text{Power Sent} = 1100 + 17.364 = 1117.36 \text{ kW}$$

\therefore Transmission Efficiency =

$$\frac{\text{Power delivered} \times 100}{\text{Power Sent}}$$

$$\text{Power Sent}$$

$$= \frac{1100}{1117.364} \times 100 = 98.44\%$$

$$1117.364$$

Note V_S and ϕ_S can also be calculated

as follow

$$V_S = V_R + I R \cos \phi_R + I X_L \sin \phi_R$$

$$= 33000 + 41.67 \times 10 \times 0.8 + 41.67 \times 15 \times 0.6$$

$$33000 + 333.36 + 3750.3$$

$$= 33708.39 \text{ V which is the same}$$

approximately as above.

$$\cos \phi_S = \frac{V_R \cos \phi_R + I R}{V_S}$$

$$\frac{33000 \times 0.8 + 411.67 \times 10}{33,708.39}$$

$$\frac{26,816.7}{33,708.39}$$

$$= 0.7958 \text{ Answer.}$$

Question no = 2

a part

Tariff:

The amount of money frame by the supplier for the supply of electrical energy to various types of consumers is known as electricity tariff. The tariff covers the total cost of producing and supplying electric energy plus a reasonable cost.

Tariff for Electric Energy:

The electricity generated is to be supplied to the consumers. The total cost of generation and profit as to be recovered from the consumers. The rate of energy sold to

the consumers as domestic commercial or industrial.

- ⇒ The rate depend upon the total energy consumed and the load factor of the consumer.
- ⇒ The tariff energy should recover the fixed cost operating cost and profit etc.

Types of tariff

- ⇒ Tariff may be a plain, two or three parts
- ⇒ Two and three part tariff consist of two components.
- ⇒ Variable component based on the actual unit being consumed.
- ⇒ Fixed component - base on installed capacity or maximum demand
- ⇒ In a plain tariff it is the cost of electricity unit in terms of kWh (1 unit = 1 kWh) actually used by consumers are charged in bill
- ⇒ The unit in terms of kWh are registered by kWh and registered by energy meter.

Two part tariff

→ Cost of the electricity supplied to consumers may be divided into fixed cost and running cost.

⇒ Two part tariff consist of fixed cost and running cost for large power consumer two part tariff is imposed. Fixed cost may vary from consumer to consumer and may be based on appliances connected to supply. Thus two part tariff usually have kVA or kW and variable portion based on the amount of electricity units consumed (i.e.)

$$\therefore \text{Tariff} = \text{Rs Per kVA} \\ (\text{kW}) + \text{Rs Per kWh}$$

Three part tariff:

⇒ Three part tariff consist of fixed part based on kVA or kW, variable portion based on kWh and maximum demand which varies depending on habit of use of appliances.

⇒ Maximum demand can be obtained from maximum demand indicator installed on distribution transformer.

Question no 2


B Part

Solution:

Fig show the single line diagram of distributor.

⇒ Impedence of distributor/km

$$= (0.2 + j0.1) \Omega$$

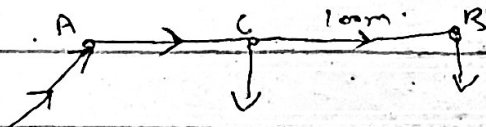

$$(I_1 = 100A) \quad (I_2 = 200)$$

$$(\cos \phi_1 = 0.707 \text{ lag}) \quad (\cos \phi_2 = 0.8 \text{ lag})$$

$$\text{Impedence of Sec AC, } \vec{Z}_{AC} = (0.2 + j0.1) \times 2000/1000$$

$$= (0.04 + j0.02) \Omega$$

$$\text{Impedence of sec CB, } \vec{Z}_{CB} = (0.2 + j0.1) \times 1000/1000 =$$

$$= (0.02 + j0.01) \Omega$$

Taking voltage at the far End B as reference vector we have Load current at point B,

$$\vec{I}_2 = I_2 (\cos \phi_2 - j \sin \phi_2) = 200(0.8 - j0.6)$$

$$= (160 - j120) A$$

Load current at point C

$$\vec{I}_1 = I_1 (\cos \phi_1 - j \sin \phi_1) = 100(0.707 - j0.707)$$

$$= (70.7 - j70.7) A$$

112-114115

Page 8.

Current in Section CB

$$\vec{I}_{CB} = \vec{I}_2 = (160 - j120) \text{ A}$$

current in section AC

$$\begin{aligned} \vec{I}_{AC} &= \vec{I}_1 + \vec{I}_2 = (70.7) - j70.7 + (160 - j120) \\ &= (230.7 - j190.7) \text{ A.} \end{aligned}$$

Voltage drop in Section CB

$$\begin{aligned} \vec{V}_{CB} &= \vec{I}_{CB} \vec{Z}_{CB} = (160 - j120)(6.02 + j0.01) \\ &= 4.4 - j0.8 \text{ volts} \end{aligned}$$

Voltage drop in Section AC

$$\begin{aligned} \vec{V}_{AC} &= -\vec{I}_{AC} \vec{Z}_{AC} = (230.7 - j190.7)(0.04 + j0.02) \\ &= (13.04 - j3.01) \text{ volts.} \end{aligned}$$

Voltage drop in distributor

$$\begin{aligned} &= \vec{V}_{AC} + \vec{V}_{CB} = (13.04 - j3.01) + (4.4 - j0.8) \\ &= (17.44 - j3.81) \text{ volts} \end{aligned}$$

Magnitude of drop =

$$\sqrt{(17.44)^2 + (3.81)^2}$$

17.85V Ans

