

2)

Name:

ID :

Mohsin Ali

13746

Paper :

final paper

Subject Name:

electrical machine

T. Name:

Sir Sannullah Sahib



Q1

A

Ans:


Speed control of DC Series motor:

1) Armature Resistance control Method:

Here The controlling resistance is connected directly in series with the supply of the motor as shown

P.T.O

2

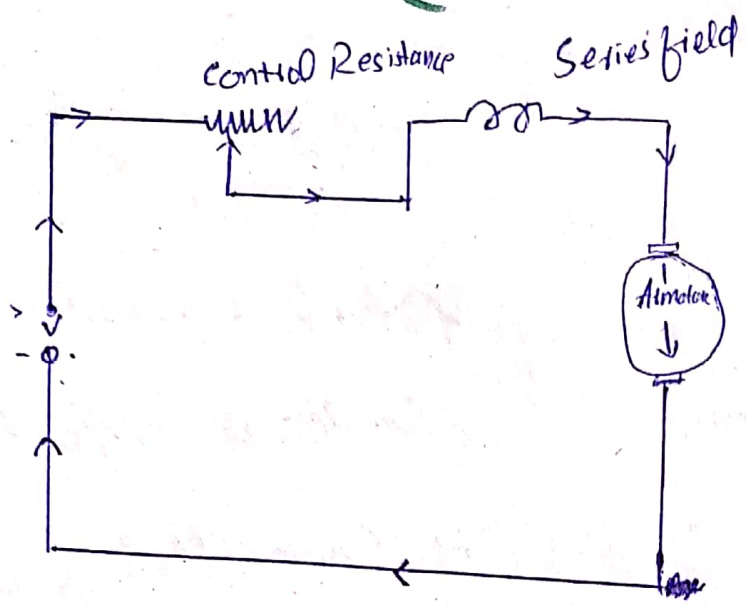

The Reduces The voltage available across the armature and hence the speed falls. by changing the value of variable resistance

This Method of speed control is most economical for constant torque.


ii) Field Diverter Method.

This method uses a diverter. Here the field flux can be reduced by shunting a portion of motor current

around the series field. Lesser than the diverter resistance less than the field current.

$$P > R > \phi$$

Less Flux there <sup>more</sup> speed.

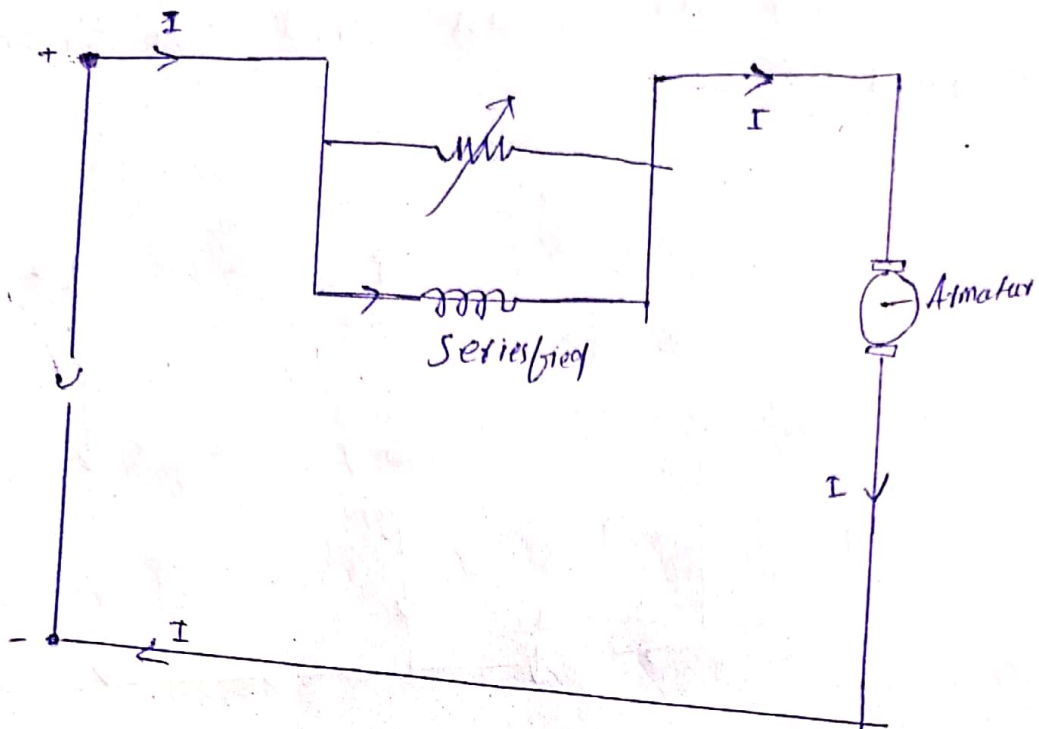

## Speed Control of DC Shunt

Motor:


i) Flux Control Method.

- In This Method, a variable resistance (known as shunt field rheostat) is placed in Series with shunt field winding as shown:
- An increase in controlling resistance

P.T.O



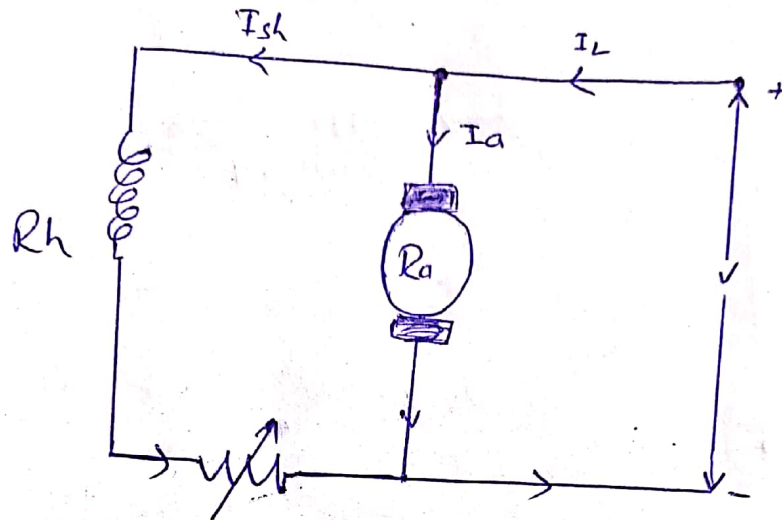reduces The field current with a reduction in Flux and an Increase In Speed




- i) This is an easy and convenient method
- ii) it is an inexpensive method since very little power is wasted in the shunt field rheostat due to relatively small value of  $I_{sh}$ .

### ii) Armature Control Method:

This is done by inserting a variable resistance  $R_c$  (known as controller resistance) in series with the armature as shown.

P.T.O

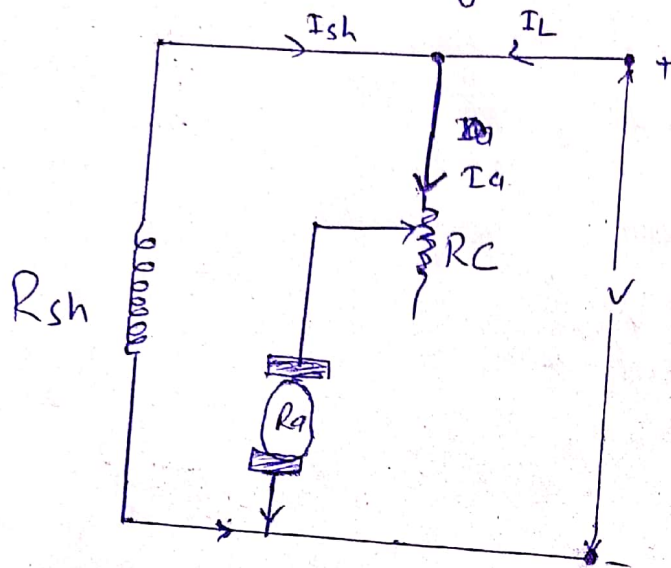- The flux remains constant while armature current is changed  
Produces change in speed.



Large amount of power is wasted in the controller resistance since it carries full armature current  $I_a$ .

# Part (b)

$$Z = 480$$

$$P = 8$$

$$emf = 2.2 \text{ V}$$

$$\text{Current} = 100 \text{ A}$$

total voltage?

o/p current=?

P=?

## Sol:

For Lap  $A = 8$

$$emf = 2.2 \times \frac{480}{8} = 132 \text{ V}$$

$$\text{Current} = 100 \times 8 = 800 \text{ A}$$

$$P = VI = 800 \times 132$$

$$= 105 \text{ kW}$$

For wave

$$A = 2$$

$$emf = 2.2 \times \frac{480}{2} = 528 \text{ V}$$

$$\text{Current} = 100 \times 2 = 200$$

$$P = 528 \times 200$$

$$P = 105 \text{ kW}$$



Q2: A

(7)

## Torque and Armature current relation Slip

$$P_e = P_m$$

$P_e$  = Electrical Power

$P_m$  = Mechanical Power

$$P_e = E_a I_a \quad \text{as } (E_a = E_b + I_a R_a) \text{ kV}$$

$$P_e = (E_b + I_a R_a) I_a$$

$$P_e = E_b I_a + I_a^2 R_a \quad (\text{as dissipate in form of heat})$$

$$P_e = E_b I_a$$

Now

$$P_m = T_g \omega \quad \therefore T_g \text{ (Torque in N.m)}$$

and  $\omega$  (angular speed in rad/sec)

$$P_m = T_g \omega \quad 1 \text{ radian}$$

$$P_m = T_g N \frac{2\pi}{60} \quad \frac{1}{2\pi} \quad \therefore \text{in RPM} = N \times \frac{2\pi \text{ rad/sec}}{60} \frac{1}{2\pi}$$

$$P_m = P_e$$

$$T_g N \frac{2\pi}{60} = E_b I_a \quad E_b = \frac{P \cdot \phi \cdot Z \cdot N}{60 \cdot A}$$

P.T.O.

$$T = \frac{P \cdot Z \cdot \Phi \cdot I_a}{2 \cdot \pi \cdot A} \quad (8)$$

Q2 B

## Difference b/w Lap winding and wave winding

- Definition
- Connection
- Parallel paths
- EMF Induced
- No of Brushes
- Types
- Efficiency
- Additional coils
- cost
- voltage and current.

P.T.O



## Basis for Comparison

### Lap winding

### Wave winding

#### Definition

- The coil is lap back to the succeeding coil
- The end of the armature coil is connected to an adjacent segment on the commutator.

- The coil of winding form the wave shape.

#### Connection.

- The end of the armature coil is connected to an adjacent segment on the commutator.
- The number of parallel paths are equal to the total of number poles.

- The end of the armature coil is connected to commutator segment some distance apart
- The number of parallel paths is equal to two.

#### Parallel path.

#### Other name.

#### EMF

#### number of brushes:

#### Types:

#### Efficiency

#### Additional coil winding cost

- Parallel winding or multiplex winding

- Less

- equal to the number of parallel paths

- Simplex and duplex lap winding

- Less

- equalizer ring

- High (more conductor is required)

- Two circuit or series winding

- more

- Two

- Progressive and Retrogressive

- High

- Dummy coil.

- Low

P.T.O

USES:

10)

**Lap winding**

in Low voltage,  
high current  
machine

**Wave winding**

In high voltages, Low  
current machine.