


Abdul Basit Khan

ID: 14564

Sub: Electric Network Analysis

To: Sir Shehryar

Date: 22. June. 2020

Signature: 

Module: Final Exam

Q1

Assume that a 2000 kW turbine generator of 0.85 power factor operates... but keep it from being overloaded?

Ans

Original load:

$$P_1 = 2000 \text{ kW}, \cos \theta_1 = 0.85 \rightarrow \theta_1 = 31.79^\circ$$

$$S_1 = \frac{P_1}{\cos \theta_1} = 2352.94 \text{ kVA}$$

$$Q_1 = S_1 \sin \theta_1 = 1239.5 \text{ kVAR}$$

Additional load

$$P_2 = 300 \text{ kW}, \cos \theta_2 = 0.8 \rightarrow \theta_2 = 36.87^\circ$$

$$S_2 = \frac{P_2}{\cos \theta_2} = 375 \text{ kVA}$$

$$Q_2 = S_2 \sin \theta_2 = 225 \text{ kVAR}$$

Total load

$$S = S_1 + S_2 = (P_1 + P_2) + j(Q_1 + Q_2) = P + jQ$$

$$P = 2000 + 300 = 2300 \text{ kW}$$

$$Q = 1239.5 + 225 = 1464.5 \text{ kVAR}$$

The minimum operating PF for a 2300kW load and not exceeding the kVA rating of the generator is

$$\cos \theta = \frac{P}{S_1} = \frac{2300}{2352.94} = 0.9775$$

or

$$\theta = 12.177^\circ$$

The maximum load kVAR for this condition is

$$Q_n = S_1 \sin \theta = 2352.94 \sin (12.177^\circ)$$

$$Q_n = 496.313 \text{ kVAR}$$

The capacitor must supply the difference between the total load kVAR (i.e.  $Q$ ) and the permissible generator kVAR (i.e.  $Q_n$ )

Thus

$$Q_c = Q - Q_n = 968.2 \text{ kVAR}$$

## Q2

A balanced abc sequence, one line voltage of a balanced..... Find phase and line current?

## Ans

Sol

$$\text{Line voltage } V_{AB} = 180 \angle -20^\circ \text{ V}$$

$$Z_{\Delta} = 20 \angle 40^\circ \Omega$$

Using formula

$$V_L = \sqrt{3} V_P \angle 30^\circ \Rightarrow V_P = \frac{V_L}{\sqrt{3} \angle 30^\circ}$$


Phase voltage

$$V_{an} = \frac{180 \angle -20^\circ}{\sqrt{3}} \angle -30^\circ = 103.9 \angle -50^\circ \text{ V}$$

$$Z_Y = \frac{Z_{\Delta}}{3} = \frac{20 \angle 40^\circ}{3} = 6.67 \angle 40^\circ \Omega$$

Line current
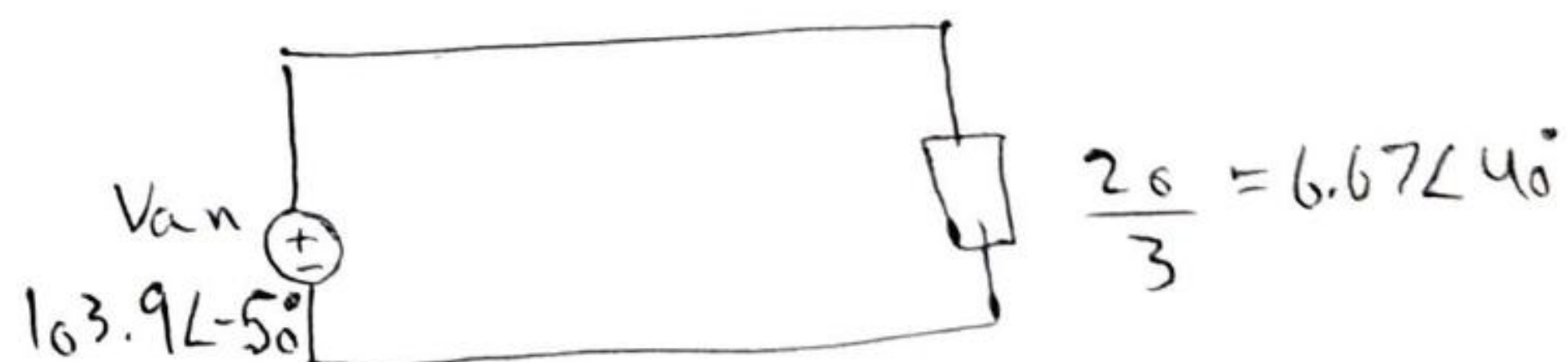
$$I_a = \frac{V_{an}}{Z_{a/3}} = \frac{103.9 \angle -50^\circ}{6.67 \angle 40^\circ}$$



$$\bar{I}_a = 15.57 \angle -90^\circ \text{ A}$$

$$\bar{I}_b = \bar{I}_a \angle -120^\circ = 15.59 \angle 150^\circ \text{ A}$$

$$\bar{I}_c = \bar{I}_a \angle +120^\circ = 15.59 \angle 30^\circ \text{ A}$$

Phase current

$$\bar{I}_{AB} = \frac{15.57 \angle -90^\circ \cdot \angle 30^\circ}{\sqrt{3}} = 9 \angle -60^\circ \text{ A}$$

$$\bar{I}_{BC} = \bar{I}_{AB} \angle -120^\circ = 9 \angle -180^\circ \text{ A}$$

$$\bar{I}_{CA} = \bar{I}_{AB} \angle +120^\circ = 9 \angle 60^\circ \text{ A}$$

Q3

Consider a load with value of  $V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$

$I_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$ . Calculate the following

- The complex and apparent Power
- The real and reactive Power
- The power factor and the load impedance

Ans

Sol:

$$\text{Given: } V_{\text{rms}} = 11 \angle 85^\circ \text{ V}$$

$$I_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$$

a) The complex power is

$$S = V_{\text{rms}} I_{\text{rms}}$$

$$S = (11 \angle 85^\circ) (0.4 \angle -15^\circ)$$

$$S = 11 \times 0.4 \angle (85^\circ - 15^\circ)$$

$$\therefore S = 44 \angle 70^\circ \text{ VA}$$

The apparent power is

$$S = |S|$$

$$\therefore S = 44 \text{ VA}$$

b) Express the complex in rectangular form

$$S = 44 \angle 70^\circ$$

$$S = 44 [\cos(70^\circ) + j \sin(70^\circ)]$$

$$S = 44 [0.3420 + j 0.9397]$$

$$S = 15.05 + j 41.35$$

$$\text{Since } S = P + jQ$$

The real power is

$$\therefore P = 75.05 \text{ W}$$

The reactive power is

$$\therefore Q = 41.35 \text{ VAR}$$

c)

The power factor is

$$PF = \cos(70^\circ)$$

$$\therefore PF = 0.342 \text{ (lagging)}$$

The power factor is lagging as the reactive power is positive. The load impedance is

$$Z = \frac{V}{I}$$

$$V = \sqrt{2} V_{\text{rms}}$$

$$I = \sqrt{2} I_{\text{rms}}$$

$$Z = \frac{110\sqrt{2} \angle 85^\circ}{0.4\sqrt{2} \angle 15^\circ}$$

$$Z = 275 \angle 70^\circ \Omega$$


$$Z = 275 [\cos(70^\circ) + j \sin(70^\circ)]$$

$$Z = 275 [0.342 + j0.9397]$$

$$Z = (94.05 + j258.4) \Omega$$

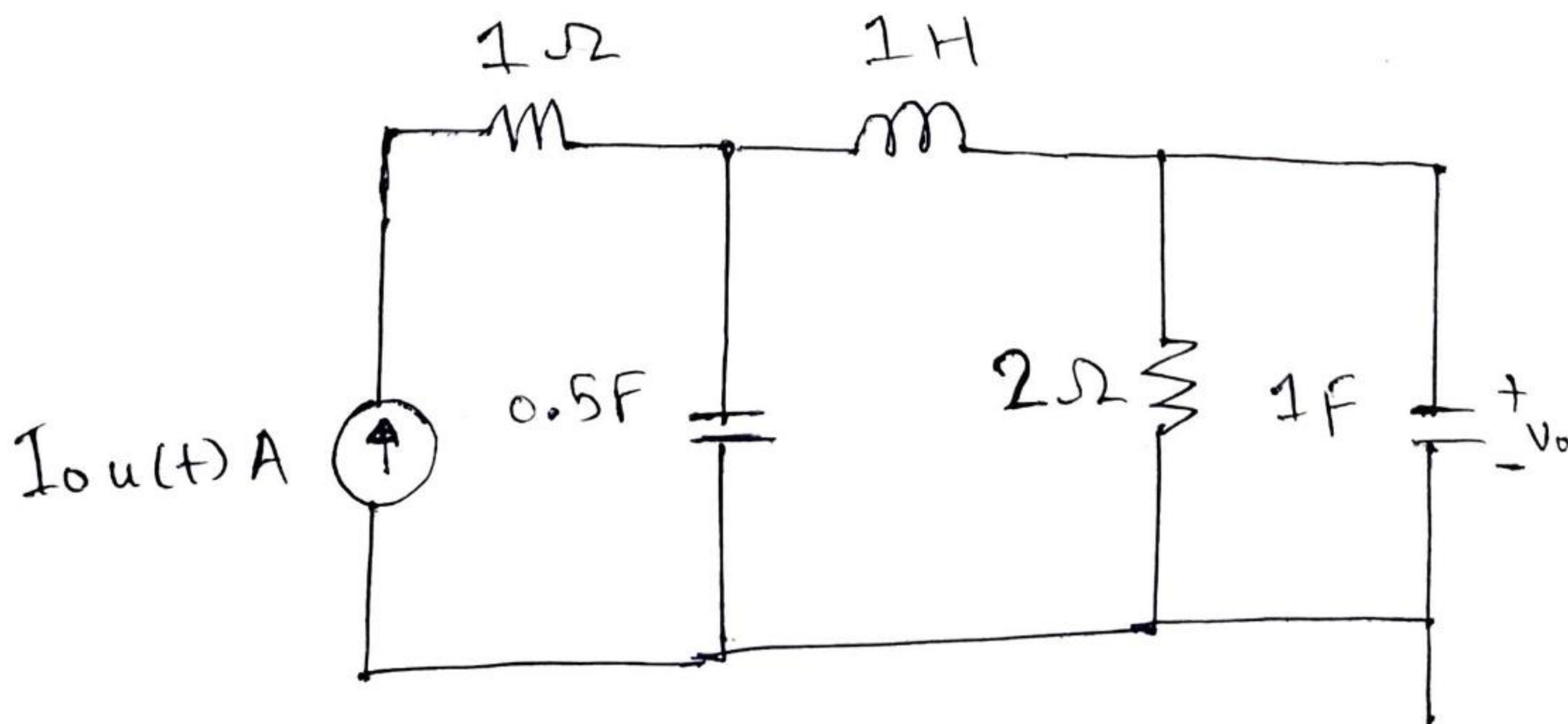Q4


Apply Laplace transform and calculate the output voltage  $V_o(t)$  in the circuit.





Ans

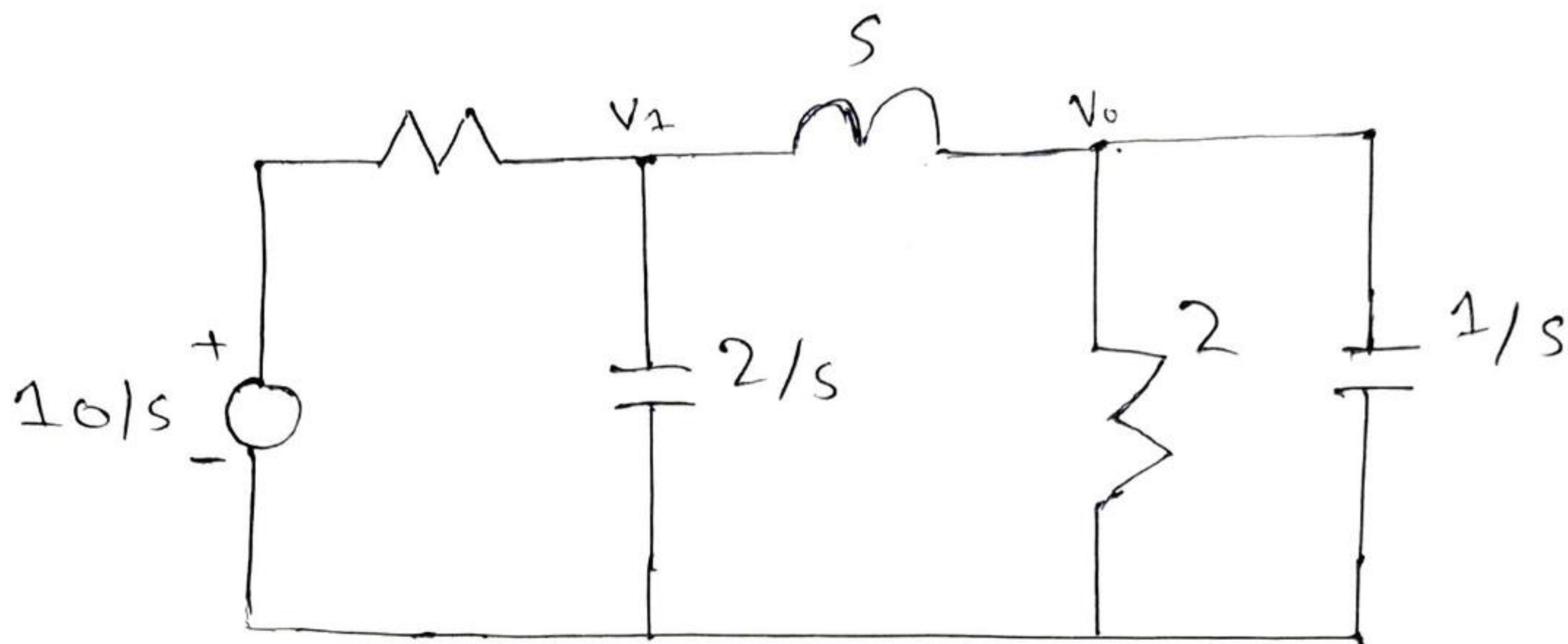The s-domain version of the circuit is shown below.



At node 1.

$$\frac{10 - V_1}{s} = \frac{V_1 - V_o}{s} + \frac{s}{2} V_o \rightarrow 10 = (s+1)V_1 + \left(\frac{s^2}{2} - 1\right)V_o \quad (1)$$

At node 2.

$$\frac{V_1 - V_o}{s} = \frac{V_o}{2} + s V_o \rightarrow V_1 = V_o \left(\frac{s}{2} + s^2 + 1\right) \quad (2)$$

Substituting (2) into (1) gives

$$10 = (s+1)(s^2 + s/2 + 1)V_0 + \left(\frac{s^2}{2} - 1\right)V_0 = \checkmark$$

$$s(s^2 + 2s + 1.5)V_0$$

$$V_0 = \frac{10}{s(s^2 + 2s + 1.5)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 2s + 1.5}$$

$$10 = A(s^2 + 2s + 1.5) + Bs^2 + Cs$$

$$s^2: \quad 0 = A + B$$

$$s: \quad 0 = 2A + C$$

$$\text{Constant:} \quad 10 = 1.5A \rightarrow A = 20/3, \quad B = -20/3 \\ C = -40/3$$

~~With the help of partial fraction decomposition we can write the above expression as follows~~

$$V_0 = \frac{20}{3} \left[ \frac{1}{s} - \frac{s+2}{s^2 + 2s + 1.5} \right] = \frac{20}{3} \left[ \frac{1}{s} - \frac{s+1}{(s+1)^2 + 0.7071^2} - \frac{1.414 \cdot 0.7071}{(s+1)^2 + 0.7071^2} \right] \checkmark$$

Taking the inverse Laplace transform finally yields



$$V_0(t) = \frac{20}{3} \left[ 1 - e^{-t} \cos(0.7071t) - 1.414 e^{-t} \sin(0.7071t) \right] u(t) \text{ V}$$

# Q5

For the circuit given below . . . . .

calculate the following

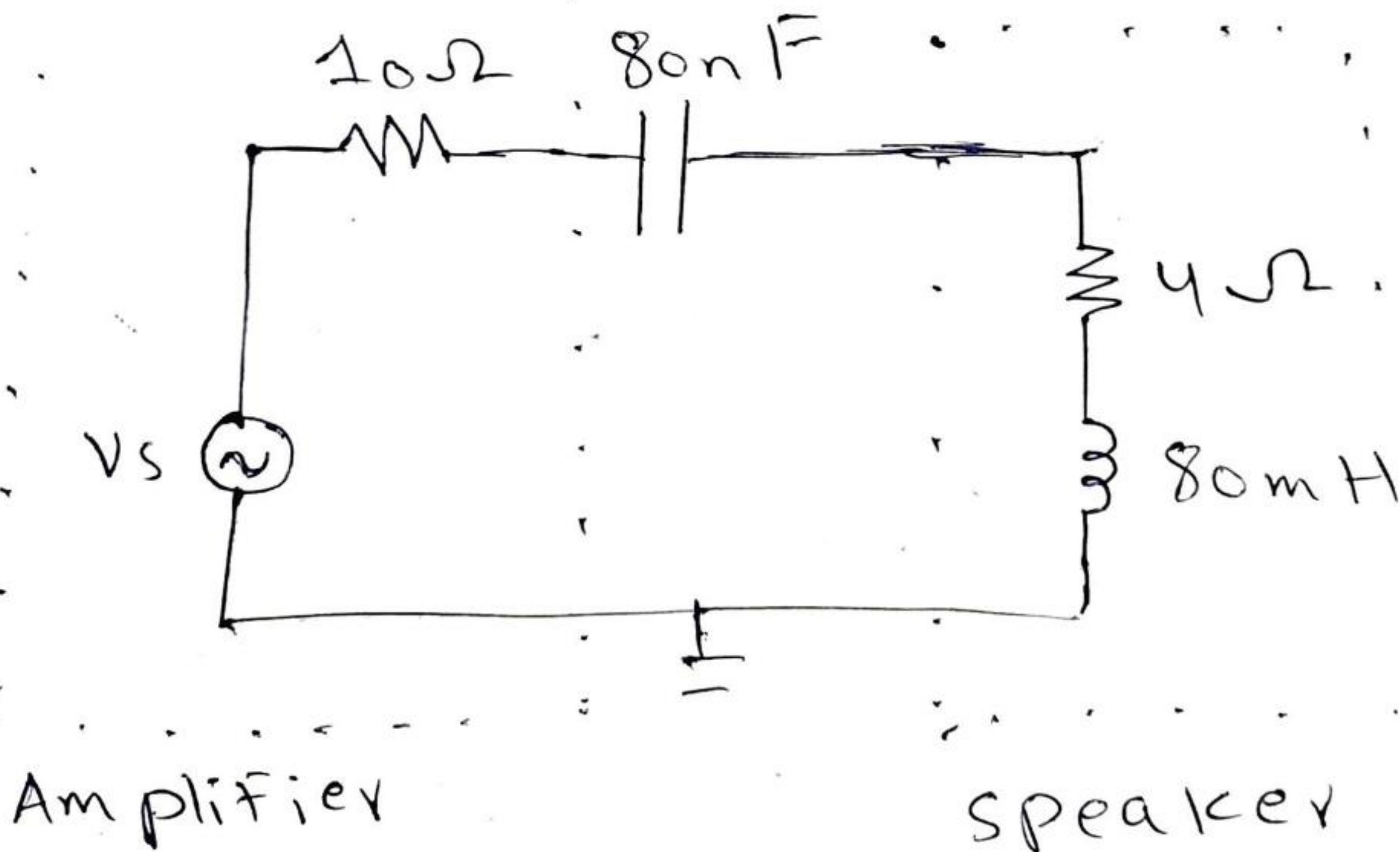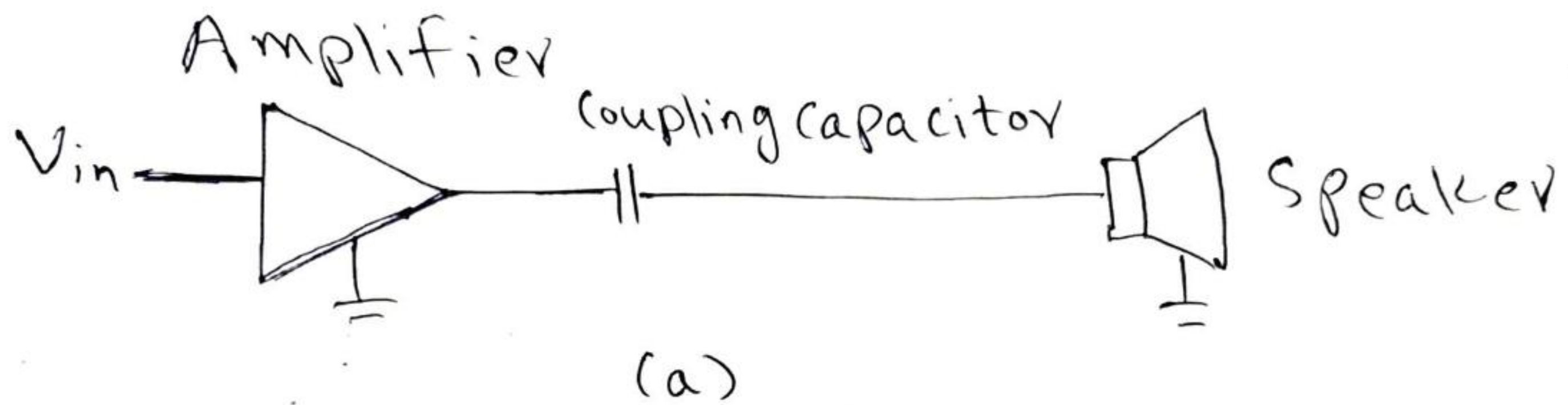- a) At what frequency maximum power is transferred to the speaker?
- b) If  $V_s = 5 \text{ V}_{\text{rms}}$  how much power is delivered to the speaker at that



Ans (a)

The amplifier and the capacitor act as a source and the speaker acts as load

So

Source impedance,  $Z_s = R_s - jX_c$

load impedance,  $Z_L = R_L + jX_L$

Maximum Power when

$$Z_s = Z_L$$

$$R_L + jX_L = (R_s - jX_c)$$

~~So~~ So

$$R_s = R_L$$

$$X_c = X_L \longrightarrow \frac{1}{\omega C} = \omega L$$

$$\text{or } \omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(80 \times 10^{-3})(80 \times 10^{-9})}}$$

$$= \frac{1}{2(3.14)(80 \times 10^{-6})}$$

$$= 1990.44586$$

$$= 2.044 \text{ kHz}$$

Thus the frequency  $f$  at which maximum power transfer to the speaker is  $2.044 \text{ kHz}$

b) A frequency of  $f = 2.044 \text{ kHz}$  the reactive power are cancelled because they are in series. So to find power

$$P = (I_s)^2 R_L$$

$$= \left[ \frac{V_s}{(R_s + R_L)} \right]^2 R_L$$

$$= \left[ \frac{5}{70 + 4} \right]^2 4$$

$$= 0.51020 \text{ W}$$

$$= 510.20 \text{ mW}$$

The power  $P$  delivered to the speaker is

$$P = 510.20 \text{ mW}$$