

-: COURSE DETAILS:-

Course title :- EDC


Module :- 3rd

Instructor :- Dr-Shahryar

-: STUDENT DETAILS:-

Name :- Naveed Alam

Student ID :- 14965

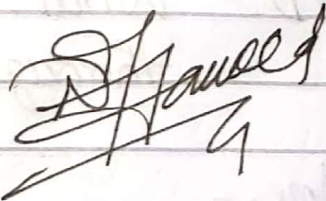Student Sign :- 

→ QNO.1:- For the circuit given in figure, answer and solve the following problems.

↳ (a):- What type of circuit is this?

Ans (a):- This type of circuit is called center tapped full wave rectifier.

↳ (b):- What is the total peak secondary voltage?


Ans (b):- $V_p(\text{sec}) = n V_p(\text{pri}) = 0.25(50)$

$$V_p(\text{sec}) = 12.5 \text{ V}$$

Q8

Find the peak voltage across through each diode?

Ans:

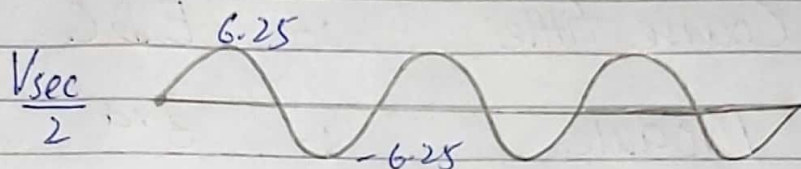

+5.55V



6.25 is peak to peak voltage the output voltage has peak value (6.25-0.7) which is diode drop-

QD:- What is the peak current through each diode?

Ans:-

$$I_F = \frac{V_p(\text{sec}) - 0.7}{2 R_L} = \frac{5.55V}{10K\Omega}$$

$$I_F = 0.555 \text{ mA}$$

QE:- What minimum PIV rating the diode have?


Ans:- PIV Rating the diode have,

$$PIV = 2V_p(\text{out}) + 0.7 \\ = 2(5.55V) + 0.7$$

$$PIV = 11.8V$$

Q NO. 2 :-

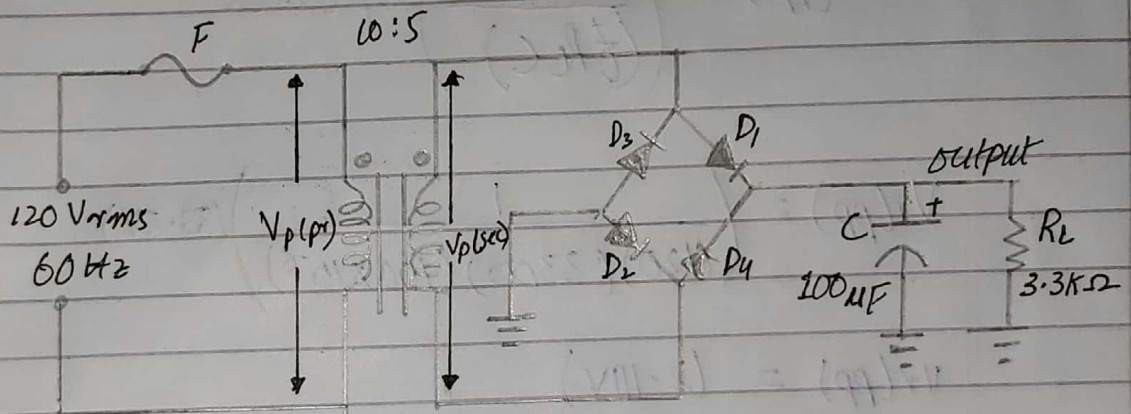Determine the ripple factor for the filtered bridge rectifier with a load as indicated in Figure 2.



↳ Solution :-

The transformer trans ratio is $m = 0.5$
The peak primary voltage is

$$V_p(\text{pri}) = 1.414 V_{\text{rms}} = 1.414(120\text{V}) = 170\text{V}$$

The peak secondary voltage is

$$V_p(\text{sec}) = m V_p(\text{pri}) = 0.5(170\text{V}) = 85\text{V}$$

The unfiltered peak full-wave rectified voltage is

$$V_p(\text{rect}) = V_p(\text{sec}) - 1.4\text{V}$$

$$V_p(\text{rect}) = 85 - 1.4\text{V}$$

$$V_p(\text{rect}) = 83.6\text{V}$$

The frequency of a full-wave rectified voltage is 120 Hz.

The approximate peak to peak ripple voltage at the output is

$$V_r(pp) = \left(\frac{1}{fRC} \right) V_p(\text{rect})$$

$$V_r(pp) = \left(\frac{1}{(120)(3300)(100 \times 10^{-6})} \right) (83.6V)$$

$$V_r(pp) = (2.111V)$$

The approximate dc value of the output voltage is determined as follows

$$V_{DC} = \left(1 - \frac{1}{2fRC} \right) V_p(\text{rect})$$

$$V_{DC} = \left(1 - \frac{1}{(240)(3300)(100 \times 10^{-6})} \right) (83.6)$$

$$V_{DC} = \left(1 - \frac{1}{79.2} \right) (83.6) =$$

$$V_{DC} = (1 - 0.012)(83.6) = 82.6$$

$$V_{DC} = 82.6$$

The resulting ripple factor is


$$\gamma_z = \frac{V_r(\text{pp})}{V_{DC}}$$

$$\gamma_z = \frac{2.111}{82.6} = 0.025$$



$$\therefore \boxed{\gamma_z = 0.025} \quad \therefore$$

Q.No. 3:-

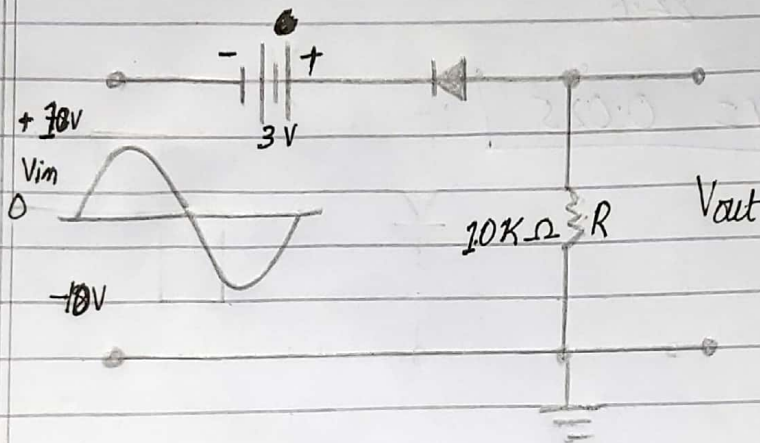
Determine the output voltage waveform for the circuit given in Figure 3.



↳ Output waveform of clipper circuit.

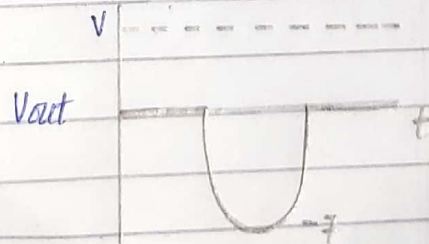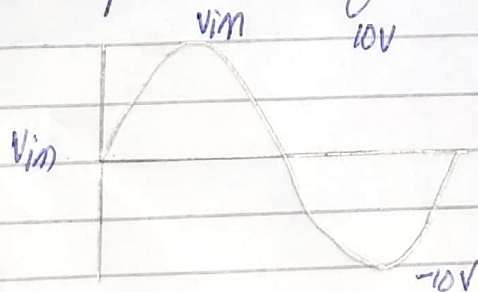

$(V_m - V)$

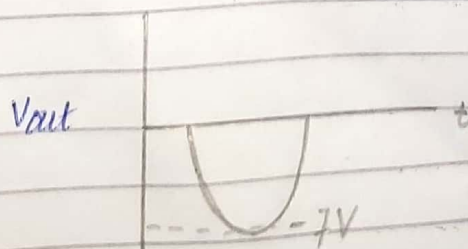

Q NO. 4:-

Determine the output voltage waveform for the circuit given in Figure 4. Assume the RC time constant is much greater than the period of the input -

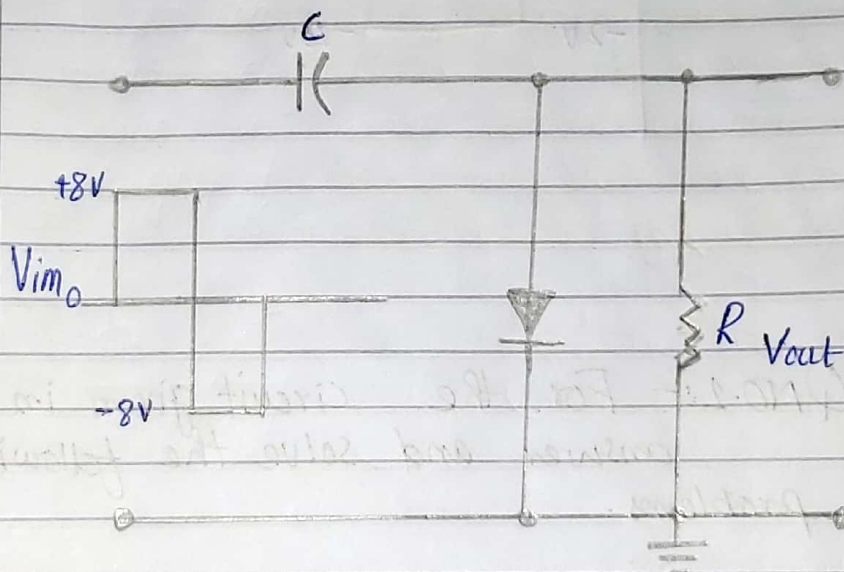


Figure 4.

Assume the RC time constant is much greater than the period of the input so if we take :-

$$(5T \text{ discharge} \geq 50 T_{1/2}) \text{ thus we}$$


obtain condition for the clamping operation.

$$T \text{ discharge} \geq 5T$$

so

$$V_o = V_i - V + V_p(\text{ov})$$

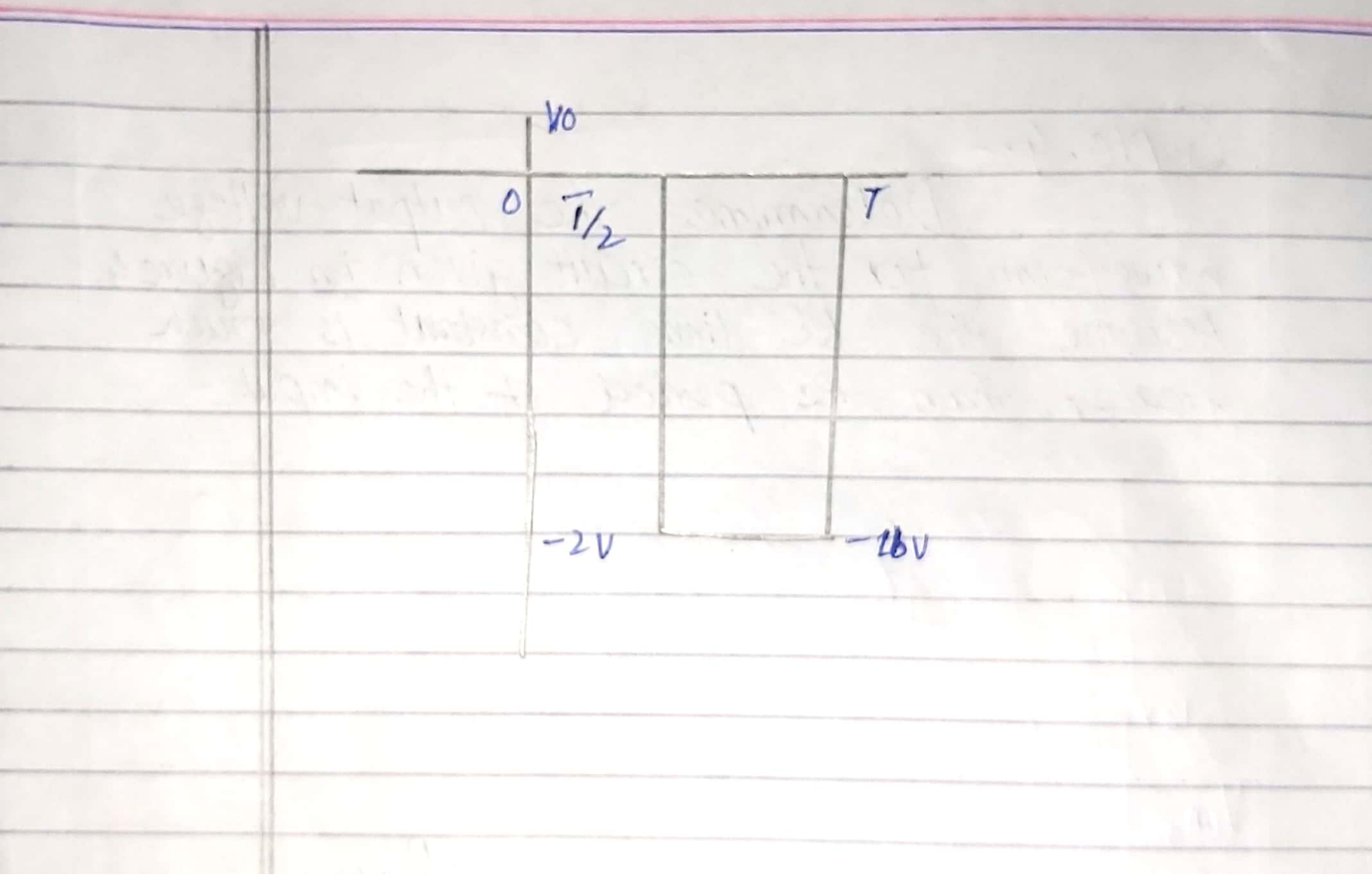$\therefore T$ is the position of input signal V_i



Q. No. 5 :-

Answer the following Questions -

(a) what is a Power supply Filter? Discuss its operation with the help of a circuit diagram -

Ans Power Supply Filters -


The power supply filter is capacitor. Capacitors are used to smooth (filter) the pulsating DC output after rectification so that a nearly constant DV voltage is supplied to the load -

Diagram :-

transformer

Rectifier Diode

AC Ripple

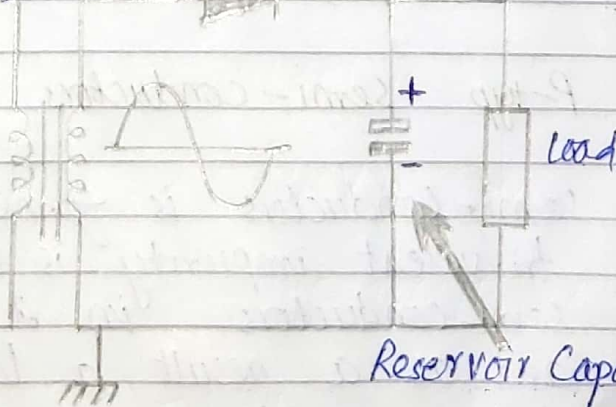

Reservoir Capacitor


→ AC Ripple :- Reducing Ripples as capacitor charging and discharging -

(B) How are n-type and p-type semi-conductors formed?

↳ N-type semi-conductor formation:-


when a small amount of pentavalent impurity is added to a pure silicon-crystal- it forms N-type semi-conductors

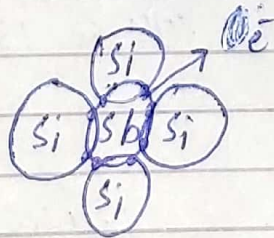The addition of pentavalent impurity produces a large no. of free electron in the host crystal.



↳ P-type semi-conductors formation:-

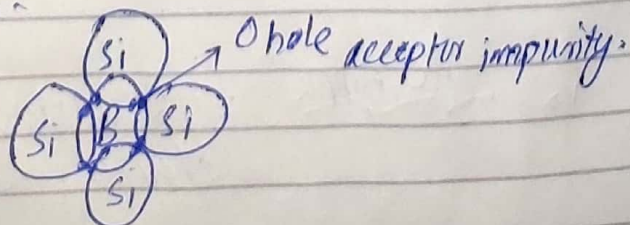P-type semi-conductors is formed when a tri-valent impurity is added to a pure semi-conductors in a small amount and as a result a large number of holes create.




Q No. C:-

What is diode limiter? what is the difference between a positive limiter and a negative limiter?



Ans:-

Diode limiter:-

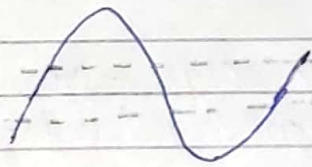It is a type of circuit which is designed to clip a part of signal or AC signal to desired waveform.





↳ Positive Diode limiter

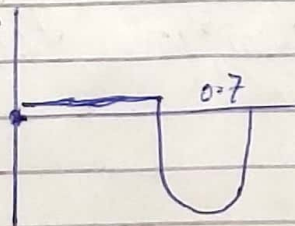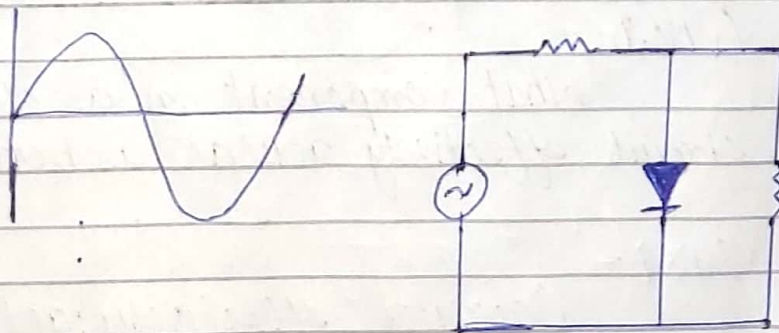

It is used to clip +ive half cycle of sinusoidal wave

↳ Negative Diode Limiter.

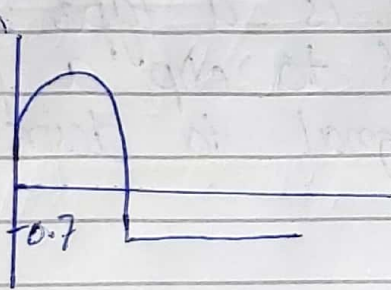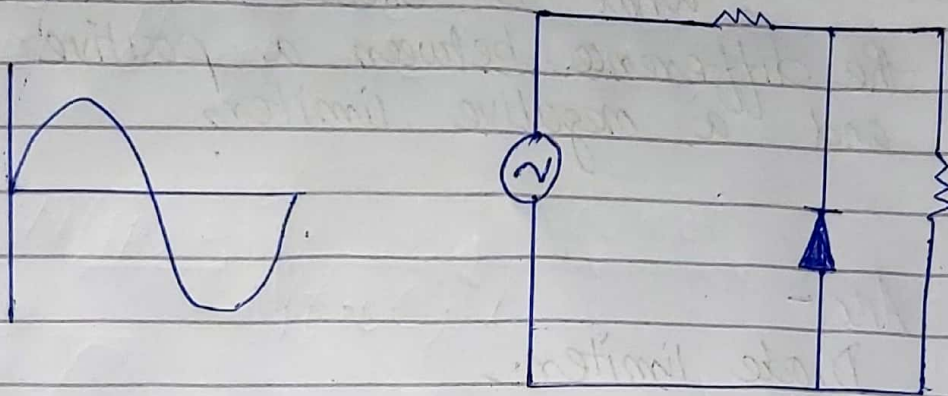

↳ It is used to clip -ive half ~~cycle~~ cycle of a desired level -

Q No. D:-

What component in a clamping circuit effectively acts as a battery?


Ans D:-

Capacitor effectively act as a battery in clamping circuit -

Q No. e:- When a 60Hz sinusoidal voltage is applied to the input of a half-wave rectifier, what is the output frequency?

Ans:-

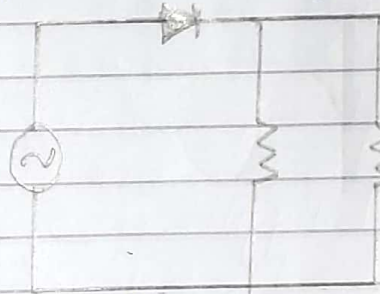The output frequency of half wave rectifier is equal as input. This means as input complete one cycle and output also complete one cycle.




$$f_{in} = f_{out}$$



Q No. f:- If the load resistance connected to a filtered power supply is decreased, what happens to the ripple voltage?

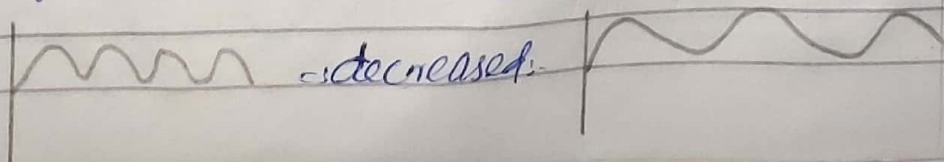Ans:- If the load resistance connected to a filtered power supply decreases, the charging and discharging time of capacitor also increases so takes longer time to charge and discharge.





Q.No.9:-

Discuss the diode limiters and diode clampers differ in terms of their functions?

↳ Diode limiter:-

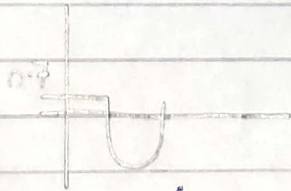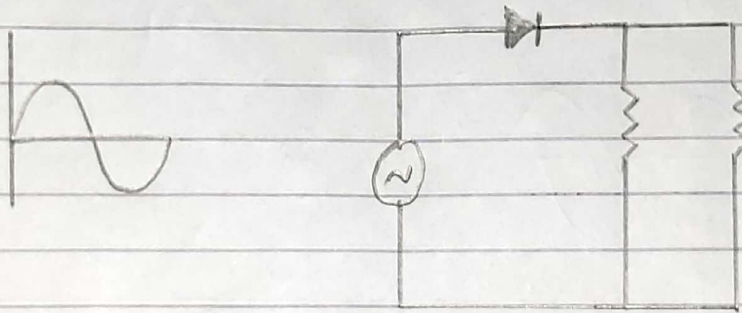It is a circuit which is used to clip a sinusoidal waveform at a desired level-





↳ It is used as a voltage regulator to keep the voltage at a desired level.

↳ Diode Clamper:-

Diode clamper is used to add a DC offset to a (+ive) and (-ive) half cycle of a sinusoidal waveform-

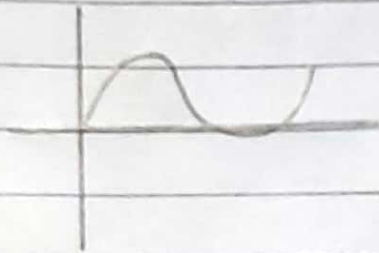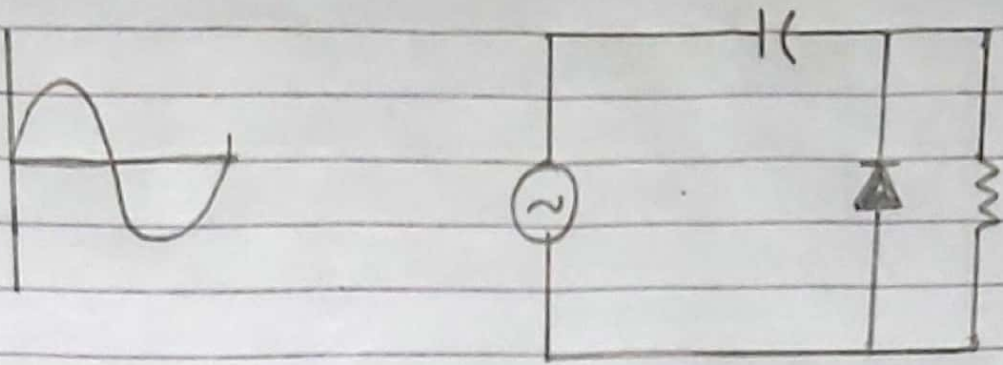It clamps the whole signal at a desired level.



↳ It is used as a voltage doubler.